

# BUILD A PREREGULATED POWER SUPPLY

*Super-stable,  
multi-purpose supply for  
the experimenter's workbench*

**A**NYONE who works with modern electronic circuits, whether he is a professional or an amateur, will eventually require a closely regulated variable power supply. While most power supplies are regulated directly from the basic rectified and filtered dc line, tighter regulation can be obtained by using a preregulated approach in the supply's design.

The preregulated power supply described here can be built for about \$15 more than you would have to pay for a conventionally regulated low-current supply. It employs two inexpensive 723 voltage regulator IC's in a circuit that can deliver 3 to 35 volts dc at load currents up to 3 amperes. The design eliminates the need for massive heat sinks and cooling fans.

**How It Works.** The power supply's circuit shown in Fig. 1 can be functionally diagrammed as an ac source, rectifier bridge, and two voltage regulators in series. The preregulator, by means of SCR1, continuously controls the potential at C1 so that the potential across Q1 remains constant. The output regulator (IC2) is a high-performance circuit that is capable of providing 0.1% regulation.

Synchronized to the 120-Hz rectified ac input, preregulator integrated circuit IC1 is connected as a time-delayed pulse generator that controls the gate of SCR1 to trigger conduction at the exact point required during each half cycle. The bias voltage applied to the inverting input (pin 2) of

IC1 is adjustable via potentiometer R9; it determines the reference level for the supply.

The zener-regulated source at pin 4 of IC1 also supplies current through R14, R15, and R18 to C4 and pin 3 (noninverting input). The current continues to flow until the reference voltage is exceeded. At this point, IC1 turns on. The resulting square-wave pulse from pin 6 of the IC is limited to 9 volts by current-sensing resistors R12 and R13, which is sufficient, at the gate of SCR1, to trigger the SCR into conduction.

The RC time constants in the circuit are controlled by the amount of current flowing through Q3, which, in turn, depends on the error voltage present at the wiper of R10A. A voltage divider consisting of R16 and diodes D7 through D10 applies a relatively constant 2.4 volts to the emitter of Q3 so that when the transistor's base goes above 3 volts there will be a voltage drop across R14 and a corresponding change in the RC time constant. Capacitors C5 and C6 stabilize the operation of Q3 to prevent SCR1 from firing erratically. When R10 is rotated counterclockwise, R17 and D13 protect Q3 and D12 from damage.


The method of synchronizing IC1 to the rectified input is graphically shown in Fig. 2. Triggered into conduction by the positive-going voltage, SCR1 cuts off when the gate signal ceases and C4 discharges sufficiently to reduce to a minimum the holding current to the SCR. The diagram also

reveals why the secondary voltage from T1 must be greater than would be normal in a conventionally regulated power supply. The SCR cannot conduct until its anode is more positive than its cathode. Simultaneously, a minimum latching current must flow. Also, SCR1 must remain conducting until the energy drawn from C1 by the output load is replaced.

Since the potential across C1 will be 41 volts at maximum output, the 18-volt difference allows the time interval necessary for maximum current. This also means that SCR1 fires only near the peak or on the negative-going side of the waveform. Resistors R1 and R2 are bleeders that carry the minimum holding current required by SCR1.

Dual potentiometer R10 establishes feedback to both voltage-regulator IC's. (A wire-wound potentiometer is best used here so that the sections will be more evenly matched. So, if an identical voltage were present across each section of the pot, the wiper voltages would be very nearly the same at any setting.) Potentiometer section R10B samples the output voltage and drives IC2 in the proper direction to maintain 3 volts between wiper and ground. The A section of the pot samples the voltage across C1 and controls the firing of SCR1, also maintaining 3 volts between wiper and ground.

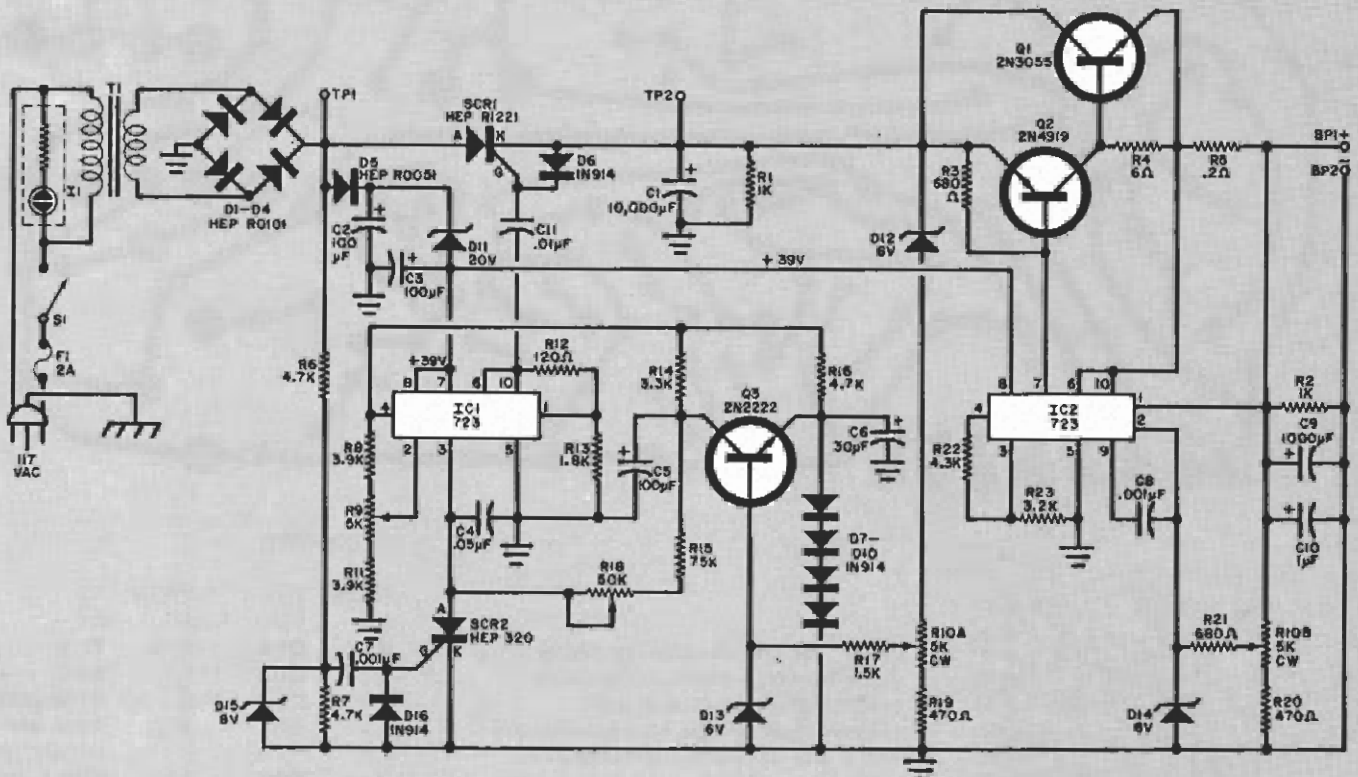Since the potential at the counterclockwise ends of R10A and R10B must be the same, the potential across



BP1, BP2—Five-way binding post (one black, one red)  
 C1—10,000- $\mu$ F, 50-volt electrolytic capacitor  
 C2, C3—100- $\mu$ F, 65-volt electrolytic capacitor  
 C4—0.05- $\mu$ F disc capacitor  
 C5—100- $\mu$ F, 10-volt electrolytic capacitor  
 C6—30- $\mu$ F, 10-volt electrolytic capacitor  
 C7, C8—0.001- $\mu$ F disc capacitor  
 C9—1000- $\mu$ F, 50-volt electrolytic capacitor  
 C10—1- $\mu$ F, 50-volt tantalum electrolytic capacitor  
 C11—0.01- $\mu$ F disc capacitor  
 D1 thru D4—100-PIV, 3-ampere rectifier (Motorola HEP R0101 or similar)  
 D5—100-PIV, 1-ampere rectifier (Motorola HEP R0051 or similar)  
 D6, D7 thru D10, D16—1N914 diode  
 D11—20-volt, 1-watt zener diode (Motorola HEP Z0421 or similar)

#### PARTS LIST

D12—6-volt zener diode (1N429 or similar)  
 D13, D14—6-volt zener diode (1N1509 or similar)  
 D15—8-volt zener diode (Motorola HEP Z0217 or similar)  
 F1—2-ampere slow-blow fuse  
 I1—Neon panel lamp with resistor  
 IC1, IC2—723 voltage regulator integrated circuit (in TO-5 can)  
 Q1—HEP 704 (Motorola) or 2N3055 transistor  
 Q2—HEP 246 (Motorola) or 2N4919 transistor  
 Q3—HEP 736 (Motorola) or 2N2222 transistor  
 R1, R2—1000-ohm, 2-watt, 10% resistor  
 R3, R21—680-ohm, 1/2-watt, 5% resistor  
 R4—6-ohm, 1-watt, 5% resistor  
 R5—0.2-ohm, 2-watt, 5% resistor  
 R6—4700-ohm, 1-watt, 5% resistor

R7, R16—4700-ohm, 1/2-watt, 5% resistor  
 R8, R11—3900-ohm, 1/4-watt, 5% resistor  
 R9—5000-ohm miniature pc potentiometer  
 R10—5000-ohm dual wire-wound potentiometer  
 R12—120-ohm, 1/4-watt, 5% resistor  
 R13—1800-ohm, 1/4-watt, 5% resistor  
 R14—3300-ohm, 1/4-watt, 5% resistor  
 R15—75,000-ohm, 1/4-watt, 5% resistor  
 R17—1500-ohm, 1/4-watt, 5% resistor  
 R18—50,000-ohm, miniature pc potentiometer  
 R19, R20—470-ohm, 1/2-watt, 5% resistor  
 R22—4300-ohm, 1% resistor  
 R23—3200-ohm, 1% resistor  
 SCR1—HEPR 1221  
 SCR2—HEP 320  
 S1—Spst switch  
 T1—Transformer, 42V, 3A Secondary  
 Misc.—Printed circuit or perforated board; suitable cabinet; heat sink; fuse holder; sockets for IC's (2); etc.

Fig. 1. Power supply employs two voltage-regulator IC's for super stability.

C1 will be 6 volts greater than the output because of the action of D12. Any change in the output voltage and/or current will affect the firing-pulse timing at the gate of SCR1, maintaining a constant potential across Q1.

**Construction.** The easiest way to assemble the power supply is by using a printed circuit board. (See Fig. 3 for actual-size etching and drilling and component placement guides.) Alternatively, you can assemble the circuit on perforated board using solder clips and sockets. Whichever method you use, refer to the table in Fig. 3 for instructions on how to interconnect the circuit board assembly and the com-

#### SEQUENCE OF EVENTS

- SCR2 fires as C7 charges; C4 then discharges and IC1 cuts off.
- D15 limits voltage on C7; SCR2 cuts off and C4 begins to charge.
- C4 has charged above reference level at pin 2 of IC1, causing the IC to conduct; a trigger pulse at pin 6 turns on SCR1 through C11.
- SCR1 current decreases as C1 voltage increases. When voltage across SCR1 is insufficient to maintain about 10 mA current, SCR1 turns off.

Note: SCR1 turns on and off at approximately C and D on the curve, when the output load is drawing 3 amperes at 35 volts. With no external load, events C and D occur near the end of the wave as indicated by the unmarked dots.

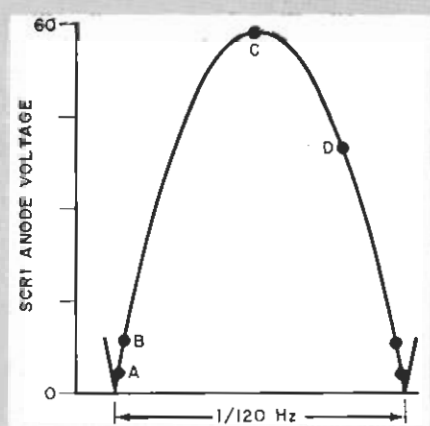


Fig. 2. Events above left are keyed to points on curve.

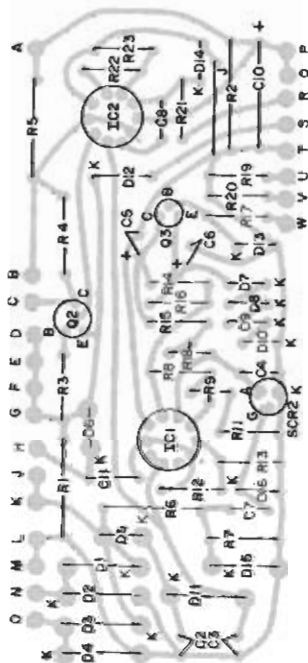
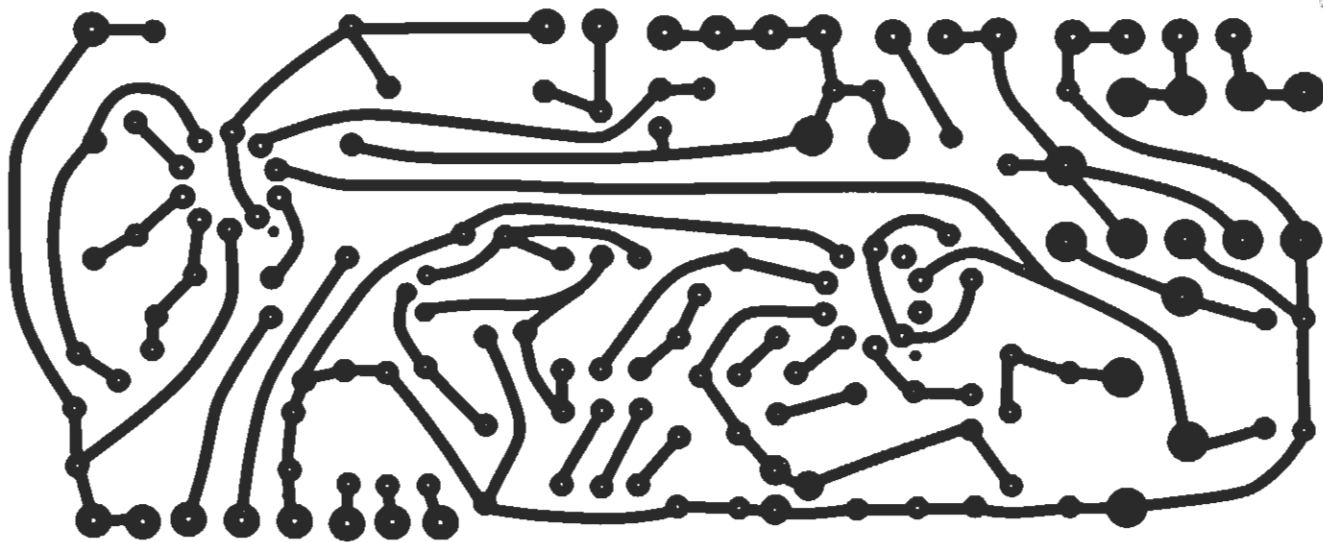


Fig. 3. Actual-size etching and drilling guide is shown above; component-placement diagram is at left; table at right details hookups between board and off-the-board components.

#### CONNECT

FROM:	TO:	FROM:	TO:
A	C9 +	M	C1 -
B	Q1 E	N, O	T1 S
C	Q1 B	P	BP1
D	Q1 C	Q	R10B CCW
E	TP2	R	R10B WIP
F	C1 +	S	R10A CCW
G	SCR1 K	T	BP2
H	SCR1 G	U	R10A CW
J	SCR1 A	V	R10B CW
K	TP1	W	R10A WIP
L	C9 -		

Mount the off-the-board components, followed by the circuit-board assembly inside the cabinet. Then refer to the table in Fig. 3 and Fig. 1 to complete wiring the system.

**Test and Use.** To balance out component tolerances, *IC1* must be initially aligned. To accomplish this, you will need an oscilloscope, high-impedance multimeter, and an improvised load. Rotate *R10* counterclockwise, set *R18* to maximum resistance and *R9* for maximum voltage gain at pin 2 of *IC1* before applying power to the supply. Connect the scope from *TP1* to ground and the multimeter from *TP2* to ground. Turn on the power.

There should be a small voltage present at *TP2*, but the scope should indicate that *SCR1* is not conducting. Keeping the voltage reference as high as possible at pin 2 of *IC1*, adjust *R18* and *R9* until *SCR1* fires regularly and the meter indicates 9 volts at *TP2*. When *R10* is rotated fully clockwise, the meter should indicate 41 volts at *TP2*.

Temporarily short out *R5* and momentarily connect a 12-ohm,

120-watt resistor (or an equivalent combination) across the output via *BP1* and *BP2*. If the *TP2* reading drops more than 0.2 volt or *SCR1* fires intermittently, adjust *R9* only enough to correct. Then, with no load connected to the output of the supply, rotate *R10* counterclockwise. The reading at *TP2* should slowly decrease to 9 volts. If it does not, adjust *R9* for a higher voltage at pin 2 of *IC1* until it does.

Rotate *R10* again and apply the load, compensating for the voltage drop by adjusting *R18*. There will be some combination of the two adjustments that will permit *Q3* to retain control over *IC1* throughout the specified voltage and current ranges. To do this, *Q3* must always be forward biased. If at any time *Q3* does not draw the proper current from *R14*, it has lost control.

Correct alignment will be achieved when the voltage at the wiper of *R10A* is the same at any output. As a further test, connect the meter across *Q1* and note the voltage change when *R10* is rotated clockwise. Any difference would correspond with *D12*'s zener voltage characteristics at bias currents of from 1 to 7mA.

Note: Components shown from foil side of board.

ponents located off the printed circuit board.

Select a cabinet for the supply that is large enough to accommodate all components without crowding. Machine the front panel for potentiometer *R10*, lamp/resistor assembly *I1*, and binding posts *BP1* and *BP2*. Mount the components in their respective holes.

Next, mount *Q1* and *SCR1* on a 4" × 2½" × 1" (10.2 × 6.4 × 2.5-cm) finned heat sink. Drill mounting holes for this assembly, the line cord, and fuse holder through the rear panel of the cabinet. Mount the fuse holder and heat-sink assembly in place. Line the remaining hole with a rubber grommet for the line cord.