

# Fault-latch circuit protects switchers


Craig Varga, National Semiconductor, Phoenix, AZ

**M**ANY POWER-SUPPLY designers like to have a regulator latch off in the event of an overcurrent situation or other fault condition. Yet, many PWM controllers do not internally support this latch-off function. Most do, however, have a power-good output and an enable function. The circuit in **Figure 1** adds that latch-off capability at low cost in little additional space. The design is based on the LMS33460, which is a power-supply monitor in a tiny, five-lead SC-70 package. You just need to combine it with a few small passive parts, and the circuit is complete. When the Enable Input signal goes high, the voltage at the top of  $C_1$  rises quickly to 5V. Because the output voltage is not yet alive,  $P_{GOOD}$  stays low, charging  $C_1$  through  $R_1$ . Because the voltage on  $C_1$  is zero at the instant of turn-on, Pin 5 of  $IC_1$  pulls up to 5V and begins to drop at a time constant that  $C_1$ ,  $R_1$ , and  $R_2$  deter-

mine. If the output does not reach its normal operating voltage before the Pin 5 voltage drops to less than 3V,  $IC_1$  pulls its output low and latches the regulator off.


If, however, the output comes into regulation before the latch times out,  $P_{GOOD}$  goes high and  $C_1$  begins to discharge, raising the voltage on Pin 5 and keeping the supply enabled.  $R_2$  provides a couple of volts to  $IC_1$  to keep the IC alive in the event of a latch condition, and  $D_1$  pulls down on the PWM's Enable when the system-enable command switches low.  $C_1$  can be a small tantalum or ceramic capacitor. If you use a ceramic unit, choose a good dielectric, such as X5R. Also, the 5V supply's rising in less than 1 msec or so may eliminate the Enable, and the whole circuit simply runs from the 5V supply. **Figure 2** shows a normal start,

and **Figure 3** shows start-up with the second output of a two-output regulator shorted. In both cases, the top trace is the system-enable signal, the second trace is  $IC_1$ 's Pin 5, the third trace is the PWM Enable at  $IC_1$ 's Pin 4, and the bottom trace is the regulator's output voltage. You can see in **Figure 3** that  $IC_1$ 's Pin 5 decays to 3V, at which point it pulls the PWM Enable low, latching off the regulator. □

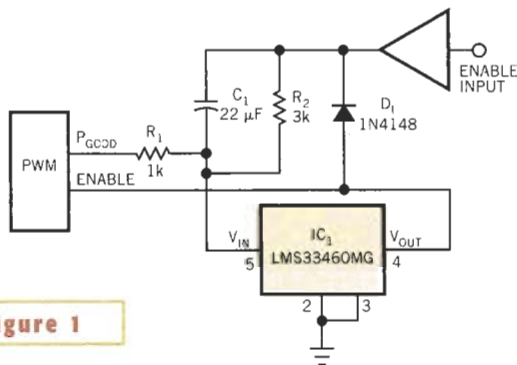


**Figure 1**

This circuit adds a latch-off function to PWM controllers lacking this feature.

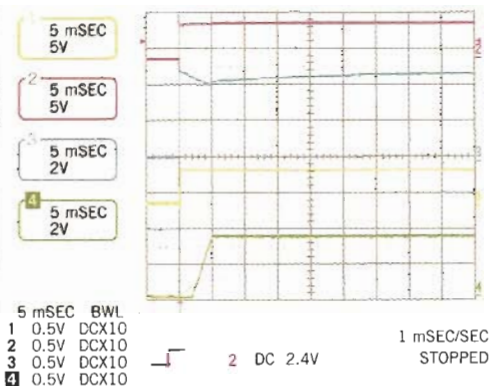

**Figure 2**

This circuit shows a normal start-up sequence for the circuit in Figure 1.

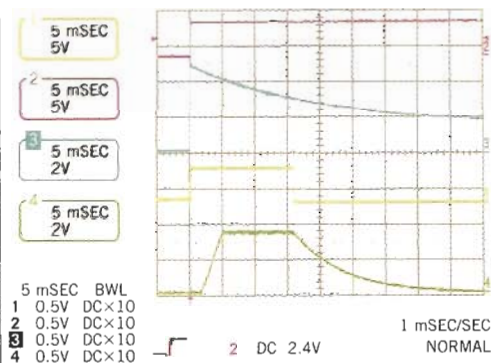

**Figure 3**

These traces represent start-up with the second output of a two-output regulator shorted.