

# HIGH-SPEED ELECTRONIC FUSE

*"Blows" within microseconds to protect sensitive components*

BY CHARLES M. LENNY AND CHESTER DAVENPORT

**FUSES**, in many cases, blow too slowly to prevent damage in solid-state circuits. Power transistors, which are prone to thermal runaway when passing excessive currents, are especially vulnerable to slow-opening fuses. The electronic "fuse" shown in the schematic is a basic crow-bar circuit that operates in a hundred microseconds or so—more than fast enough to save low-power transistors—and can safely handle load currents up to 60 amperes.

**How It Works.** When an overcurrent triggers *SCR1* into conduction, base drive is diverted from series-pass transistors *Q1* and *Q2*, which cut off and stop the flow of current to the load. Incandescent lamp *I1* has about a 10-ohm resistance when cold, and drops very little voltage. When *SCR1*

fires, the lamp glows, and the filament resistance increases to about 100 ohms, minimizing the load on *SCR1* and acting as an indicator to show that the circuit has tripped.


Potentiometer *R3* establishes the desired trip current. When the current passing through *R2* (and *R1* when *S1* is set to HI), exceeds the desired limit, transistor *Q3* turns on. The resulting positive voltage generated across *R5* turns on *SCR1*. Resistor *R6* limits the SCR gate current to a safe value. Diode *D1* permits operating the electronic fuse with an inductive load, removing any probability of punch-through of *Q1* or *Q2*.

**Construction.** At 60 amperes, resistors *R1* and *R2* can dissipate 45 watts each and should be provided with suitable heat sinking. A similar

heat sink should be used for *Q1*, *Q2* and *SCR1*. These two heat sinks should be mounted on two exterior sides of the selected chassis. A socket for *I1* can be mounted on top of the chassis. Input and output power connectors *S1*, and *R3* can be mounted on an empty side as desired. The Solitron SDT96306 can handle 70 amperes at 325 volts. A 2N3055 that can handle 15 amperes at 60 volts is an acceptable substitute.

Calibration of *R3* is performed by using various resistive loads to draw specific currents, with *R3* adjusted so that the lamp glows when the specific current is reached. A dial plate on *R3* is used to identify the calibration points. Remember that the trip current must be within the pass transistor's rating.

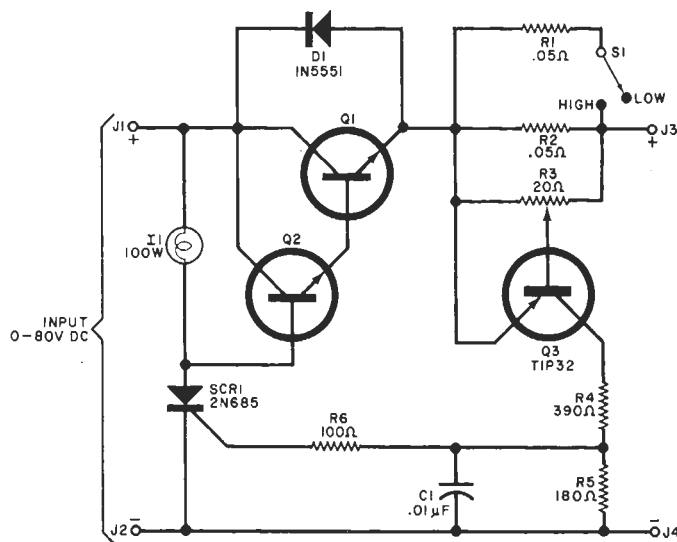Since the SCR is powered by dc, once it fires it will remain in the conductive state until the applied dc voltage is removed. This can be done either by installing a series switch in either of the supply leads or by turning off the driving power supply. ♦



## PARTS LIST

- |   |  |
|---|--|
| C1—0.01- $\mu$ F disc capacitor                     | R3—20- $\Omega$ , 5-W potentiometer  |
| D1—1N5551 diode                                     | R4—390- $\Omega$ , 10-W resistor   |
| J1 through J4—5-way binding post, color coded       | R5—180- $\Omega$ , 1-W resistor  |
| I1—100-W incandescent lamp                          | R6—100- $\Omega$ , 1/2-W resistor  |
| Q1, Q2—SDT96306 (70 amperes) or 2N3055 (15 amperes) | S1—Spst switch   |
| Q3—TIP32 or any silicon transistor                  | SCR1—2N685 or similar SCR  |
| R1, R2—0.05- $\Omega$ , 50-W resistor               | Misc.—Suitable heat sinks (2), socket for I1, enclosure, terminal strips, mounting hardware. |

