

THE  
**JIM WILLIAMS**  
P A P E R S


# Filters and oscillators

Filters get rid of a signal's unwanted frequency components. Oscillators create signals at predictable frequencies. As you might imagine, the two types of circuits have more than a little in common.

Jim Williams, *Linear Technology Corp*


**F**ilters and oscillators share a common point of view—they deal with signals in the frequency domain. You can define a filter's function as rejecting frequencies you don't want (the job of a band-reject filter, for example) or including only the frequencies you want (what a bandpass filter does). If you reorient your thinking slightly, though, you realize that all filters reject unwanted frequencies. (The bandpass filter rejects frequencies outside the band of interest.) When you view filters in this way, you see that any filter's function is the inverse of an oscillator's; oscillators synthesize individual frequencies or ranges of frequencies. Although there are more kinds of filters and oscillators than any magazine article of reasonable length can hope to touch on, herein are a few types of circuits that can meet a range of needs.

**Fig 1a** shows a highly selective bandpass filter using a resonant ceramic element and a single amplifier. Except at its resonant frequency, (in this case, 400 kHz) the ceramic element looks like a high impedance. For off-resonance inputs, IC<sub>1</sub> produces no output; it acts as a follower whose input is grounded. At resonance,

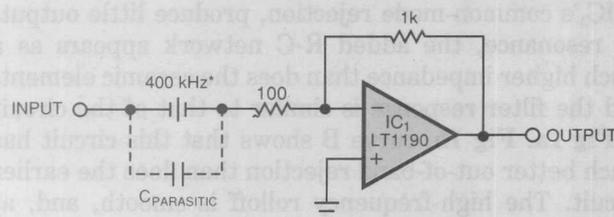

\*CERAMIC RESONATOR MURATA-ERIE CORP

(a)

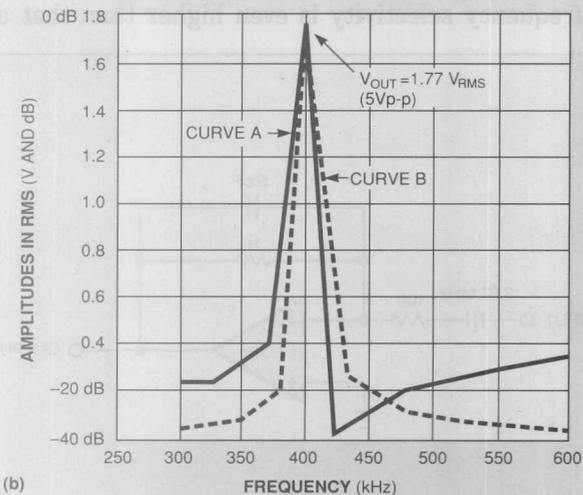


**Fig 1—One amplifier and a ceramic resonator create a bandpass filter (a). The solid curve of b shows the filter's frequency response. Note the dip to -40 dB on the high side of resonance. The dip is the result of the resonator's parasitic capacitance.**

# THE JIM WILLIAMS PAPERS

the ceramic element has a low impedance, and IC<sub>1</sub> behaves as an inverter with gain. The 100Ω resistor isolates IC<sub>1</sub>'s summing point from the ceramic element's capacitance. This capacitance is quite substantial and limits the circuit's out-of-band rejection. Fig 1b, curve A shows this effect. This plot shows very steep rejection, with IC<sub>1</sub>'s output down almost 20 dB at 300 kHz and 40 dB at 425 kHz. The device's stray parasitic capacitance causes the gentle rise in the output at higher frequencies and also sets the -20-dB floor at 300 kHz.

Fig 2 shows how to use a nulling technique to partially correct problems caused by the ceramic element's parasitic capacitance. This circuit is similar to the previous one, except that a portion of the input goes to IC<sub>1</sub>'s positive input. The R-C network at that input has an impedance close to the ceramic resonator's off-null impedance. Therefore, out-of-band components produce similar signals at IC<sub>1</sub>'s inputs, and, because of IC<sub>1</sub>'s common-mode rejection, produce little output. At resonance, the added R-C network appears as a much higher impedance than does the ceramic element, and the filter response is similar to that of the circuit in Fig 1a. Fig 1b, curve B shows that this circuit has much better out-of-band rejection than does the earlier circuit. The high-frequency rolloff is smooth, and, at 475 kHz, over 20 dB deeper than that of the circuit in Fig 1a. At 375 kHz and below, on the low-frequency side of resonance, the circuits behave similarly.

By using quartz crystals, you can make filters whose high-frequency selectivity is even higher than that of

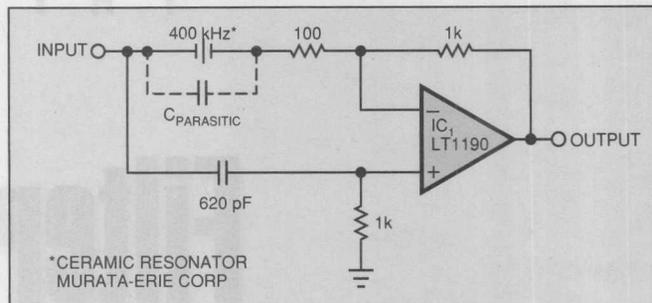


**Fig 2**—A slight modification of the circuit in Fig 1a allows you to cancel out the effects of the resonator's parasitic capacitance. The dashed curve of Fig 1b shows the effects on the filter response. Below resonance, the modified circuit attenuates by an extra 20 dB. Above approximately 525 kHz, the improvement is even more dramatic.

filters based on ceramic resonators. Fig 3a replaces Fig 1a's ceramic element with a 3.57-MHz quartz crystal. Fig 3b shows almost 30 dB of attenuation only a few kHz on either side of resonance! The differential nulling technique used with the ceramic elements is less effective with quartz crystals. Crystals have significantly lower parasitic capacitance, making the cancellation less effective.

### Oscillators use crystals and resonators

The circuit in Fig 4 places a crystal within the amplifier's feedback path, creating an oscillator. With the crystal removed, the circuit is a familiar noninverting amplifier with a grounded input. The impedance ratio of the elements associated with IC<sub>1</sub>'s negative input sets the gain. Inserting the crystal closes a positive

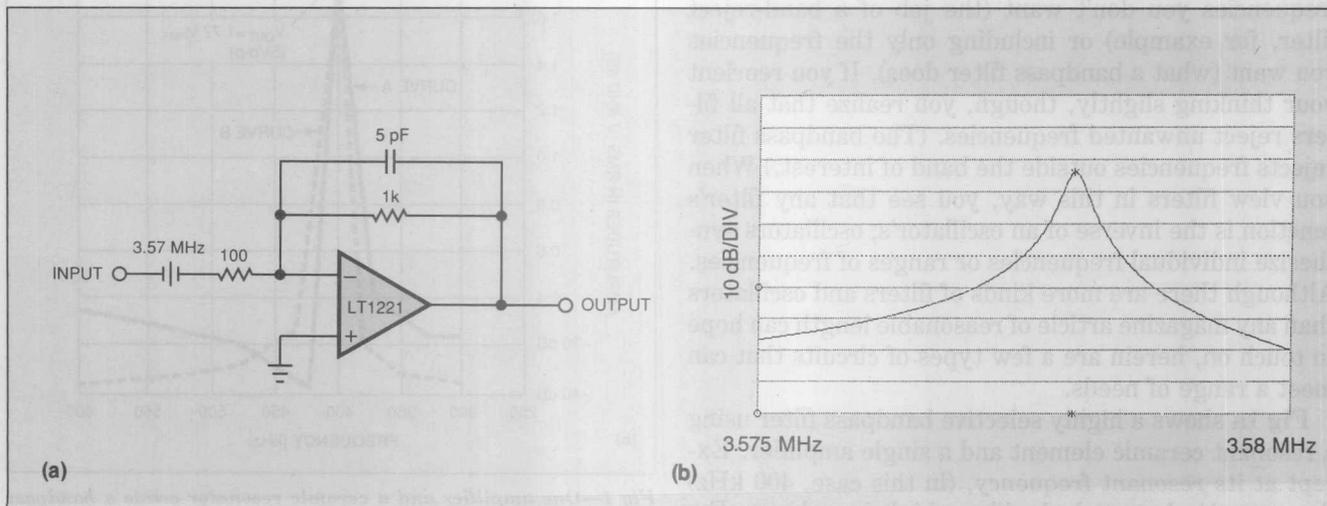

**Fig 3**—Replacing the ceramic resonator of Fig 1a with a 3.57-MHz crystal is the most significant change that leads to this crystal filter (a). You can see the crystal filter's response in b.




# THE JIM WILLIAMS P A P E R S

50 dB down, occurs at 60 MHz. Resolution bandwidth for the spectrum analysis is 1 kHz.

The circuit in Fig 6a replaces the quartz crystal with a Wien network at IC<sub>2</sub>'s positive input. IC<sub>1</sub> controls Q<sub>1</sub> to stabilize the amplitude of IC<sub>2</sub>'s oscillations. The operation is identical to that of the circuit in the previous figure. Although the Wien network is not nearly as stable as a quartz crystal, it has the advantage of a variable-frequency output. Normally, you vary the frequency by varying either R or C or both. The use of manually adjustable elements, such as dual potentiometers and 2-section variable capaci-

tors is common. The circuit in Fig 6a uses fixed, 360Ω Wien-network resistors and uses varactor diodes as capacitors. The varactor diodes' voltage-variable capacitance allows dc tuning of the oscillator. Applying 0 to 10V dc to the varactors shifts the oscillation frequency from 1 to 10 MHz. The 0.1-μF capacitor blocks the dc bias from IC<sub>2</sub>'s positive input but lets the Wien network function normally. IC<sub>2</sub>'s 2V p-p output minimizes the varactors' junction effects and thereby limits distortion.

This 5V-powered circuit requires a voltage step-up to develop adequate varactor drive. IC<sub>3</sub> and the

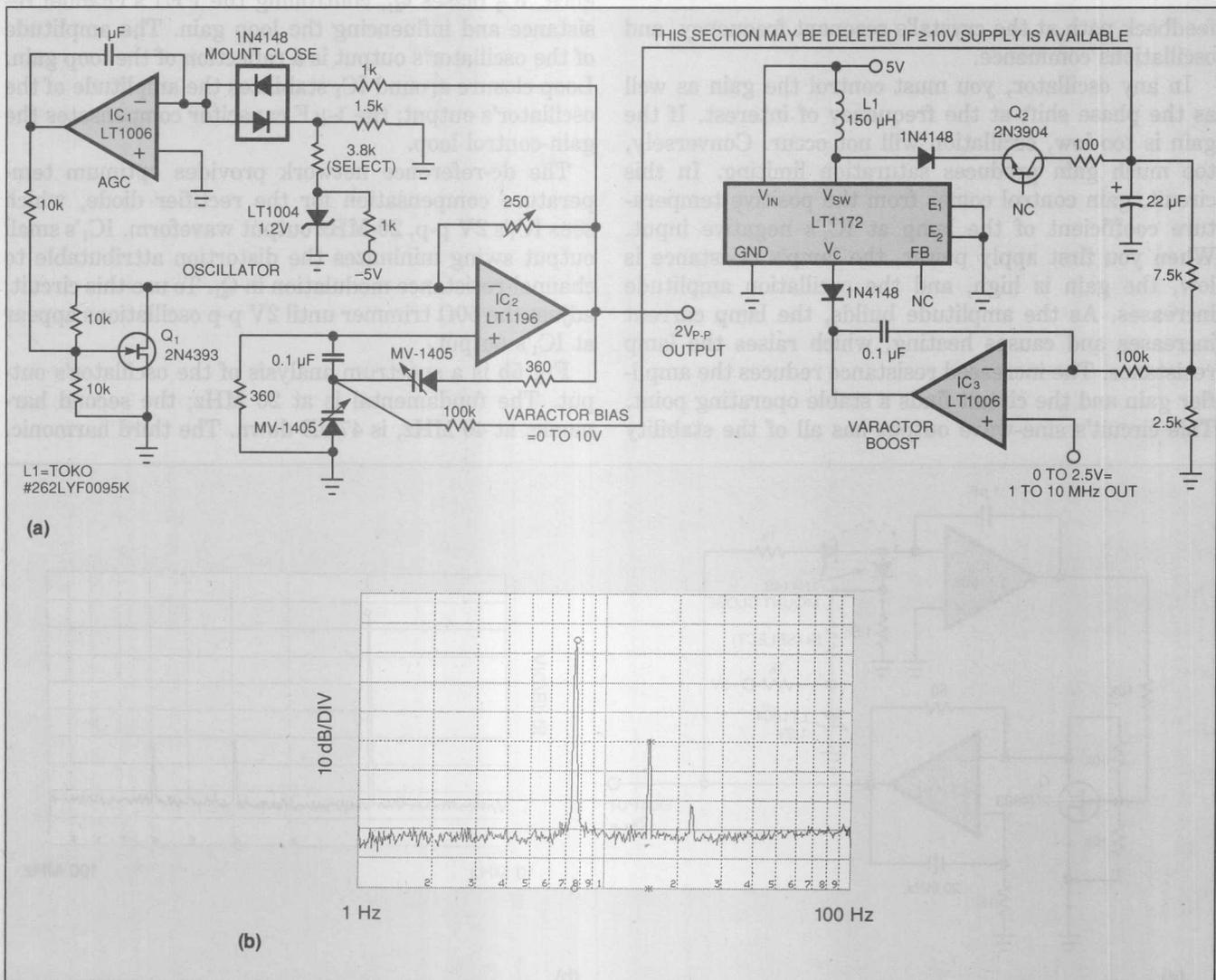

**Fig 6**—A pair of varactor diodes lets you tune this Wien-bridge oscillator (a) from 1 MHz to 10 MHz by applying a 0 to 10V signal. Adding the components in the right half of the schematic lets you operate the circuit from a 5V supply and permits controlling the frequency with a 0 to 2.5V signal. The spectrum analysis in b shows that the sinusoidal output is quite clean.

LT1172 switching regulator form a simple voltage step-up regulator. IC<sub>3</sub> controls the LT1172 to produce whatever output voltage is required to close a loop at IC<sub>3</sub>'s negative input. The 22- $\mu$ F output capacitor stores L<sub>1</sub>'s high-voltage inductive-flyback pulses after they have been rectified by the diode-and-zener-connected Q<sub>2</sub>. The 7.5-k $\Omega$ /2.5-k $\Omega$  divider closes the loop by providing a sample of the output value to IC<sub>3</sub>'s negative input. The 0.1- $\mu$ F capacitor stabilizes this feedback action. IC<sub>2</sub>'s zener drop allows the circuit to produce controlled outputs at voltages as small as zero. This arrangement permits a 0 to 2.5V input at IC<sub>3</sub> to produce a corresponding 0 to 10V varactor bias. Fig 6b, a spectral plot of the circuit running at 7.6 MHz, shows the second harmonic down 35 dB and the third harmonic down almost 60 dB. The resolution bandwidth is 3 kHz.

Fig 7a shows the schematic of an AM radio station—complete from microphone to antenna, but lacking a Federal Communications Commission license. IC<sub>1</sub>, set up as a quartz-stabilized oscillator similar to the one in Fig 4, generates the carrier. IC<sub>1</sub>'s output feeds IC<sub>2</sub>, which functions as a modulated RF power-output stage. The bias applied to offset pins 1 and 8 restricts IC<sub>2</sub>'s input-signal range. (See the LT1194 data sheet for details.) IC<sub>3</sub>, a microphone amplifier, supplies bias to the offset pins, resulting in an amplitude-modulated RF carrier at IC<sub>2</sub>'s output. The dc voltage summed with the microphone output biases IC<sub>3</sub>'s output to the appropriate level for good quality modulation characteristics. Calibrating this circuit involves trimming the

100 $\Omega$  potentiometer in the oscillator for a stable 1V p-p 1-MHz output from IC<sub>1</sub>.

Fig 7a does not show on-air personalities—or, in keeping with current trends in AM radio—a means of providing any kind of program other than a talk show. There is no phonograph pickup or connection to the output of a compact-disc player. Nevertheless, you can connect such a music source to the microphone input. Fig 7b shows a typical AM carrier output at the antenna. In a throw-back to the days when top-40 formats reigned on the AM band, the modulating signal is Mr Chuck Berry singing the rock-'n'-roll classic "Johnny B. Goode."

#### Start with a triangle; end up with a sine

The oscillators presented to this point have limited tuning-frequency range. Although the circuit in Fig 8a is not a true oscillator, it produces a synthesized sine-wave output over a wide dynamic range. Many applications such as audio, shaker-table driving, and automatic test equipment require voltage-controlled oscillators (VCOs) that have sine-wave outputs. This circuit meets this need, spanning a range of 1 Hz to 1 MHz (equal to 6 decades or 120 dB) for a 0 to 10V input. The circuit maintains 0.25% frequency linearity and 0.40% distortion.

To understand the circuit, assume Q<sub>5</sub> is on and its collector (Fig 8b, trace A,) is at -15V, cutting off Q<sub>1</sub>. IC<sub>3</sub>, which inverts the positive input voltage and biases the summing node of integrator IC<sub>1</sub> through the 3.6-k $\Omega$

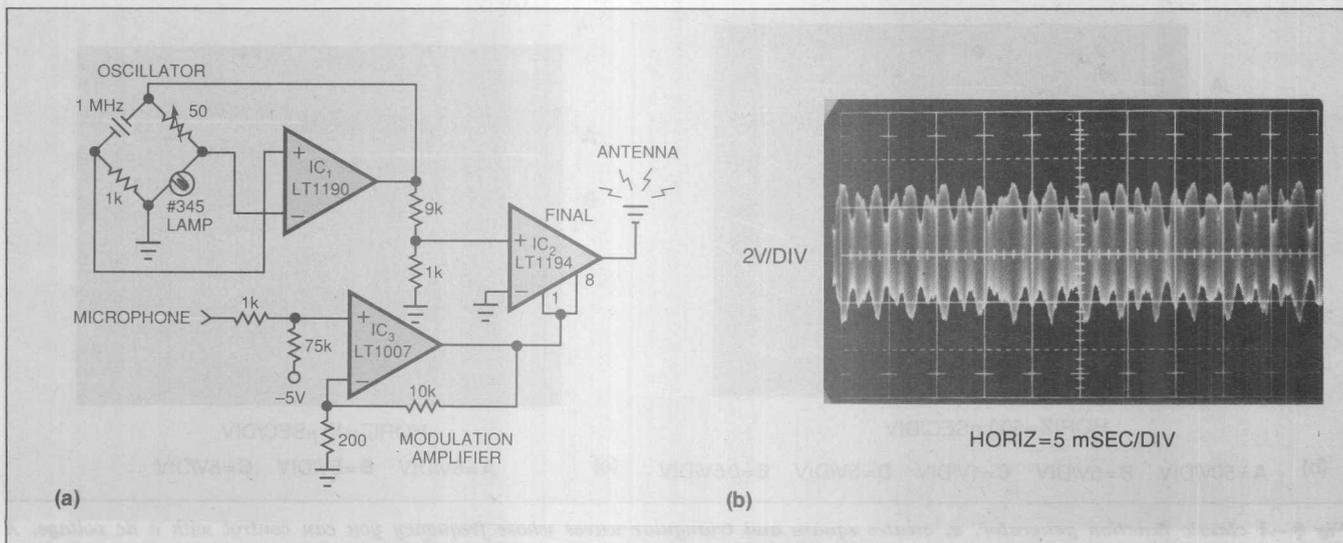



Fig 7—Though perhaps not worthy of Wolfman Jack or Dick Biondi, the circuit of a is still a complete AM radio station. When Chuck Berry picks his guitar and belts out "Johnny B. Goode," the modulated output looks like what you see in b.

# THE JIM WILLIAMS P A P E R S

resistor and the self-biased FET's, pulls a current,  $-I$ , from the summing point. IC<sub>2</sub>, a precision op amp, provides dc stabilization of IC<sub>1</sub>. IC<sub>1</sub>'s output, (trace B,) ramps positive until IC<sub>5</sub>'s input, (trace C,) crosses zero and causes IC<sub>5</sub>'s inverting output to go negative. The Q<sub>4</sub>/Q<sub>5</sub> level shifter then turns off, and Q<sub>5</sub>'s collector goes to +15V, allowing Q<sub>1</sub> to come on. The values of

the resistors in Q<sub>1</sub>'s path result in a current,  $+2I$ , exactly twice the absolute magnitude of the current,  $-I$ , that flows out of the summing node. As a result, the net current into the junction becomes  $+I$ , and IC<sub>1</sub> integrates negatively at the same rate it did during its positive-going excursion.

When IC<sub>1</sub> integrates far enough in the negative di-

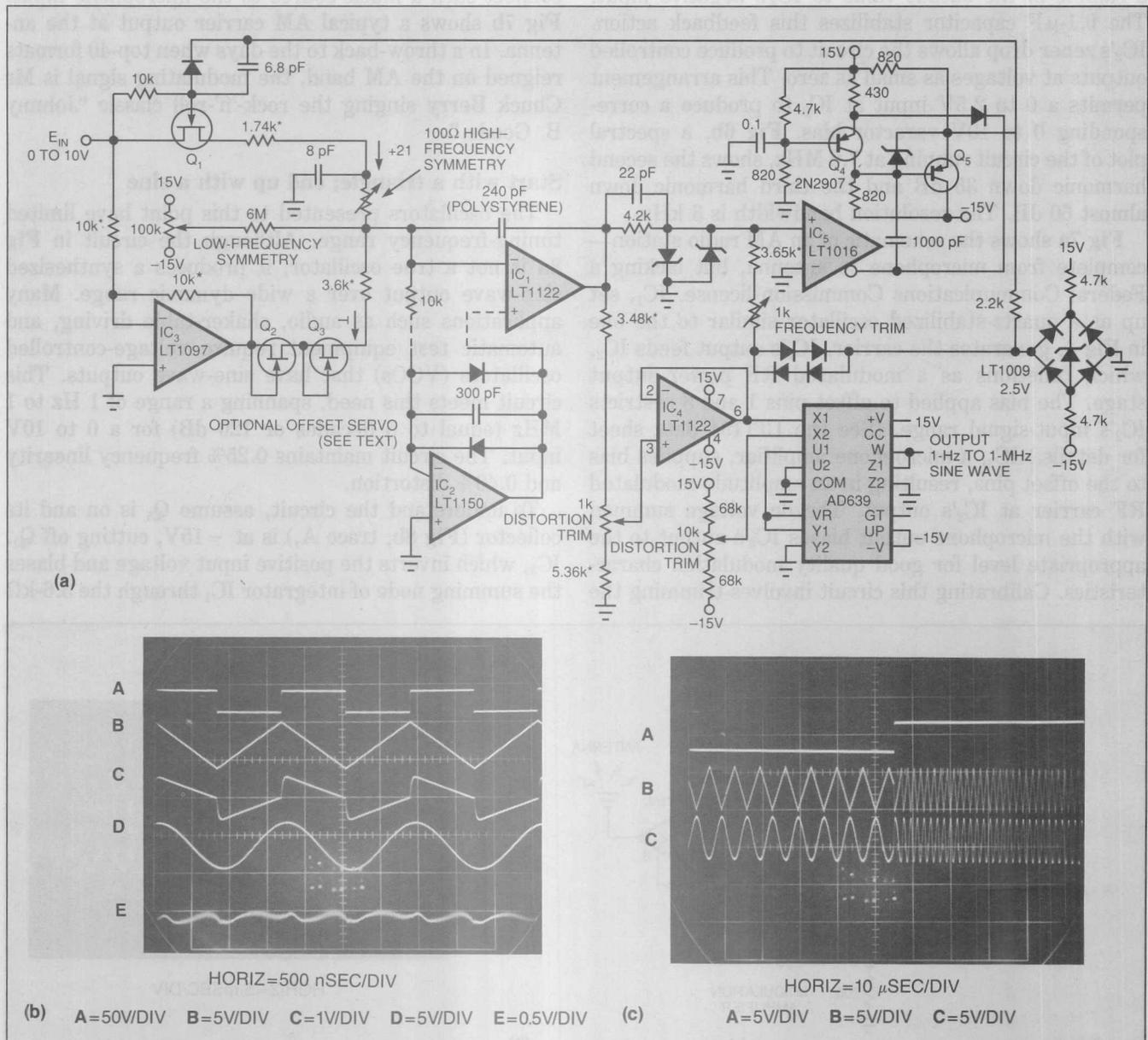

**Fig 8—A classic function generator.** a, creates square and triangular waves whose frequency you can control with a dc voltage. A trigonometric-function generator IC converts the triangle to a sine. The traces in b show waveforms within the circuit. The lowest trace shows the residual distortion after you remove the output's fundamental-frequency component. In c, you see the circuit's quick and clean response to a command to change frequency.

THE  
**JIM WILLIAMS**  
P A P E R S

rection,  $IC_5$ 's + input crosses zero and the circuit's two outputs change state. The state change switches the  $Q_4/Q_5$  level shifter's state, causing  $Q_1$  to go off and the entire cycle to repeat. The result is a triangular waveform at  $IC_1$ 's output. The frequency of this triangle depends on the circuit's input voltage and varies from 1 Hz to 1 MHz with a 0 to 10V input. The LT1009 diode bridge and the series-parallel diodes provide a stable bipolar reference that always opposes the sign of  $IC_1$ 's output ramp. The Schottky diodes bound  $IC_5$ 's + input, ensuring its clean recovery from overdrive.

### Sine of the times

The AD639 trigonometric function generator, biased via  $IC_4$ , converts  $IC_1$ 's triangular output into a sine wave, (trace D). To avoid output distortion, you must supply the AD639 with a triangular wave that does not vary in amplitude. At higher frequencies, delays in the  $IC_1$ -integrator switching loop result in late turn-on and turn-off of  $Q_1$ . Unless you minimize these delays, the triangle amplitude will increase with frequency and cause the distortion level to increase.  $IC_5$ , the  $Q_4/Q_5$  level shifter, and  $Q_1$  generate a total delay of 14 nsec. This small delay, combined with the 22-pF feed-forward network at  $IC_5$ 's input, keeps distortion to just 0.40% over the entire 1-MHz range. At 100 kHz, the distortion is typically less than 0.2%. The 8-pF capacitor in  $Q_1$ 's source line minimizes the effects of gate-source charge transfer, which occurs whenever  $Q_1$  switches. Without this capacitor, a sharp spike would occur at the triangle peaks, increasing distortion. FETs  $Q_2$  and  $Q_3$  compensate for the temperature-dependent on-resistance of  $Q_1$  and keep the +2I/-I relationship constant with temperature.

This circuit responds very rapidly to input changes—something most sine-wave generators cannot do. Fig 8c shows what happens when the input switches between two levels, (trace A).  $IC_1$ 's triangle output (trace B), shifts frequency immediately, with no glitches or poor dynamics. The sine output, (trace C), reflecting this action, is similarly clean. To adjust this circuit, apply 10.00V and trim the 100 $\Omega$  potentiometer for a symmetrical triangle output at  $IC_1$ . Next, apply 100  $\mu$ V and trim the 100-k $\Omega$  potentiometer for triangle symmetry. Then, apply 10.00V again and trim the 1-k $\Omega$  frequency-trim adjustment for a 1-MHz output frequency. Finally, adjust the distortion-trim potentiometers for minimum distortion as measured on a distortion analyzer (Fig 8b, trace E). You may have to readjust the other potentiometers slightly to achieve the lowest



possible distortion. If you won't operate the circuit below 100 Hz, you can delete the  $IC_2$ -based dc-stabilization stage. If you make this change, you should ground  $IC_1$ 's positive input.

Many of the filter and oscillator circuits presented here are simple as well as useful. Their simplicity shows that clever circuit designers often take a minimalist approach. When you speak or write, you are more likely to get your point across if you use short words that are familiar to your audience. So it is with circuits. The simplest design that does the job usually costs the least and operates more reliably than complex alternatives. **EDN**
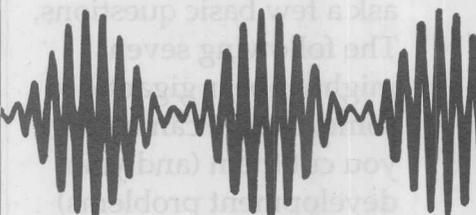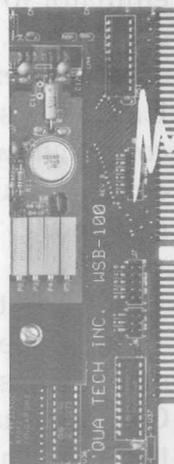
### Author's biography

For more information on this article's author, turn to pg 163 in the October 10, 1991, issue.

Article Interest Quotient (Circle One)  
High 494 Medium 495 Low 496



**WSB-100 Waveform Board:**  
**20MHz/32K**  
**\$1290**

The WSB-100 waveform synthesizer offers speed and memory at a price that's half what you'd expect to pay.

With its analog module, the WSB-100 becomes a 12-bit waveform board for the PC-AT and compatibles that can be used in a wide range of testing and control applications. Multiple boards can be connected to store longer waveforms or to run several waveforms simultaneously.

Optional modules enable the WSB-100 to act as a digital pulse generator or 16-bit word generator.

A 10 MHz/32K configuration is available at an even lower price.

Call for our free  
Interface Handbook:  
**1-800-553-1170**



662 Wolf Ledges Parkway  
Akron, OH 44311

PC-AT is a registered trademark of IBM Corp.

CIRCLE NO. 239