

Library 12

Jensen & John Hardy



Menu


[\[Page 1\]](#)[\[Page 2\]](#)[\[Page 3\]](#)[\[Page 4\]](#)[\[Page 5\]](#)
[\[Page 6\]](#)[\[Page 7\]](#)[\[Page 8\]](#)[\[Page 9\]](#)[\[Page 10\]](#)
[\[Page 11\]](#)[\[Page 13\]](#)[\[Page 14\]](#)[\[Page 15\]](#)[\[Page 16\]](#)

[\[Home\]](#)


990 operation amplifiers of 1980's.



JE-990

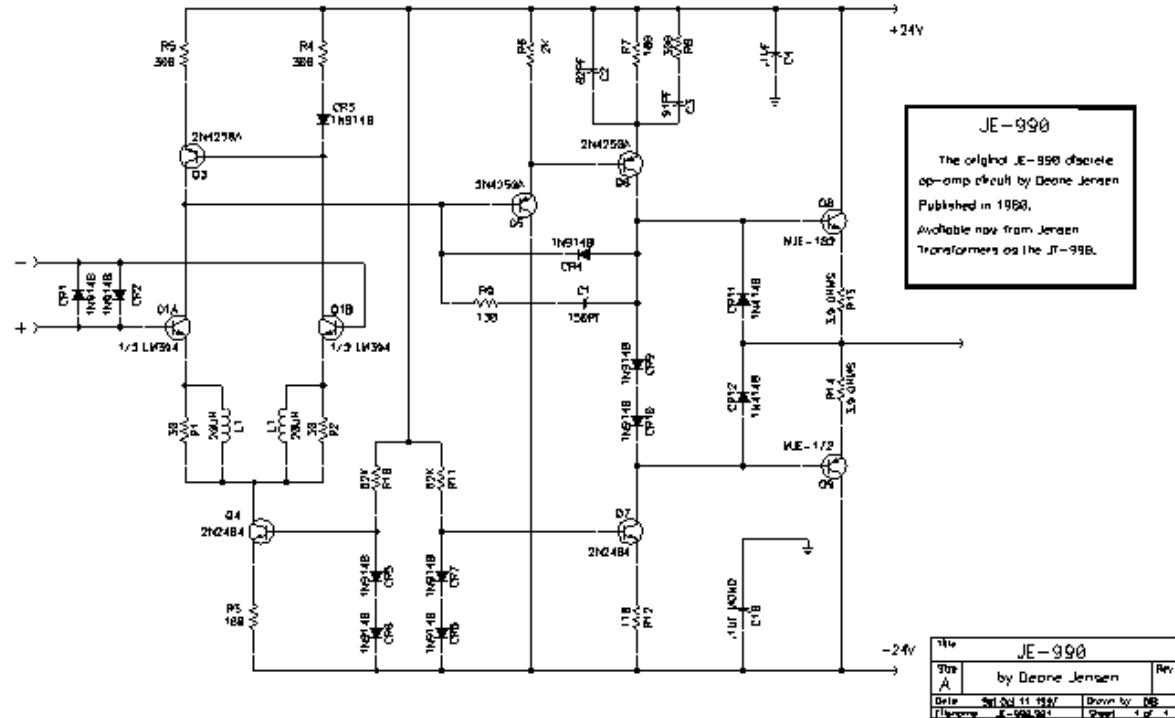

JE-990-1

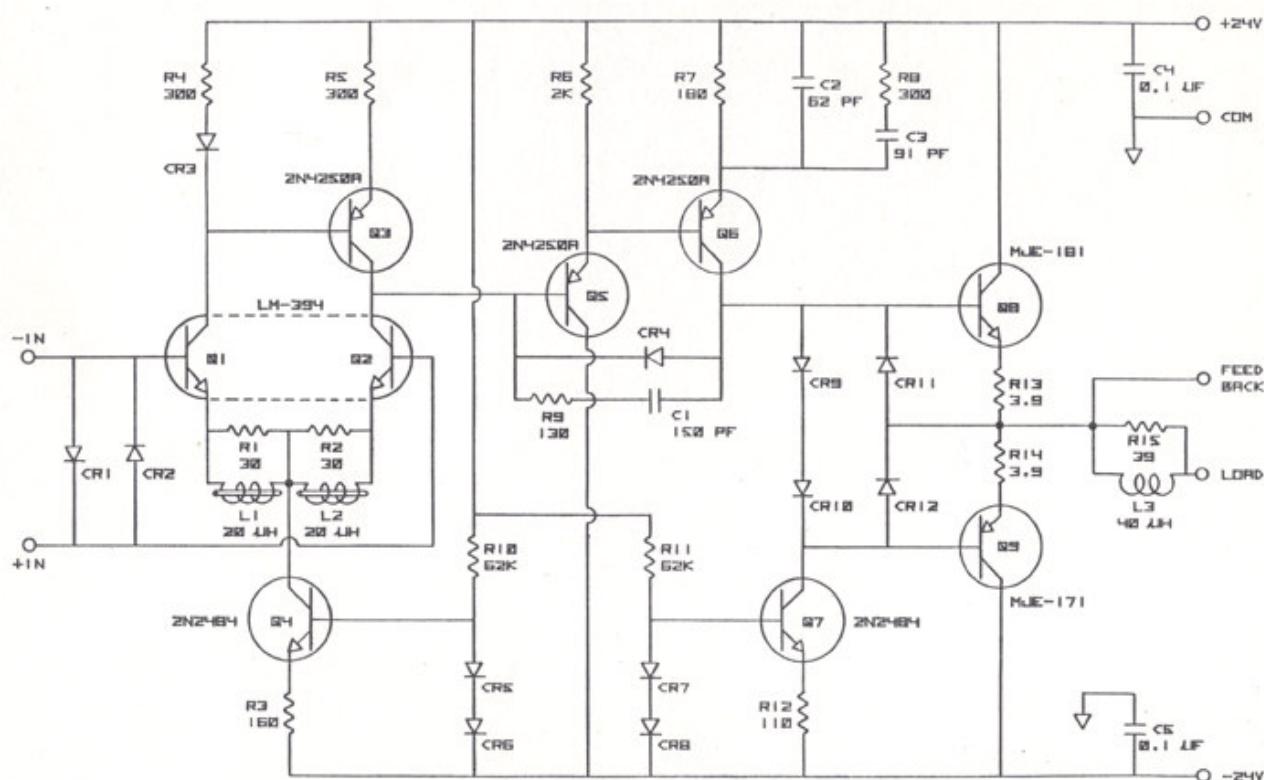

990 OPERATIONAL AMPLIFIER

JE-990-2

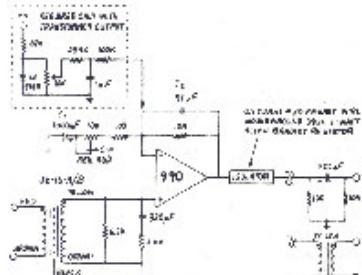
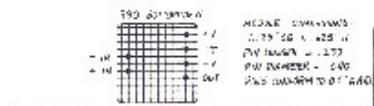


FIGURE 1: MICROPHONE PREAMPLIFIER

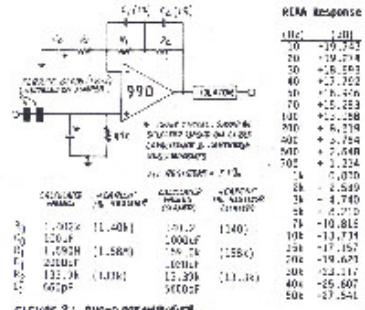


FIGURE 2: RADIO PREAMPLIFIER

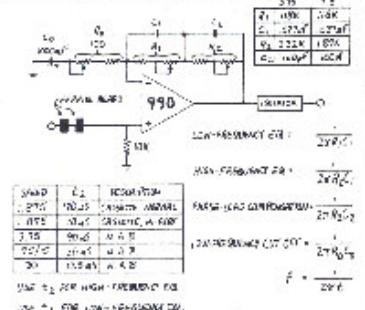


FIGURE 3: TAPE-HEAD PREAMPLIFIER

THE JOHN HARDY CO.

1720 Diamond St. • Eugene, OR 97401 USA
P.O. Box AAG3 • Eugene, OR 97404 USA
Phone 541-345-8000

APPLICATION NOTES

FOLLOWING ARE SEVERAL CIRCUITS FOR USE WITH THE 990 DISCRETE OPERATIONAL AMPLIFIERS. WITH THE PROPER ATTENTION TO DETAIL, YOU SHOULD ACHIEVE EXCELLENT RESULTS.

MICROPHONE PREAMPLIFIER

Figure 1 shows a traditional transformer-input microphone preamplifier. The complete circuit is adjustable from 1.0 to 40.0 dB of gain, including the transformer ratio of 5.5 dB, with a bandwidth of 10 Hz to 10 kHz. The Jensen JE 16-A2-B microtransformer has become a favorite for the 990. It is used in one of the offshoots of the 990 constant current source. The offshoot uses a 100 ohm resistor to provide a 100 picofarad charge at the 50V DC offset. This adjustment, being an inverting stage, will also change the DC resistance to ground with the non-inverting input as a new reference. Since 100 picofarads develop 10 millivolts at the input sites (currents flow through nonlinear 100 millivolt paths) the voltage across a millivoltmeter at 100 picofarads, they will be 10 mV. The output of the 990 is a 100 millivolt signal whose value is determined as the difference between the two inputs, with different DC resistances at the inputs, with 100 millivolts at the inverting input. If 100 picofarads, 100 millivolts at 100 millivolts at the inverting input (charge (assuming the 20 offshoot to change), but the circuit uses 100 millivolts gain at 100 millivolts gain instead of going down to 10 millivolts at 100 millivolts gain).

The stage is followed by a 100 millivolt differential amplifier. The stage regulator also biases the input capacitor at the inverting input which compensates for the unequal DC resistances seen at the inputs. The offset voltage at each input is found by multiplying the input bias current (10.0 uA) by the DC resistance of the anti-transformer secondary, multiplied by 100 ohms by the 100 millivoltmeter. For the inverting input, the 100 millivoltmeter is the only DC path. Since the closed-loop DC gain of the amplifier is unity, the offset at the output is equal to the difference of the offset voltages at the two inputs. The compensation current required into the inverting input is 100 millivolts divided by the feedback resistance (100 ohms). Thus the offset compensation will significantly reduce the offset at the output for those applications without an output coupling capacitor.

To provide the proper phase-linear compensation with a high-frequency cutoff of 175 kHz,

The use of a capacitor in series with the compensation as a means of obtaining the offshoot is traditional. So too is the use of an output capacitor to obtain a flat response. For additional information on these capacitors, please see the separate article "MICROPHONE PREAMPLIFIER WITH ZERO CONTROL OF DC OFFSET", found later in these notes.

PHONO PREAMPLIFIER

Figure 2 shows a simple phono preamp with related component values and mathematical RERA response figures. The circuit will result in extremely accurate RERA response, typically better than +/- 0.1 dB, provided the values and tolerances are as indicated. The values are taken from Figure 3 above or from Figure 1 which thoroughly covers RERA calculation methods and their design. For specific design information, formulas, etc., refer to that paper.

Figure 1 shows the exact calculated bias stage and component values as listed in the paper, with the closest 1% resistor values shown in parentheses. Figure 2 shows these values scaled by a factor of 1/2, to take advantage of the increased noise figure of the 990 at these source impedances.

To AC-couple, the input biasing DC bias to be unity. It could be coupled out of the compensation network. See "TWO-CHANNEL PHONO PREAMPLIFIER" for more details.

The tone controls at the input are optional to reduce RFI.

The circuit sets in approximately 41.7 dB at 1 kHz. Any changes or component values should be carefully evaluated based on the original paper.

REFERENCES

1. JOURNAL OF THE RADIOTELEVISION SOCIETY, Journal, Audio Engineering Society, Vol. 71, No. 6179, Pt. 458-461.

TAPE HEAD PREAMPLIFIER

Figure 3 shows a basic head preamp. The component values for 3.75 and 7.5 mils. tape width are given in parentheses. These values and equivalent circuits are easily obtained using the formulas provided. Gain and select frequencies and characteristics vary widely, so the values listed will probably require retuning, and the final results should be carefully examined for any irregularities.

Inputs with extremely low output levels will require additional gain, and a low-cut filter should be considered for test purposes. The low-cut filter parts (C1, R1) should be set for 400 Hz at 20 dB down at high frequencies (10 kHz).

This circuit is very similar to the RERA phono review, except that this one is tunable, and the RERA numbers (3.75 at 200 ohms performing the phase-shift network rather than the critical RERA equalization function. See "PHONO PREAMPLIFIER" for comments on tape ferrite heads).

JE-990-3


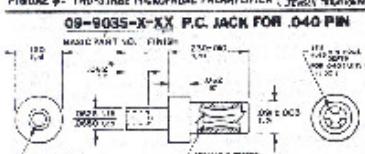
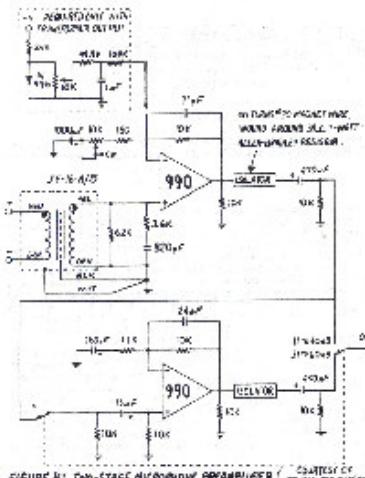


FIGURE 5: SOCKET FOR .040 PIN

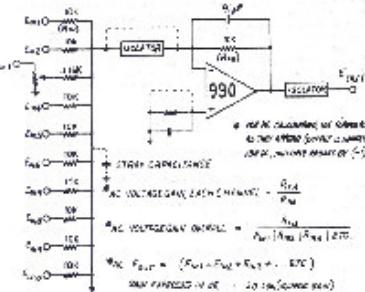

THE JOHN HARDY CO.

1125 Burwell St., Evanston, IL 60206 USA
P.O. Box AKESI, Evanston, IL 60204 USA

Phone 847/864-8088

TWO STAGE MICROPHONE PREAMPLIFIER

Figure 4 shows a two-stage transistor coupled microphone preamplifier. It is recommended for situations where extremely high gain is required. The biasing is essentially that of the single-stage preamp of Figure 3, except the second stage has a higher current. This allows the second stage to provide a choice of single-stage operation, up to +3 dB of total gain, or double stage operation with up to +10 dB of total gain. The 2nd stage could be changed from fixed to variable gain; ideally, each stage would have the same amount of gain in the open-gain amplifiers, and a variable 2nd stage would provide a choice of +3 dB of total gain, as determined by the single-stage switch. Note that the 2nd stage will have a low Z_{out} because the inverting and non-inverting inputs are taken off the source resistors (100Ω).

SOCKETS

Two types of sockets are available from several manufacturers. A common socket is shown in Figure 5, reprinted from the Burson catalog. The same part is available from Carbone as well. This socket is available from stock from the Hardy Co. (see the parts list).

This particular socket may be soldered in place, or snaged (special tool required).

CARBONE ELECTRONICS CORP. (1022) 214-3574
30 Great Jones St.
New York, NY 10003 Part #20-3185-2-02

CARBONIC
485 Congress Ave.
Carbridge, MA 02338 Part #40-2755-02-03

A good selection of sockets is also available from:

BURSON MFG. INC. (1022) 245-0201
900 E. 8th St.
New Albany, IN 47150

SUMMING AMPLIFIER

Figure 6 shows a summing amp with several optional features. Some applications require signals to be combined at unity gain, others require different gains. For example, the signal of channel 3 is attenuated by a potentiometer (typically 10 to 40 dB of attenuation) just before it enters the summing circuit. To restore the 10 to 40 dB through the pot, a lower value is used for R₃, in this case 100Ω, which then changes before the summing junction. Thus, the overall response signal at the output of the summing amp would become inaccurate, resulting in treble/bass失真. The ideal value for R₃ would therefore be lower than the number of channels, signal levels, and settings, etc.

The non-inverting input may be grounded directly, or through a resistor. The value of the resistor should not be too large, as indicated by the following table, which gives the approximate value of all the input resistors. The inverting input, which has no advantage of all the input resistors, has a noise resistor (R₁₀) and R₉. With both inputs of the 990 having identical DC source resistances, the total offset voltage will be the lowest. This resistor can result in increased noise when compared to a directly terminated input. This problem can be overcome by adding a capacitor in parallel with this terminating resistor. The value of the capacitor should be approximately 10 pF. The terminating resistor is the only resistor in the input stage that is terminated. The influence of the capacitor becomes much lower than that of the terminating resistor since 10 pF is 10 times the noise performance of the 990, so it is not significantly detrimental. The value of the capacitor will depend on the noise performance of the type of opamp being used, number of channels being summed, noise limitations of the channel being summed, etc.

With direct input termination, a smaller value is better for the non-inverting input is critical. If larger capacitors with many losses, there can be much noise appearing in the ground bus, since even a heavy ground bus will have a small air-resistance noise source, with voltages appearing across the resistance. These voltages can be in the form of power-supply noise, return currents from balanced feed-back loops, etc. In this case, the noise of the summing amp may be an unity gain. The overall result of the summing amp is dependent on the total parallel resistance of all the input resistors (or the value of R₃). If the gain formula is, for example, 25 times with R₃ of 100 ohms, the value of R₃ is 4.17 ohms, for a voltage gain of 24.326 (4.16 dB). That is, even though the ground bus noise would be amplified if the non-inverting input were terminated for three, the signal current would increase according to $\sqrt{3}$.

Larger values of feedback capacitors usually result in slow response. It appears that the inverting input, whose capacitance causes phase-shifting in the feedback signal, yet is sufficient quantities, can cause oscillation. Additional capacitance can be used in the feedback loop to compensate. Also, an isolator (normally just at the output of the 990) could be inserted between the inverting bus and the inverting input, with the isolator as close to the inverting input as possible. The isolator has an inductance of 1.2 ohms at 100 Hz, current only 5 ohms at 100 kHz, so the audio bandwidth passes through relatively unaffected. Above 100 kHz, the impedance is 33 dB/oct, reducing the effects of the stray capacitance.

JE-990-4

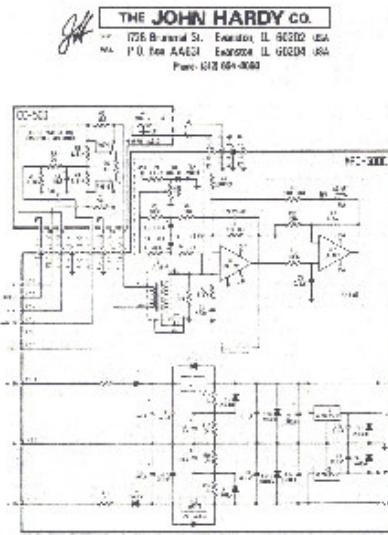


FIGURE 7a MPC-500C Mic-Preampl Card & QI-500 Control Card

MICROPHONE PREAMPLIFIER WITH SERVO CONTROL OF DC OFFSET

Figure 7 shows a single stage microphone preamplifier with a special servo circuit, input bias current compensation circuit, and balanced power supplies. The circuit is similar to the preamplifier shown in Figure 1, except that the servo circuit has been added to the circuit to allow for remote control of the DC performance of the circuit, making it possible to eliminate the gain-set resistor and output coupling. This results in a substantial improvement in audio quality since even the best film capacitors are compromised.

As discussed in the earlier application note, VARIABLE STAGE SEPARATION PREAMPLIFIERS provide significant advantages in the design of servo-controlled DC offset cancellation systems. The servo parameter T_s in Figure 4 would cause changes in the DC offset of up to 50 mV. Other offsets result from drift due to time and temperature. A capacitor in series with the output is often used to keep these various offsets from reaching the outside world.

With the servo approach, the LM113 can monitor the output of the 990. In the presence of any DC offset, it provides a corrective voltage to the input of the 990, which reduces the DC offset of the 990 to within the DC offset limits of the LM113.

There are two capacitors (polypropylene) in the servo circuit, but the only signal that is affected by these capacitors is the ultralow frequency and DC currents. These capacitors are working in their respective resistors as a very-low-frequency low-pass resistance. Essentially, the signal that passes through the servo circuit is the DC offset. In this case, the servo feedback is coupled in antiphase. The servo keeps the DC offset of the preamp circuit well below 1 mV under servo conditions.

The LM113 was chosen as the servo op-amp because it has exceptional DC characteristics, with a typical offset voltage of 0.2 mV and a drift of 0.02 mV per degree centigrade of temperature change. Since the servo system only sees extremely low frequency signals, it does not need a high slew rate.

An input bias current compensation circuit is also shown. It performs two important functions. First, it nulls the small DC voltage that appears at the inputs of the 990 due to the normal flow of input bias current. This eliminates the noise that would occur during gain-set pot adjustments, caused by DC voltage shifts at the pot. Second,

since the input bias current is compensated for and the DC voltages at the inputs are nulled, the DC offset of the 990 will no longer change as the gain pot is moved. Without this circuit, the offset of the 990 could shift as much as 10 mV during a gain-set adjustment, depending on the bias voltage. The source follower provides a high input bias current and DC offset of the individual 990. It is important to note that the servo circuit would still reduce the bias current to less than 1 mA in just a few seconds, but the bias compensation circuitry eliminates these statics and corrections. The servo circuit's only task is to do 200 mV with a 10 mV input offset of the 990. The trim pots adjustment procedure for the 990 bias current compensation circuit is shown. The pot of 1MΩ/1000 ohms provides a reference voltage of 0.3 volts. The 10K trimmer adjusts this voltage and applies it to the inputs of the 990 as a current through the 10K resistors. The total source-follower compensation set is bias-free to remove noise from the compensation circuit.

Figure 7 shows the complete circuitry of the MPC-500C mic-preampl card and the QI-500 control card, referred to as the MPC-500C series console. Both cards are available from the Party Co. The MPC-500C assumes two sets of values for some of the parts. The first values shown are those used in the stock MPC-500C card, and are chosen for compatibility with the 10K gain-adjust pot in the MCL tuners. The second set of values is for the 100K gain-adjust pot in the MCL tuners. The 100K gain-adjust pot is not recommended for use with the MPC-500C, as it is an inexpensive off-the-shelf, no-name version of the MPC-100C. It is available. The QI-500 is intended to be available in MCL-compatible and non-MCL versions, making conversion of the MCL consoles possible. The unique feature values of the stock MPC-500C (and the preamp of Figure 7) are as follows: trim pot is set to 100 mV, the value of the 10K trimmer is 1000 ohms, and the 10K trimmer is set to 0.3 mV. The 10K trimmer is set to 0.3 mV to prevent the trimmer from becoming too great. Elimination of this trimmer removes these restrictions, making the user more comfortable.

The complete power supply as shown on the MPC-500C card is excellent for any audio application. There are actually two sets of regulators. The first set of LM117 and LM327, across the ±12 volt supplies of the 990, provides down to 100 mV voltage drops by the 990. The second set of LM117 and LM327 provides a ±12 volt supply voltage for the LM113, which is rated at a maximum of ±20 VDC. The 2nd set of regulators can be eliminated by using the 990-113 or 990-114, or setting the main regulators at the appropriate lower voltage. However, currents would be reduced by as much as 4 dB due to the reduced current available to the 990.

The power supply or chain requires a minimum of +10 VDC for proper operation and to the individual differential input of the 317/333 regulators and the voltage drop of the 25 ohm resistors [R13 and R15]. These resistors provide more effective filtering, but can blow if either supply is shorted to ground. Alternatively, they can be eliminated.

The LM117/LM327 regulators are similar to the conventional 7810/7910 or 7805/7905 linear regulators, but offer improved performance in a number of areas. There are several classes used in the circuit. The input diodes protect the regulators from reverse polarization. The balance of the diodes protect the regulators and us-ams from various possible destructive sources. These diodes are absolutely required. To completely eliminate the diodes, contact component part numbers, etc., consult the manufacturer's data sheets.

The LM117 and LM327 regulators are available from National Semiconductor and Texas Instruments. The 7810/7910 are common items available from several different manufacturers. The LM113 op-amp is available from Texas Instruments and Motorola. These are servo op-amps. For complete details, a good reference is an article by Brian Clark in *The Microphone Handbook*, page 37982. Contact The Austin Amateur, P.O. Box 576, Peterborough NH 03682.


ADJUSTMENT PROCEDURE: A DC voltmeter with 0.1 mV resolution or better is required. The LM113 input is a precision 25-turn device.

1. Align the MPC-500C so none of its trimmers are set to the "MAX" position.
2. Turn the slide switch (SW1) on the MPC-500C to the "MAX" (bottom) position.
3. Connect the DC voltmeter to the output of 990, at the output connector.
4. Measure and record the DC offset of the 990 with the gain set about 12. Maximum, that is.
5. If the bias compensation trimmer is correctly adjusted, the two measurements you just made will be equal (within 1 mV of each other). The measurements could be as much as 100 mV or more, as long as they are equal. Adjust the trimmer and repeat steps 4 and 5 until the measurements are equal. When they are, the input bias current of the 990 has been completely eliminated.
6. Now, turn the 10K trimmer to the "MIN" position. The LM113 will quickly null the remaining DC offset to less than 1 mV, and this offset will remain there even during extreme adjustments of the gain pot. If the compensation trimmer were out of adjustment, the DC offset of the 990 could potentially go as high as 100 mV during extreme gain adjustments (maximum to minimum, or vice versa). Even then, the LM113 would null that offset to less than 1 mV in a couple of seconds.

JE-990-5

NOTES:

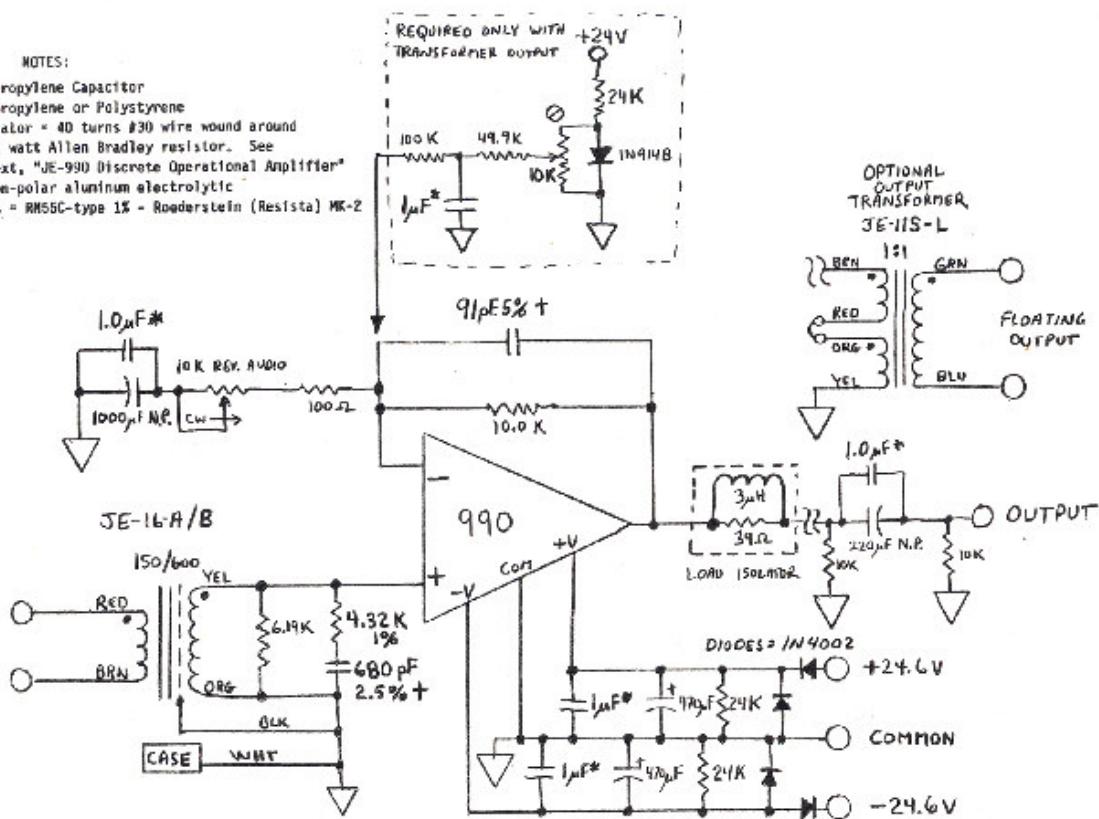1. * = Polypropylene Capacitor
2. + = Polystyrene or Polystyrene
3. Load Isolator = 40 turns #30 wire wound around 39 Ohm, 1 watt Allen Bradley resistor. See Jensen Text, "JE-990 Discrete Operational Amplifier"
4. N.P. - Non-polar aluminum electrolytic
5. Resistors = RM55C-type 1% - Roederstein (Resista) MK-2



SIMPLE MICROPHONE PREAMP WITH OFFSET COMPENSATION & 12 TO 45 dB ADJUSTABLE GAIN
REV. 3-20-84

JE-990-6

JENSEN TWIN SERVO MICROPHONE PREAMPLIFIERNOTES

1. *Capacitors = $\pm 10\%$ polypropylene or polycarbonate
2. +Capacitors = $\pm 2.5\%$ Polystyrene or Polypropylene (Mallory SXM Series or equal)
3. Resistors are RN55C-type 1% metal film; Roederstein (resista) MK-2 preferred
4. All diodes = 1N4002 unless marked otherwise
5. Servo amplifier = LM11C
6. +18 Volt Regulator = LM317L
7. -18 Volt Regulator = LM337L
8. Trimpots = Multiturn Cermet, Bournes 3006P or 3299 series or equal
9. Load Isolator = 40 turns of #30 Magnet wire around a 39 ohm, 1-watt Allen Bradley resistor.
10. Gain Adjust = Reverse Audio taper, dual, 1K conductive plastic potentiometer
11. **100 Ohm 2 Watt Metal Film Roederstein (Resista) MK-8 Preferred

CAUTION


Protect speakers from damage due to preamp's turn-on and turn-off D.C. transients. Use A.C. coupling or A.C. operated relay to prevent catastrophic "thumps".

Adjustment Procedure

1. With all 3 jumpers to dotted line position, bring 990's to operating temperature before adjusting bias.
2. Monitor TP1 and adjust 'Amp 1 Bias Trim' for minimum offset change between minimum and maximum preamp gain.
3. Connect Jumper 1 to solid line position, and adjust 'Servo 1 Offset Trim' for 0 μ V offset.
4. Monitor Output and adjust 'Amp 2 Bias Trim' for minimum offset change between minimum and maximum preamp gain.
5. Connect Jumper 2 to solid line position. Slightly readjust 'Amp 2 Bias Trim' if necessary for minimum offset change between minimum and maximum preamp gain.
6. Connect Jumper 3 to solid line position and adjust 'Servo 2 Offset Trim' for 0 μ V offset at preamp output.

REV 10-15-84

JE-990-7

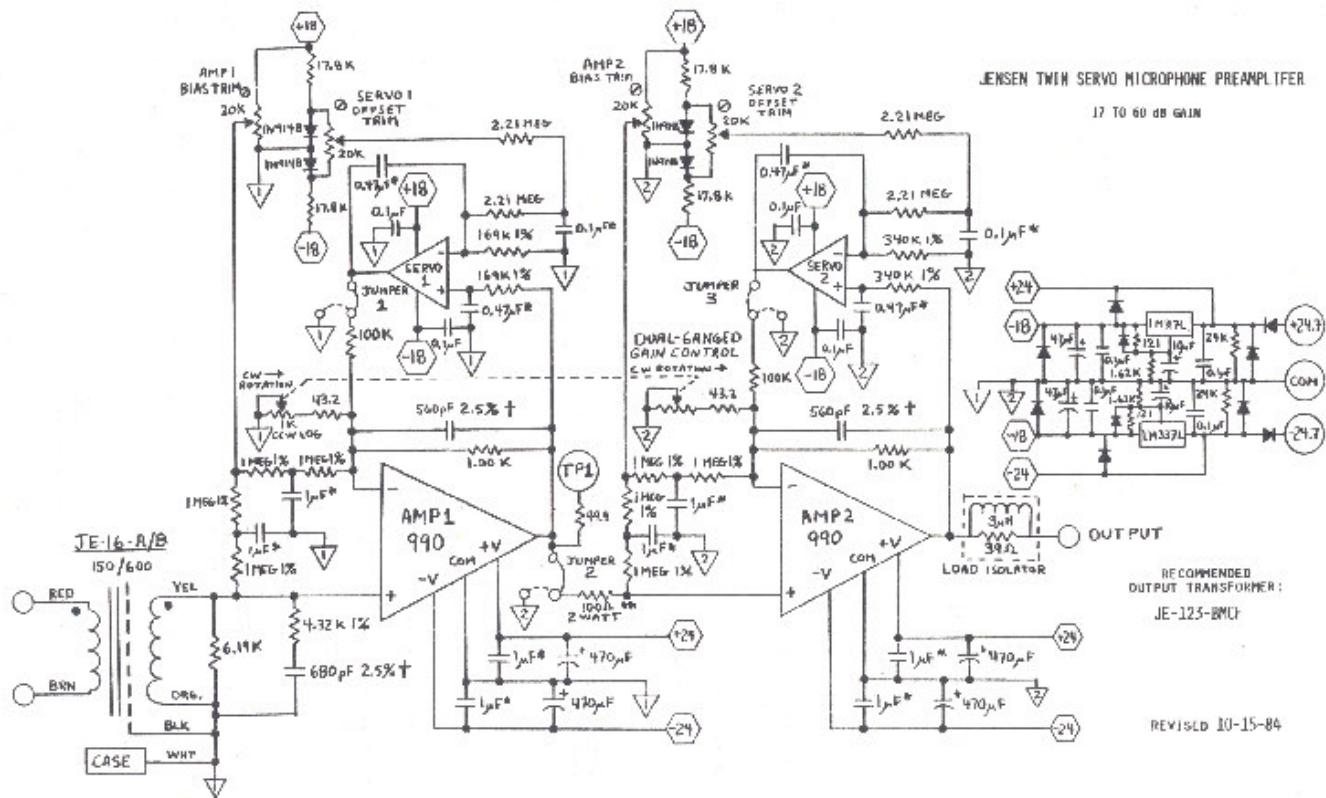

Menu

[\[Page 1\]](#)[\[Page 2\]](#)[\[Page 3\]](#)[\[Page 4\]](#)[\[Page 5\]](#)
[\[Page 6\]](#)[\[Page 7\]](#)[\[Page 8\]](#)[\[Page 9\]](#)[\[Page 10\]](#)