
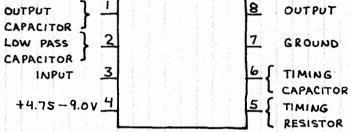
## TONE DECODER

CONTAINS A PHASE-LOCKED LOOP WHEN THE INPUT PIN & GOES LOW MATCHES THE CHIP'S FREQUENCY CENTER FREQUENCY (fo). THE LATTER FREQUENCY IS SET BY THE TIMING RESISTOR AND CAPACITOR (RAND C) (1.1) ÷ (RC). R SHOULD BE AND IS BETWEEN 2K-20K. THE 567 CAN BE ADJUSTED TO DETECT ANY INPUT BETWEEN O. O. Hz TO SOOKHZ. NOTE: I SECOND OR MORE MAY BE REQUIRED FOR THE 567 TO LOCK ON TO LOW FREQUENCY INPUTS! SEE THIS CHIP'S SPECIFICATIONS FOR MORE INFORMATION.



THE VALUE IN MICROFARADS OF THE LOW PASS CAPACITOR SHOULD BE N / fo WHERE N RANGES BETWEEN 1300 (FOR UP TO 14% fo DETECTION BANDWIDTH) TO 62,000 (UP TO 2% fo DETECTION BANDWIDTH). THE OUTPUT CAPACITOR SHOULD HAVE ABOUT TWICE THE CAPACITANCE OF THE LOW PASS FILTER CAPACITOR.

## BASIC TONE DETECTOR CIRCUIT

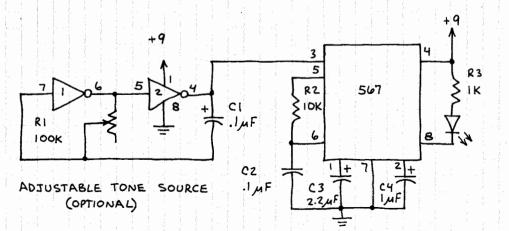

THIS CIRCUIT IS HANDY FOR LEARNING TONE DECODER BASICS. THE 567 PORTION CAN BE USED IN MANY DIFFERENT APPLICATIONS (SEE BELOW). THE PREDICTED fo is II KHz. THE TEST CIRCUIT fo WAS 1.3KHz.