

# Circuit detects rapidly falling signals and rejects noise

Vladimir Rentyuk, Zaporozhye, Ukraine

▶ Detecting a rapidly falling signal over some threshold is important for ultrasonic or location equipment as well as for seismology systems. You can combine a rail-to-rail operational amplifier with a Schmitt-trigger logic gate to perform this function (Figure 1). This example works well in an ultrasound machine. It controls a sample-and-hold amplifier that sets the gain of an AGC (automatic-gain-control) system.

The circuit works only with positive signals, so the signal must pass through a full-wave rectifier before it is applied to the circuit input. You configure the main part of the circuit, op amp IC<sub>1</sub>, as a comparator with hysteresis. It produces a high-level output when an input signal is higher than the specified threshold. The output goes to a low level when the input signal begins to fall

but only when the input falls faster than an established rate of change or if the level of the input signal will be lower than the established threshold of sensitivity. This circuit detects the moment when a signal is above the established threshold and the falling signal—or a mix of the signal and noise—has higher-than-specified speed.

R<sub>1</sub> and C<sub>1</sub> form an input lowpass filter to smooth the input signal. You set the values of R<sub>1</sub> and C<sub>1</sub> to create a filter roll-off for the input signal you are processing. Resistors R<sub>3</sub> and R<sub>4</sub> establish a small hysteresis, which is necessary so that slow signals with noise don't cause the output to change state. You set the threshold level with voltage divider R<sub>6</sub> and R<sub>7</sub>. D<sub>1</sub>, R<sub>5</sub>, and C<sub>2</sub> form a peak detector. R<sub>5</sub> establishes a time constant of the discharge of C<sub>2</sub> and provides

## DI's Inside

42 Hack into a stopwatch to make a phototimer

44 Comparator directly controls power-MOSFET gate

46 AGC circuit uses an analog multiplier

▶ To see all of EDN's Design Ideas, visit [www.edn.com/design\\_ideas](http://www.edn.com/design_ideas).

sensitivity to a falling signal's rate. You establish the circuit's sensitivity to a falling signal's rate of change using the time constant, which the values of C<sub>2</sub> and R<sub>5</sub> set. Hysteresis resistor R<sub>4</sub> is more than a decade larger than R<sub>5</sub>, so the effect of resistors R<sub>3</sub> and R<sub>4</sub> is negligible.

A rising input signal greater than the threshold charges C<sub>2</sub> to approximately the level of the input signal. The output amplifier is at a high level because the


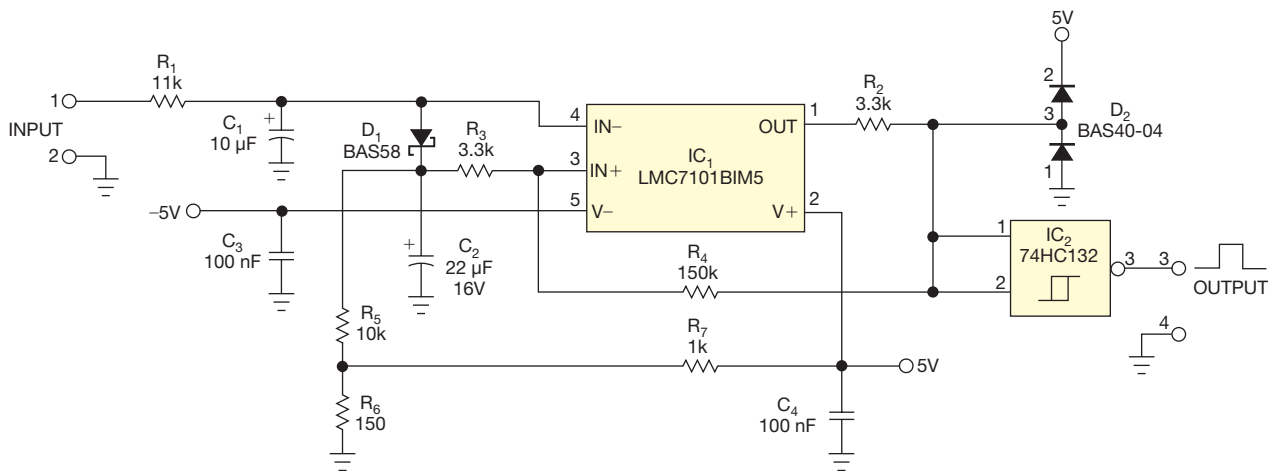


Figure 1 This circuit detects signal excursions higher than a set threshold and rejects noise and recognizes fast falling signals.

# designideas

voltage on  $C_2$  is always lower than the value of the rising input signal due to  $D_1$ 's voltage drop. When the input drops faster than  $C_2$  can discharge through  $R_3$ , the output level of the device changes to a low level because the voltage on  $C_2$  is higher than the value of the falling input signal. If the input signal falls more slowly than the discharge of  $C_2$  through resistor  $R_3$ , the output remains high. Schottky diode  $D_1$  prevents the discharge of  $C_2$  through the input.  $R_2$  and  $D_2$  clamp the amplifier's output to positive values. Feed the clamped signal to Schmitt-trigger logic gate  $IC_2$  to give a logic-level output with fast transitions (**Figure 2**). [EDN](#)

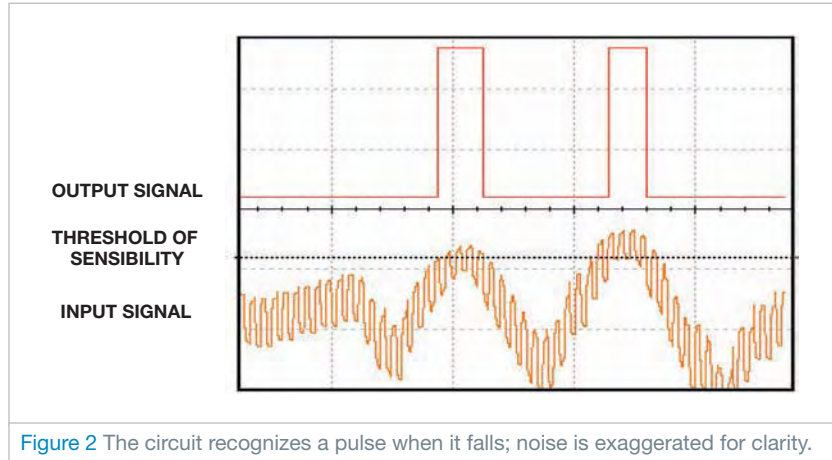

**Figure 2** The circuit recognizes a pulse when it falls; noise is exaggerated for clarity.