


## Full-wave rectifier circuit

### Design Goals

| Input      |            | Output     |            | Supply   |          |           |
|------------|------------|------------|------------|----------|----------|-----------|
| $V_{iMin}$ | $V_{iMax}$ | $V_{oMin}$ | $V_{oMax}$ | $V_{cc}$ | $V_{ee}$ | $V_{ref}$ |
| $\pm 25mV$ | $\pm 10V$  | 25mV       | 10V        | 15V      | -15V     | 0V        |
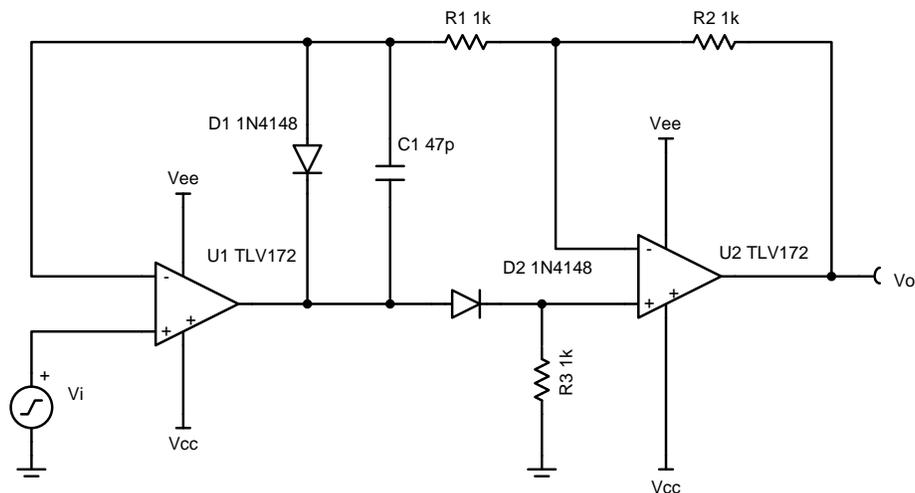
### Design Description

This absolute value circuit can turn alternating current (AC) signals to single polarity signals. This circuit functions with limited distortion for  $\pm 10\text{-V}$  input signals at frequencies up to 50kHz and for signals as small as  $\pm 25\text{mV}$  at frequencies up to 1kHz.



### Design Notes

1. Be sure to select an op amp with sufficient bandwidth and a high slew rate.
2. For greater precision look for an op amp with low offset voltage, low noise, and low total harmonic distortion (THD).
3. The resistors were selected to be 0.1% tolerance to reduce gain error.
4. Selecting too large of a capacitor  $C_1$  will cause large distortion on the transition edges when the input signal changes polarity.  $C_1$  may not be required for all op amps.
5. Use a fast switching diode.

### Design Steps

1. Select gain resistors.

- a. Gain for positive input signals.

$$\frac{V_o}{V_i} = 1 \frac{V}{V}$$

- b. Gain for negative input signals.

$$\frac{V_o}{V_i} = - \frac{R_2}{R_1} = - 1 \frac{V}{V}$$

2. Select  $R_1$  and  $R_2$  to reduce thermal noise and to minimize voltage drops due to the reverse leakage current of the diode. These resistors will appear as loads to  $U_1$  and  $U_2$  during negative input signals.

$$R_1 = R_2 = 1 \text{ k}\Omega$$

3.  $R_3$  biases the non-inverting node of  $U_2$  to GND during negative input signals. Select  $R_3$  to be the same value as  $R_1$  and  $R_2$ .  $U_1$  must be able to drive the  $R_3$  load during positive input signals.


$$R_3 = 1 \text{ k}\Omega$$

4. Select  $C_1$  based on the desired transient response. See the Design Reference section for more information.


$$C_1 = 47\text{pF}$$

Design Simulations

Transient Simulation Results

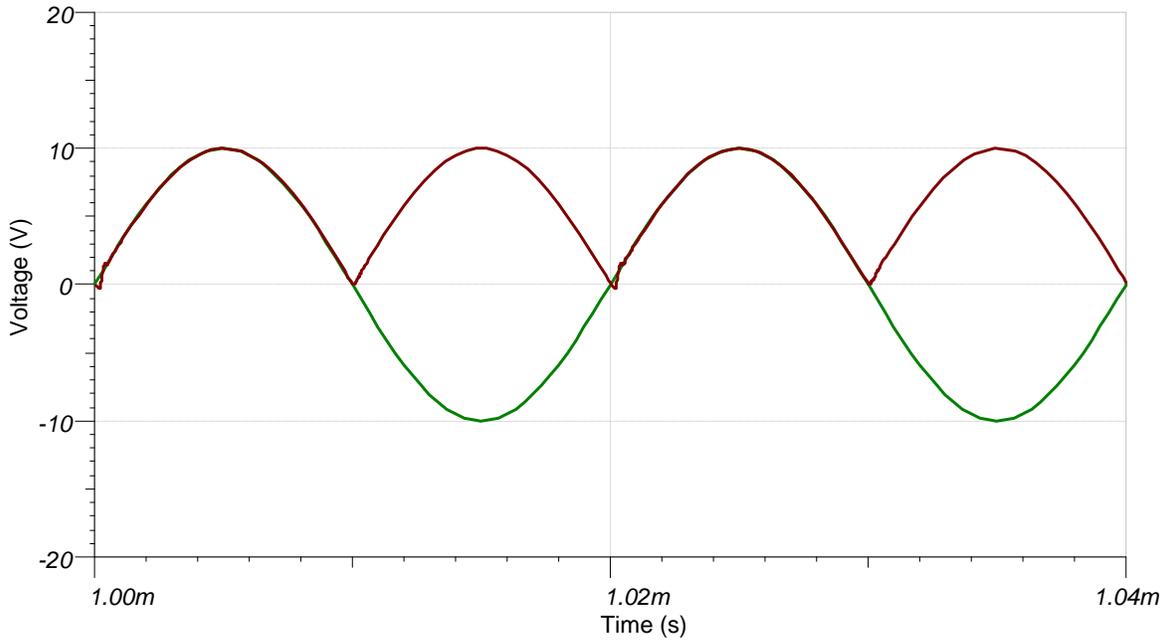

**±10V at 50-kHz Input**

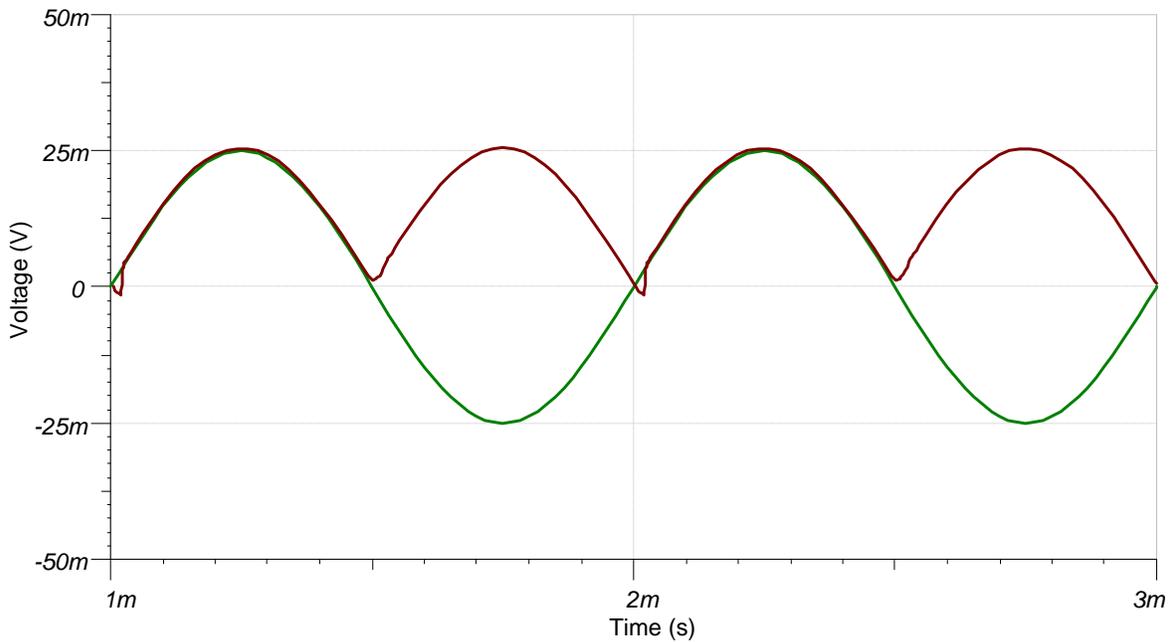

**±25mV at 1-kHz Input**

## Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See circuit SPICE simulation file [SBOC517](#).

See TIPD139, [www.ti.com/tool/tipd139](http://www.ti.com/tool/tipd139).

## Design Featured Op Amp

| TLV172   |                        |
|--|------------------------|
| $V_{cc}$   | 4.5V to 36V            |
| $V_{inCM}$   | Vee to ( $V_{cc}-2V$ ) |
| $V_{out}$  | Rail-to-rail           |
| $V_{os}$   | 0.5mV                  |
| $I_q$  | 1.6mA/Ch               |
| $I_b$  | 10pA                   |
| UGBW   | 10MHz                  |
| SR   | 10V/ $\mu$ s           |
| #Channels  | 1, 2, 4                |
| <a href="http://www.ti.com/product/tlv172">www.ti.com/product/tlv172</a> |                        |

## Design Alternate Op Amp

| OPA197   |              |
|--|--------------|
| $V_{cc}$   | 4.5V to 36V  |
| $V_{inCM}$   | Rail-to-rail |
| $V_{out}$  | Rail-to-rail |
| $V_{os}$   | 25 $\mu$ V   |
| $I_q$  | 1mA/Ch       |
| $I_b$  | 5pA          |
| UGBW   | 10MHz        |
| SR   | 20V/ $\mu$ s |
| #Channels  | 1, 2, 4      |
| <a href="http://www.ti.com/product/opa197">www.ti.com/product/opa197</a> |              |

## Revision History

| Revision | Date         | Change  |
|----------|--------------|---|
| A        | January 2019 | Downscale the title and changed title role to 'Amplifiers'.<br>Added link to circuit cookbook landing page and Spice simulation file. |