

## VOLTAGE CONTROLLED AMPLIFIER

When the voltage at the gate of a n-channel MOSFET is varied from 0V — supply volts its resistance varies from about 1k $\Omega$  to several tens of megohms. This fact is utilised in the following VCA. The inverter is biased into linear operation by the 10m $\Omega$  resistor. When feedback is applied the gain is set by  $\frac{R_F}{R_{IN}}$ . By allowing a MOSFET to be  $R_{IN}$  and  $R_F$  fixed, with the values shown as the control voltage varies from  $V_{DD} - V_{SS}$  the gain of the amplifier varies from cut-off to just over unity.

