

HUM ELIMINATION

Some New Ideas on an Old and Important Subject

HUM, that bane of every engineer's existence, the spoiler of recorded and transcribed music, can be eliminated. It merely requires careful analysis and a large dose of common sense. There is a myriad of ways that this insidious nuisance can creep into an otherwise well-designed piece of equipment, either through faulty design or from aging or faulty components.

First, hum may be eliminated through proper design. One of the most violent sources of hum is lack of filtering. Proper filter components are arrived at by designing the power supply—for the unit under consideration—to have a certain percentage ripple when loaded with the load the unit will draw. This is not always enough. It is sometimes necessary to utilize a voltage-regulated power supply to reduce the ripple to the desired amount. This may take the form of the well-known RCA circuit which uses a sharp cut-off pentode to receive the variations in the D.C. output voltage and with a resistor in its plate circuit to influence the grids of several power tubes such as 6B4G or 2A3's, connected in series with the power supply. Their resistance is increased or decreased, and, thereby, the voltage held constant and the ripple wiped out. For smaller loads, a gaseous regulator of the VR-150 type may be employed.

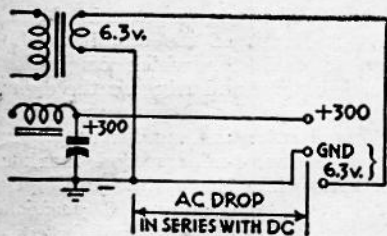


Fig. 1—Piping A.C. hum into a D.C. circuit.

In the former case, the regulator may function well with a resistive load, but when coupled to the circuit it is intended to power, ripple develops. This may be caused by several things. First and foremost is the shielding of the grid circuit of the pentode which controls the regulator tubes. If 60 cycles is introduced at this point, the tube will amplify the 60 cycles and swing the D.C. voltage at this frequency. Secondly, this type of power supply cannot be overloaded. It must be designed to handle the maximum current to be delivered. The regulation and ripple increase very rapidly after its maximum output has been reached.

If a VR tube is used as a regulator, its current range cannot be exceeded. This tube must be supplied with a minimum of 5 milliamperes, else it will not remain in a conducting condition. It must be remembered that the line voltage may change, so a low line voltage condition should be used to figure the minimum current value and the highest line voltage for the maximum

current value. This current should not exceed the current rating for the tube.

These tubes under certain conditions will oscillate. This condition may be cured in some cases by inserting a series resistance of about twenty ohms between the VR tube and ground. It is interesting to note that VR tubes have an effective resistance in the order of 40 ohms.

MAGNETIC FIELD COUPLINGS

The power supply should be laid out with the fields generated by the power transformer and chokes properly oriented. The chokes and power transformers should be magnetically shielded and placed so their cores are at right angles to each other, as there is no point in building a good low-ripple power supply and then inducing a volt or so of 60 cycle from the power transformer into the chokes. This hum source will cause even more trouble if audio transformers are involved, as there is usually a considerable amount of amplification following these items and the induced hum is amplified accordingly.

Audio transformers should of course be kept away from power transformers and chokes and should be oriented properly as well. If these components are mounted on a common iron or steel chassis, their cores should be kept away from the chassis by mounting them on aluminum or brass bushings, as the magnetic chassis becomes a common lamination in the core of each transformer and comprises a convenient path for the transference of magnetic fields.

In general, the smaller an audio transformer is, the fewer external magnetic lines will cut it and, consequently, the less it will be bothered by external fields.

Remember that the field around a conductor is proportional to the current that conductor is carrying, so be very careful with leads such as supply lines for the power and filament transformers, and filament wiring which supplies a large number of tubes. Grounding one side of the heater winding on the filament transformers in one place is helpful, but keep the filament wiring to itself. This, of course, applies also to high voltage wiring to the rectifier tubes. Don't forget to shield all mercury-vapor rectifiers.

"GROUND" CIRCUIT COUPLINGS

Where the power supply and the unit to be powered are separated, do NOT run the negative B voltage and the grounded side of the filament through a common wire, because (as a look at Fig. 1 will show you) you will effectively connect an A.C. voltage in series with the D.C. supply which you consider hum-free. Although this voltage is small, being due to the filament current, it may be amplified many times by several tubes and assume much greater proportions in the output of your device.

It is somewhat risky to ground the filaments of high-gain amplifiers in several places or depend on the chassis to carry

one side of the filament current. This is quite all right from the current standpoint, but if a previous plate is by-passed at Point A in Fig. 2 and a subsequent grid

J. Carlisle Hoadley was born in Washington, D. C., November 22, 1916. Began his radio career at the age of ten, and was president of his High School radio club (McKinley Tech) a few years later.

After ten years in the servicing and sound apparatus business, sometimes with repair organizations and sometimes on his own, Mr. Hoadley went to the Naval Research Laboratories at Anacostia, D.C., as a radio engineer. Was engaged on pre-Pearl Harbor radar research, later studied captured enemy equipment and ran tests on Navy gear.



Went to the Bryant Chucking Co. of Springfield, Vermont, as Electronics Engineer, in 1943. At completion of the project on which he was engaged, he accepted a position with the Raytheon Manufacturing Co. of Waltham, Mass., as engineer on design and development of radar apparatus. Started radio writing while at Springfield, Vt. Still spends most of his waking hours in his radio laboratory. Engaged at present in high-fidelity reproduction of music.

is returned to point B, then a hum voltage may be placed in series with the grid of the second tube. Even though this voltage is in the order of .01 volts or smaller, if that tube is a pentode with an amplification of several hundred followed by several more amplifier stages, as in a micro-

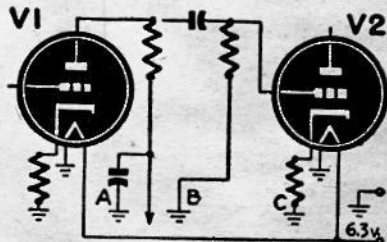


Fig. 2—Effect of voltage drops on a chassis.

phone amplifier, then this hum voltage can be very appreciable.

In high-gain stages, incidentally, hum (Continued on page 355)

HUM ELIMINATION

(Continued from page 313)

may be caused by emission from the heater to the cathode, or emission from the cathode to the heater. This condition may be reduced or eliminated, in the first instance by applying a positive voltage on the heater, sufficient to make it as positive as the cathode. In the second instance, the application of a negative voltage on the heater sufficient to make the heater-cathode voltage difference small is the remedy.

It must be remembered that although a tube is supposedly cut off by the application of bias to the cathode, the cathode does not always cover the heater completely, and that emission can occur from the heater to the plate. If this emission takes place from one exposed heater wire, said emission will not be from an equipotential surface and will vary as the heater supply frequency.

It is best, in audio amplifier design, not to rely on multiple grounds to the chassis. It is better to carry the ground circuit from point to point with a heavy copper wire, and this ground, insulated from the chassis, should be grounded in one spot only. This spot will have to be found by trial and error. This is particularly effective in high-gain amplifiers. A spot will be found at which the hum will drop appreciably and even reduce to the vanishing point.

RESISTANCE-CAPACITY FILTERS

It sometimes becomes impractical from an economic standpoint to use brute force methods, such as complicated filters and regulators, to effectively filter the entire power supply, when the addition of an RC network, in one or more circuits, will accomplish the desired result. This may be either keeping the supply ripple from this stage, or isolating the plate excursions of this stage from the power supply RC filter networks are usually figured on the basis of $T = RC$ (see Fig. 3) where T is the time in seconds, R is the resistance in ohms and C is the capacity in farads.

It might be pointed out that a lot of time can be saved and time-constant problems can be worked in the head, if you remember that microseconds equals ohms times microfarads or that microseconds equals megohms times micro-microfarads. One of these formulas puts the parameter you want in the terms that you want it and eliminates converting farads, for instance, to microfarads or micro-microfarads, or ohms to megohms. This will also eliminate the possibility of error in adding and subtracting negative and positive exponents.

This formula states the time, T, it takes the voltage across the Condenser, C, to charge to 2/3 of its full value or to discharge to 1/3 of its original value. These fractions are approximate, as the exact amount that the value C charges to is

equal to $1 - \frac{1}{e}$ and the value it discharges

to is $\frac{1}{e}$.

The condenser charges or discharges according to an exponential function so that it takes a much longer time to change even a much smaller additional amount in the direction we are considering. (See Fig. 4.) It is interesting to note that C may charge to 95% of its maximum in 3RC (seconds) or it will discharge to 5% of its total

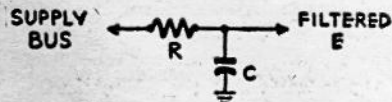


Fig. 3—Charging time is set by R and C.

value in the same time, as the case may be. This figure is accurate to about three decimal places.


If we compute our RC value on the basis of $T = RC$ in an isolation filter, we will still have 1/3 of the original amount of ripple left, which in most cases is not reducing it to a sufficiently low value. We could compute the necessary RC to reduce the ripple to any premeditated value but

(Continued on following page)

Electricity

Models range from 350 to 35,000 watts. A. C. types from 113 to 660 volts, 50, 60, 180 cycles, single or three-phase and 400, 500 and 800 cycles, single phase. D. C. types from 6 to 4000 volts. Also available in dual voltage and special frequency types.

ONAN

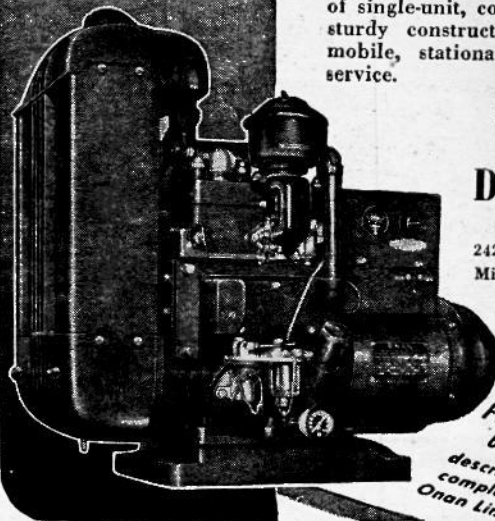

FOR RADIO AND ELECTRONIC APPLICATIONS

ONAN ELECTRIC GENERATING PLANTS supply reliable, economical electrical service for electronic and television applications as well as for scores of general uses. Driven by Onan-built, 4-cycle gasoline engines, these power units are of single-unit, compact design and sturdy construction. Suitable for mobile, stationary or emergency service.

Model shown is from W2C series; 2000 to 3500 watts; powered by Onan-built, two-cylinder, water-cooled engine.

D. W. ONAN

AND SONS

2424 Royalston Avenue
Minneapolis 5 Minn.

Write For Folder 690-A describing complete Onan Line

FREE

TO
RADIO
MEN



COLOR CODE and OHMS LAW CALCULATOR

Burstein-Applebee of Kansas City offers you this great convenience FREE. Easy to work. Solves many problems in a jiffy. FREE to radio men, electronic engineers and others in the business. Attach coupon to your letterhead.

MAIL COUPON NOW

BURSTEIN-APPLEBEE CO.
1012 McGEE, KANSAS CITY 6, MO.
Send me FREE Color Code and Ohms Law Calculator along with latest catalog.

I am _____
STATE CONNECTION IN INDUSTRY

NAME _____

ADDRESS _____

TOWN _____

STATE _____

Spell radar backward and you get confusion, says Frederick C. Othman, newspaper columnist. He refers to the confusion surrounding both the early censorship of the subject and the subsequent "revelation," which was not entirely revealing.

Possibly to illustrate the confusion, the distinguished columnist goes on to declare: "My professor says that radar some day

Get Started in Radio



10 "HOW-TO-DO-IT" BOOKS

Get a solid foundation in radio by means of these 10c timely text books. Each clearly written, profusely illustrated, contains over 15,000 words. You'll be amazed at the wealth of information packed into these handy books. Excellent for reference—ideal for technical library. Your money back if not satisfied.

5 BOOKS for 50c

10 BOOKS for \$1.00

Sent to You Postpaid

No. 1—How To Make Four Dierle Short Wave Sets
No. 2—How To Make The Most Popular All-Wave 1 and 2 Tube Receivers
No. 3—Alternating Current for Beginners
No. 4—All About Aerials
No. 5—Beginners' Radio Dictionary
No. 6—How To Have Fun With Radio
No. 7—How To Read Radio Diagrams
No. 8—Radio for Beginners
No. 9—Simple Electrical Experiments
No. 10—Television

Remit by check or money order—register letter if you send cash or stamps.
RADIO PUBLICATIONS, 25F West B'way, New York (7)

French Firm, selling radio articles in France and North Africa, is looking for representation of an American make of radio, accessories, receivers, tubes, etc. Please write to: Le Materiel-Radiophonique, Service Commercial, 7, Boulevard de Brou, Bourg (Ain), France.

FOR SALE 250, five-tube chassis, with 4 octal sockets, I.F. and power transformer, variable condenser, Antenna and Oscillator coils, by-pass Condensers and Resistors, 'phone jack, and tie-strip—\$3.50 each; lots of 10 or more, \$3.00 each.
Also 600 Chassis blanks with sockets only and assorted parts.

LEE DE FOREST LABORATORIES

5106 Wilshire Boulevard
Los Angeles, California

will become television, without scanning discs, synchronous motors and all the other complicated innards now in use."

The ghost of Nipkow will be pleased to hear that in this day of cathode-ray tube television, the scanning disc is still referred to, even if the reference is due to confusion caused by publicity on radar.

Attention! HAMS

... FINISH YOUR OWN CRYSTALS



NEW Complete Crystal Finishing Kit

Meet F.C.C. regulations for frequency control with Quartz Crystals. Finish your own crystals to meet your individual requirements. It's fun—it's easy—it's economical. Kit contains four AT or BT low drift Quartz Crystals cut to U.S. Signal Corps wartime specification. Complete accessories including a holder with stainless steel hand lapped electrodes and special device for making limited frequency adjustments—flat glass grinding plates—coarse and fine special grinding abrasives—cleaning brush and syntax beads and complete instructions. Be sure to specify frequency desired so we can send blanks within easy grinding range.

only \$4.95 postpaid

ALL AT AMAZING LOW COST—
Send money order, check or cash for your kit today.

COMMERCIAL EQUIPMENT CO.
Dept. B
1416 McGee Street
Kansas City 6, Missouri

FREE INSTRUCTION

I Guarantee this Book will Earn You 5 TIMES ITS COST!

Or It's Yours FREE!

Here's a book that will make money for you. Let me prove it with one of the greatest satisfaction guarantees in technical book history. **COYNE TROUBLE SHOOTING MANUAL** is 4 great books in 1. 610 large pages packed with over 500 valuable wiring diagrams, plans, etc. Shows you new methods for shooting trouble on motors, appliances, refrigerators, automotive devices, air conditioning and diesel equipment.

SEND NO MONEY

Here's my sensational offer—Fill in and mail the coupon below. Send no money. Look the book over 7 full days FREE—then decide if you want to keep the book. If you keep the book you can pay \$8.00 cash or send \$3.00 after 7 days and \$3.00 a month until \$8.95 is paid. And further I GUARANTEE that the book must earn 5 times its cost in one year or I'll refund every cent you paid and you keep the book FREE. You can't possibly lose on an offer like this—the book must pay its cost 5 times over or your money is refunded. Offer Limited—Act Now! Send 7-day trial coupon today!

H. C. LEWIS, Pres., COYNE ELECTRICAL SCHOOL, Dept. 29-T1
500 S. PAULINA STREET, CHICAGO 12, ILLINOIS

Send me the COYNE TROUBLE SHOOTING MANUAL for 7 days FREE examination. After 7 days I'll either return the book and owe nothing or send \$3.00 and \$3.00 per month until \$8.95 is paid or I'll pay cash price of \$8.00. You agree to refund my entire payment if this book does not earn 5 times its cost in one year.

NAME _____ Age _____
ADDRESS _____
TOWN _____ Zone _____ STATE _____

IF YOU WANT BOOK sent C.O.D. (you pay postman \$8.00) check here. Same satisfaction guarantee or your money back.

Make your own Talkies 8mm • 16mm
WITH PAID
FILMGRAPH RECORDER
and Instantaneous Permanent
FREE **PLAYBACK UNIT**. Lengthy Recordings; Clear, Powerful; Eliminates Titles.

MILES REPRODUCER CO., INC. 812 BROADWAY, N.Y.3 RC-2

HUM ELIMINATION

(Continued from page 355)

for a reasonably close estimate we may use the formula $T = \frac{RC}{25D}$ where D is the duty

cycle expressed in a fraction of one. This will yield an RC filter which will reduce the ripple to approximately 1% of its unfiltered value. The duty cycle is the ratio of time of duration of a wave form to the period of successive wave forms. In the case of a sine wave these values are equal, so D will equal .5.

Remember when using RC filters that the choice of R is limited to the largest value that will give the required filtering but which will not drop the average DC potential on the tube plate to a value lower than the value which was used in designing the components for that stage.

The importance of this factor "D" will be more evident when a non-sinusoidal circuit is to be decoupled. For instance, a multivibrator which produces a square wave ten microseconds wide and then rests for ten thousand microseconds will draw current for 10 μsec., whereas one which produces a square wave three thousand μsec. wide and rests for seven thousand μsec. will draw current for 3000 μsec. and will, therefore, discharge our C to a much lower voltage, indicating the necessity for a bigger C or a larger R.

In any event, when unequal wave forms are considered, it is more convenient to consider time constants rather than impedances and reactances.

MISCELLANEOUS METHODS

Decoupling is necessary where several stages are to be cascaded, as oscillation can result. It is conventional, therefore, to isolate several or all the stages, not only in the interest of hum reduction, but to eliminate the unwanted regeneration introduced by common coupling in the power supply.

Hum which cannot be eliminated in any other manner can be reduced by the application of degeneration which will reduce the hum, within the loop, proportional to the amount of feedback. In several cases, this feedback loop could be resonant at the hum frequency only, so that a maximum of degeneration is introduced at the hum frequency.

In cases where the low-frequency response is not important, it is feasible to reduce the coupling time constants by reducing the coupling condensers and grid resistors, reducing the gain at the hum frequencies. When all other means fail or when economy dictates, hum may be balanced out by applying to the circuit in question a hum voltage of proper amplitude and 180° out of phase. This voltage may be applied to any of the tube elements in a number of ways.

Remember that the field of a dynamic speaker, when used as choke in the power supply, has a very strong hum field surrounding it and an input transformer should not be located close thereto. A velocity microphone will pick up a strong hum voltage when located as far as 8 or 9 feet from such a speaker field. Microphone orientation will reduce this pickup to a minimum.

When connecting a self-powered tuner to an amplifier, remember to reverse the line connections if undue hum results. If both units have by-pass condensers from one side of the line to ground, it is possible to plug the units into the supply mains in such a way as to place some, or all, of the

110 V A.C. 60 cycle power source in series with the common ground between the units.

Consider, when using a cathode follower, that the cathode is swinging with the signal, and, at some parts of the cycle, it may well be a hundred volts above the filament, which may give rise to cathode-filament emission, or capacitive hum coupling.

Electrolytic condensers are a potential hum source. Their capacity reduces with age and their impedance increases, which can also give rise to oscillation. They should not be depended upon for R.F. by-passing and, in such instances, should be paralleled with a good paper or mica condenser.

Don't forget to by-pass to ground all the cathodes in which degeneration is not desired. The value of the condenser should be large so that its impedance at 60 cycles will be much lower than that of the cathode resistor, so that any hum developed between the heater and the

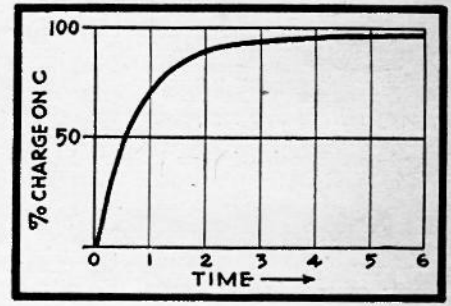


Fig. 4—Graph of condenser charging time.

cathode will be by-passed to ground. It is important that this condenser be grounded to the same place as the grid and cathode resistors, so that an AC circulating current in the chassis is not connected in series with the cathode by-pass condenser. (See Fig. 2.) Electrolytics used for by-passing sometimes give rise to tunable hums in radio tuners. Tunable hums have also been known to be caused by unwanted 60 cycles introduced into the oscillator of a superheterodyne receiver, due either to faulty by-passing or a faulty tube.

Hum can be caused by induction from a phonograph motor to a magnetic pickup. This can be reduced by magnetically shielding the pick-up and using an iron turntable. Of course, the leads from the pick-up should be run through shielded wire and, in low-level pickups or microphones, the shield braid should not be relied upon for the ground return. Rather, use double wire shielded cable, connecting shield braid to the amplifier chassis and the ground wire to the amplifier ground. In this instance, do NOT connect the braid to the ground at the microphone or pickup but only to its frame. In connection with phonographs, it may be noted that what appears to be a hum only when records are played, may be turntable rumble. This may be reduced by replacing the rubber drive wheel on the rim drive models or by reducing the low frequency response of the amplifier.

Last, but not least, mechanical vibration can be responsible for hum. In such cases mechanical isolation is indicated. Mounting on rubber or removal of the source is the answer.

There are very few cases where the annoying hums cannot be eliminated or reduced to the point where they are no longer objectionable and the full capabilities of the unit under consideration can be realized.