

By **JIM ROWE**

# Two-Way SPDIF/Toslink Digital Audio Converter

**Need to convert the Toslink digital audio optical signal from your DVD player into coaxial SPDIF form, to feed the only remaining digital input on your home-theatre amplifier? Or do you want to convert from a coaxial SPDIF signal to Toslink form? This low-cost unit converts digital audio bitstreams either way.**

**M**URPHY'S LAW SEEMS to apply to digital audio bitstream signals and inputs just as much as it does to any other aspect of electronics.

For example, let's say that you have only one digital audio input left on your home-theatre amplifier and it's an optical one. Now guess which kind of digital audio output you'll find on your new DVD recorder or DTB set-top box when you bring it home?

That's right, Murphy's Law will ensure that it will be a coaxial output. It won't be an optical one, because that would match the remaining input on the amplifier and make things easy for

you. On the other hand, if your amplifier has only a coaxial digital input remaining, you can bet your last dollar that your new set-top box will have an optical digital output instead!

Either way, these are both situations where the easiest solution is to use a converter – one that can convert coaxial digital audio signals into optical, or vice-versa. And that's exactly what this little gadget does. It uses only a handful of parts, yet can easily convert coaxial digital bitstream signals into optical form and/or the other way around.

It's also easy to build and will set

you back significantly less than a pair of commercial converters.

## Digital audio signals

Basically, the digital audio signals found in domestic equipment are all in the form of SPDIF (Sony/Philips Digital Interface) bitstreams – either as 400mV electrical signals sent along 75-ohm coaxial cables or as optical signals (pulses of 660nm red light) sent along fibre-optic cables. The optical signal form is often called "Toslink".

Although domestic digital bitstream audio is split almost equally between the coaxial and optical forms, they're both virtually identical in terms of the SPDIF/BMC encoding and serialisation used (see panel). So it's relatively easy to convert between the two, in either direction. In fact, once you get hold of suitable Toslink optical transmitter and receiver modules, the rest is no problem at all.

## How it works

Fig.1 shows the circuit details for the converter. It's based on a pair

of low-cost Toslink optical modules which are now being sold by Jaycar Electronics: the ZL-3002 receiver and the ZL-3000 transmitter.

The receiver is used at the input of the optical-to-coaxial converter section at the top of Fig.1, while the transmitter is used at the output of the coaxial-to-optical converter section in the centre of the diagram. The bottom part of Fig.1 is the power supply section and this provides a +3.3V DC rail for the other two sections.

In operation, the ZL-3002 optical receiver accepts the incoming Toslink optical bitstream and converts it into an electrical signal with roughly TTL logic levels at its pin 1 output. This is then fed through CMOS inverter stage IC1f and then through parallel-connected inverter stages IC1a, IC1b & IC1c which together act as a buffer.

The resulting “squared-up” signals are then fed through a 150nF DC blocking capacitor to a voltage divider consisting of 390Ω, 220Ω & 160Ω resistors. This divider network delivers a 400mV peak-to-peak SPDIF signal to output connector CON2 and also ensures correct impedance matching, so the output signal is at the required 75Ω impedance level. And that’s all there is to the optical-to-coaxial converter.

The second converter stage is just as straightforward. The incoming coaxial bitstream signal is fed to CON1 and then fed via a 100nF capacitor to a Schmitt trigger stage based on IC1e and its associated 100Ω and 10kΩ feedback resistors. This stage “squares up” the bitstream signal and converts it into a 3.3V p-p CMOS signal.


The 300Ω resistor connected across CON1 is included for impedance matching. It acts in conjunction with the 100Ω resistor in the signal path to give a 75Ω input impedance.

The output from IC1e appears at pin 10 and is fed to inverting buffer stage IC1d. This in turn drives the ZL-3000 Toslink transmitter module where it is converted into an optical bitstream signal.

## Power supply

The power supply section has been designed so that the converter can be operated from almost any source of 9-12V DC capable of supplying about 55mA. This means you can operate it from either a small plugpack supply or from batteries.

The incoming 9-12V DC is first

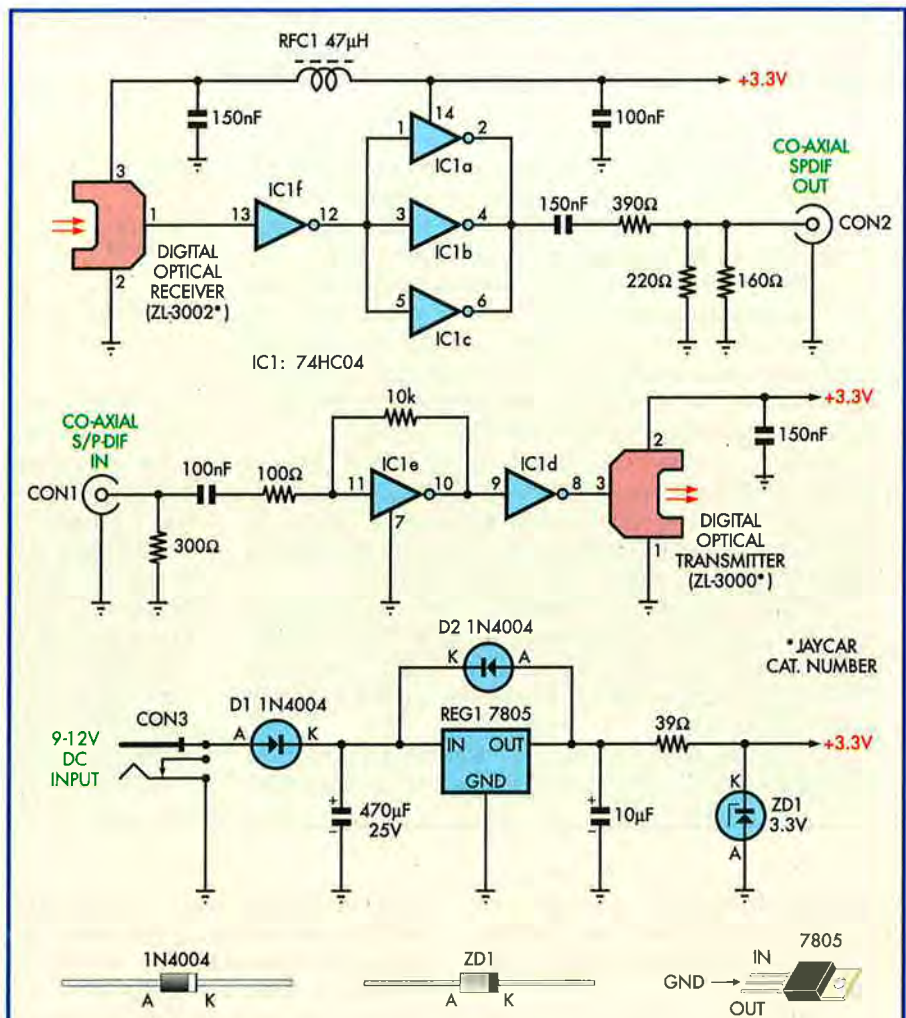

## SC TWO-WAY SPDIF/TOSLINK CONVERTER

Fig.1: the circuit is based on a pair of Toslink optical modules (a receiver and a transmitter) plus hex inverter stage IC1 to buffer the output and input signals. Power can come from any 9-12V DC source – eg, a plugpack or batteries.

passed through reverse-polarity protection diode D1 and filtered using a 470µF capacitor. The resulting DC rail is then applied to 3-terminal regulator REG1 (7805) to derive a well-regulated +5V rail. This is then further regulated down to +3.3V (as required by the Toslink modules) using a 39Ω resistor and zener diode ZD1.

Diode D2 protects REG1 from damage if the 9-12V DC input is disconnected while the 10µF electrolytic capacitor across the regulator’s output is fully charged.

## Construction

This unit is a cinch to build. As shown on Fig.2, all the parts (including the connectors) are mounted on a

single PC board coded 01106061 (76 x 46mm). This fits neatly inside a UB5-size jiffy box (83 x 54 x 31mm) – or more accurately, it mounts directly on the inside of the lid, with the outside of the lid being used as the base.

Note that the board has a rounded cutout at each corner, so that it clears the integral pillars in the box.

Fig.2 shows how to install the parts. Begin by fitting the resistors, making sure you fit the correct value in each position. Table 1 shows the colour codes but we recommend that you also check them using a digital multimeter, just to make sure.

Follow these with the 47µH RF choke, then fit the monolithic and MKT capacitors. The 10µF tantalum

## What Are SPDIF And Toslink?

The acronym SPDIF (or S/PDIF) stands for Sony/Philips Digital Interface. Basically, it is a standardised serial interface for transferring digital audio data between consumer-level equipment such as DVD and CD players, DAT and DVD recorders, surround-sound decoders and home-theatre amplifiers.

SPDIF is very similar to the AES3 serial digital interface used in professional recording and broadcasting environments. In operation, each digital audio sample (16-24 bits) is packaged along with status, control and error-checking information into a 32-bit binary word. This is then modulated or encoded into a serial bitstream using the Biphasic Mark Code (BMC).

BMC involves combining the data bits with a clock signal of twice the data bit rate, in such a way that a binary "1" results in two polarity reversals in one bit period, while a binary "0" results in a single polarity reversal. This double bit-rate signal is self-clocking at the receiving end and has no DC component.

The BMC encoded serial bitstream is then transmitted as a 400mV peak-to-peak signal along a single 75-ohm coaxial cable. In most cases, the cable connectors used are standard RCA or "Cinch" connectors, as also used for analog audio and composite video.

Although originally developed for conveying linear PCM (LPCM) digital audio signals as used in CD and DAT audio, SPDIF

## Digital Audio Bitstream Formats

SOURCE & CODING	CD-Audio (LPCM)	DVD-Video & DAT (LPCM)	DVD-Video (COMPRESSED)		
			DOLBY DIGITAL (AC-3)	MPEG-2 AUDIO	DTS AUDIO
SAMPLING RATE	44.1kS/s	48kS/s	48kS/s	48kS/s	48kS/s
MAX DATA BIT RATE	2822kb/s	3072kb/s	448kb/s	456kb/s	754.5kb/s
SPDIF (Toslink) BMC BIT RATE	5644kb/s	6144kb/s	896kb/s	912kb/s	1509kb/s

has also been adapted for conveying compressed digital audio, including Dolby Digital (AC-3), DTS and MPEG-2 audio.

Toslink is essentially just the SPDIF signal format converted into the optical domain, for transfer along optical-fibre cables. The accompanying table (see above) shows the most common domestic audio bitstream formats and the SPDIF/Toslink bit rates for each one. Note that LPCM audio is rarely used for DVD-Video, because even a stereo audio track requires a BMC bit rate of 6.1Mb/s.

Many current-model DVD players and recorders are provided with either coaxial SPDIF or Toslink digital audio inputs and outputs, or quite often a mixture of both. Similarly, many home-theatre amplifiers are provided with coaxial SPDIF and/or Toslink inputs. This is also the case with many up-market PC sound cards.

and 470µF electrolytic capacitors can then go in, taking care to ensure they are correctly orientated (since they are polarised).

Next, fit the two 1N4004 diodes (D1 & D2), followed by zener diode ZD1. Once again, these parts are polarised so be sure to fit them with their banded ends orientated as shown.

Regulator REG1 is next on the list. This mounts horizontally with its three leads bent down by 90°, so that they pass through their respective holes in the PC board.

To do this, first bend its leads downwards about 5mm from its body, then fit the device in position and secure its metal tab to the board using an M3 x 6mm machine screw and nut.

The Toslink receiver and transmitter modules can now go in. These are very similar in appearance but it's impossible to get them mixed up since the receiver module has five pins while the transmitter has just three connection pins plus two plastic locating spigots.

The final component to fit to the board is IC1. An IC socket was fitted to the prototype but this is optional and you can solder the IC straight in instead. Make sure that the device is orientated as shown in Fig.2, with its notched end towards the left.

If you are soldering the IC in directly, take care because it's a CMOS device and easily damaged by static electricity. The rules are quite simple: use

an earthed soldering iron, discharge yourself of static before handling the device, avoid touching the pins and solder pins 7 & 14 first (to enable the internal protection diodes).

## Final assembly

The board assembly is now complete and the next step is to drill and cut the various holes in the box. Fig.3 shows the details.

Note that the round 9mm hole for CON2 on the righthand end of the box has an 8mm-wide slot cut below it, to allow final case assembly with the board mounted on the lid. Note also that the 9mm hole for the power connector (CON3) must go in the rear of the box – see Fig.3 and the photo.

### Table 1: Resistor Colour Codes

No.	Value	4-Band Code (1%)	5-Band Code (1%)
1	10kΩ	brown black orange brown	brown black black red brown
1	390Ω	orange white brown brown	orange white black black brown
1	300Ω	orange black brown brown	orange black black black brown
1	220Ω	red red brown brown	red red black black brown
1	160Ω	brown blue brown brown	brown blue black black brown
1	100Ω	brown black brown brown	brown black black black brown
1	39Ω	orange white black brown	orange white black gold brown


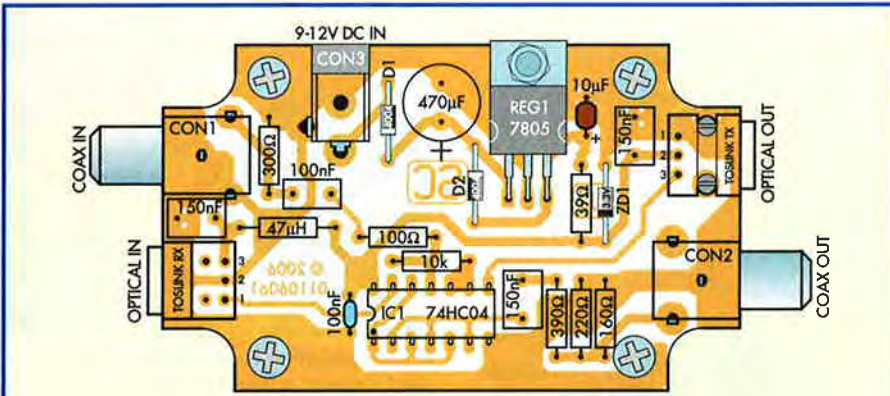


Fig.2: here's how to assemble the parts onto the PC board. Make sure that the semiconductors and electrolytic capacitors are correctly orientated.

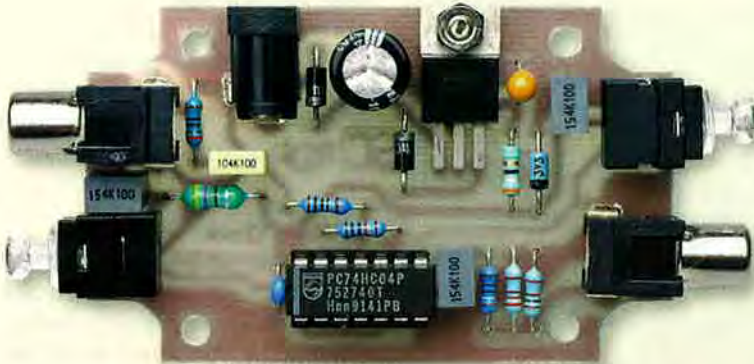

An IC socket was fitted to the prototype but you can solder the IC in if you wish. Note how the 3-terminal regulator (REG1) is mounted.

The two rectangular holes are for the Toslink optical transducers. These can be made by drilling a series of small holes around the inside of the marked cutouts, knocking out the centre pieces and filing to shape.

The four holes in the lid are for mounting the PC board. After drilling, these should each be fitted with an M3

x 10mm countersink-head screw, a star lockwasher and an M3 Nylon nut – ie, the Nylon nuts form the mounting pillars for the PC board assembly. That done, the PC board can be fitted in position and secured using four M3 metal nuts.

The final assembly step is to fit the lid assembly to the case. To do this, you

## Parts List

- 1 PC board, code 01106061, 76 x 46mm
- 1 UB5 Jiffy box, 83 x 54 x 31mm
- 1 Toslink optical receiver (Jaycar ZL-3002)
- 1 Toslink optical transmitter (Jaycar ZL-3000)
- 1 47µH RF choke (RFC1)
- 2 RCA sockets, PC-mount (CON1, CON2)
- 1 2.5mm concentric DC socket (CON3)
- 4 M3 x 10mm machine screw, csk head
- 4 M3 star lockwashers
- 1 M3 x 6mm machine screw, round head
- 5 M3 nuts, metal
- 4 M3 nuts, Nylon

### Semiconductors


- 1 74HC04 hex inverter (IC1)
- 1 7805 +5V regulator (REG1)
- 1 3.3V 1W zener diode (ZD1)
- 2 1N4004 diodes (D1,D2)

### Capacitors

- 1 470µF 25V RB electrolytic
- 1 10µF 16V tantalum
- 3 150nF MKT metallised polyester
- 1 100nF multilayer monolithic
- 1 100nF MKT metallised polyester
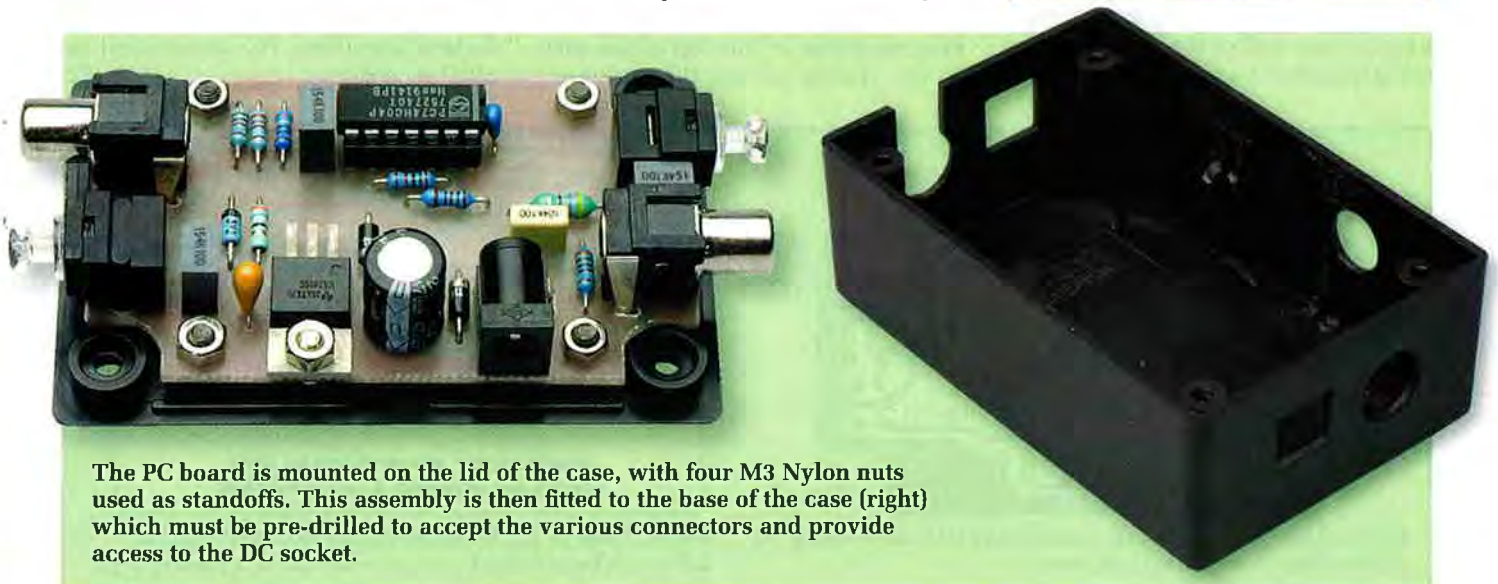
### Resistors (0.25W, 1%)

- 1 10kΩ
- 1 160Ω
- 1 390Ω
- 1 100Ω
- 1 300Ω
- 1 39Ω
- 1 220Ω



The PC board is mounted on the lid of the case, with four M3 Nylon nuts used as standoffs. This assembly is then fitted to the base of the case (right) which must be pre-drilled to accept the various connectors and provide access to the DC socket.

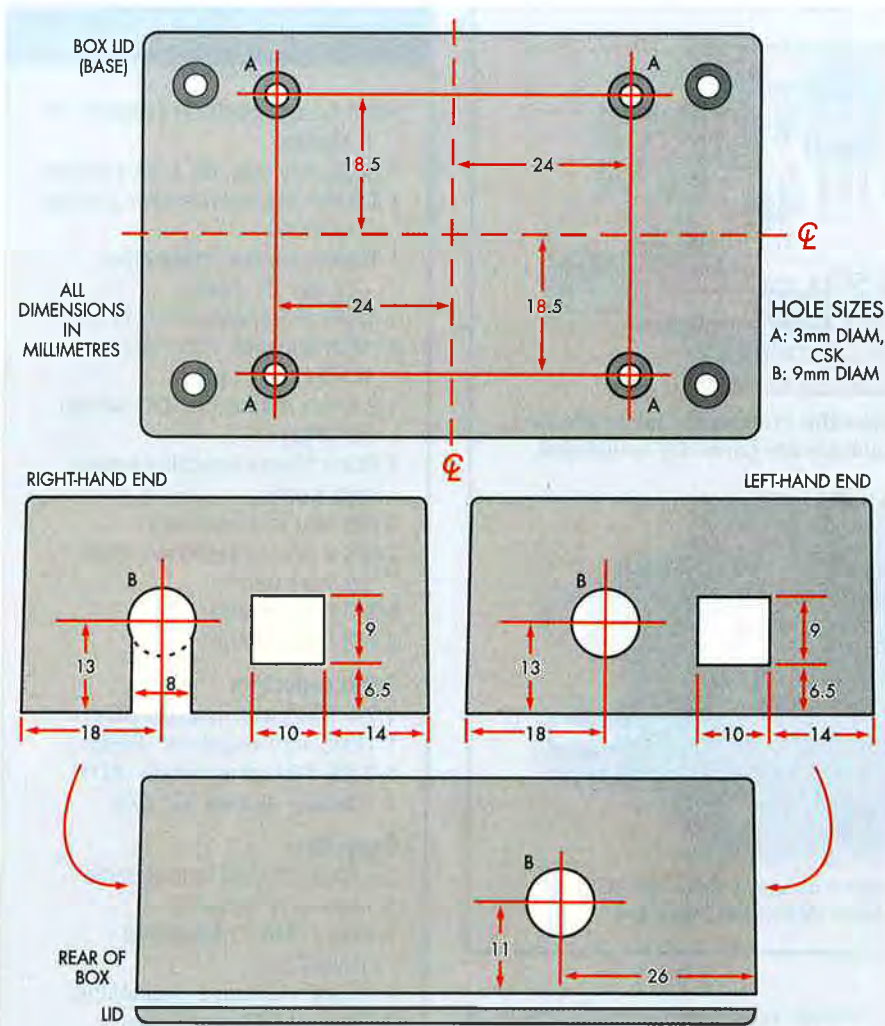


Fig.3: this full-size diagram can be used as a template to mark out and drill the various holes in the plastic case.

first have to remove plastic protection caps from the Toslink connectors. That done, it's just a matter of slipping the two input connectors through their holes in one end of the case and lowering the other (output) end of the lid

assembly into position (ie, by sliding CON2 through its 8mm-wide slot).

Now check that the power connector (CON3) is visible through its matching hole in the rear of the case. If not, you've got the lid the wrong



It's a good idea to leave the plastic dust caps in place on unused Toslink connectors, to keep dust off the lenses.

way around (just remove it, rotate it through 180° and replace it).

Finally, turn the complete assembly over and fasten the lid down using the four self-tapping screws provided. Your Two-Way SPDIF/Toslink Converter is now ready for use.

### Quick checkout

There are no setting-up adjustments but if you'd like to give it a quick functional check first, this is easily done. Simply apply power to CON3 from your 9-12V DC plugpack (centre pin positive) and check that a small beam of red light emerges from the Toslink transmitter on the righthand end of the box. If it is, the odds are that your converter is working as it should.

A "no red beam" condition means that you've probably connected one of the diodes the wrong way around, or wired up the DC power input plug with the wrong polarity. Otherwise, you can go ahead and use the finished converter to connect your new digital audio source to that otherwise incompatible SPDIF input on your home theatre amplifier, PC sound card or DVD recorder. **SC**

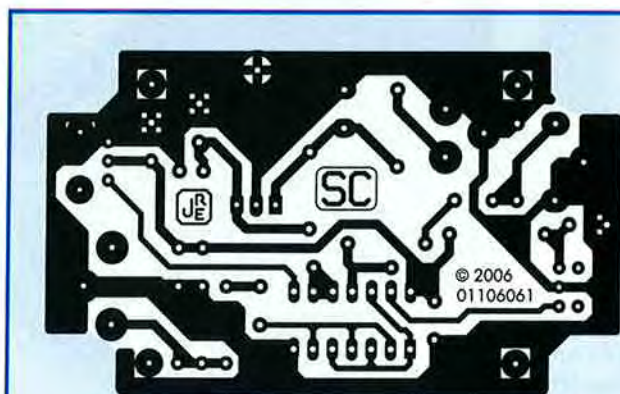


Fig.4: check your PCB against this full-size etching pattern before installing the parts.

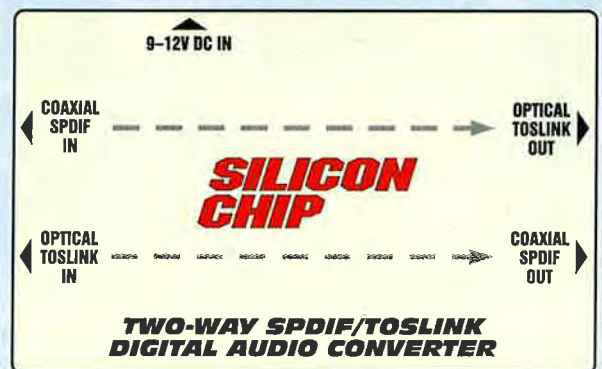


Fig.5: if you're not building from a kit, this full-size label can be attached using double-sided adhesive tape.