

TONE CONTROL CIRCUIT

This simple single-transistor circuit will give approximately 15 dB boost or cut at 100 Hz and 15 kHz respectively. A low noise audio type transistor is used, and the output can be fed

directly into any existing amplifier volume control to which the tone control is to be fitted.

The gain of the circuit is near unity when controls are set in the "flat" position.

