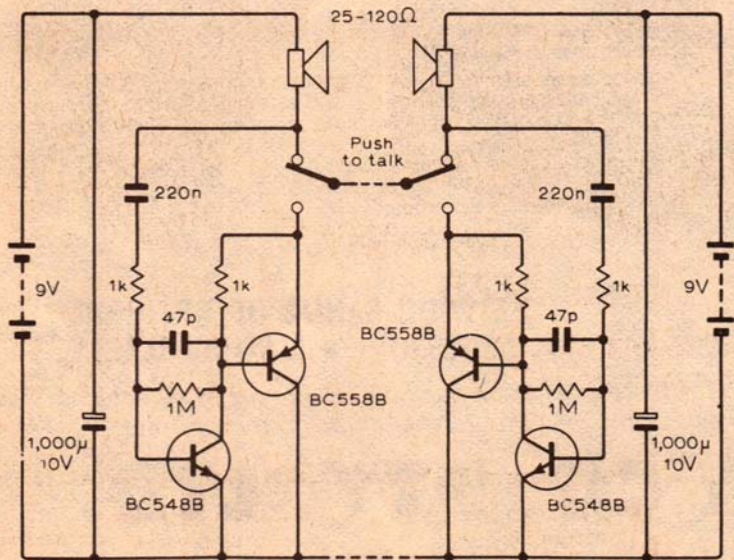


An interesting two-wire intercom



The circuit shows a simple battery powered two-station intercom which does not dissipate any standby power. If NiCd batteries are used, trickle

charging at one station will also charge the other through the loudspeakers. (By Ole Holmskov, in "Wireless World".)