

WAA-WAA EFFECTS PEDAL

ROBERT PENFOLD



How to easily and inexpensively add expression to your playing.

THE waa-waa effect has been popular with guitarists for many years now, and one reason for this popularity is that it provides an easy means of adding great expression to your playing. It is also a relatively simple effect that can be implemented using inexpensive circuitry.

A waa-waa unit is basically just a tunable filter that boosts a narrow band of frequencies. As the pedal is operated, the operating frequency of the filter is moved up and down, giving the familiar "waa-waa" sound. The filtering boosts certain harmonics in the signal, and operating the pedal changes the harmonics that are affected.

For good results, it is essential that the processed signal contains reasonably

strong harmonics, but an electric guitar is unlikely to be found lacking in this respect.

A waa-waa pedal represents an easy project for the home constructor as far as the electronics are concerned, but the mechanical side of construction can be problematic. The difficulty is that the effect is normally controlled by a pedal which operates a potentiometer. Producing a pedal mechanism that is genuinely reliable and will not let you down at the worst possible moment is more difficult than one might expect.

Most waa-waa units for the home constructor use some form of alternative approach that avoids the need for a pedal mechanism. The most simple of these

alternatives is to use a low frequency oscillator to automatically operate the effect at a preset rate, but this gives rather "mechanical" results with no real opportunity for the player to add expression to the music.

The other alternative, and the one used here, is to have the effect controlled via a pushbutton switch. The switch is foot operated, and acts as a sort of pseudo foot-pedal. Operating the switch results in the effect being swept upwards in frequency, and releasing the switch results in the effect being swept back down again.

This is not quite as versatile as using a conventional foot-pedal mechanism, since the pushbutton switch does not give any control over the rate at which the effect is swept up and down.

However, these rates are individually adjustable via front panel controls and can be set at appropriate rates prior to

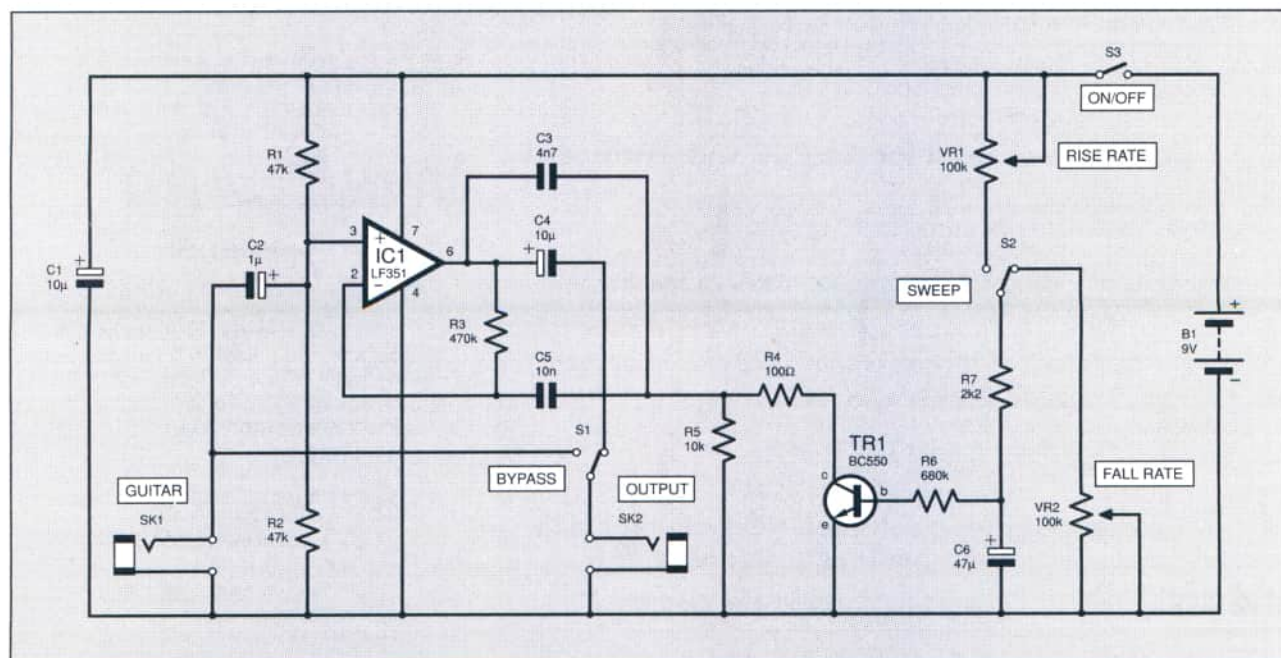


Fig.1. Complete circuit diagram for the Wah-Wah Effects Pedal.

commencing a piece. This gives the player much better control of the effect than simple automatic control, and does enable the effect to be used in an expressive fashion.

CIRCUIT OPERATION

The circuit diagram for the Waa-Waa Effects Pedal is shown in Fig.1. IC1 is an operational amplifier which is used in the non-inverting mode, with input biasing provided by resistors R1 and R2. These set the input impedance at 11 kilohms.


The negative feedback circuit includes a simple *R-C* (resistor-capacitor) network that provides frequency selective feedback, and produces a bandpass filter action. The configuration used is almost the standard op.amp bandpass filter circuit, with the frequency selective negative feedback provided by capacitors C3, C5 and resistor R3, together with the series resistance of R4 and R5.

These components set the centre frequency of the circuit at a middle audio range, but in this application we need the filter frequency to be variable over middle to high audio frequencies.

It is possible to tune the filter by adding a variable resistance in parallel with resistor R5. This is the purpose of transistor TR1, which acts as a sort of crude voltage controlled resistor. The resistance across TR1's collector (c) and emitter (e) terminals depends on its base (b) input current, with higher currents giving reduced collector to emitter resistance.

Resistor R6 effectively converts TR1 from current to voltage operation, and also provides a boost in input resistance. There is a slight drawback in using an ordinary bipolar transistor as a voltage controlled resistor, which is simply that it does not provide pure resistance.

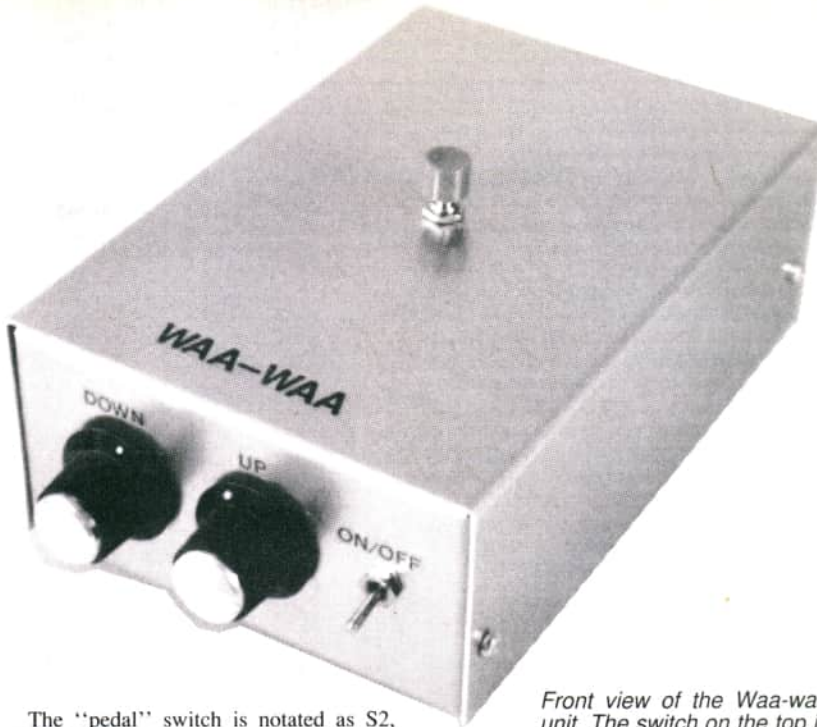Changes in the signal voltage result in variations in the effective resistance provided by TR1, which in turn produce distortion on the output signal. Hi-fi performance is not really essential in this application, but the distortion will be reasonably low provided the circuit is not fed with an excessive input level.



Front view of the Waa-waa unit. The switch on the top is the sweep control, S2.

The "pedal" switch is notated as S2, and it is biased to the position shown in Fig.1. Under standby conditions, no current flows into the base of TR1, and the resistance provided by TR1 is, therefore, so high that it has no significant affect on the circuit.

Operating S2 results in capacitor C6 starting to charge via potentiometer VR1 and resistor R7. As the charge potential on C6 rises TR1 receives an increasing base bias current. This results in its collector to emitter resistance steadily reducing, and the centre frequency of the filter being swept upwards.

This continues until the charge voltage on C6 reaches almost the full supply potential, but the filter frequency then remains constant until S2 is released. C6 then starts to discharge via R7 and VR2, causing the resistance provided by TR1 to increase and the centre frequency of the filter to decrease. This action continues until the charge on C6 drops below about 0.7 volts, at which point TR1 becomes cut off and once again has no significant affect on the circuit.

The required action is therefore obtained, with the filter frequency being swept upwards when S2 is operated, and swept back down again when it is released. VR1 controls the rate at which the filter frequency rises, and VR2 controls the rate at which the filter frequency falls. In both cases the rate of change is very rapid at minimum resistance, but takes several seconds for a full sweep at maximum resistance.

This type of voltage controlled bandpass filter is very simple, but it is slightly flawed in that the *Q* (quality) value of the filter rises as the operating frequency is increased. This results in a narrower response and higher maximum gain at high frequencies, and a broader response with lower maximum gain at low operating frequencies.


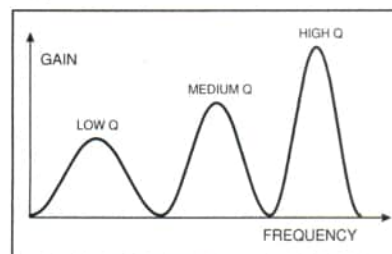


Fig.2. Filtered frequency response.

In Fig.2 is shown the general way in which the response changes as the filter frequency is altered. In practice, this does not seem to have a detrimental affect on results, and the effect obtained is perfectly acceptable. In fact, it is probably better to have things this way, as it avoids having a high level of boost on the fundamental signal, which could easily cause overloading.

Switch S1 enables the circuit to be bypassed when the waa-waa effect is not required.

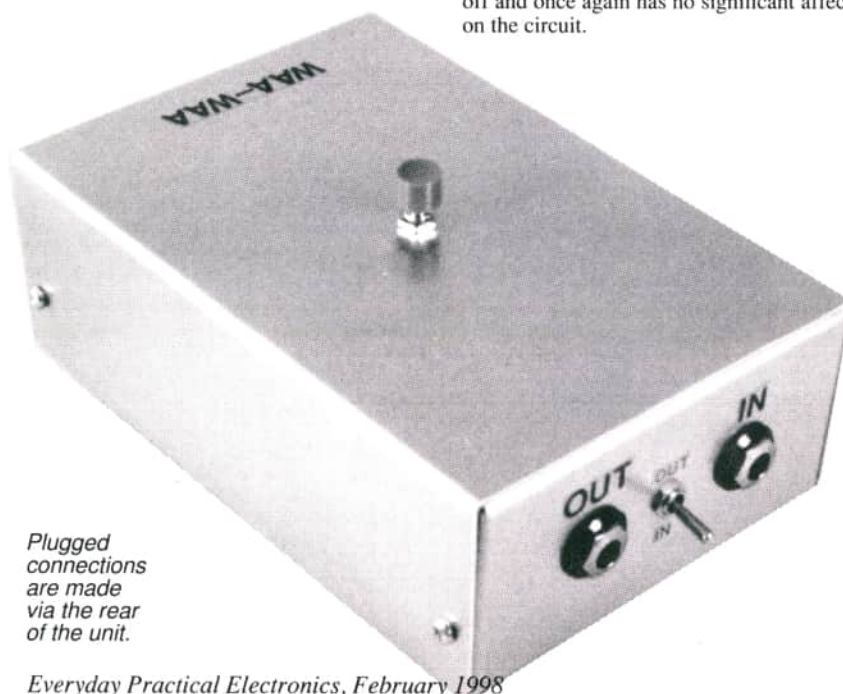The circuit is powered from a small 9V battery, and this should have a very long operating life as the current consumption of the circuit is typically just under two milliamps.



Plugged connections are made via the rear of the unit.

COMPONENTS

Resistors

R1, R2	47k (2 off)
R3	470k
R4	100Ω
R5	10k
R6	680k
R7	2k2

All 0.25W 5% carbon film

Potentiometers

VR1, VR2	100k rotary carbon lin. (2 off)
----------	---------------------------------

Capacitors

C1, C4	10μ radial elect. 25V (2 off)
C2	1μ radial elect. 50V
C3	4n7 mylar
C5	10n mylar
C6	47μ radial elect. 16V

Semiconductors

TR1	BC550 npn transistor
IC1	LF351N bifet op.amp

Miscellaneous

S1	s.p.d.t. min. toggle switch (see text)
S2	s.p.d.t. pushbutton switch (see text)
S3	s.p.s.t. min. toggle switch
SK1, SK2	standard mono jack socket (2 off)
B1	9V battery (PP3 size)
Printed circuit board, available from the EPE PCB Service, code 932; metal case (see text); control knob (2 off); battery connector; 8-pin d.i.l. socket; wire; solder; nuts and bolts, etc.	

Approx Cost
Guidance Only

£20

excluding batteries

See
SHOP
TALK
Page

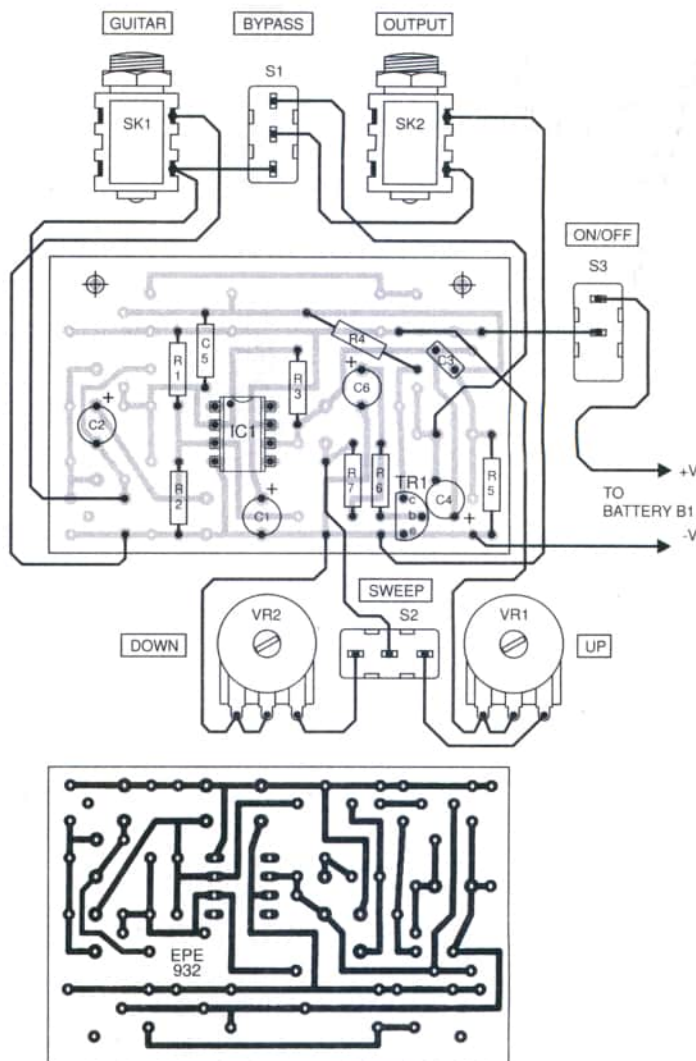


Fig.3. Printed circuit board component layout and full size underside copper foil track master pattern for the Waa-Waa Effects Pedal.

CONSTRUCTION


The Waa-Waa Effects Pedal is built using the EPE multi-project printed circuit board. This board is available from the EPE PCB Service, code 932.

Construction of this board is mainly straightforward, but the usual warning has to be given. This is not a custom printed circuit board in the conventional sense, and many of the holes in the board are left unused. Consequently, it is relatively easy to get a component fitted in the wrong place and extra care, therefore, has to be exercised when fitting the components.

The board's component overlay, master track pattern and hard wiring details are shown in Fig.3.

IC1 is not a static sensitive device, but it is a good idea to use a holder for any d.i.l. integrated circuit. Be careful to fit IC1 and the electrolytic capacitors with the correct orientation. From the electrical point of view, C3 and C5 can be any form of plastic foil capacitor, but mylar capacitors are the easiest type to fit into this layout.

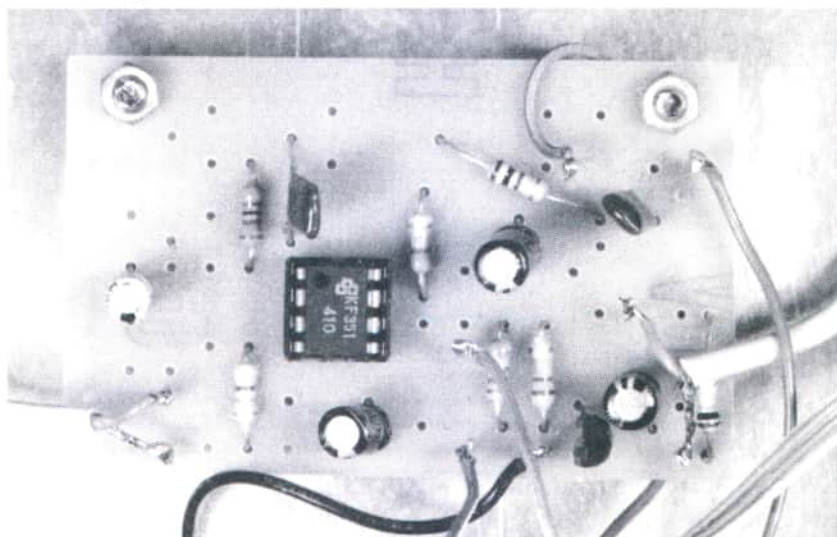Fit single-sided solder pins to the board at the points where connections will be made to the controls and sockets. "Tin" the tops of the pins with plenty of solder, but do not make any connections to them at this stage.



As this project will be controlled by foot, it is clearly essential for it to be housed in a tough case that will not crush or crack easily. It is also a good idea to use a metal case as this will provide the circuit with good screening from mains "hum" and other electrical noise.

A diecast aluminium box is ideal, but might prove to be rather expensive. A case of folded aluminium construction is just about strong enough, and represents a good low-cost alternative. It is possible to fit everything into quite a small case, but the use of a medium size box is

