

## 37 Musical Modulator

□ Feed this circuit a sample audio tone, and it

gives you back a musical note with selectable

### PARTS LIST FOR MUSICAL MODULATOR

**C1**—0.33- $\mu$ F capacitor, 35-WVDC

**C2, C3**—0.1- $\mu$ F mylar capacitor, 35-WVDC

**C4**—0.005- $\mu$ F electrolytic capacitor, 16-WVDC

**C5**—2.2- $\mu$ F electrolytic capacitor, 16-WVDC

**D1, D2**—1N914 diode

**IC1**—RCA CA3080

transconductance amp

**J1, J2**—phone jack

**Q1**—2N3904 NPN transistor

**R1**—9100-ohm,  $\frac{1}{2}$ -watt 10% resistor

**R2, R3, R4**—1000-ohm,  $\frac{1}{2}$ -watt 10% resistor

**R5**—2.2 Megohm-ohm,  $\frac{1}{2}$ -watt 10% resistor


**R6**—15,000-ohm,  $\frac{1}{2}$ -watt 10% resistor

**R7**—1 Megohm trimmer potentiometer

**R8, R9**—5600-ohm,  $\frac{1}{2}$ -watt 10% resistor

**R10, R11**—250,000 linear-taper potentiometer

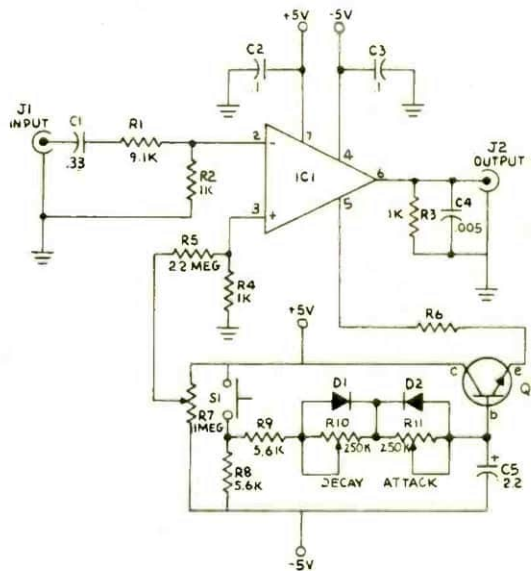**S1**—normally open SPST pushbutton switch



attack, sustain and decay. Input impedance is 10,000-ohms, output impedance is 1000-ohms, and the gain is unity. Best results will be obtained with signal inputs having amplitudes of 1-volt peak-to-peak or less. When S1 is pressed, the output volume rises at a rate determined by attack control R11. As long as S1 is pressed, the sound will be sustained. Releasing S1 causes the note to

decay at a rate determined by decay control R10. Try sine, square or triangular wave inputs for musical notes. With a noise input you can imitate such things as gunshots and explosions. Trimmer R7 can be adjusted to cancel out any audible "thumping" (noticeable with very rapid attack or decay).