

For some time our design team have been exploring the possibilities of a successor to the Formant, the Elektor synthesiser. Following the trend in technology, it was felt that a new concept was needed rather than just a rehash of a basic idea.

As regular readers know, the Curtis ICs have just recently made their appearance on this side of the water. These have been specifically designed for synthesisers and are probably the farthest that any company has dared to venture in terms of musical 'chips' so far. No

Throughout the series, readers will be expected to be familiar with the structure and operation of synthesisers in general. However, anyone who is new to this rather complex field can find the basics in FORMANT Book One.

the new synthesizer

programmable and portable

The success of the Elektor Formant synthesiser led us to the opinion that there is a great interest among our readers in the field of electronic musical instruments, especially synthesisers. The availability of the new Curtis IC described in last month's issue prompted us to embark on an entirely new design.

Since the size of the Formant did not lend itself to portability it was decided that the new synthesiser should be truly portable without any lack in terms of performance. The new synthesiser is of modular construction and can be expanded into a polyphonic instrument with 'programming' facilities. This, the first article in the series, explains the basics behind the design.



further prompting was required to look into the possibilities of utilising these new ICs to form the basis of an entirely new synthesiser.

It was felt that a modern synthesiser should take on a new look together with simpler operation. This is the first article in a series describing a truly portable and fully operational instrument that can be constructed in modular form allowing expansion up to a polyphonic keyboard. Further it was decided that the ability to 'program' different sounds was a facility that could be extremely useful.

In this article we begin by discussing the fundamentals behind the new design. Basically, the concept of the new synthesiser is that of a set of modules which could be combined in various ways leaving the reader free to build four different types of synthesisers using the same basic printed circuit boards. The possibilities are as follows:

1. a simple synthesiser
2. a simple synthesiser including a preset facility
3. a polyphonic synthesiser
4. a polyphonic synthesiser including a preset facility.

Why the preset facility?

You only have to analyse the synthesiser sounds used in Pop, Rock-and-Roll and Jazz to realize that the number of different presets required is surprisingly few. The audience recognizes the characteristic sound immediately, which is why a lot of rock bands use one particular sound regularly as a kind of 'label'. Furthermore, setting individual modules is extremely time-consuming and, on stage especially, this can be a real nuisance. Things can be simplified by providing a 'manual/preset' switch for all the elements required to produce a complex sound effect: filter frequencies, attack and decay times, VCO resonance factors, the interval between two VCOs or the envelope amplitude and so on. This is illustrated in figure 1 where inputs 1...4 are for the preset control voltages.

Since only very few variations are regularly used in practice, they can easily be stored as 'programs' and 'called' when needed with the aid of a single switch or a decimal keyboard. If only four situations are required per parameter, say, it is not even necessary to store the exact control voltage values in memory. CMOS analog switches can be used to select the desired voltages as shown in figure 2. In effect, this works like the rotary switch shown in figure 3b. The only data that must be stored is the 'setting of the switches'.

Obviously, the possibility of full manual control by means of knobs on the front panel must be maintained as an option — if only for special effects.

The individual boards belonging to the compact model do not need to be modified if the circuit is provided with a preset facility at a later date. The voltages which control the filter frequency, attack times, etc. are fed to the corresponding modules in the compact model by way of the potentiometers on the front panel.

For the preset option, provision must be made to break the connection from the front panel controls, as required, and drive the modules from some fixed (preset) voltage instead. As mentioned above, CMOS switches are the obvious solution. For the VCOs, four different preset voltages can be selected as shown in figure 3. The envelope waveform from an ADSR module can be 'voltage controlled' by passing it through a VCO (figure 4), and selecting any desired waveshape from the VCO output only slightly more complicated, illustrated in figure 5.

As can be seen, eight voltage control switches are needed to select the

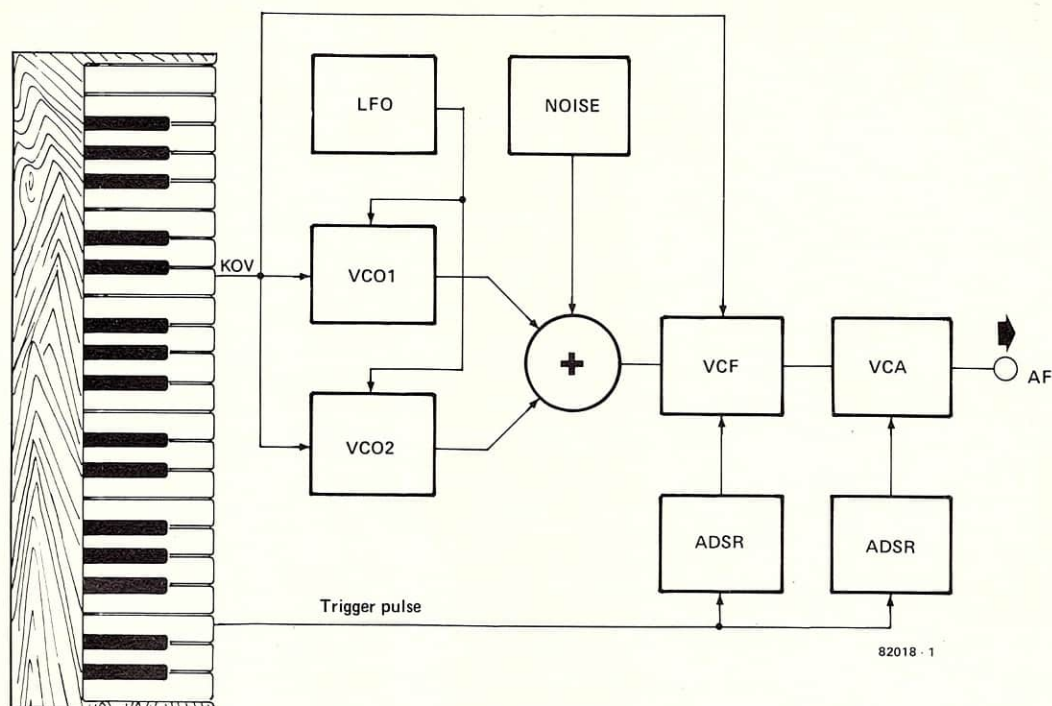


Figure 1. A block diagram of the most straightforward version of the new synthesiser. Two VCOs, a VCF, a VCA and two ADSR units are all that is needed for a 'bare-bones' system. With the addition of an LFO, which only produces a triangle signal, and a noise generator, a large number of different sounds can be achieved.

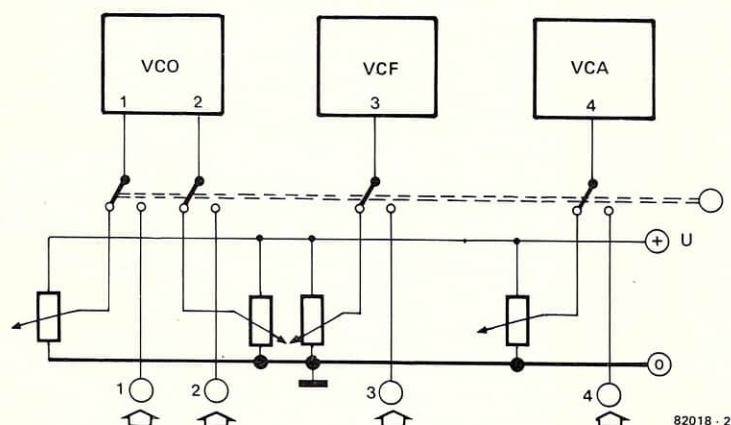


Figure 2. The control inputs 1...4 on the various boards can either be linked to the wipers of potentiometers on the front panel or to external control voltage inputs.

waveforms (but if a 4066 is used, only 2 ICs are necessary). The principle is fairly straightforward. When the preset/manual switch S2 in figure 5 is in position A, S1' in IC2 will be closed. The waveform can now be selected with S1. Since the analogue switches in IC3 are switched 'off' when the manual/preset switch S2 is in position A, the data at the BCD inputs will have no effect on switches S2'...S4' in IC2. Resistors R6...R10 make sure the switches are held fully 'off' when no voltage is applied to the control inputs. With S2 in position B, however, external data at the BCD inputs of IC3 will select the output waveshape.

As can be seen in figure 5, the octave 'range' switch and the fine tuning

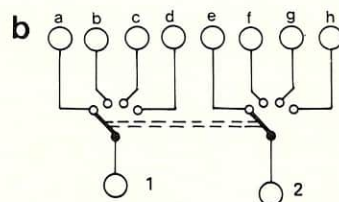
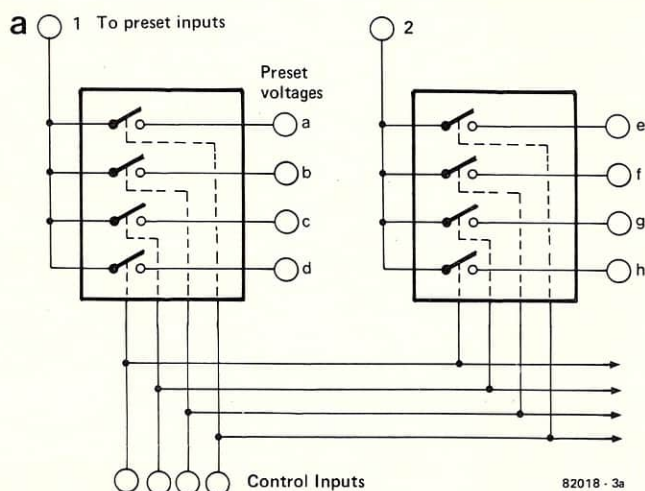


Figure 3. The circuit in figure 3a is little more than an electronic version of the rotary switch shown in figure 3b.

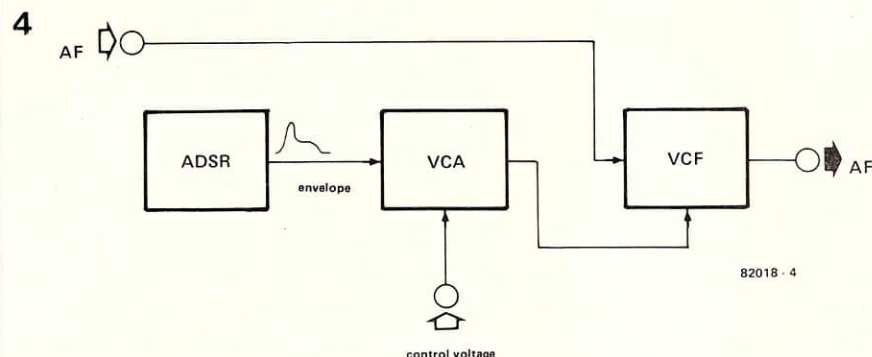


Figure 4. A VCA can be used to control the amplitude of the ADSR signal.

potentiometer are connected to the VCO control input via IC4, in the 'manual' mode. When S2 is switched to 'preset', the pre-programmed control voltage is selected instead.

Driving the preset inputs

Since the synthesiser is made up of individual modules it can be controlled with the aid of external voltage. That's all very well, but how can this be put into practice? As an example let's assume that sixteen preset voltages are required for any given setting. Corresponding digital information can

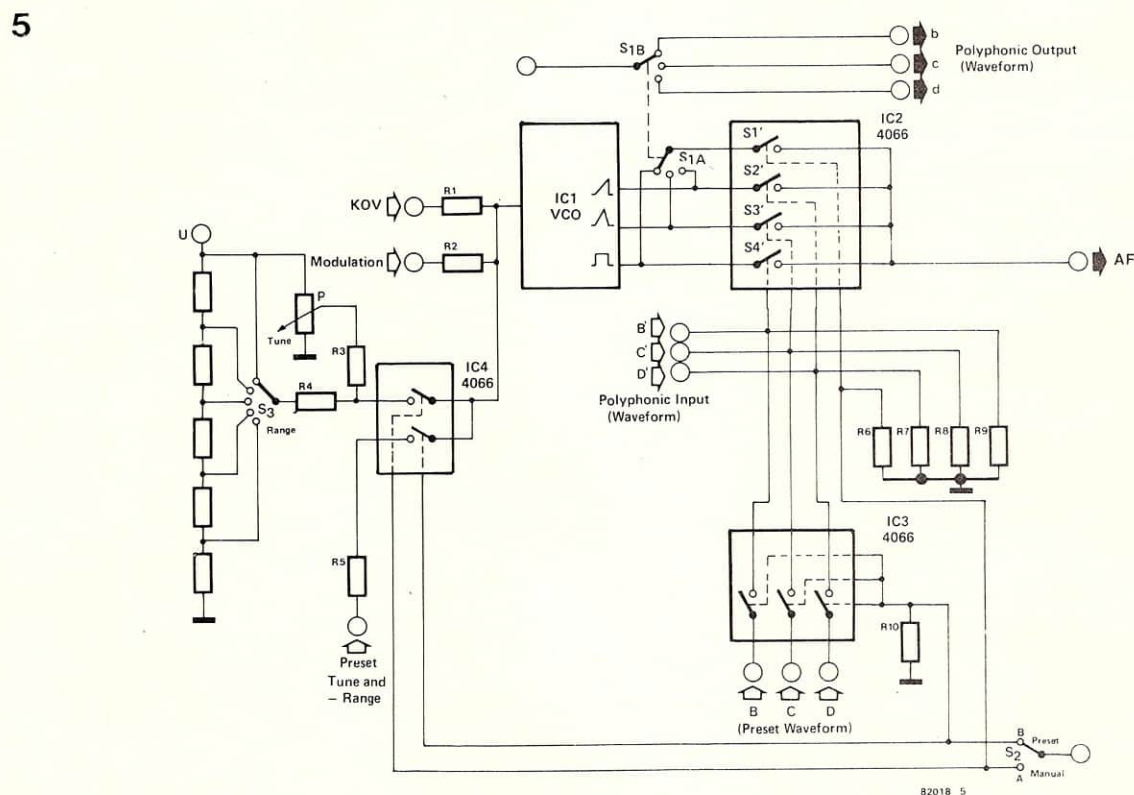


Figure 5. The complete VCO block diagram. The wiring of the CMOS switches gets rather complicated, since provision must be made for switching both the control voltage input and the output waveform.


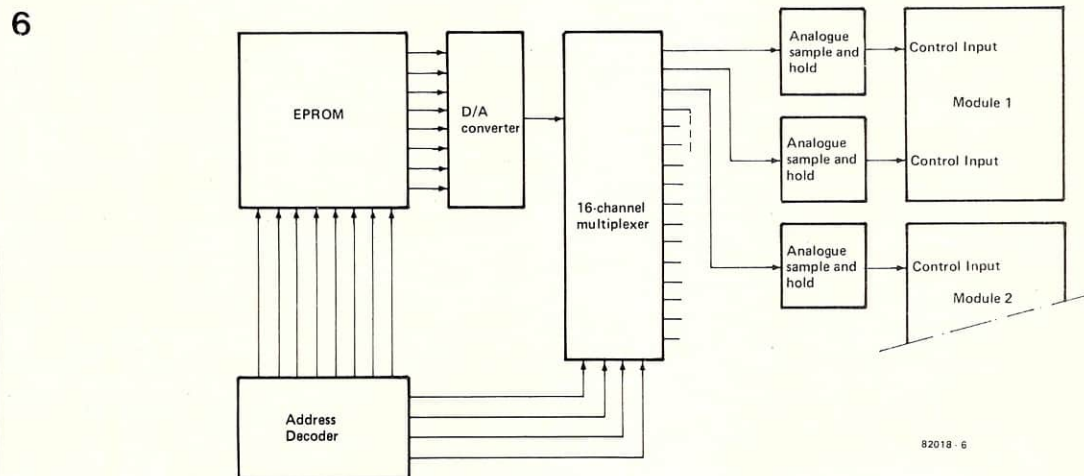


Figure 6. A simplified view of the preset circuit which can be included in an extended version of the synthesiser.

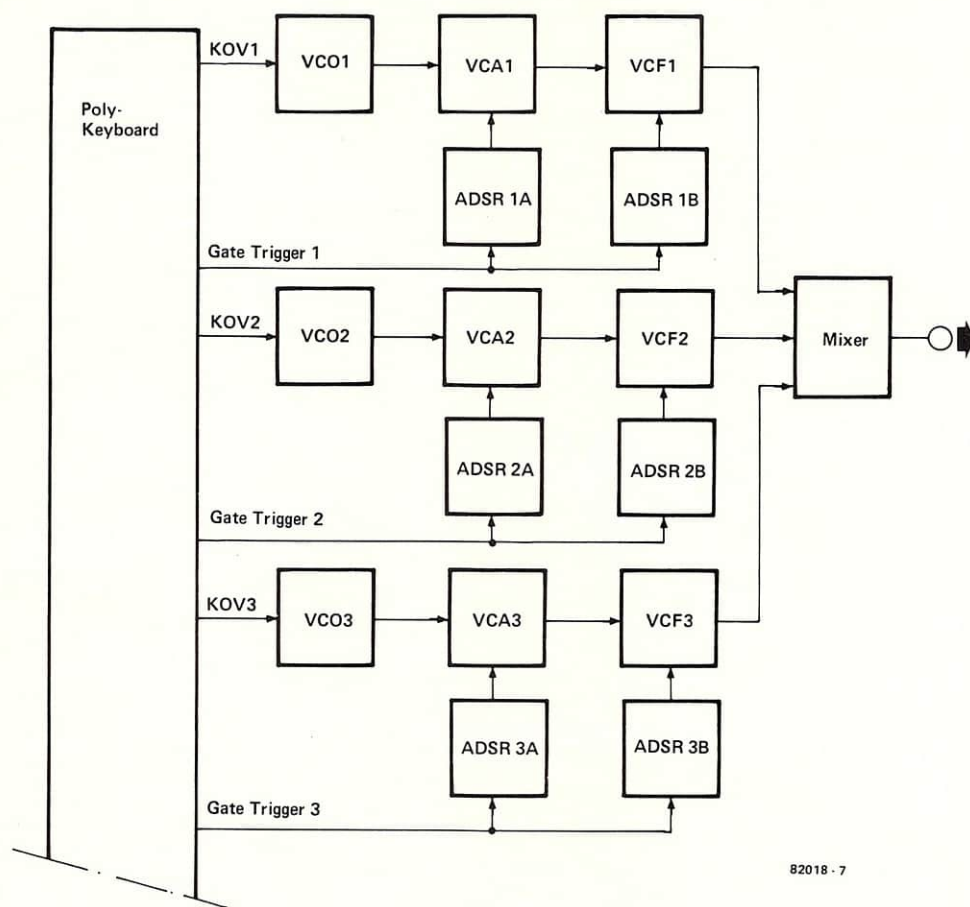

82018 - 7


Figure 7. The block diagram of a polyphonic synthesiser. A polyphonic keyboard provides various control voltages (KOV) and gate pulses which control a complete unit (VCO, VCA, VCF and two envelope generators).

stored in EPROM, as shown in Figure 6. The locations for any given key can be scanned in rapid succession and passed through a D/A converter and 16-channel (analogue!) multiplexer to sixteen sample-and-hold capacitors. These, in turn, drive the control inputs of the various modules.

8

The polyphonic version

In the polyphonic version (Figure 7) the number of basic units required depends on the number of keys that are to be played at the same time. Each key has to be provided with a VCO, a VCF, a VCA and the corresponding envelope generators. All the parameters are controlled centrally either by the knobs or switches on the front panel or by stored preset information. This means that when the synthesiser is expanded into a polyphonic instrument there is no need to modify the front panel. This has the advantage that the user does not have to buy everything at once; instead, the monophonic unit can be extended by adding other boards. It is important however to have a polyphonic keyboard with separate control voltage outputs.

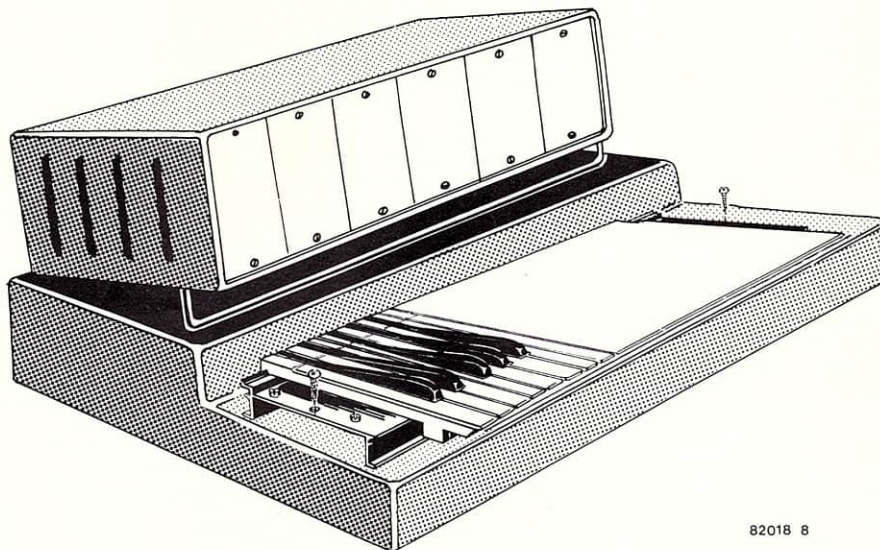

82018 8

Figure 8. The compact synthesiser version can be housed in a small case and is truly portable. The expanded version will require a second case which is connected to the first by way of a multicore cable. For monophonic purposes the FORMANT keyboard can be used.