

27 Metronome

□ Transforming IC pulses into sound, this tiny ticker goes both tick *and* tock, at a rate of about 2

seconds per tic to 6 tocks per second. The timing capacitor, C1, should be a low leakage mylar type

PARTS LIST FOR METRONOME

C1—2 to 5- μ F low-leakage mylar or tantalum capacitor, 15 VDC

C2—2.2 to 10- μ F electrolytic capacitor, 15 VDC

D1, D2, D3—1N4148 diode

IC1—4011A quad NAND gate

Q1—2N4401 transistor

Q2—2N4403 transistor


R1—47,000-ohm, $\frac{1}{2}$ -watt resistor

R2, R3—500,000-ohm linear-taper potentiometer

R4, R6—10-ohm, $\frac{1}{2}$ -watt resistor

R5—1,000-ohm linear-taper potentiometer

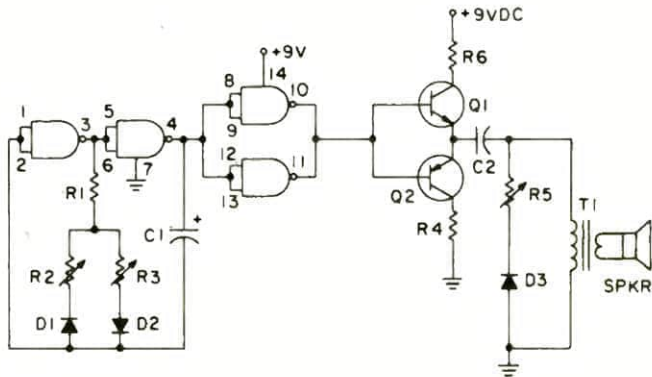T1—audio output transformer 500-ohm primary/8-ohm secondary



of about 2- μ F or else a quality tantalum of about 4.7- μ F. Although the reversed flow of current through the transformer's primary winding causes a different sound in the speaker from the positive-

going inrush, diode D3 and potentiometer R5 can be added to make the "tock" more definitive in its sound quality.