

Sound Effects Generator

This circuit was sent to us by **Tom Mollenmane**, aged 14. It is a simple sound generator, the frequency depending on the values in the RC network consisting of R1, C1 and VR1. The variable resistor VR2 is inserted to let you make allowance for changes in the battery voltage as it decays.

