

Noise Simulator

Sick of being woken by noisy neighbours or traffic? Fed up with barking dogs?

The EA Noise Simulator provides a soothing noise, like rain on the roof or waves on the beach, to mask the sounds that irritate.

As many flat dwellers will know, modern high density residential tend to have poor sound proofing. Between the numerous TV sets, stereo systems, tomcats, and noisy vehicles in the vicinity, the devotee of serenity can be driven to the point of distraction. Of course, some people have a high level of tolerance for noise pollution but, for those unfortunates who resort to stuffing their ears with cotton wool at 2am so that they can get some peace, the Noise Simulator may be a more pleasant solution.

The problem of getting a good


“night’s” sleep is more acute for shift workers who may in fact be trying to sleep during the day. And tinnitus sufferers, no matter when they are trying to sleep, have to put up with continual ringing in their ears. Both groups of people could benefit from a Noise Simulator.

There are, of course, other ways to mask irritating sounds. An air conditioner provides a useful pseudo white noise source but is certainly not viable in this capacity alone. Similarly, a TV set tuned between stations may help but who could justify its all night

operation. A radio tuned between stations can be quite acceptable — provided it has a tone control and can be powered from the mains. It should preferably have a large speaker (15cm or more). If your radio doesn’t quite fit the bill, or is not portable, then a Noise Simulator may be a better solution.


There is another aspect of the Noise Simulator’s operation which diverges slightly from the original concept. The noise can be modulated. In fact the design incorporates two modulation circuits which can provide a number of familiar sounds. The most startling is the surf simulation — sounds just like the beach with a high surf. This may be useful as a sound effect for recording or theatrical effects.

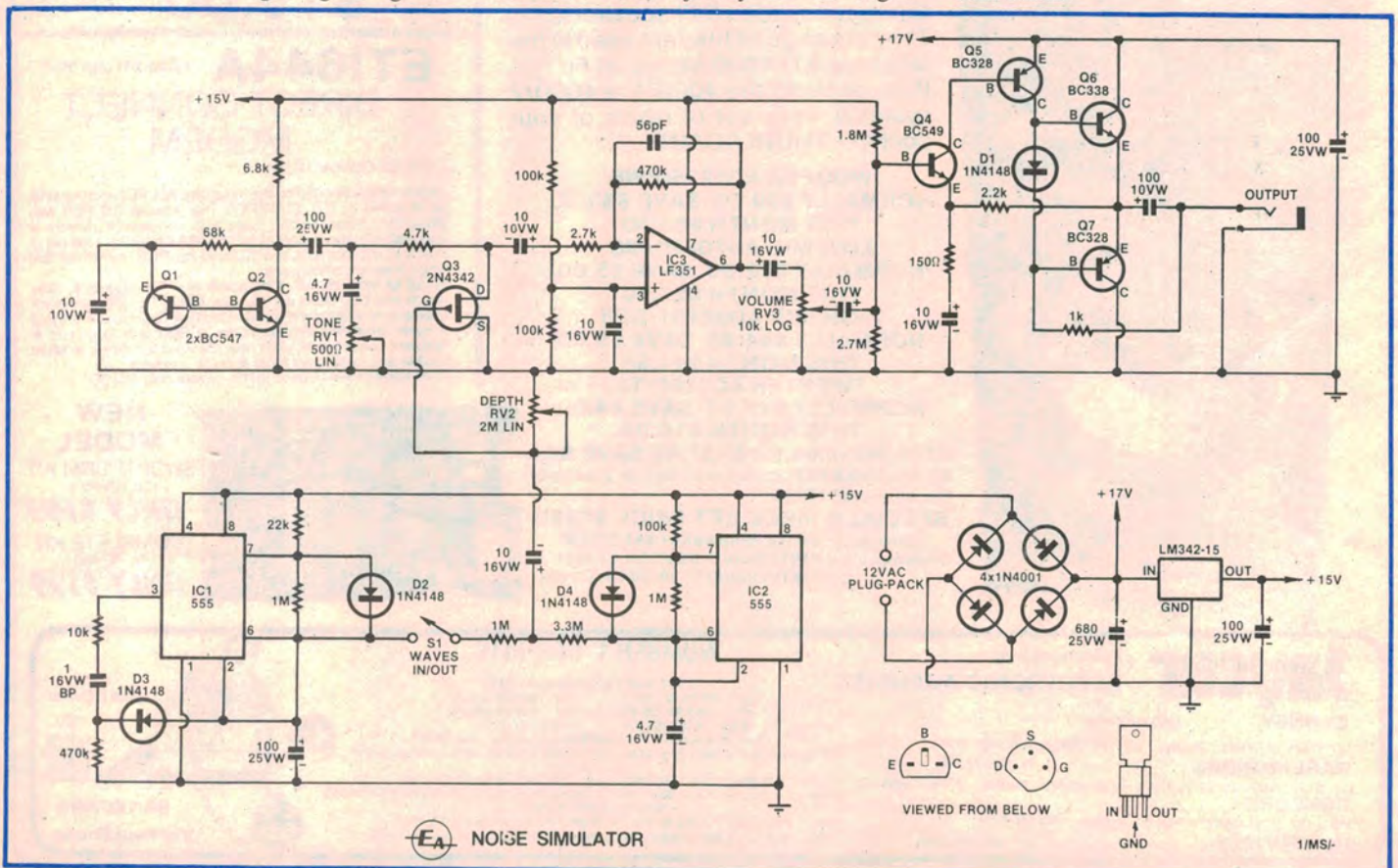The depth of modulation can be adjusted so that the sound is more like that of a beach in the distance. Or the “waves” can be switched out to leave a simple repetitive modulation more like a rain storm.





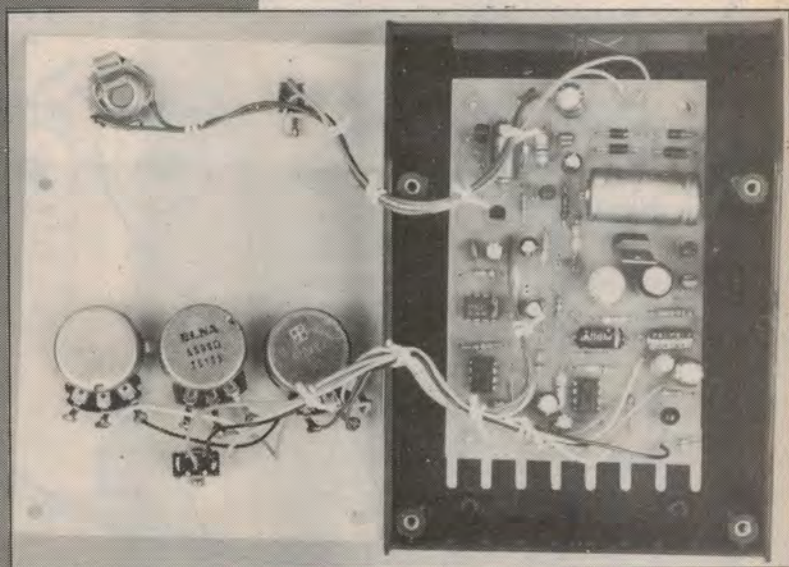Left: the finished unit and, below, interior shot showing board assembly and controls.



We estimate that the current cost of components for this project is approximately

\$30

This includes sales tax but not the cost of a plugpack.

Part of the inspiration for this project came from an advertisement in an overseas magazine. We had already decided to design a modified white noise generator as a sound masker. We were undecided with respect to the surf simulation, until the advertisement. This described a device almost identical in concept, except that it had surf, rain and waterfall simulation. Besides noise masking, there was a claimed increase in "Alpha" sleep (we suppose that's an advantage — we're not too sure what "Alpha" sleep is!).

We are certain, however, that sleeping is preferable to lying in bed pondering the most satisfying form of retribution to the various noisy miscreants.

White noise

Actually, "white" noise — an equal distribution of sound energy across the audio spectrum — is not ideal for the function of noise masking. It tends to sound too urgent and irritating, like a tyre being deflated rapidly. Far more acceptable is a modified white noise, ie, with some of the high frequency content removed. The Noise Simulator has a tone control which provides an adjustable amount of treble cut. This can vary the sound from a hiss (useful for the surf simulation) to a rumble.

To mask irritating sounds, a rumble is

the preferred noise. Most people will quickly become oblivious to this and hopefully the offending sounds will be relegated to "background" where they are not so troublesome.

As well as the big "breakers", we found that small fill-in waves were needed. It just doesn't sound right to have a thunderous wave arriving periodically with virtual silence in between. The circuit is designed so that the "big" waves and "little" waves can interact, producing a moderate amount of irregularity in the sound.

How it works

The most important parts of the circuit are the white noise generator and the amplifier. This accounts for about half of the components. The rest are used to derive the control necessary for the "effects" — it turns out that a convincing wave sound requires a surprising circuit complexity.

The white noise is actually generated by a reverse biased BC547 (Q1). Initially, various diodes were tried in this role but the BC547 proved more suitable for low voltage operation. Even with this device, a useful amount of white noise cannot be generated with a power supply of much less than 11V.


Given that the project may be operating for hours at a time, and the

voltage limitation of the BC547, batteries are clearly out. Instead, a 12VAC plugpack is used. In fact, the output of these plugpacks will frequently be closer to 13V for this circuit, yielding 18V after rectification. Only the power amplifier section of the circuit operates directly from this "raw" supply. The rest of the circuit is powered via a 15V regulator.

Amplification of the white noise is provided by Q2, another BC547. About 600mV of signal will appear at its collector. This is fed to the tone control which consists of a 4.7 μ F capacitor and 500 Ω potentiometer. Quite severe treble cut can be achieved with this control, providing the desired rumble.

The modified white noise is taken from the tone control and fed to the amplifier section of the circuit. The amount of noise reaching the amplifier can be affected by the modulation circuitry, but for the moment, assume that this is not working. A steady level of noise would therefore reach the inverting input (pin 2) of IC3. This is a FET input op-amp (LF351 or TL071) configured as an inverting amplifier with a gain of 37.

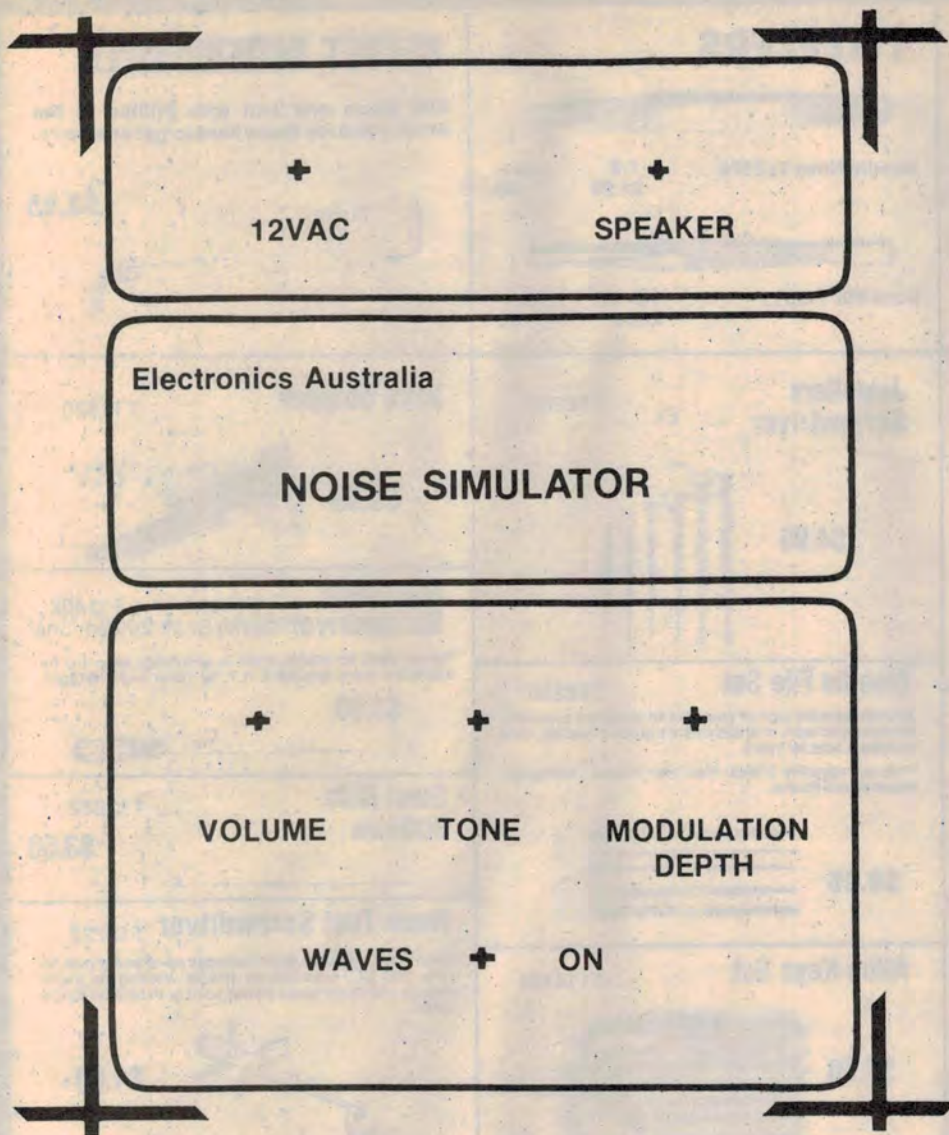From IC3, the signal is fed to a 10k Ω volume control and subsequently to a four transistor power amplifier. With the tone control set for maximum treble cut, much of the sound energy has been removed from the signal. Consequently, quite high volume settings may be needed for a large room.



The operation of IC1, then, is as follows: about once every 15s, the wave begins to build up. This takes only three or four seconds whereupon the wave breaks. For about 0.5s immediately after the break, a very rapid decay occurs. After this period, decay continues more slowly until the beginning of the next build-up.

Switch S1 in the output circuit of IC1 allows the sound of the large waves to be switched in or out of circuit as required. Since the output of IC1 is coupled to the FET gate circuit via a 1M Ω resistor, compared to the 3.3M Ω coupling resistor of IC2, it has a far greater effect on the sound.

Construction

The printed circuit board (PCB) is coded 84ms4 and measures 72 x 110mm. There is one wire link to be mounted on the board — this should be done first. The other components can then be mounted, starting with the small horizontal devices such as resistors and diodes.

We have prepared a Scotchcal front panel label which suits the plastic sloping front project box. If you intend to use this label apply it first so that it can be used for a template for drilling the front panel.

When mounting the input sockets, make certain that the 12VAC input and the speaker output do not share a common earth. This means that, with a metal front panel or Scotchcal label, one of the sockets (preferably the 12VAC socket) should be insulated. This can be done by placing a short length — about 2mm — of plastic tubing over the shaft of the socket and placing an insulated

PARTS LIST

- 1 PCB, 72 x 110mm, code 84ms4
- 1 plastic project box (Bimbox No. 6005 or similar)
- 1 6.5mm panel socket (mono)
- 1 6.5mm jack plug (mono)
- 1 3.5mm panel socket (mono)
- 1 3.5mm jack plug (mono)
- 3 knobs to suit potentiometers
- 1 SPST toggle switch

Semiconductors

- 2 BC547 NPN transistors
- 1 BC549 NPN transistor
- 1 BC338 NPN transistor
- 2 BC328 PNP transistors
- 1 2N4342 P-channel FET
- 1 LF351 or T1071 FET input op-amp
- 2 555 timer ICs
- 1 LM342-15 or LM340-15 regulator
- 4 1N4001 diodes
- 4 1N4148 diodes

Capacitors

- 1 680 μ F/25VW axial electrolytic
- 4 100 μ F/25VW PC electrolytics
- 1 100 μ F/10VW axial electrolytic
- 5 10 μ F/16VW PC electrolytics
- 2 10 μ F/10VW axial electrolytics
- 2 4.7 μ F/16VW PC electrolytics
- 1 1 μ F/16VW bipolar electrolytic
- 1 56pF ceramic

Resistors

- 1 x 3.3M Ω , 1 x 2.7M Ω , 1 x 1.8M Ω ,
- 3 x 1M Ω , 1 x 470k Ω , 4 x 100k Ω , 1 x 68k Ω , 1 x 22k Ω , 1 x 10k Ω , 1 x 6.8k Ω , 1 x 4.7k Ω , 1 x 2.7 Ω , 1 x 2.2k Ω , 1 x 1k Ω , 1 x 150 Ω , 1 x 2.2M Ω log potentiometer, 1 x 10k Ω log potentiometer, 1 x 500 Ω linear potentiometer.

washer under the retaining nut.

To test the Noise Simulator, set the volume to near minimum, the tone to low and the waves to Off. After applying power there will be a delay of about 2 to 4 seconds before any sound is produced (it takes that long for the white noise generator to become operative). Once the sound begins, vary the controls to verify the operation. Remember that only one wave occurs every 15 seconds.

BASIC ELECTRONICS

For the beginner, or for the hobbyist as a reference book and almost certainly the most widely used manual on basic electronics in Australia.

It is used by radio clubs, in secondary schools and colleges, and in WIA youth radio clubs. Begins with the electron, introduces and explains components and circuit concepts, details the construction of simple receivers. Separate chapters on test instruments, servicing amateur radio, audio techniques, stereo sound reproduction.

Available from "Electronics Australia", 57 Regent St, Chippendale 2008. PRICE \$4.50 OR by mail order from "Electronics Australia", PO Box 163, Chippendale 2008. PRICE \$5.40.