



Four-input mixer

Mr D. Marzolla of Leichhardt claims that this mixer circuit has very low current drain and can give an operating life of three to four months from a No. 216 9-volt battery with moderate use.

The input impedance is 47k and the gain of the mixer is 3 dB. Perhaps a good use for those old germanium transistors you were going to throw out but knew they would come in handy sometime!

Any ideas?