

designideas

READERS SOLVE DESIGN PROBLEMS

Audio-test accessory isolates and matches loads

Richard M Kurzrok, RMK Consultants, Queens Village, NY


Connecting a 600Ω audio circuit to a 50 or 75Ω circuit or test instrument requires an impedance-matching circuit or, when isolation of the circuits is necessary, a transformer. Both approaches offer advantages and disadvantages. A conventional transformer can match impedances with low typical losses of 1.5 dB, provide dc isolation, and operate from either a balanced or an unbalanced, 600Ω primary circuit. A high-quality transformer's pass-

band can accommodate an audio-frequency range of 300 Hz to 15 kHz with minimal amplitude variation. However, transformers that can match 600 to 50 or 75Ω may not be readily available or may command a cost premium.

A minimum-loss, fixed-value impedance-matching circuit, or pad, provides frequency-invariant audio-impedance transformation and can comprise as few as two resistors. Although a pad can provide useful impedance

TABLE 1 INSERTION LOSS VERSUS FREQUENCY

| Frequency (kHz) | Insertion loss (dB) 600 to 50Ω | Insertion loss (dB) 600 to 75Ω |
|-----------------|--------------------------------|--------------------------------|
| 0.1 | 11.7 | 8.7 |
| 0.3 | 10 | 7 |
| 0.5 | 9.5 | 6.7 |
| 1 | 9.2 | 6.5 |
| 2 | 9 | 6.3 |
| 5 | 8.9 | 6.1 |
| 10 | 8.8 | 6.1 |
| 20 | 8.8 | 6 |
| 50 | 8.9 | 6.1 |
| 100 | 9.5 | 6.7 |

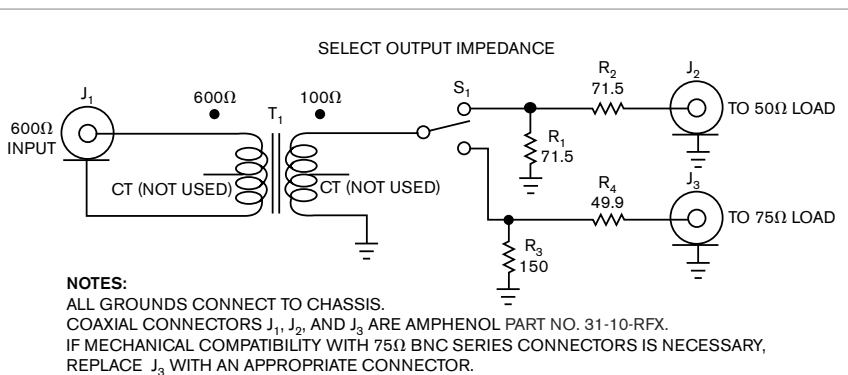

DIs Inside

78 One oscillator drives multiple solid-state relays

80 Low-dropout linear regulators double as voltage-supervisor circuits

84 External components provide true shutdown for boost converter

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to edndesignideas@reedbusiness.com.

matching, it introduces a significant insertion loss of 14.8 dB for a 600-to-75Ω transformation or 16.6 dB for a 600-to-50Ω transformation, either of which might impose an unacceptable loss of dynamic range.

Part of a suite of test accessories, this low-cost, switchable, dual-impedance transformation circuit comprises a single conventional transformer and two minimum-loss pads (Reference 1). A single inexpensive, conventional transformer steps down the 600Ω primary input impedance to an intermediate impedance level of 100Ω (Figure 1). Switch S₁ selects a 100 to 50Ω or a 100 to 75Ω minimum-loss pad. Construction of the unit involves noncritical point-to-point wiring, although this design uses a Hammond 1590LB die-cast-aluminum box to provide shielding and a rugged enclosure to support three Amphenol (www.amphenolrf.com) RFX series BNC panel-mounted, insulated-frame input and output jacks. T₁ is a Mouser Electronics (www.mouser.com) 42TM031 audio transformer, and the resistors are 0.5W, metal-film units with ±1% tolerances. With quantity discounts, the overall bill-of-materials cost is less than \$20.

To verify frequency response and

Figure 1 A handful of passive components creates a handy test fixture for matching impedances in audio-test circuits.

designideas

attenuation in a 600Ω test setup, connect two identical units back to back through their 50 or 75Ω terminals. You obtain the measured data (**Table 1**) for a single unit by halving the 600 -to- 600Ω transmission-loss measurements.

Calculated insertion loss for the 100 to 50Ω minimum-loss pad is 7.7 dB, and insertion loss for the 100 to 75Ω minimum-loss pad is 4.8 dB. Subtracting these values from the measured losses indicates that the transformer con-

tributes a midband loss of 1.3 to 1.5 dB. Insertion loss due to stray coupling from the selected output port to an unused output exceeds 40 dB. Combining a conventional transformer with two minimum-loss pads takes advantage of the best of both techniques.

The low-cost transformer contributes moderate insertion losses and provides dc isolation and good frequency response. In addition, the transformer's low-frequency roll-off

helps reduce 60 -Hz hum and low-frequency noise. The electrically isolated input jack allows connection of the transformer's input to balanced or grounded 600Ω sources.**EDN**

REFERENCE

■ Kurzrok, Richard M, "Simple Lab-Built Test Accessories for RF, IF, Baseband, and Audio," *High Frequency Electronics*, May 2003, pg 60.