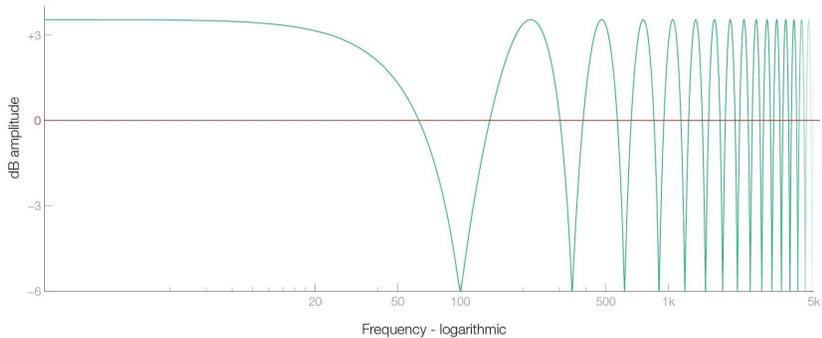


ABSOLUTE PHASE IN AUDIO GEAR

DM Fraser
Radial Engineering Ltd.

In any piece of audio gear that does not have variable phase shift it is important that all inputs and outputs to be in phase. This includes intermediate looping sends and returns. This is important because if signals reaching the speakers are unintentionally out of phase with other parts of the signal off cancellations and reinforcements may occur.

Sometimes one gets a comb filter effect in the frequency response such as shown to the right.




COMB FILTER



This is critical even in intermediate loops. Because the output is sometimes used as a tap for some intermediate use. While the return may be used as an input when a user only wants to use part of the product. It cannot be assumed that loops will only be used as intended.

To keep track of the phase through a product, the writer puts “+” and “-“ signs along connections in the schematic.

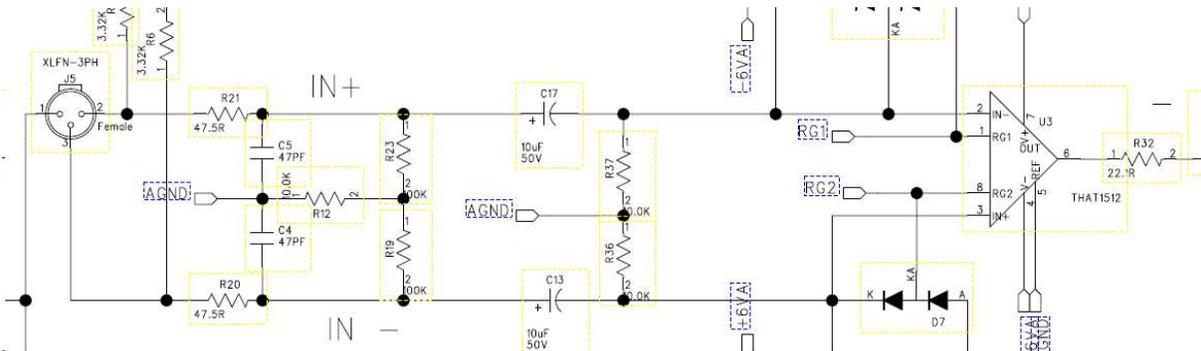Using the microphone input of the Voco Loco as an example, on the XLR input pin 2 is always considered the + phase and pin 3 is the - phase.




It can be seen the Pin 2 input is feeding the IN- pin on U3 which results in inverted phase on the output indicated by - sign. The reason for this inversion was that it was found that when the entire product was designed with the + in feeding IN+ the loop send was out of phase. Swapping the inputs of U3 was the easiest thing to do to bring the loop send int phase. It must be noted that U3 is a


special microphone pre-amp chip and not a standard opamp. This use of the +/- symbols made it easy to predict the phase.

In doing this sort of thing we try not to say the - phase in 180 degrees out of phase. That is because this describes a time delay. In this case the peak of the - phase is occurring at exactly the same time as the + phase. Except that the signal is inverted. So we just say we have an in phase signal or an inverted signal.

The following stage is a standard Baxandal tone control with bas and treble controls. Though in pro audio we avoid such consumer grade terms and refer to these as LF and HF EQ. It is to be noted that the signal enters into the CW (clockwise) ends of the controls. The wipers connect to the - inputs of the opamp which means this is an inverting circuit. Because the signal entering from the previous circuit was inverted, this inverting circuit puts the signal back into phase as indicated with a + sign in the TONE_OUT line.

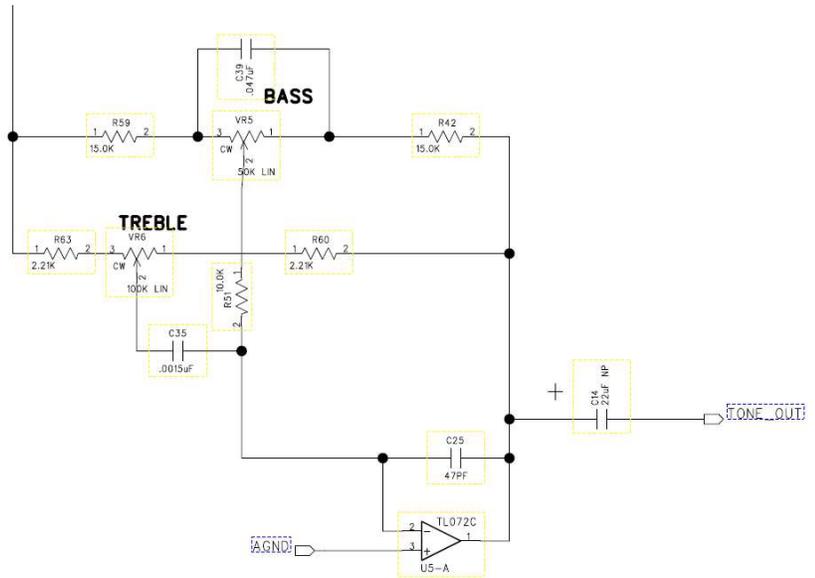

LOOP PHASE

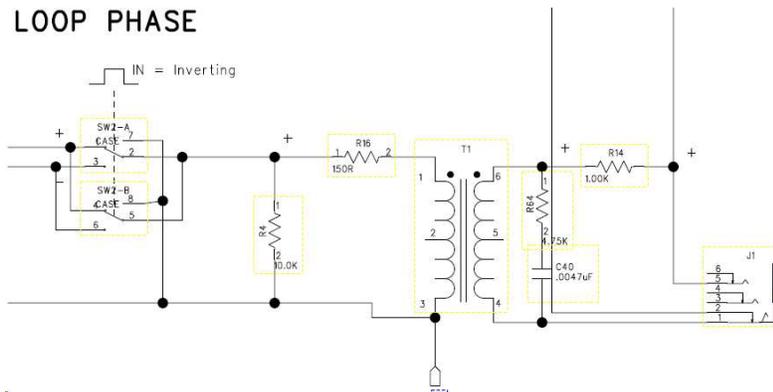

Here in the effects send circuit we always show the switches in the OUT position. In this case for a phase switch it is the position where the signal stays in phase Thus there are + signs on both sides.

On the transformer there is a dot at one end of each winding's symbol. If the dots are aligned, the phase will stay the same. Thus by feeding a + phase signal into pit 1 with the dot and we make the pin with the dot on the secondary is the "hot" lead, phase will be maintained through the transformer. Or if pins 4 and 5 were reversed then the output signal would be of inverted phase. But here we wanted phase to be maintained. These dots or some other indication may or may not be on the actual transformer.

