

Radon  
monitor

# ON TOR



PAUL NEHER

## monitor to detect a possible health threat in le doing it, learn more about radioactivity.

environmental radon in excess of the natural rate because of the time they spend indoors. This first article explains what radon is, why it is a health hazard, and the importance of knowing the level of radon in the rooms of your house where you spend most of your time while indoors. It also includes the information needed to build the ionization chamber, its amplifier circuitry, and alternative circuits for charging the chamber's internal high-voltage capacitor to 500 volts.

The second part of this article covers pulse-rate measurement, instrument calibration, and the conversion of pulse rates to radon density units. The article also offers alternative methods and circuits for performing these functions.

Even if the BERM is only crudely calibrated, it can warn you of unsafe radon levels in your home. However, when properly calibrated, it can give readings that compare favorably with those obtained from professional radon monitoring instru-

to-point wiring difficult. An etched and drilled PC board is available from the source mentioned in the parts list. Foil patterns are provided here for readers who wish to make their own boards. The rest of the parts are readily available. A parts-placement diagram is shown in Fig. 9. Begin by installing all parts on the board, but do not insert the ICs in their sockets at this time.

With no ICs installed in the sockets, attach a 5-volt DC supply to J1 and check the  $V_{CC}$  pins for all the IC sockets. Table 5 shows the power and ground

allow the charges to bleed from the electrolytic capacitors. Plug the ICs in their respective sockets, taking care to orient them properly. Figure 10 shows the completed prototype.

A parallel connection to the EP705N can be made with any standard parallel printer cable. If you are using a parallel printer now, disconnect the cable at the printer end and connect it to the EP705N. Serial connection to the EP705N might be more difficult. The EP705N is designed as a DCE (data communications equipment) device. It uses a 9-pin

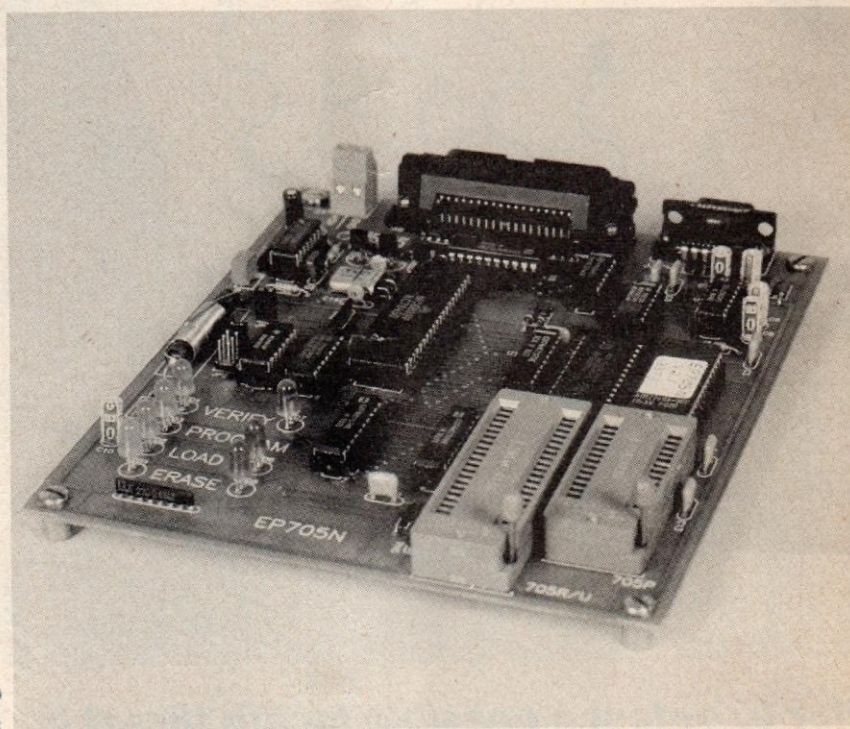


FIG.—THE COMPLETED PROTOTYPE. Any 5-volt power supply can be connected to power-input terminal block J1.

pins for all the ICs making it easy to check.

Install the DC-to-DC converter chip, IC1, in its socket. Turn on the power and measure the voltage at pin 1 of IC1. Adjust trimmer R4 to get a reading of 21 volts. Now measure the voltage on pin 7 of the IC15 target socket; it should be about 4.9 volts. If it is close to 21 volts there is a problem in the circuitry around Q1 and Q2. Measure the voltage on pin 8 of the IC15 target socket; it should be 12 volts.

Turn off the power supply and

female D connector that is directly compatible with the 9-pin serial ports found on most IBM-standard computers. The pin assignments and signal directions for the EP705N are shown in Table 3.

With the power off, install an erased 68705 in its appropriate ZIF socket. Note that the power to the EP705N should always be turned off whenever a 68705 is installed or removed. You are now ready to work with your EP705N and begin programming your own 68705s and putting them to work.  $\Omega$

ents costing thousands of dollars. Constructing the BERM will give you "hands on" experience in measuring a common form of radioactivity, and give you a better understanding of how it produces isotopes, subjects not easily grasped in lectures or from reading.

The cost of parts to build the BERM, exclusive of a power supply, is typically less than \$20. Because most of the components are readily available, you might be able to reduce even that modest cost by making use of parts you already have on hand. You will need the standard electronic technician's set of hand tools as well as such basic electronic test equipment as a two-channel oscilloscope and either an analog or digital multimeter.

### What is radon?

Radon is a natural, inert, radioactive gas emitted from the earth. Odorless, colorless, and invisible, it is a byproduct of the radioactive decay of uranium. Because it is inert and does not chemically bond to elements, it is released from the soil into the atmosphere. Radon is emitted almost everywhere on earth, but some geographical regions have higher concentrations than others, depending on the local geology and soil porosity.

Radon becomes a health problem when it decays and produces other short-lived isotopes called *daughter products* or *progeny*. These chemically active isotopes are usually formed as charged particles (ions). They bond readily to other substances such as dust and smoke particulates. Table 1 lists a portion of the decay chain of radon 222 and its short-lived progeny.

When radon decays, it releases alpha particles with an energy of 5.5 million electron volts (5.5 MeV). That would seem to be a large amount, but alpha particles travel only 4 to 7 centimeters (1.5 to 2.5 inches) in air before dissipating their energy in the ionization of air molecules. A piece of paper or even human skin is thick enough to stop alpha particles.

Direct exposure to radon, unlike direct exposure to beta particles, gamma rays, X-rays, or even ultraviolet light, poses little risk for humans.

The health threat from radon is indirect. Energetic alpha particles can cause chromosomal damage to the thin layers of lung tissue when humans breath air contaminated by radon and its progeny. That damage is a potential cause of lung cancer, especially when coupled with the effects of cigarette smoke in the lungs.

There are several different forms of radon, but radon 222 is the most prevalent form, and is of the most concern to health researcher. The number 222 refers to its isotope number. The alpha particles emitted by radon and its progeny are helium nuclei.

Most of the radon 222 that is inhaled is either exhaled directly or it diffuses into the bloodstream where its alpha emission does little detectable damage. However, radon's short-lived progeny such as polonium 214 and polonium 218 are more likely to emit alpha particles that are capable of damaging sensitive human tissue.

The alpha particles from the decay process of polonium 218 have 6.0 MeV of energy while those from polonium have 7.7 MeV, both higher than the 5.5 MeV of radon 222. For this rea-

son, researchers believe that they are the agents primarily responsible for inducing lung cancer in situations where radon 222 is present in amounts considered to be above the safe level.

Radon has been a constituent of the air for millions of years. We became aware of its existence only when instruments were developed that could detect and measure it. Its presence is of concern because of the alarming statistics on death due to lung cancer. Its presence has long been considered a contributing factor to those deaths. However, it is difficult to separate cancer attributable to radon alone from that attributable only to smoking or to smoking in the presence of radon.

The harmless concentration of radon in the outdoor air is about one-thousandth of its concentration in the ground. This can be demonstrated by placing an inverted bucket on bare ground over a suitable radon monitor. The radon emanating from the soil collects inside the bucket until an equilibrium condition is reached. The monitor will probably indicate a radon concentration that is several orders of magnitude higher than that in the surrounding air, but less than the soil concentration in the soil.

A house with a foundation, walls, floors, and a roof can be

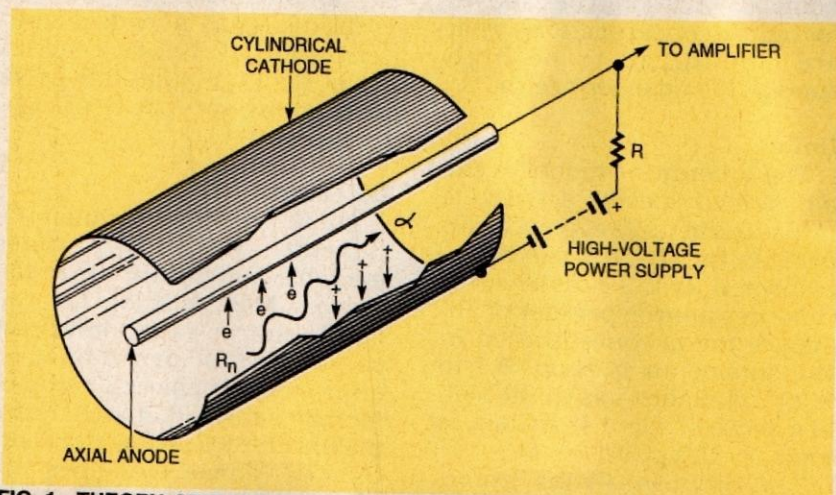


FIG. 1—THEORY OF RADON MONITOR IONIZATION CHAMBER. Positively charged anode wire attracts electrons and negatively charged cathode attracts positively charged ions. The recombination of electrons and ions causes a current that produces a voltage pulse.

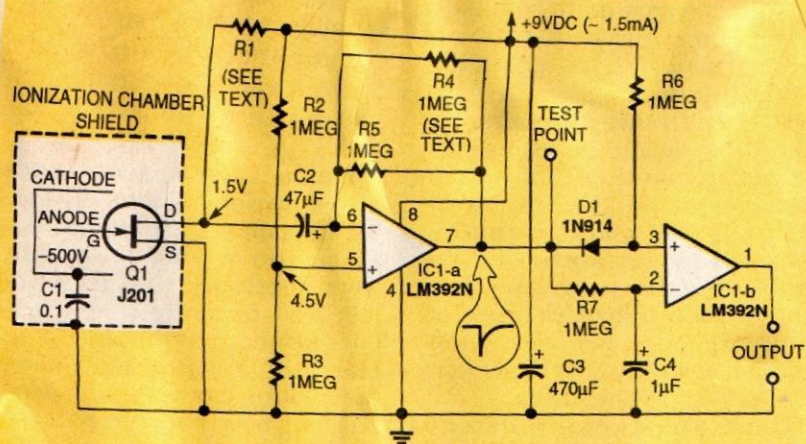


FIG. 2—RADON MONITOR AMPLIFIER amplifies voltage pulses across resistor R1 and then detects them for counting by separate pulse-rate counting circuitry.

TABLE 1  
THE DECAY CHAIN OF RADON 222

Isotope	Name	Half life	Decay process	Energy
Rn 222	Radon	3.82 day	alpha	5.49 MeV
Po 218	Polonium	3.05 min	alpha	6.0 MeV
Pb 214	Lead	26.8 min	beta	1.0 MeV
Bi 214	Bismuth	19.7 min	beta	3.3 MeV
Po 214	Polonium	164 µs	alpha	7.7 MeV

considered analogous to a bucket. It will also trap radon that leaks into the indoor airspace, especially if all the doors and windows of the house are closed. Under these conditions, the indoor radon might be 10 to 100 times more concentrated than outdoor radon. People in developed countries typically spend most of their time indoors at work, at school, or at home, so they could be exposed to radon concentrations that are considered to be high enough to endanger health.

### Units

The amount of radon in the air, termed specific activity, is measured in units of picoCuries per liter (pCi/l). This can be interpreted as 2.22 disintegrations per minute per liter of air. Typical radon concentration in the outside air is about 0.1 to 0.2 pCi/l. Radon gas in the soil, at a depth of about 15 inches, is typically 100 pCi/l.

The Environmental Protection Agency (EPA) has stated that a radon level within a home of 4 pCi/l or less will present little or no health threat. It has

published recommendations for specific actions to be taken where higher concentration levels are found. These include follow-up testing in other rooms in the home. Nevertheless, it is ultimately up to the homeowner to decide what radon level is acceptable for his home in the absence of a scientifically established absolute safe threshold level for radon exposure.

Published risk comparisons indicate that a radon concentration of 30 pCi/l carries about the same cumulative risk as smoking two packs of cigarettes per day.

### Detectors

There are many commercial instruments and techniques available for measuring radon indoors. Most detectors for evaluating indoor radon levels are passive in that they do not require external power. Examples include activated charcoal canisters or nuclear-track etch detectors. These detectors are exposed to indoor air under specified test conditions. After exposure, they are sent off to a laboratory for analysis, the

same approach used in detecting X-ray exposure with passive detection badges.

The principal drawback to passive detectors is that they measure radon concentration at only one specific location for a specified period of time. Many variables influence radon concentration levels; therefore, a single estimate of radon concentration is likely to have a significant error.

Obviously, radon concentration surveys based on two or more passive measurements will provide a more accurate assessment than a single measurement, but they are expensive because the price of a "one-time-only" passive detector can range from \$25 to \$100. If you conduct only one test, the EPA recommends that it be run under *worst-case conditions*.

By worst case conditions, the EPA means that the test should be made in any living space in the home or building that is closest to the ground (just above the floor slab, crawl space or basement) at a time of the year when ventilation is at a minimum—typically during the winter.

The air exchange rate and type of heating and cooling system in a house or building can cause wide variations in the amount of radon present due to differences in the way air is introduced, circulated and exhausted. There can also be daily variations in radon concentration. Because radon readings might exceed limits considered to be safe, it is recommended that radon concentration levels be measured over a one-year period in different locations in the home to obtain the best estimate of long-term risk.

Only an active radon monitor such as the BERM is capable of monitoring radon continuously. Commercial instruments capable of doing that typically cost several thousand dollars. The BERM radon monitor has many of the features of the expensive instruments at a far lower price.

BERM readings will be not very accurate unless they a

compared against those of a properly calibrated test instrument. Nevertheless, even if it is not calibrated, the BERM will yield relative data that is accurate enough to indicate if a radon hazard exists in your home. You can use a BERM to locate the "worst case" room in your house where a follow-up test with a precisely calibrated monitor should be performed if you suspect excessive levels.

### Ionization chamber theory

The easiest way to measure the presence of radon is to detect the high-energy alpha particles that it emits as a result of radioactive decay. As can be seen in Table 1, the alpha particle has a kinetic energy of about 5.49 MeV which ionizes the air passing through it. On average, about 34 eV is required to ionize air.

Therefore, assuming that an alpha particle dissipates all of

its energy ionizing air, about 100,000 ( $10^5$ ) electron-ion pairs are generated over a path length of about 4 centimeters (1.5 inches). As a result, a charge of  $10^{-14}$  coulombs can be collected by the electric field inside the ionization chamber.

The BERM ionization chamber, shown schematically in Fig. 1, has a cylindrical form factor because it is constructed from an aluminum beverage can. It has an axial, positively charged wire anode that extends the length of the can.

Negatively charged electrons (e) are attracted to the positively charged anode and arrive a few microseconds after an ionizing event while positively charged ions (+) are attracted to the negative cathode cylinder liner. A few milliseconds later the ions recombine with electrons from the high-voltage, DC-power supply.

The resulting current flow

produces a small voltage pulse across the resistor in series with the power supply. That pulse is then amplified, detected, and counted. The number of counts per minute can then be multiplied by a constant that includes the effective volume of the chamber to determine specific radon activity in units of pCi/l. The presence of radon "daughters" produced in the chamber increases the count rate.

The BERM ionization chamber design is based on the assumption that the air inside the chamber is a representative sample of the air in the room that is being monitored. The air in the BERM is slowly exchanged by diffusion through openings in the chamber.

### Chamber size

A 12-ounce aluminum beverage can was selected for making the ionization chamber

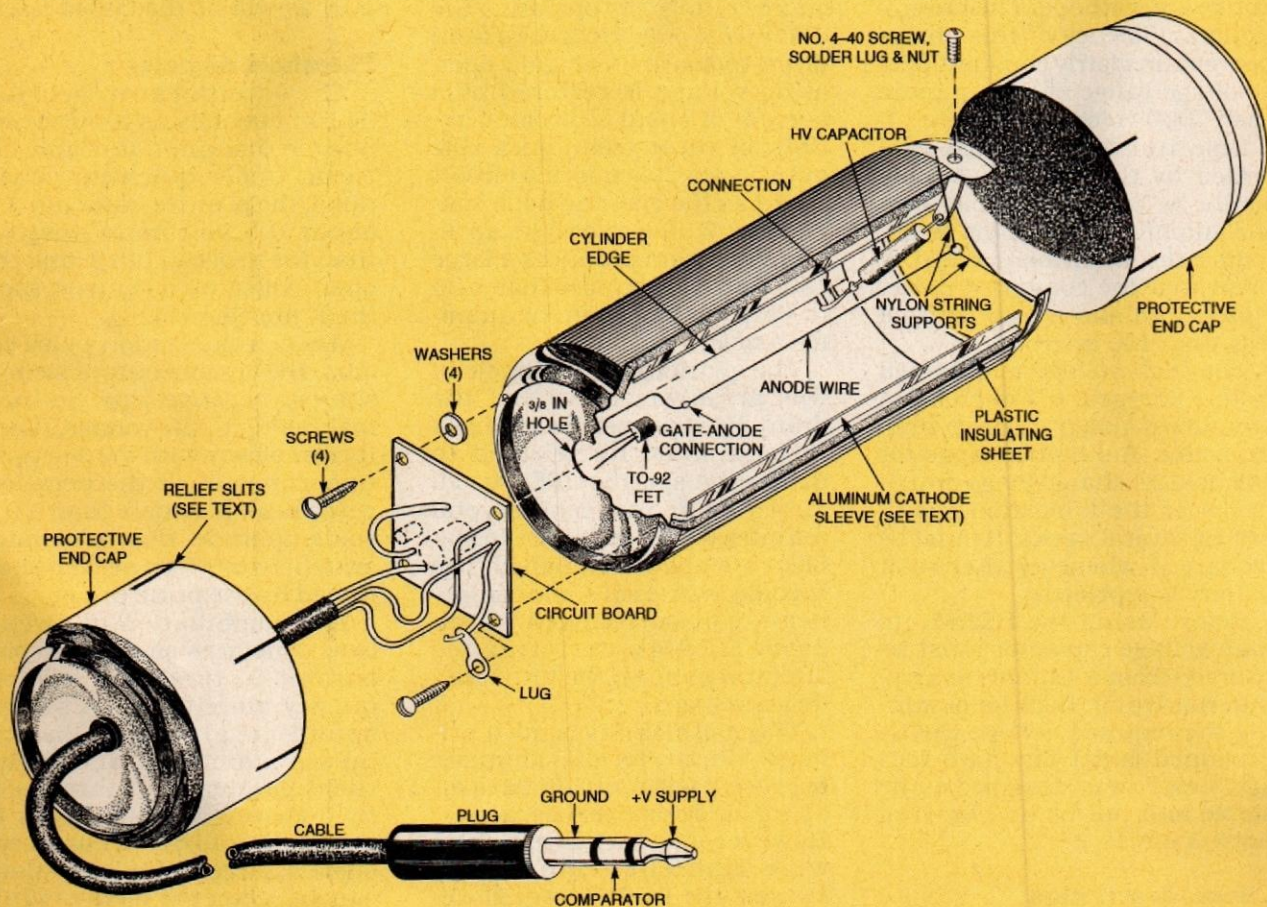


FIG. 3—CUTAWAY OF RADON MONITOR IONIZATION CHAMBER. A beverage can forms the chamber, an aluminum can forms the cathode, and half cans form protective end covers. Amplifier circuit board is shown left of center.

because, in addition to its ready availability, its size is standardized. This size uniformity permits BERM calibration based on chamber size. The can's dimensions are large enough for alpha particles to dissipate most of their energy ionizing air. As stated earlier, the amount of charge generated determines the amplitude of the current pulse collected on the anode.

Ionization caused by beta particles and other naturally occurring radiation, primarily gamma rays, causes lower amplitude pulses in a chamber of this size. This means that it is easier to discriminate the larger alpha ionization pulses from those caused by beta particles and gamma rays as well as by amplifier noise.

#### High-voltage supply

A nominal but stable 500-volt differential is required to set up an electric field between the anode and cathode. The ion collection efficiency of this chamber remains fairly constant over a voltage range of 200 to more than 1000 volts.

Unfortunately, any noise generated by the 500-volt supply would be coupled directly into the amplifier input. This establishes the additional requirement that the combined noise, ripple, and short-term drift be less than 100 microvolts.

The high voltage is obtained from a charged, 0.1-microfarad metallized-polypropylene-film capacitor. A suitable capacitor will hold its charge long enough to power the ionization chamber for several weeks. It must be recharged whenever the 9-volt battery is replaced.

Before using the BERM, its high-voltage capacitor must be charged from a suitable source. (Alternative methods for obtaining the required voltage will be explained later.) The high-voltage supply was designed to be stable and not be an electrical noise source.

#### Circuit description

Figure 2 is the schematic for the amplifier. To maximize the amplifier input signal, its ca-

pacitance must be minimized. This is done by connecting the chamber's anode wire directly to the gate of JFET Q1. The effects of excess capacitance and leakage current that would be present if a printed circuit had been used for the connection are eliminated. This approach holds total input capacitance to around 7 picofarads. An input pulse charges the gate of Q1 about 1 millivolt.

The charge must be kept on the gate long enough for the amplifier to respond. An input resistance large enough to maintain a long pulse width would introduce too much thermal noise for a good signal-to-noise ratio.

This problem was avoided by letting the gate float or self-bias. The result is that input impedance is maximized and noise is minimized.

A JFET can be self-biased because its gate leakage pulls the gate towards the drain-to-source voltage. By operating the JFET with only 1 to 2 volts from drain-to-source, the gate operating voltage is restored by a current of about 1 picoampere. Both of these techniques rule out the possible use of a circuit board as the gate-to-anode connection. With this design, an alpha ionization produces a large 100-millisecond pulse that is 20 to 40 dB greater than the amplifier's noise.

The principal drawback of this arrangement is that the drain resistor and the feedback resistor must be selected to match the specific JFET used. Moreover, it can take several minutes for the amplifier to stabilize after power is applied. The specified values of some components can be changed to improve BERM's performance after you perform the initial calibration steps.

Thermal stability is not a primary concern for this amplifier because it will normally be operating at room temperature. However, even with relatively wide ambient temperature swings, the BERM's overall calibration is very stable and remains unaffected by amplifier gain changes.

#### Operational amplifier

The LM392N is a low-power operational amplifier/voltage comparator performs as both an amplifier and comparator. The high-gain, internally frequency compensated op-amp is IC1-a, and the comparator is IC1-b. Both can operate from a single power supply over a wide range of voltages (3 to 32 volts). Current drain is 600 microamperes—essentially independent of supply voltage. The LM392N shown on Fig. 2 is in an 8-pin DIP package, but the LM392H in a metal can package can be substituted.

The op-amp functions as a current-to-voltage converter following the JFET's transconductance stage. Overall voltage gain is about 60 dB. However, amplifier power gain, due to the impedance transformation, is about 160 dB! To prevent regenerative feedback, the JFET's input must be electrically shielded from the op-amp's output, as will be discussed later.

#### Threshold detector

The comparator section (IC1-b) operates as a pulse-amplitude discriminator and detector. Under quiescent conditions, the positive input pin 3 is about 0.5 volt more positive than the negative pin 2, and the open collector output is high (high impedance).

When an ionization pulse occurs, the op-amp output swings sharply negative from its normal (half) supply voltage. Then it rises slowly with a 0.1 second time constant. If the negative-going peak has more than a 0.5 volt amplitude, the comparator switches state for a period determined by the pulse decay.

The combination of circuit time constants allows the comparator to track the low-frequency amplifier drift yet respond to alpha ionization pulses which are about five times greater than threshold. By adjusting amplifier gain to match the ionization chamber's signals, large alpha ionizations can be detected easily, while much smaller beta particle gamma ray, and noise ionizations are rejected.

The comparator's output is an open collector which goes low (low impedance) whenever an alpha particle is detected. This output can be interfaced to any logic device, digital counter, or count-rate meter. This will be discussed in detail in Part 2 of this article.

### Low-voltage power supply

The optimum low-voltage power supply for the amplifier is a 9-volt battery. The BERM draws only a few milliamperes, so a 9-volt alkaline transistor battery is should provide an effective life in excess of 50 hours—in addition to permitting it to be a portable instrument. However, if you would prefer to power your BERM from the AC line, a schematic for a suitably filtered 120-volt AC to 9-volt DC converter will be in Part 2 of this article.

### Chamber arrangement

Refer to Fig. 3, a cutaway drawing of the ionization chamber. The amplifier is built by point-to-point wiring methods on a prepunched 1 $\frac{3}{4}$ -inch square circuit board with solder pads on one side. It can be seen, however, that all amplifier components except JFET Q1 are mounted and soldered on the component side of the board.

The drain and source leads of JFET Q1 are to be soldered onto the solder-pad side of the circuit board so that its plastic TO-92 package can extend into the can that forms the chamber through a hole formed in the bottom of the can. This arrangement effectively shields Q1's sensitive input from the rest of the amplifier circuit. As mentioned earlier, the anode wire is a direct extension of Q1's gate lead, bent 180° away from the other two leads.

### Cathode sleeve

Refer to Fig. 3. The approximate 500 volts from charged capacitor C1 are applied between the aluminum can chamber, which is grounded, and a cathode made as an aluminum inner sleeve or lining separated from the can's inner wall by sheet plastic insulation. This

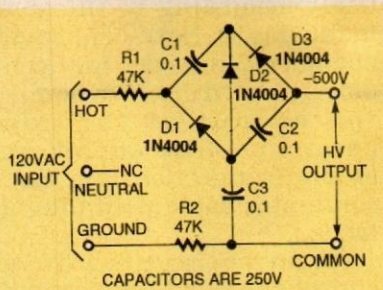


FIG. 4—VOLTAGE TRIPLER CHARGES ionization chamber capacitor. It is powered from the 120-volt AC line.

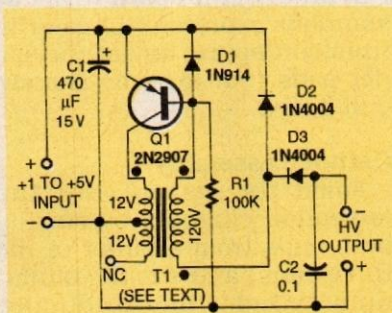


FIG. 5—BLOCKING-OSCILLATOR flyback circuit powered from DC is an alternative for charging the ionization chamber capacitor.

### PARTS LIST

Figure 2 amplifier All resistors are 1/4-watt, 5%.

R1—selected value (see text)

R2—R7—1,000,000 ohms, carbon composition

All capacitors are aluminum electrolytic, 15-volts, unless otherwise specified

C1—0.1  $\mu$ F, 630 volts, metallized-polypropylene film, Sprague 730P104X9630 or equivalent

C2—47  $\mu$ F

C3—470  $\mu$ F

C4—1  $\mu$ F

#### Semiconductors

IC1—LM392N operational amplifier/voltage comparator, National Semiconductor or equivalent

Q1—J201 JFET, National Semiconductor or equivalent

Miscellaneous 3 aluminum 12-ounce beverage cans, 1 $\frac{3}{4}$ -inch square, punched circuit board with solder pads (Radio Shack No. 276-159 or equivalent), 4 No. 4 self-tapping sheet metal screws and matching washers, 1 4-40 screw and nut, polyethylene sheet (see text), 30-inch length of 3 conductor cable, 1/4-inch diameter phone plug, 9-volt alkaline transistor battery, solder lugs, electrical tape, solder.

sleeve-within-a can construction provides the unit with excellent shielding from electrical noise.

With this design, the effective volume of the ionization chamber is considerably reduced, compared to its physical volume, because the electric field includes the end surfaces of the can. These end-surface fields must be accounted for during instrument calibration.

### Chamber assembly

Obtain three identical clean, undented, 12-ounce aluminum beverage cans. (They are 4.8 inches high.) Cut the top from the tab end of one can to form the ionization chamber with a can opener so that a crimped-on ring remains. Form a 3/8-inch hole in the center concave bottom of the can.

Then, using the blank 1 $\frac{3}{4}$ -inch square circuit board specified as a template, drill four small pilot holes on the rim at bottom of the closed end of the can, on top of its circular ridge. Later in the assembly procedure, self-tapping machine screws will be used to mount the circuit board on the end of the can as shown in Fig. 3.

Hold the circuit board in position on the end of the can with the solder tabs directed toward the can. Look in the open end of the can through the 3/8-inch hole and mark the locations of the solder pads that are suitable for Q1's drain and source pins. Plan your parts layout carefully so that one of those pads can be common to the ground or negative power supply pin on op-amp IC1-a.

### Circuit assembly

Refer to Fig. 2. The selection of the value for drain resistor R1 will depend on the characteristics of the specific J201 JET (Q1) to be used in the circuit. Short the JFET's gate to its source and measure the drain-to-source current ( $I_{DS}$ ) with a drain-to-source voltage of about 1.5 volts. Then calculate the drain resistor value based on this current and the voltage of the power source you intend to use:

Drain resistor  $R1 = (V_S - 1.5)/I_{DS}$   
For a J201 FET and a 9-volt battery, R1 should have a value between 10 and 33 kilohms.

When constructing the amplifier, use 1-megohm resistors for both parallel resistors R4 and R5. Form the axial leads of both resistors and solder them so that R5 will remain permanently in position while provision is made for the easy removal of R4 during the calibration process. By doing this, gain can be adjusted later by shunting 1-megohm resistor R5 with another value for resistor R4 until an optimum value is found.

Solder a short tinned wire to the output pin 7 of op-amp IC1-a to act as a test point to permit attaching an alligator clip lead or oscilloscope probe. Place a solder lug under one of the sheet metal screws holding the circuit board in position on the end of the can to act as a convenient circuit common or ground lug.

Other than this restriction on the placement of Q1 on the circuit board, the layout of the other components is not critical. Use the convenient pad locations bridged by the components you've selected and any necessary jumper wires to complete the wiring of the circuit. Complete the insertion and soldering of all components on the circuit board except for JFET Q1.

Insert and solder the source and drain leads of JFET Q1 on the solder-pad side of the board. Then carefully bend the gate lead directly away from the other two leads so that it is perpendicular to the solder-pad side of the circuit board.

Solder a length of bare copper wire (28 to 32 AWG) about 4 inches long to the gate lead of Q1, and straighten it so that it is perpendicular to the circuit board. Cut the free end of the anode wire to a length that is about 4½ inches long. Twist a small loop (about ¼-inch in diameter) on the end of the anode wire and solder the joint.

Carefully examine the circuit assembly to be sure that it was

made according to the schematic, Fig. 2. Next, connect the chamber can solder lug to the circuit-board ground, connect the output of the comparator, positive supply, and ground connection to a three-conductor cable with plug attached.

Fasten the circuit board to the end of the chamber can with four No. 4 self-tapping sheet metal screws. Use small matching washers between the can rim and circuit board to act as standoffs to prevent the can rim from contacting any of the solder pads that exist on the circuit board.

### Cathode assembly

Form the cathode for the ionization chamber by cutting both ends from another of the three cans, and slit the aluminum cylinder longitudinally, being careful not to deform or flatten it. Trim, square the ends of this aluminum sleeve to a length of about 3.7 inches. File off any sharp edges or burrs that could cut through the thin plastic insulation layer to be applied later.

The aluminum in the can has intrinsic spring qualities, so that if its slit edges are overlapped about ¼-inch they will retain their tendency to spring open. Cut two slots about ¼-inch deep and about ⅛-inch apart at right angles to the slit edge of the aluminum cylinder. Those slots form a "digit" for later termination of one end of capacitor C1.

Wrap and crimp a short length of tinned lead wire around this digit as shown in Fig. 3 so that when the cathode sleeve is installed in the can, the lead can be soldered to one end of C1.

The inner wall and ends of these cans have a plastic coating, but it is not dependable as an insulator between the cathode sleeve and the chamber can. Cut a sheet of polyethylene plastic approximately 2 mils thick sheet so that it will extend about ¼-inch beyond each end of the cathode sleeve and overlap its circumference. This material can be taken from sandwich

bags, cleaner's garment bags, or other sources.

Drill a small hole in the rim of the can and fasten a small solder lug inside with a No. 4-40 machine screw and a nut as shown in Fig. 3. After being sure that all the metal chips and filings have been cleaned from the chamber can, insert the insulating film and press it against the inner wall of the can and then insert the cathode sleeve. After the insulated cathode has been inserted, check to be sure that there is no metal-to-metal contact between the can and sleeve.

### Capacitor installation

Carefully select high-voltage capacitor C1 to make sure that it is a high-quality, low leakage component. If left fully charged, it should retain at least 37% of its charge for at least a month at room temperature.

Solder capacitor C1 to the internal lug with as short a length of lead as possible, as shown in Fig. 3. Position the capacitor in the mouth of the can against the side wall as shown in Fig. 3. Then solder the short wire stub on the cathode to the free end of capacitor C1. Clip its lead short and bend it toward the center of the can so that an alligator clip can be attached to it. Finally, check the resistance between the cathode sleeve and chamber can to be sure that it is effectively infinite.

### Protective covers

Cut a third can in half and bend the tab of the top end back to its original unopened position. Carefully slip this top can half over the open end of the chamber can. Expect that it will form a tight "press fit." If the fit is too tight for easy removal, cut several longitudinal slits in the can half to permit slight expansion (see Fig. 3).

Drill a hole in the bottom of the other half can large enough to be able to insert a small rubber grommet which will pass the three-conductor cable. This can end will cover the circuit board and shield it from 60-Hz noise.

*Continued on page*



## RADON MONITOR

continued from page 62

### Initial checkout

Apply power to the ionization chamber with the cable and connect an oscilloscope to the op-amp test point shown in Fig. 2. After several minutes, JFET Q1 should have stabilized at its normal operating point with the drain at about 1.5 volts. The output of op-amp IC1-a should be half the 9-volt supply voltage with about 50 to 200 millivolts of low frequency noise riding on top of it.

When the amplifier is working properly, try to avoid bumping or vibrating the chamber because it is a sensitive vibration sensor, made even more sensitive as long as the anode wire remains unsupported. Shocks or vibrations will show up as large-amplitude, slow decaying sinewaves.

If the amplifier oscillates, produces square waves, or will not settle down after several minutes, check the drain voltage of JFET Q1 and the quality of the coupling capacitor C2. The amplifier circuit might have too much gain which can be reduced by substituting smaller values for resistor R4. Start with a 333 kilohm resistor which will reduce gain about 50%.

### Anode support

Punch two small holes on the opposite sides of the can's rim as shown in Fig. 3. Insert a length of nylon monofilament fishing line through one hole, pass the free end through the loop at the end of the anode before passing it through the second hole. Pull both free ends of the line together around the outside rim of the can and, keeping tension in the line, tie them together with a knot. If the tension on the line is sufficient, the end of the anode will remain centered in the mouth of the can.

If a persistent 60-Hz waveform appears at the test point, pass a length of insulated hook-up wire through the cable grommet in the bottom of the end cap

and hook it up to repeat the test. Press on the end cap and examine the waveform again. If this shielding doesn't cure the problem, check carefully for other construction errors such as a missing ground connection or a noisy power supply.

### Gain adjustment

Assuming that the ionization chamber and amplifier comply with the initial checkout requirements, it should be ready to detect alpha particles. However, additional amplifier gain adjustments might be necessary. Charge the capacitor C1 to -500 volts, and put the end cap back on. If you have no means for charging the capacitor, this can be done with either the voltage-tripler circuit shown in Fig. 4 or the DC converter shown in Fig. 5.

The voltage tripler shown in schematic Fig. 4 operates directly from the 120-volt AC line. It will produce a voltage close enough to 500 volts for satisfactory operation of the BERM. Because of the shock hazard associated with line-powered circuits, the use of a grounded, three-wire plug and line core is strongly recommended. This circuit should be enclosed in a suitable protective case to prevent accidental contact with the power line and any of the three large electrolytic capacitors C1, C2, and C3.

The DC converter schematic shown in Fig. 5 is a blocking-oscillator flyback circuit which can be powered from an adjustable, low-voltage DC supply. It will produce an output of several hundred volts with an input as small as 1 volt. Measure the converter's output with any voltmeter capable of measuring 100 volts before connecting the output to capacitor C1. Transformer T1, used as a step-up transformer in Fig. 5, can be any stock 20 VA transformer with a 120-volt primary and a 12-volt secondary.

Apply power to the amplifier and wait for its activity to settle. Typically, it will take several minutes for JFET Q1's gate to charge up and probably will take another minute for the

coupling capacitor to charge before amplifier output reaches half supply voltage.

With the oscilloscope set for 1 volt per division and very slow sweep (0.2 second per division), the test point voltage should vary slightly as you wait to see an event. Expect the appearance of a large negative pulse (see the waveform in Fig. 2) on the oscilloscope screen indicating that you have just been lucky enough to capture your first alpha particle.

In a typical home you will see a few of these pulses each minute. However, because you are observing a random radioactive process, you might see several pulses or none in any given minute. Watch the oscilloscope screen for a few minutes and estimate the pulse amplitudes.

If the BERM amplifier has too much gain, the amplifier's output will saturate. However, if most of the pulses have an amplitude less than 1/2-volt, gain must be increased. The optimum gain setting occurs when pulses with peak amplitudes of about 2- to 3-volts appear without saturating the amplifier. Adjust the values of feedback resistors R4 and R5 to accomplish this.

### Comparator

The last step in the check-out procedure, after gain adjustment has been completed, is to verify comparator operation. With an external pull-up resistor (100 kilohm to 1 megohm) connected to the positive supply, check its output with the second channel of your oscilloscope.

You should be able to verify that pulses with amplitudes over 1/2 volt drive the output low. Then complete the assembly of the BERM by putting the circuit board end cap back on.

### Pulse counting and calibration

The second part of this article covers alternative pulse-rate counting techniques, calibration, sources of error and the conversion of pulse counts to specific activity to determine estimated amounts of radon present in the air.