By D.BOLLEN

PEAC

ANALOGUE COMPUTER

The constructional details for UNIT "A" were completed last month. UNIT "A" is, itself, a complete, self-contained computing equipment, and the method of operation, with practical examples, is described in this article.

PATCHING LEADS

The best plugs to use for patching the computer are those of "split-pin" construction, as they can quickly be attached to wires without the aid of a screwdriver. It is a help if plugs are obtained in various colours, and are mated to different coloured wires to allow easy identification.

For the majority of problems capable of solution by UNIT "A", certain patching leads may be left in position on the front panel. For example, coefficient potentiometers are almost always used with the "0" end of their resistance track connected to earth (link SK3 to SK4 for CP1, CP2, CP3, and CP4, Fig. 2.7).

Similarly, until such time as integrator mode switching is brought into use, the integrator sockets depicted in Fig. 2.9 are joined together by means of a special three-way patching lead consisting of two short lengths of wire joined by a plug, with a plug at each end. Looking at Fig. 2.9, OA1/SK4, SK9, and SK10 are linked, and repeat for OA2 and OA3. Three more semi-permanent patching leads are made up to link each operational amplifier to its companion summer network. Connect OA1/SK8 to S1/SK5, and do the same for OA2/SK8-S2/SK5, and OA3/SK8-S3/SK5.

The rearrangeable patching leads should be of assorted lengths and colours, the longest to patch from, say, CP4/SK2 to S3/11/SK1, diagonally across the UNIT "A" front panel, and the shortest to link nearly adjacent sockets.

COMPUTING RESISTORS

If a comprehensive range of ± 1 per cent high stability computing resistors was purchased all at once, to meet every requirement, the cost would probably exceed £20. There are after all 101 preferred values in a ± 1 per cent range covering resistors from only 10 kilohm to 100 kilohm. Nevertheless, in the period when the computer operator is learning how to handle PEAC, and a high degree of accuracy is not essential, the majority of ordinary problem set-ups can be catered for by a small number of ± 1 per cent and ± 2 per cent plug-in resistors. A resistor selection list, with suggested values of R_r and R_{in} for standard op-amp closed-loop gains, is given in Table 4.1. Also, a component list included in this article sets out minimum quantities, with tolerances, of computing resistors.

Computing capacitors will be discussed later, in connection with integration.

SETTING UP THE VOLTAGE SOURCE

To set up all voltage source outputs, first remove the dials from VR6 to VR10 (Fig. 2.2), and turn the potentiometer spindles fully anticlockwise. If the potentiometers have flats on their spindles, make up blanking pieces consisting of small segments of hardwood or plastic, so that control knobs can be conveniently located at a selected position on each spindle. Connect the positive lead of a sensitive d.c. voltmeter (0-1V, 20 kilohm/V) to VS1/SK1, and the negative voltmeter lead to VS1/SK4 (Fig. 2.6), then set slide switch S1 for a positive voltage output. Switch on the computer power supply and S6.

Carefully rotate VR6 spindle clockwise until a very small voltage appears, just sufficient to slightly deflect the meter pointer away from zero. Now place a dial knob on VR6 spindle, without disturbing the potentiometer setting, and align so that the "0" division on the dial is vertical and opposite the pointer mark on the surface of the front panel. Tighten the dial knob grub screw.

Switch off S6 and replace the 0-1V meter with the 0-10V d.c. meter which has been chosen to serve as a voltage standard for the computer, while retaining the same meter lead polarity. Rotate VR6 dial until the "10" division is opposite its pointer, and switch on S6. Now adjust slider resistor VR1 from the back of the UNIT "A" box, for a precise reading of 10V on the "standard" meter. Repeat the above procedures for outputs VS2, VS3, VS4, and VS5, and remember to adjust only the particular slider (VR1-VR5) which is associated with the output being set up.

When all the voltage source dials are aligned, return to VS1 and make sure that its output is still +10V. Switch off S6, reverse the "standard" voltmeter leads, and set S1 for a negative output. Switch on S6 again and check the voltmeter reading; if it is not exactly 10V, go to the back of the UNIT "A" box and trim the power pack control VR2 (Fig. 3.4), this ensures that voltage source negative and positive outputs are equal.

SETTING UP THE COEFFICIENT POTENTIOMETERS

Insert a patching lead to link CP1/SK3 to CP1/SK4 (Fig. 2.7), and do the same for CP2, CP3, and CP4. Take a long patching lead from VS1/SK1 to CP1/SK1. Remove the dial from VR11 (Fig. 2.5) and rotate spindle fully clockwise. With the negative lead connected to any earth socket, insert the "standard" meter positive lead into CP1/SK2 after first setting S1 for a positive output. Adjust VS1 dial for a meter reading of 10V. Rotate CP1 spindle carefully anticlockwise until the meter pointer just beings to drop below the 10V division. Replace CP1 dial knob on VR11 spindle, align the "10" division with the pointer, and tighten the grub screw. Repeat for CP2, CP3, CP4.

With a 10V input to CP1/SK1, and a 0-10V meter connected to CP1/SK2, it is a simple matter to check the agreement between dial divisions and voltage output from the coefficient potentiometer. If there are serious discrepancies between voltage output and dial reading this will indicate that the effective electrical rotation of the potentiometer differs from the 270 degree dial calibration. Errors can often be minimised by slight readjustment of the dial knob on its spindle, to spread the error over the entire scale. Generally



TABLE 4.1 SUGGESTED VALUES OF COMPUTING RESISTOR FOR STANDARD CLOSED-LOOP GAINS

Op-amp gain	All resistors ±2%	All resistors $\pm 2\%$ unless otherwise stated			
$\frac{R_f}{R_{in}} = -G$	R _{in}	. R _t			
0.1	100kΩ	10kΩ			
0.2	100kΩ	20kΩ			
0.3	33kΩ	IUK12			
0.4	$40k\Omega \pm 1\%$	IUK12			
0-5	20kΩ	10K12			
0.6	33kΩ	20K12			
0.7	13k12	7.1K12			
0.8	20812	10K12			
0.9	20K12	10632			
1.0	1 10652	1004.0			
20	1000	20k 0			
2.0	(3.340	10k Q			
3.0	1 3340	100kΩ			
	440 + 1%	l0kΩ			
4-0	$40k\Omega + 1\%$	100kΩ			
5.0	20kΩ	100kΩ			
6.0	3-3kΩ	20kΩ			
7.0	13kΩ	9lkΩ			
8.0	2kΩ	l6kΩ			
9.0	2kΩ	18kΩ			
10.0	l0kΩ	100kΩ			
20.0	5kΩ ± 1%	100kΩ			
30-0	3·3kΩ	100kΩ			
40-0	$4k\Omega \pm 1\%$	100kΩ			
50.0	2kΩ	TOUK			

speaking, the dial setting error should not be worse than 5 per cent at all settings between "1" and "10" dial divisions. The whole question of computing potentiometer accuracy will be raised later, in connection with the Master Potentiometer of UNIT "B".

SETTING UP THE OPERATIONAL AMPLIFIERS

It is usual to check operational amplifiers either before the start of a computation, or at the beginning of the day, but the computer builder may wish to assure himself that his amplifiers are all that they should be when first brought into service. The zero-setting procedure given at the end of Part 3 of this series will have eliminated all but obscure faults. The front panel balance controls (VR15, VR16, and VR17, Figs. 2.4 and 2.9) are deliberately designed to have a limited range of adjustment, so that an amplifier fault will be clearly indicated as an inability to zero-set from the front panel.

To quickly check each amplifier, insert 10 kilohm feedback resistors into miniature sockets SK11 and SK12 for OA1, OA2, and OA3 (Fig. 2.9), and ensure that the operational amplifiers are already linked to their summing networks. Insert 10 kilohm input resistors into S1/11/SK3–SK4, S2/11/SK3–SK4, and S3/11/SK3–SK4 (Fig. 2.8). Patch VS1/SK1 to S1/11/SK1 (Figs. 2.6 and 2.8) and connect the negative lead of a voltmeter to OA1/SK13, with the positive lead going to any convenient earth socket.

Check that OA1 output is exactly zero when S6 is off. If not, zero-set by means of balance control VR15. Obtain a positive voltage from VS1 by switching on S6 and setting S1 and VR6, and monitor VS1 output with a second voltmeter connected to SN1/SK2 red, and an





how the operational amplifier can be used to solve various algebraic equations

earth socket. Remember that a positive input voltage results in a negative operational amplifier output voltage.

Since input and feedback resistors are both 10 kilohm, the operational amplifier gain will be unity, and both voltmeters should give precisely the same readings. Double check by interchanging voltmeters. Now see that the operational amplifier will faithfully "track" any input voltage of $\pm 10V$ or less when a temporary output load of 2 kilohm is connected from OA1/SK7 to earth.

The above tests are repeated for OA2 and OA3 by transferring the patching lead from VS1-S1/I1/SK1 to S2/I1/SK1, and then to S3/I1/SK1, and at the same time reconnecting voltmeters to the appropriate summer and operational amplifier sockets.

SOFTWARE

Under the heading of "software" comes all the paperwork associated with drawing up a programme for the computer. The time spent on preparing a programme for PEAC can vary from a few minutes to several days, depending on the skill of the programmer and the nature and complexity of the problem.

The intention is to give a few typical programme examples as an introduction to using the computer.



They will consist of a short written *routine*, plus programme layouts. The layouts will be in a duplicated form, of symbolised diagram and patching circuit, so that the reader can compare analogue computer symbols with actual circuits and patching procedures. A newcomer to analogue computers will best learn programming techniques by working with PEAC, and this will also help to increase his knowledge of more advanced mathematics.

ROLE OF THE OPERATIONAL AMPLIFIER

Now that the time has come to consider UNIT "A" as a computer, instead of as a collection of circuits handling voltages, it is appropriate to adopt a slightly different approach. Voltages will now be replaced by the letters or numbers of an algebraic equation, *a*, *b*, *c*, *d*, *x*, *y*, 2, 3, 4, 5, and so on. Computing resistors loose their individual identity and are considered only as ratios $\frac{R_t}{R_1}$, $\frac{R_t}{R_2}$, etc., which are also denoted by equation letters or numbers. The same applies to coefficient potentiometer settings.

Sign change. In the circuit of Fig. 4.1a, an input voltage classified as term a, reappears at the op-amp



Fig. 4.2 Programme layouts for $\frac{3a-2b}{a} = d$

output as term -a, when the $\frac{R_t}{R_{in}}$ ratio is unity. One way of looking at this operation, which is common to all single operational amplifier configurations, is to assume that a has been multiplied by -1, hence $\frac{R_t}{R_{in}} = -1$. In effect, to multiply by -1 is to move a mathematical term from one side of its equation to the other, so sign change can be used to transpose.

The operational symbol of Fig. 4.1a avoids the bother of inserting resistors and their values when drawing up a programme layout on paper. The figure inside the triangle—in this case "1"—merely indicates that the computing resistor ratio, or alternatively the operational amplifier gain, is unity.

Addition. In Fig. 4.1b, positive terms a and b are added to yield an output -(a + b), which can also be written -a - b. If -(a + b) is applied as an input to a second unity gain operational amplifier, to give two sign changes, it will be converted to a + b. Note that the figures in the operational symbol triangle show

that $\frac{R_f}{R_1} = 1$, and $\frac{R_f}{R_2} = 1$.

Subtraction. The only difference between Fig. 4.2b and Fig. 4.2c is that term b has been made a negative quantity. The operational amplifier output is therefore -(a - b) or -a + b.

Multiplication. In Fig. 4.1d, R_t and R_{in} are adjusted so that $\frac{R_t}{R_{in}} = b$. Hence, *a* is multiplied by factor *b* to become an output -ab. The letter inside the operational symbol triangle shows that the $\frac{R_t}{R_{in}}$ ratio is *b*.

Fig. 4.1e gives an alternative method of achieving multiplication. A computing potentiometer is connected to the op-amp input to multiply a by a factor b. Therefore, with an input ab, and $\frac{R_t}{R_{in}}$ adjusted to equal c, the result is an output -abc.

Division. When a computing potentiometer is wired as in Fig. 4.1f, with R_t connected to its slider, term *a* will be divided by constant *b* when $R_t = R_{\text{In}}$. Note that R_t is written inside the symbol triangle to show that *b* is a divisor.

It can sometimes happen that a feedback resistor is inadvertently left plugged into an operational amplifier when it is re-programmed for a division operation, and this will result in the circuit of Fig. 4.1g. Instead of an

output $-\frac{a}{b}$ the operational amplifier will yield $-\left(\frac{a}{b+1}\right)$.

EXPERIMENTER'S PRINTED CIRCUIT KI

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 44" × 24". (2) I Board for Match-box Radio. (3) I Board for Writzwarch Radio, etc. (4) Resist. (5) Resist Solvent. (5) Etchant. (7) Cleanser/Degreaser. (8) I6-page Booklet Printed Greüts for Amoteurs. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for building.

40 TRANSISTORISED PROJECTS

A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



South Africa, Canada (1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Relfex. (7) Matchbox or Photoceil Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Trifferon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" × 95" × 25". (11) Wristwatch Radio 1-15" × 60" × 55". (12) Ring Radio. 70" 70" × 55". (13) Batteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor PJP Amplifier. (16) Intercom. (17) Lvalve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal. Guided Missile. (20) Perptual Motion Madiation Detector. (24) Mani/Woman Ort Control Torasmitter. (26) Pocket Transceiver (Licence required). (27) Cinamintor. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Inductive Lolume Intercom. (29) Remote Control of Modeis by Induction. (27) Inductive Lolume Intercom. (30) Portex Triple Reflex Radio. (31) Wrist-Marking Missile. (30) Pocket Transceiver (Licence required). (29) Inductive Lolume Intercom. (32) Risense Door Bell. (33) Witrasonic Switch/Alarm. (38) Shicrophone. (32) Wiresless Door Bell. (33) Wirtson Division Division Panalifier. (35) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

PHOTOELECTRIC KIT

BUILD 12 EXCITING PHOTOELECTRIC DEVICES

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Cadmium Sulphide Photocell, Latching Relay, 2 Transistors, Condenser, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. in fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-Light Alarm. (4) Relay-Less Alarm. (5) Warbling-Tone Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector Modulator. (9) Mains Power Supply. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: l, Invisible-Beam Projector and I Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE OPTICAL KIT 29/6 p.p. 1/6





ELECTRONICS **Through this ICS 3-way Training Method:**

MASTER THE THEORETICAL SIDE

From basic principles to advanced applications, you'll learn the theory of electronic engineering, quickly and easily through ICS. That's because each course is set out in easy-to-understand terms.

MASTER THE PRACTICAL SIDE



ICS show you how to develop your practical abilities in electronic engineering-alongside your theoretical studies. It's the only sure way to success. All training manuals are packed with easy-to-follow illustrations.



MASTER THE MATHEMATICAL SIDE

To many this aspect is a bitter problem. Even more so because no electronic engineer is complete without a sound working knowledge of maths. But new ICS teaching makes mathematics easier to learn.

Wide range of courses available include:

Radio, TV Engineering and Servicing, Closed Circuit TV, Electronics, Electronic Maintenance, Servomechanisms, Computer Engineering, Numerical Control Electronics, etc.

EXPERT COACHING FOR:

INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS CITY AND GUILDS TELECOMMUNICATION TECHNICIANS CITY AND GUILDS ELECTRONIC SERVICING R.T.E.B. RADIO/TV SERVICING CERTIFICATE RADIO AMATEURS' EXAMINATION P.M.G. CERTIFICATES IN RADIOTELEGRAPHY

Build your own radio, transistor portable, and professional-type test instruments with an ICS Practical Radio and Electronics Course. Every-thing simply explained and easy to handle. All components and tools supplied. For details post coupon below.

Member of the Association of British Correspondence Colleges

FOR FREE HANDBOOK POST THIS COUPON TODAY I.C.S., Dept. 151, INTERTEXT HOUSE, PARKGATE ROAD, LONDON, S.W.11 NAME ADDRESS OCCUPATION. AGE 4/68 INTERNATIONAL CORRESPONDENCE SCHOOLS

ORGAN BUTLDERS! N. per 100. TRANSITOR BARGAN OC44, OC45, OC81D not OC71, OC72 equivalent	P.N. Sil. Planar Transistors. All SALE: NEW STOCK AT UN ronly 1/6 each: 26.0 1/- each: 25.0 1/- each: 53.0	Tested, 1/6 each or 45,0,0 BEATABLE PEICES! 10 per 100 10 per 100 10 per 100							
AS YZZ SWILCHIG ITALISEOFS Z/6 EACL: X10,0 per 100 20153 N.P.N. Silicon Planar, 300mW. 250M6/a. High speed switching . 2/6 each: BS Y28 N.P.N. Silicon Planar, Epitaxial, 300mW. 300Mc/s									
AFZ12 F.N.F. Germanium Alloy Diff. low noise V.H.F. amplifier 2/6 each! Complete scit of transitions for radio: 2G344A/2G345A/2G345A/2G371A/2G378A/2G378A + diole 10/- only: 0ET120.2 watts. Heat sink included 2/6 each!									
Translator Driver Transformers 2/6 sach: Translator Output Transformers (suitable for our kits above) 2/6 sach: OC88 BVZ313 6 ann rectificrs 5/- sach									
BYZ13, 6 amp rectifiers Light sensitivity transis UNMARKED, UNTEST	ora similar to OCP71 ED TRANSISTORS TO CLEAN	2/6 each 1 							
1/- each; 20 for 10/ BY100 type rectifiers. h £7,10,0 per 100; £50.0.0	PECIAL REDUCED PRICE! (per 1,000.	NLY 2/8 each; 24/- doz.;							
ELECTROLYTIC CONDI	INSERS! FANTASTIC BELECTIC 20 + 4	275 volts 10d							
50µF 450 volts . 64µF 275 volts . 800µF 15 volts .	1/3 $32 + 321/3$ $8 + 161/2$ $50 + 50$	275 volts 1/6 450 volts 1/9 275 volts 2/-							
500µF 25 volts	. 10d 40 + 40 + 2	0 275 volts 2/1							
50/50/50, 350V 2/ 1,0094P, 70V 3/3	150/350, 300V 4/-	30,000µF, 30V 25/-							
100/200, 275V 3/1 100/200/200/50, 275V 4/-	2,000/2,000, 25V 4/6	1,000μF, 15V 1/6 1,000μF, 18V 1/-							
1,000μF, 35V 8/6 0-25μF 3 volt	250μF, 50V 10d	500μF, 15V 19d 50μF 9 volt							
1μF 50 volt 1μF 350 volt	8µF 3volt 8µF 6 volt	64μF 2·5 volt 64μF 9 volt							
1-25μF 16 voli 2μF 3 voli	8μF 350 volt 8μF 450 volt	100µF 3 volt 100µF 6 volt							
2μF 9 volt 2μF 70 volt	8μF 50 volt 8μF 275 volt	100µF 9 volt 150µF 12 volt							
2μF 150 volt 2μF 350 volt	10μF 25 volt 16μF 150 volt	200µF 3 volt 200µF 4 volt							
2·5μF 16 voli 2·5μF 25 vol	20µF 3 volt 20µF 6 volt	200μF 16 volt 250μF 2-5 volt							
3μF 3 volt 3μF 25 volt	20µF 9 volt 20µF 15 volt	200μF 9 volt 320μF 2-6 volt							
3-2µF 64 volt	25µF 12 volt	350μF 9 volt 350μF 10 volt							
4μF 12 vol	25µF 15 volt	400µF 20 voit 400µF 15 volt							
4µF 64 volt	30µF 6 volt	500µF 4 volt							
δμF 6 volt	40µF 3 volt	640µF 2-5 volt							
All at 1/- each, 9/- per e	ozen. Mixed Packets of 20 (our	760µF 12 voit selection) 10/							
PAPER CONDENSERS	1 0.00.11 600 a a 1	0.05.uP 250 wolt							
0.001µF 1000 vol	0.02µF 350 volt	0.5µF 150 volt							
0-005µF 750 volt	0.1µF 750 volt	0-5µF 500 volt							
MULLARD POLYESTER	CAPACITORS, ALL HALF PR.	ICE							
0-0022µF 400 volts 0-0018µF 400 volts		60 volta 7d 60 volta 7d							
0-0015µF 400 volts 0-001µF 400 volts		60 volts 84 25 volts 74							
0-01µF 400 volts 68pF Tubular pulse cera	mic 6d each	25 volte 1/6							
120pF Disc pulse cerami VERY SPECIAL VALU	c 6d each E! Silver Mica, Ceramic, Polyst	vrene Condensers.							
Well assorted. Mixed ty	pes and values, 10/- per 100.	to 3 matt							
6/6 per 100 or 55/- per 1 Also 1 to 3 watt close to	,000. erance. Mixed values, 7/6 per l	00: 55/- per 1.000.							
WIRE-WOUND RESIST	ORS. 1 watt, 8 watt, 6 watt, 6d	each, 7 watt and 10 watt							
CONNECTING WIRE.	THIN, P.V.C. INSULATED.	Mi- (most Ri-)							
VALVES. BRAND-NET	AND BOXED. ROCK-BOTTO	M PRICES !							
EABC80 7/-	EY86	PCL86 8/5 PFL200 11/8							
ECC83	PABC80	PL36 10/1 PL81 8/5							
ECL80 7/1 ECL86 8/4	PCC84	PL83 8/5 PL84 6/6							
EF80	PCF86 8/5 PCF86 10/1	PL500 12/5 PY32 9/~							
EF183 9/1	PCL82	PY81 6/9							
EY61 8/8	PCL84	P¥800 6/9							
A further 10% discount	will be given on lots of 50 of any	one type.							
Sonotone Mono, 10/-: A 20/-: Acos GP93/1 Stere	cos (1P67/29 Mono, 15/-; Aces (1) n, 25/ All with needles.	P91/35C Storeo compatible,							
Signal Injector Kit-10/	Signal Tracer Kit-10/								
21in × 1in 0-15 matri	c 1/1 17in - 32in	0-15 matrix 14/8							
21in × 51in 0-15 matri 31in × 31in 0-15 matri	x 3/11 5in 21in 3/11 31in 21in	0-1 matrix \$/11 0-1 matrix \$/9							
3%in × 5in 0-15 matri 17in × 2%in 0-15 matri	x 5/6 5in 31in	0-1 matrix 5/2 0-1 matrix 3/11							
Cutter and 5 Boards 21in	.4 lin, 9/9, Cutter only, 7/8. Pin	Insert Toul, 9/6. Terminal							
Pins. Packet of 36, 3/6.									
Yew only Multimeters, 1	000 per volt, 45/-: 20,000 p	er volt, 80/~.							
G. F. MILWARD, I	PEEL CLOSE, DRAYT	ON BASSET, Staffs.							
Please include suitable a be included with any en-	mount to cover postage. Htampo Juirles.	ed addressed en elope must							
For customers in the Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Bock Boad, Birmingham 8. (All POST orders to Drayton.)									

R .	S.	T.	VA	LVE	M	AIL		R CO. M, S.W.16	
Spe	ecia	al 24	1 1	Hour	1	Aail	Order	Service	
A61	7/9	EL90	6/-	QQV03/10) 30/-	Z803U	15/- 11E3 6/3 12AC6	42/- 9003 9/ 10/- BV100 5/	
CIC CY30	12/-	EL360 EL820	22/-	QQV03/20	05/-	OB2 OC3	6/~12AD6 5/6 12AE6	11/- BIG TRANSISTORS	
DAF91 DAF95	4/-	EL821 EL822	6/	QQV04/1	5	OZ4 IB3GT	4/6 12AH8 8/- 12AT6	30/- 18131 4/ 4/6 2152 4/	
DCC90	7/-	ELL80 EM34	20/-	QQV06/4	90/-	1R5 2D21	5/6 12AT7 5/-12AU7	3/9 2G210 12/ 4/9 2G381 5/	
DF96	6/9	EM80 EM81	7/6	QQV5/10	70/-	2E26	20/- 12AX7 7/- 12BA6	6/3 2G382 6/ 8/- 2G401 5/	
DH77 DK91	4/6	EM84 ENS2	7/6	QS70/20 QS75/20	5/6	3B28 3C45	40/- 12BE6 47/- 12E1	5/9 2G402 6/ 17/6 2G414 6/	
DK92	8/-	EY51 EY81	7/6	Q875/60	20/-	4X150A	95/- 12K7GT	6/- 2G415 6/ 8/- 2G416 6/	
DL66	15/-	EY83	8/6	QS83/3	7/3	SU4G	4/- 12Q7GT	4/6 2G417 6/	
DL94	5/9	EY86	7/-	0895/10	5/6	5Y3GT	5/6 20P4 6/9 20P5	19/- 2N555 12/ 19/6 AC107 9/	
DLS10	12/6	EZ41	10/-	QS150/15	8/-	6/30L2	13/- 2524 A/8 9575GT	6/3 AC127 7/	
DLS19	30/-	EZ81	5/6	QS150/36	901-	GAKS	6/6 25Z6GT	8/6 ACY19 4/	
DY86	6/-	GZ30	10/-	QS150/45	201	6AM6	3/6 30017	15/6 ACY21 4/	
ESSCO	12/-	GZ34	11/-	QS150/80	201-	6AQ4	4/- 30F5	15/6 AF114 7/	
E182CC	22/6	H63	8/-	QS1209	7/3	6AS6	6/0 30FL12	16/- AF116 7/	
EAF42	10/-	KT61	13/6	QV04-7	12/6	6AT6	4/6 30L15	15/3 GET875 6	
EBC33	3/-	KT66 KT67	16/- 45/-	QV05-25 QV06-20	25/-	6B4G	16/- 30L17	13/6 NKT214 4/	
EBC90	9/9 4/6	KT81(7C	5) 15/-	R17	8/-	6BE6	5/~ 30P19 5/~ 30PL1	15/- NKT217 8	
EBF80 EBF83	7/- 8/3	KT81(G.	EC) 35/-	R18 R19	7/6	6BH6 6BJ6	7/6 30PL13 9/- 30PL14	16/3 NKT218 6/	
EBF89 EBL21	6/6	KT88 KTW61	27/6	RG5/500 8130	80/~ 25/-	6BK4 6BN6	27/6 35L6GT 7/6 35W4	5/9 NKT404 12, 4/6 NKT675 6/	
EBL31 ECLL800	27/6	KTW62 ML4	10/-	S130P SP41	25/-3/6	6BQ7A 6BR7	7/- 35Z4GT 8/6 50C5	5/6 NKT677 5/ 6/3 NKT713 7/	
ECC33 ECC40	15/- 9/6	N37	17/6	SP61 STV280/4	3/6	6BR8 6BS7	5/6 50CD6G 16/9 80	31/- OC16 20/ 5/- OC19 17/	
ECC81 ECC82	3/9	PC86	11/6	STV280/8	25/-	6BW6	14/- 85A1 14/- 85A2	25/- OC20 15/ 7/3 OC24 15/	
ECC83	6/3	PC88 PC97	11/6 8/9	8119150	90/-	SCD6G	22/- 90AG	45/- 0025 11/	
ECC88	71-	PC900 PCC84	9/6 6/3	SU2150A	12/6	6CB6	5/-90C1	12/- 0028 16/	
ECF82	7/-	PCC89 PCC189	11/-	U24	24/~	6CH6	5/9 90CV	25/- 0025 11/	
ECH42	11/-	PCF80 PCF86	7/- 9/-	U26	13/6	6CW4	8/6 100B2 12/- 150B3	8/6 OC45 4/	
ECH81 ECH83	5/9 8/-	PCF801 PCF802	10/-	U301	16/3	6D4 6DK6	15/- 801 9/- 803	35/- 0C72 6/	
ECL80 ECL82	7/	PCF806	13/6	U404 U801	11/9 23/6	6F23 6F24	13/6 807 13/- 811	30/-0075 6	
ECL83 ECL86	10/3 9/-	PCL83	9/3	UABC80 UAF42	6/- 10/3	6F25 6F28	12/- 813 11/6 866A	75/- OC76 6, 13/6 OC77 8,	
EF9 EF37A	20/-	PCL85	9/3	UBC41 UBC81	8/6	6J50 6J6	2/6 872A 3/- 6651	57/6 OC78 6 7/6 OC81 4	
EF39 EF41	6/-	PENB4	20/-	UBF80 UBF89	6/9	637G 6K7G	4/9 5654 2/- 5672	8/- QC81D 4	
EF80	5/-	PEN40L	12/-	UCC85 UCH21	7/~	6K8G	3/- 5687	10/- OC81DM 6/ 25/- OC82 6/	
EF89	5/-	PFL200 PL36	14/-	UCH42	10/6	6Q7G	6/- 5749	10/- OC82D 6	
EF92	2/6	PL81 PL82	8/-	UCL82	8/-	6SJ7M	7/- 5842	65/- OC169 5, 10/- OC170 7	
EF183	6/6	PL84 PL500	6/9	UF41	10/-	6SN7OT	4/6 6057	10/- OC171 8	
EF804	21/-	PX4 PX25	14/~	UL41	9/6	6X4	3/6 6059	18/-8X642 3	
EH90	7/8	PY32	8/6	UY41	71-	6X5GT	8/- 6001	12/- XA111 3	
EL33 EL34	12/6	PY81	6/6	VP4B	25/-	7B6 7B7	7/6 6063	7/- XA112 5	
EL41 EL42	10/-	PY83	6/6	VR105/3	0 5/-	708	6/6 6060	9/- XA141 8	
EL81 EL84	7/9 4/9	PY800 PY801	10/-	W81 Z66	15/-	7117	6/6 6087 20/- 6080	25/- THEE	
EL85 EL86	7/6 7/6	PZ30 QQV02/0	10/-	Z319 Z759	26/-28/-	7¥4 10P13	8/6 6096 16/3 6146	8/ 10005 25/ 1CP31 80	
ODEN	1.0	All valve	s bra	ind new	and	boxed.	Postage 6d	valve.	
C.W.	0.	Martin	T	el, 01-7	69 0	199 &	1649	No C.O.D.	
	- 9	END	S.A	E. FO	R L	AST C	F 2,000 T	TPE3	
					_			-	
	R					-			
PEAK-									
	1					100	0	UIND	
				the second	1	1 50	30	UND	
			-	-	-	and the second second	8	+ 8W.	
TR	ANS	SISTO	R	STER	EO	AMP	LIFIER	IN KIT FORM	
Build	this 1	or \$9.10	0 (4/	6 post). P	ower	Pack Ki	£2,10,0 (4/-	post), Cabinet (see	
illustri and fu	ation) il det	50/- pos	paid rea w	or #14.10	Oth.E.I	e three ite Circuit of	ms post paid.	Parts List Booklet ; 8W per Channel	
into 3 Outpu	to 15 t tron	ohm Spe Tape R	aker.	60mV inp	at. C	eramic, C 20 to 20	ooo Hz + 3dB	, Radio Tuner or . Neg, Feed Back	
18dB.	12in.	× Sin, 1	AC	(Sin. Cal	200-	Cir-Kit	Board Constru	ction. Bass, Treble	
Litt.)	Lift, Fully built \$2 extra. Delivery by return of post.								

GLADSTONE RADIO (2 mins. from Station and Buses.) CLOSED WEDNESDAY AFTERNOON CATALOGUE 6d.

COMBINED OPERATIONS

The configurations of Fig. 4.1 have many similarities, which lead naturally to the combination of several operations. In fact, it is possible to perform, say, ten additions or subtractions, three multiplications, and one division operation all at once using a single operational amplifier with several inputs and coefficient potentiometers.

PROBLEM EXAMPLE 1. SOLVING A SIMPLE EQUATION

UNIT "A" can solve a linear algebraic equation consisting of more than ten unlike terms, but a simple example with only four terms will serve as an adequate practical introduction to programming.

Take
$$\frac{3a-2b}{c} = d$$
 (Eq. 4.1)

the letters a, b, and c are regarded as known quantities, and d is the unknown, but the equation can be transposed to solve for any unknown.

Eq. 4.1 is implemented on the computer as shown in the Fig. 4.2 patching circuit. Two voltages corresponding to a and -b are taken from the voltage source to

summer S1, where a is multiplied by $\frac{R_t}{R_1} = 3$, and -b

is multiplied by $\frac{R_f}{R_2} = 2$.

The machine equation for the problem is,

$$\frac{\underline{R}_{t}a - \underline{R}_{t}b}{c} = d \qquad (Eq. 4.2)$$

and if R_t is made 100 kilohm the equation will take the form of

$$\frac{\frac{100}{33}a - \frac{100}{50}b}{c} = d$$
 (Eq. 4.3)

Computing resistor values could equally well be $R_t = 10$ kilohm, $R_1 = 3.3$ kilohm, and $R_2 = 5$ kilohm, to yield the same multiplication ratios. Since a 50 kilohm resistor is not included in the short list of Table 4.1, two 100 kilohm resistors are patched together in parallel in the patching circuit Fig. 4.2.

Routine. To set up Eq. 4.1 on UNIT "A", first of all ensure that the voltage source switch S6 is off. Insert computing resistors into the positions shown in Fig. 4.2 patching circuit, and connect the computing elements together with patching leads. Set VS1 and VS2 dials to zero, and CP1 to "10", corresponding to a divisor of 1. Wire a voltmeter to OA1/SK13 and zero-set the operational amplifier by means of VR15. Next connect a voltmeter to S1/I1/SK2, and switch on S6. Set VS1 dial for a trial value of a = 2V. Transfer the voltmeter from S1/I1/SK2 to S1/I3/SK2, and set VS2 dial for a trial value of b = -2V.

UNIT "A" will now be computing

$$\frac{(3 \times 2) - (2 \times 2)}{1} = 2$$
 (Eq. 4.4)

with a = 2, b = -2, c = 1, and therefore d = 2. When a voltmeter is linked to OA1/SK13 it will be discovered that the output voltage d is actually -2V, due to the operational amplifier sign change. Remedy by reversing the readout meter leads. If the output voltage is not exactly -2V, recheck voltages for a and -b. To check the exact setting of CP1 dial for any value of c, temporarily remove the patching lead from CP1/SK1. Patch CP1/SK1 to a precise +10V from a



Fig. 4.3. Voltmeter method of determining coefficient potentiometer settings

spare voltage source output, and connect a voltmeter to S1/I5/SK2. The voltmeter will then indicate the potentiometer coefficient while taking into account the loading effect of R_t (see Fig. 4.3). A voltmeter reading of 4.75V is equivalent to a coefficient of 0.475. CP1 can now be patched back into the problem set-up. With a 100 kilohm resistor for R_t , CP1 will be dividing by numbers equal to or less than unity. If R_t is changed to 10 kilohm, the range covered by CP1 will become 0–10. Therefore, increasing c by a factor of 10 can be seen quite clearly to be the same as decreasing computing resistor ratios by a factor of 10. With UNIT "A" now programmed for Eq. 4.1, it is

with UNIT "A" now programmed for Eq. 4.1, it is possible to investigate fully the problem for all reasonable values of a, b, c, and d, and for any unknown without the need for transposing terms or altering the problem set-up. For example, to find a when b, c, and d are known, set b and c and adjust a for an operational amplifier output equal to d. Always monitor an input voltage with a voltmeter when it is being adjusted.

To see how serious computing errors can occur at extreme limits, set VS1 and VS2 so that terms 3a and -2b are virtually equal, and $d \simeq 0$. Also, set CP1 to near zero and observe that d will pass beyond the 10V operational amplifier maximum output swing.

PROBLEM EXAMPLE 2.

ANALYSIS OF VOLTAGE DIVIDER CIRCUIT The voltage divider of Fig. 4.4a is often encountered in electronic circuits. At first sight, a network consisting of only two resistors might be considered far too simple to merit investigation by means of a computer,





Fig. 4.4. (a) voltage divider circuit; (b) direct simulation of (a); (c), (d) and (e), three variations on (a)

but it does involve at least six variable quantities V_1 , V_2 , I_1 , I_2 , R_1 , and R_2 , and to solve a problem for any unknown, one of six equations would be required, based on

$$R_1 = \frac{V_1 - V_2}{I_1 + I_2}$$
 (Eq. 4.5)

and

$$R_2 = \frac{V_2}{I_2}$$
 (Eq. 4.6)

Thus, although it would be ridiculous to use the computer to find one specific answer to one particular voltage divider problem, the paperwork involved in solving six equations for several sets of variables could become surprisingly laborious. What the computer does in fact allow is the solution to literally any voltage divider problem under any conditions, without the need for re-programming.

To solve Eq. 4.5 and Eq. 4.6 simultaneously on UNIT "A', the equations are first transposed for terms V_2 and I_2 , which are common to both.

$$V_2 = V_1 - R_1(I_1 + I_2)$$
 (Eq. 4.7)

and

$$I_2 = \frac{V_2}{R_2}$$
 (Eq. 4.8)

Next, both equations are linked to give a self-enforcing systems, shown diagrammatically as,

$$V_1 - R_1(I_1 + I_2) = V_2 \xrightarrow{V_2} R_2 = I_2$$

where the answer to Eq. 4.5 is one of the terms of Eq. 4.6 (V_2) , and the answer to Eq. 4.6 is one of the

Fig. 4.5. Programme layouts for voltage divider analysis (a) (right) symbolised diagram, (b) (below) patching circuit





CHECK VOLTAGES AND POT. SETTINGS SHOWN THUS -SV



terms of Eq. 4.5 (I_2) . To see how the problem is set-up on the computer, refer to Fig. 4.5, and note the changes of sign involved.

Routine. Switch off S6 and 'insert all computing resistors and patching leads, except the link between OA3 output and OA1 input, which carries the voltage analogue of I_2 . Zero-set OA1, OA2, and OA3 in that order, using a voltmeter applied to each operational amplifier output socket in turn. Now patch the link between OA3 output and OA1 input into circuit. Set VS1 to "0", and VS2 to "+10". The voltmeter method of Fig. 4.3 is employed to set CP1 and CP2 both for a coefficient of 0.5. Temporarily remove the patching leads from CP1/SK1 and CP2/SK1, and connect the "top end" of the potentiometer tracks to a 10V reference voltage. Adjust CP1 and CP2 for outputs of 5V. Exactly the same procedure is adopted when it is necessary to "read off" values for R1 and R2, although approximate readings can be taken from CP1 CP2 dials

necessary to "read off" values for R1 and R2, although approximate readings can be taken from CP1, CP2 dials. The check voltages in the diagram of Fig. 4.5 correspond to the above voltage source and coefficient potentiometer settings, and provided that there is general agreement with Ohm's law, any desired values can be given to the voltages, currents, and resistances in Fig. 4.4a. The check voltages could apply to actual voltage divider quantities of, say, $V_1 = 10V$, $V_2 = 5V$, $I_1 = 0mA$, $I_2 = 1mA$ (1 machine volt = 1mA), $R_1 = 5$ kilohm, and $R_2 = 5$ kilohm, where VS1 covers the range 0-10mA, VS2 0-10V, CP1 0-10 kilohm, and CP2 0-10 kilohm. Suppose instead that V_1 had been assigned the value of 1,000V, when R_1 and R_2 were both only 5 ohms. One machine volt would now be equivalent to 100A, and V_2 would equal 500V. The ranges covered by computing potentiometers in the latter case would then be VS1 0-100A, VS2 0-1,000V, CP1 0-100, and CP2 0-10 ohms.

Unless informed otherwise, the computer assumes that V_1 is an ideal voltage which originates from a source of infinitely small resistance. Hence, if $V_1 = 0$, this corresponds to a short-circuit, and gives the variation of Fig. 4.4c. Alternatively, if I_2 is made equal to nought, the voltage divider circuit is transformed into a load resistor R_2 in series with a source resistor R_1 . given by Fig. 4.4d.

One further variation will serve to show the flexibility of the programme. In Fig. 4.4e the resistance network R_1 and R_2 is made to couple two sources of voltage V_1 and $-V_2$, and this occurs when I_1 is made larger than $I_1 + I_2$, or in other words, when I_2 swings negative. The layout of Problem Example 2 is an instance of

The layout of Problem Example 2 is an instance of indirect simulation, where the computer solves equations and imitates the behaviour of the simulated circuit. In this indirect "model" of a voltage divider, relationships between governing equations and actual circuit parameters are made obvious, and the abstractions of mathematics are brought to life as tangible voltmeter and dial readings.

Another way of simulating the Fig. 4.4a circuit is by a direct "model", shown in Fig. 4.4b, which employs coefficient potentiometers for R_1 , R_L , and R_L , voltmeters for V_1 and V_2 , and current meters for I_1 and I_2 . Although feasible, the direct model is less elegant, is not so adaptable to extreme cases, and is subject to errors which do not occur when the voltage divider is simulated indirectly.

Next month: Using UNIT "A" to solve a second order differential equation. Indirect simulation of LC circuits, spring pendulums, and servomechanisms by means of integrators.