

Expand linear circuit functions with nonlinear design schemes

Circuits implementing logarithmic or exponential functions provide instrumentation and control designs with many features unobtainable using linear-only characteristics. Such circuits can gauge fuel level or a grape's ripeness.

Jim Williams, National Semiconductor Corp

Just because a control or instrumentation design requires a logarithmic or exponential transfer function, don't assume that it must be complex, troublesome and expensive. It needn't be if you employ the correct basic circuit (see box, "Straightforward nonlinear circuits"). Indeed, the same concepts apply whether you must measure a tank's contents or control a motor's speed.

Govern a pump's rate

Although peristaltic pumps are generally driven by a continuously rotating motor, this technique isn't suitable when your application requires precise delivery at low rates as well as a high-throughput capability. (This situation often occurs in chemical or biological process-


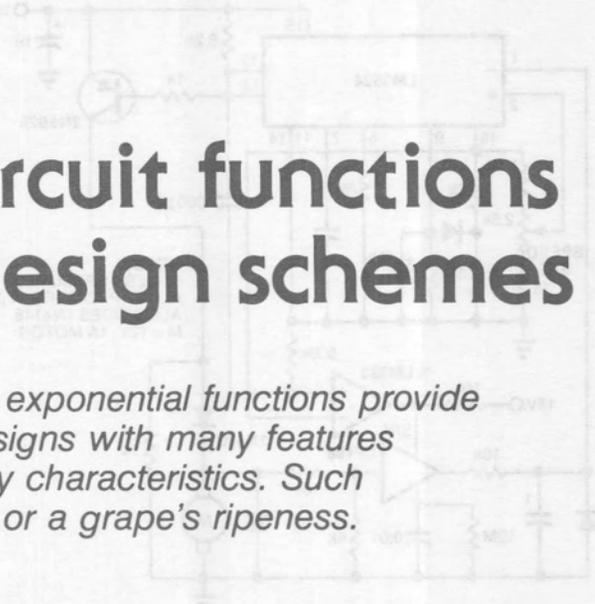


Fig 3—A motor's back EMF provides the error signal in this

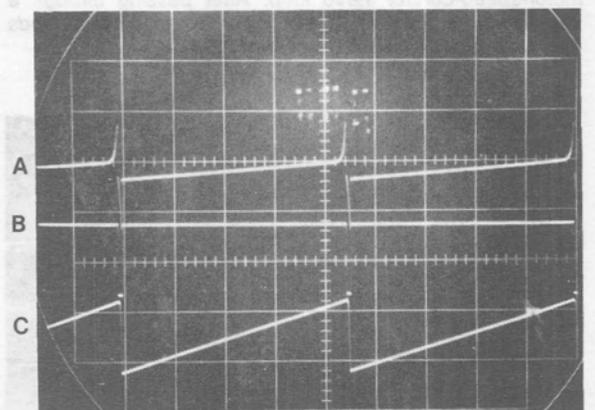

TRACE	V/DIV
A	5
B	20
C	20

HORIZONTAL SWEEP = 200 μSEC/DIV

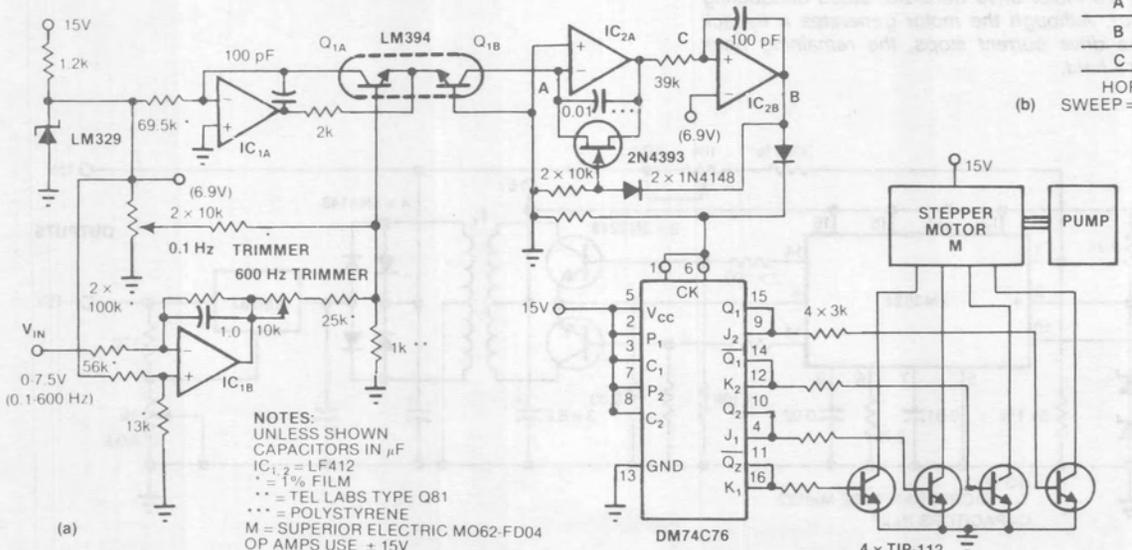


Fig 1—A stepper motor's speed varies exponentially when driven by this voltage-to-4-phase converter. Using this approach, you can precisely govern a peristaltic pump's output flow for tight process control at low rates, yet speed it up for high throughputs. The waveforms correspond to points indicated on the schematic.