

## 17 Diode Thermometer

□ In another project, it was shown how a package of silicon diodes could be developed into a solid-state thermostat. Here is an analog version, which can be interfaced with a voltage-to-frequency converter for use with a frequency counter, or can be directly read by a 10 to 20 thousand-ohms-per-volt multimeter. The circuit utilizes a pair of 4009 inverter sections, biased into the linear region to amplify the temperature effects upon the diode

probe. In this application, the adjustment potentiometer, R1, is set to give a mid-scale reading at room temperature on a typical multimeter set on the 6-volt DC scale. If a separate 0-1 DC milliampere meter is available, it could be calibrated directly in degrees F or C, with a suitable resistance in series with the amplifier output.

### PARTS LIST FOR DIODE THERMOMETER

**C1**—0.1- $\mu$ F ceramic capacitor, 15 VDC

**D1 through D6**—1N4148 diode

**IC1**—4009A hex buffer

**R1**—100,000-ohm linear-taper potentiometer

**R2, R3**—1,000,000-ohm, 1/2-watt resistor

