


# Circuit converts DAC's outputs from single-ended to differential mode

Liam Riordan, Analog Devices, Limerick, Ireland

 High-speed DACs, such as Analog Devices' AD9776/78/79 TxDAC family, offer differential outputs, but, for low-end ac applications or high-precision level-setting applications, a single-ended current-output DAC with a differential-conversion circuit provides a novel approach to generating differential-waveform-control functions. The basic circuit in **Figure 1** combines a current-output DAC, IC<sub>1</sub>, such as the 8-bit

AD5424 DAC, with a single-ended-to-differential op-amp stage—IC<sub>2</sub>, IC<sub>3A</sub>, and IC<sub>3B</sub>—to generate the desired outputs. For dual-power-supply applications, you select the DAC's unipolar mode of operation to achieve optimum performance from the DAC. Using a single op amp, the DAC provides two-quadrant multiplication or a unipolar output-voltage swing. The DAC's output requires a buffer because changing the code applied to the DAC's input

varies its output impedance.

This equation defines the circuit's output voltage:  $V_{OUT} = -V_{REF} \times (D/2^N)$ , where N defines the number of input bits, V<sub>REF</sub> is the reference voltage, and D is the decimal equivalent of the binary code. To generate a positive common-mode voltage, you use a negative voltage for the DAC's reference voltage. The DAC's internal design accommodates ac reference input signals of -10 to +10V. In this mode, the DAC provides a 5M-sample/sec maximum update rate for one-quarter full-scale code changes when you operate it from a 5V power supply. Use resistors R<sub>1</sub> and R<sub>2</sub> only if your application requires adjustable gain.


The single-ended-to-differential stage comprises two cross-coupled op amps, which resistors  $R_3$  and  $R_6$  configure as a unity-gain follower. To yield a symmetric circuit, the outputs also drive each other as unity-gain inverters through  $R_7$  and  $R_8$ . The voltage you apply to the positive terminal of op amp  $IC_2$  sets the circuit's common-mode voltage. Resistors  $R_3$  and  $R_4$  control the amplitude of the differential voltage. Review your application's output-load

requirements and the op amps' input and output-voltage capabilities.


For single-supply applications, you can use a current-output DAC in reverse mode, in which you apply the reference voltage,  $V_{IN}$ , to the DAC's  $I_{OUT1}$  pin and take the output voltage from the DAC's  $V_{REF}$  terminal (Figure 2). In this configuration, a positive reference voltage produces a positive output voltage. This circuit does not use the DAC's feedback resistor,  $R_{FB}$ , and

its connection to  $I_{OUT1}$  prevents stray capacitance effects. The DAC's reference input "sees" an impedance that varies with the applied code and thus requires a low-impedance source.

Note that the switches in the DAC ladder no longer have the same source-to-drain drive voltage, which in turn limits the input voltage to low voltages. As a result, the switches' on-resistances differ and degrade the DAC's linearity. Also, this mode limits the max-

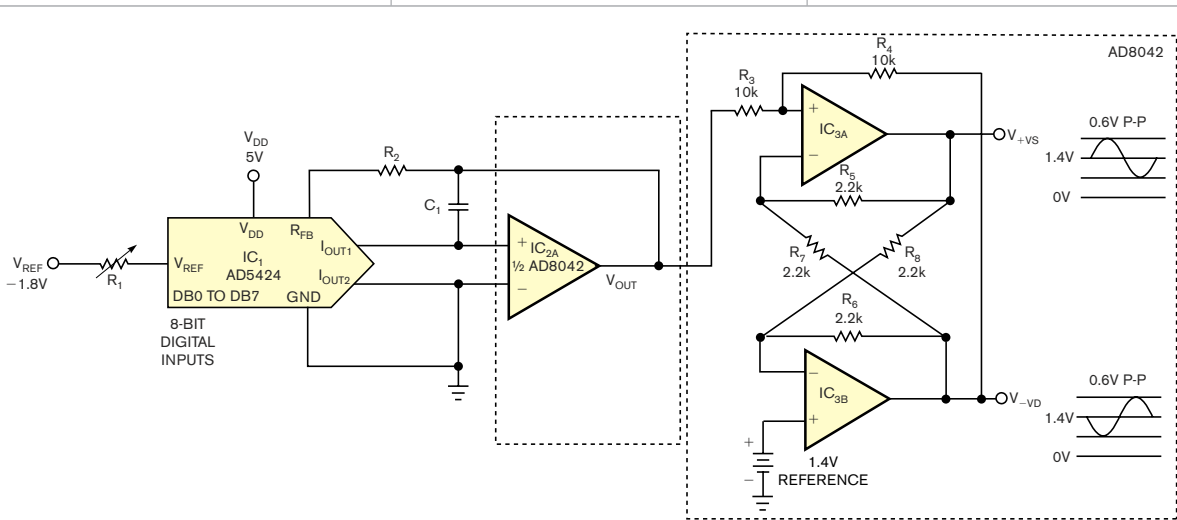


**Figure 1** This basic circuit combines a current-output DAC,  $IC_1$ , with a single-ended-to-differential op-amp stage— $IC_2$ ,  $IC_{3A}$ , and  $IC_{3B}$ —to generate the desired outputs.

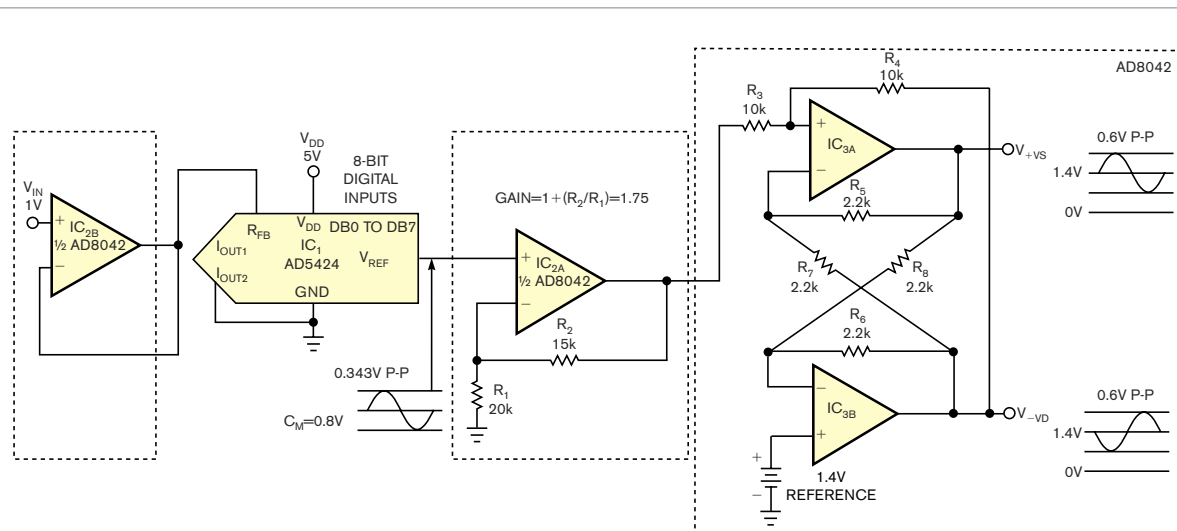

**Figure 2** In this configuration, a positive reference voltage produces a positive output voltage.

imum update rate to 1.5M samples/sec. You can use sections of a dual op amp to buffer the DAC's input and to amplify the DAC's output voltage (Figure 3). The circuit's intended application determines your choice of supporting amplifiers. For lower speed, precision applications, the op amp requires low input-bias currents and low input-offset voltage to avoid degradation of the DAC's DNL (differential-nonlinearity) performance. For example, the AD8628 offers 100-pA maximum bias current at room temperature and 5- $\mu$ V maximum input-offset voltage. The op amp's low-frequency noise is important in precision level-setting applications, and the AD8628 specifies 0.1- to 10-Hz noise of less than 0.5  $\mu$ V p-p. Its rail-to-rail inputs and outputs make it ideal for use in single-supply circuits.

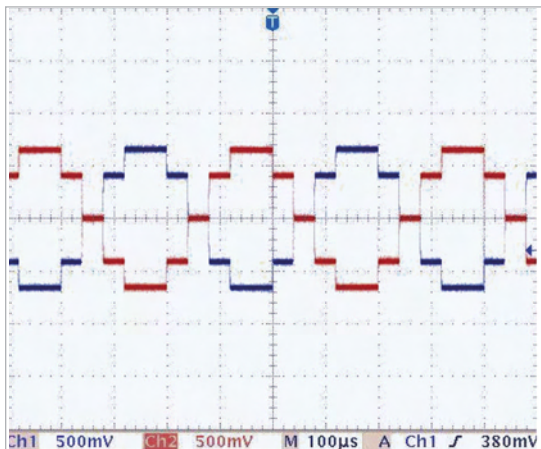

**Figure 3** The single-ended-to-differential conversion of a digitized, eight-point sine wave produces differential outputs.

For high-speed-system applications, the op amp's slew rate must not dominate the DAC's slew rate. The op amp's bandwidth must be large enough to drive the feedback load and must not limit the circuit's overall bandwidth, and the DAC's output-voltage settling

time should determine the circuit's maximum update rate. The AD8042 in figures 1 and 2 offers 170-MHz bandwidth and a 225V/ $\mu$ sec slew rate, allowing it to easily achieve these results. Other high-speed op amps, such as the AD8022, AD8023, and AD8066, also work well in this application.

The DAC consumes only 0.4  $\mu$ A of power-supply current, and the op amps thus dominate the circuit's power consumption. To minimize the area for the circuit on a pc board, you can replace all four op amps in Figure 2 with a single AD8044 quad op amp. The single-ended-to-differential conversion of a digitized, eight-point sine wave in the presence of a 1.4V common-mode voltage and a 0.6V differential signal produces differential outputs (Figure 3).**EDN**