

Pushbutton or logic controls nonvolatile DAC

Stephen Woodward, University of North Carolina, Chapel Hill, NC

FOR MANUAL CONTROL of analog signals, it's hard to beat the venerable precision multiturn potentiometer's simplicity, resolution, and power-off nonvolatility. When digital control of an analog parameter is the design objective, a universe of DACs is available to the designer. The circuit in **Figure 1**, however, has manual-pushbutton and CMOS/TTL-compatible digital interfaces to a 10-bit, nonvolatile, two- or four-quadrant multiplying DAC. The heart of the circuit is the Xicor (Milpitas, CA) X9511 PushPot series of digitally controlled potentiometers. These devices implement a convenient up/down response to either ground-referenced contact closures (with built-in debounce and pullup provisions) or open-collector/drain digital signals.

Other useful features of these digital potentiometers include a $\pm 5V$ analog-signal range and automatic storage and retrieval of settings with power-on/off

cycles via an on-chip EEPROM. The potentiometer's only shortcoming in this context that its resolution is inadequate for precision applications (only 32 distinct settings, equivalent to a mere five bits). To overcome this limitation, the circuit combines two PushPots with a summing op-amp buffer to achieve nearly 10-bit resolution. IC₁ provides a weighted sum of the wiper voltages of P₂ (coarse input) and P₁ (fine input) in the ratio of 25.5-to-1. This operation provides a composite resolution of $32 \cdot (25.5 + 1) = 848$ distinct settings, equivalent to 9.7 bits.

The missing 0.3 bits are lost to the good-but-still-only-finite differential linearity of the X9511 (Xicor specifies ± 0.2 LSBs) and the consequent need to give a less-than-ideal weight (32×0.8 instead of 32) to P₂ to guarantee overall DAC monotonicity. The resultant two-quadrant ($R_2 = 10\text{ k}\Omega$, R_3 omitted) gain equation

is $V_{OUT}/V_{IN} = (25.5 \times P_2 + P_1 - 31) / 761$. Thus, two-quadrant gain runs from -0.04 to 1.04 in steps of 0.0013 , as P₁ and P₂ settings vary from (0,0) to (31,31).

Optionally, you can obtain four-quadrant multiplication by adding one resistor to the circuit, with the value $R_3 = R_2 = 20\text{ k}\Omega$. Gain then becomes $V_{OUT}/V_{IN} = (25.5 \times P_2 + P_1 - 410) / 380$ and ranges from -1.08 to 1.08 in steps of 0.0026 , as P₁ and P₂ vary from 0 to 31. The loading of P₁ by R₁ is light enough to produce a negligible effect on linearity. Connecting Pin 7 (automatic store enable) of P₁ and Pin 7 of P₂ to ground enables automatic storage of potentiometer settings to internal EEPROM upon power-down. The circuit then automatically retrieves the settings on power-up. (DI #2269).

To Vote For This Design,
Circle No. 412

Use a pushbutton or provide a digital signal to choose a nonvolatile analog output with nearly 10-bit resolution.

