





example of the technique can be seen in Figure 2, a circuit that produces an analog quotient of two digital words, multiplied by a constant or variable reference.

In this circuit, two CMOS d/a converters are used. Converter A1 is connected in the forward path of op amp A3, producing an output,  $V_1 = -B V_{REF}$ , where B is the fractional binary value corresponding to the input code. Converter A2 is connected in the feedback path of op amp A4, producing an output,  $V_O = -V_1/A$ , where A is the fractional binary value associated with A2's input code. The overall relationship, therefore, is

$$V_O = \frac{B}{A} V_{REF} \quad (1)$$

$V_{REF}$  may be of any value in the range  $\pm 10V$ , B may be any number from 0 to 1023/1024, in steps of 1/1024, and A may be any such number from 1/1024 to 1023/1024. Naturally, the ratio is limited to values for which the output,  $V_O$ , is within bounds.  $V_{REF}$  may be positive or negative, ac or dc, and the output will be of the same polarity.

Like analog division circuits, this circuit has an output error-characteristic inversely proportional to the denominator, A.

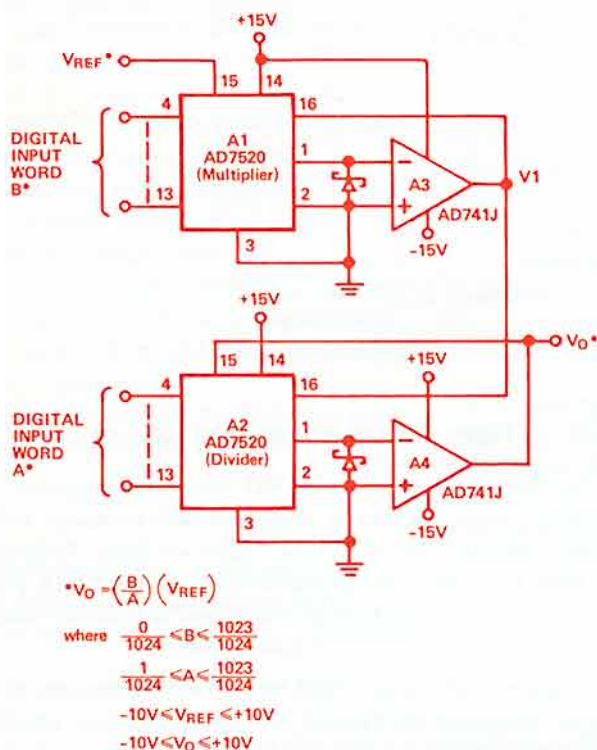


Figure 2. Algebraic manipulations — Analog quotient of two digital words.

## 8-BIT-PROGRAMMABLE SQUARE-WAVE OSCILLATOR

Programmability is an important new degree of freedom in analog circuit and system design. Virtually any circuit parameter can be made digitally controllable with little difficulty, using a/d and d/a conversion devices. It is important to be aware that "digitally controllable" doesn't necessarily mean that programmed circuits must interface with computers, processors, or even digital systems. In many cases, the digital input can be provided by manually operated switches, which

need not be fancy, since they need only to switch binary levels. This circuit and those that follow illustrate a variety of practical examples of programmable circuits.

Figure 3 shows an 8-bit (255-frequency) programmable oscillator with square-wave output. The circuit comprises a current-output d/a converter (AD1408 family) and a current-to-frequency converter (AD537 family). The digital input produces a linearly related current from the DAC; this current, driven directly to the input of the VFC, produces a square-wave that has a frequency proportional to the numerical value of the digital input word.

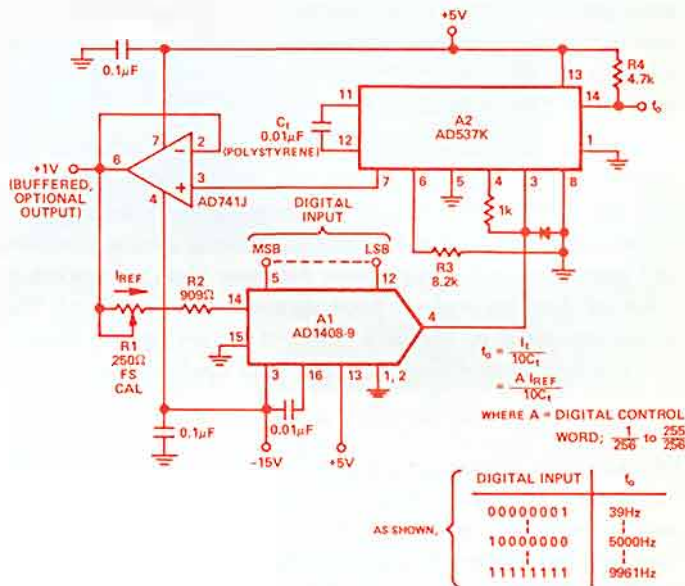


Figure 3. 8-bit programmable oscillator, square-wave output.

The AD1408-9 (9-bit-linearity) DAC is scaled for 1mA full-scale current output, to match the 1mA full-scale input of the AD537K. The 1mA reference current for the DAC is derived from the 1V reference output of the AD537, buffered by the AD741 follower-connected op amp. Since the basic reference source is common to both devices, errors due to its drift tend to cancel out.

A polystyrene capacitor is used for  $C_T$ , and its tempco is compensated for by loading the AD537's  $V_T$  output with  $R_3^4$ .  $R_3$  can be adjusted to trim the overall system tempco. The circuit, as shown, has a nominal full-scale frequency of 10kHz (9961Hz for all-1's), with  $C_T = 0.01\mu F$ . Worst-case nonlinearity of the specified DAC-VFC combination is 0.16%. The output is a TTL-compatible square wave.


## PROGRAMMABLE GAIN TRIMMING OR CALIBRATION

It is usual, in the design of devices such as converters or amplifiers, to concentrate design attention on linearity, since gain and offsets are considered to be reducible errors. Nevertheless, in high-precision applications, the gain must eventually be calibrated. D/A converters are improved substitutes for potentiometers, if the gain of the device-to-be-calibrated is set at a value near the nominal value, and the programmed converter provides the difference. Calibration can be performed automatically, under software control, with the required incremental value retained in a counter or latched; or it can be performed manually, using a thumbwheel switch.


<sup>4</sup> AD537 data sheet, page 4.



In the circuit of Figure 4a, an AD1408-9 (256 adjustment steps) provides the incremental adjustment range for the scale factor of an AD562 12-bit DAC. When pin 5 of the AD562 is connected to a 10V reference, the gain will be 0.2% high. In this circuit, a programmable 0 to  $-2\mu\text{A}$  current applied at the summing point will provide a  $\pm 0.2\%$  range of gain change in 15.6ppm/LSB increments (1/16 of an LSB in the AD562).

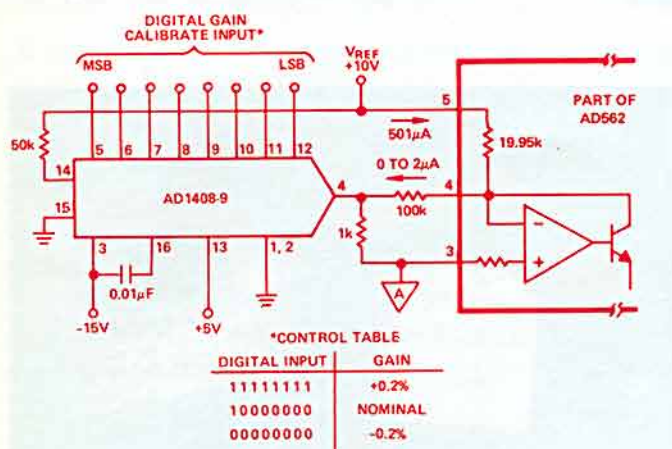

(a) D/A gain calibration.

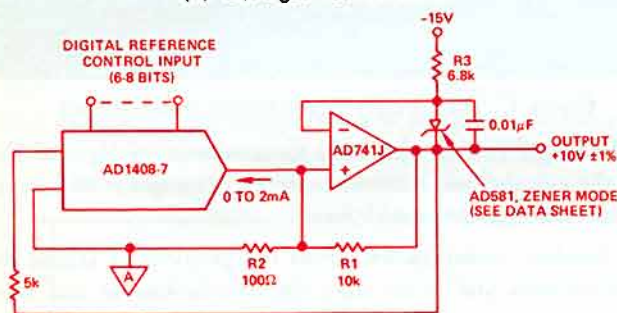

(b) Direct reference voltage calibration.

Figure 4. Gain calibration methods.

The performance of the components used to achieve this function is not highly critical, since their contribution to overall gain error is reduced by their small weighting. The use of this scheme with an AD562 DAC is a simple example, but it is applicable wherever automatic calibration to high absolute accuracy is required.<sup>5</sup> Coarser steps (fewer bits) could have been used (6 bits of a 1408-7) if appropriate.

In Figure 4b, a related scheme is used to calibrate the output of a buffered reference circuit. The basic reference is an AD581 10V bandgap reference, connected as a 2-terminal "Zener diode", in the feedback path of an op amp. The 1% positive feedback increases the output voltage to 10.1V, and the 2mA full-scale output from the AD1408-7 DAC, flowing in the 100Ω resistor, can reduce the output voltage to about 9.9V. Thus, the adjustable range is 10V  $\pm 0.1\text{V}$ , in increments of about 780µV/bit, for 8-bit control.

Amplifier gain can also be trimmed by using a DAC to set incremental gain values in the neighborhood of nominal gain. A typical scheme for programming inverting-amplifier gain would employ a CMOS DAC, with its input attenuated, in shunt with the input resistor of an inverting operational amplifier.

<sup>5</sup> For another example, see the AD572 12-bit ADC data sheet, Figure 11.

<sup>6</sup> See the AD521 data sheet, Figure 4, page 4.

## PROGRAMMABLE OFFSET

A programmed constant offset (or offset-zeroing voltage) can be introduced at the *reference* input of an instrumentation amplifier, to provide an output offset, independent of gain. Figure 5 shows how an AD521 instrumentation amplifier might operate in conjunction with an AD561 10-bit d/a converter. In this case, the nominal full-scale output range of the AD561 is  $\pm 1\text{V}$ , when loaded by 2.5kΩ. Larger offset ranges than  $\pm 1.67\text{V}$  would be available by using a follower-with-gain between the DAC output and the amplifier's *reference* input, or by providing a portion of the AD521 gain via *sense* feedback,<sup>5</sup> the offset would be amplified by the same amount. Smaller offset voltages are obtained by simply reducing  $R_X$ .

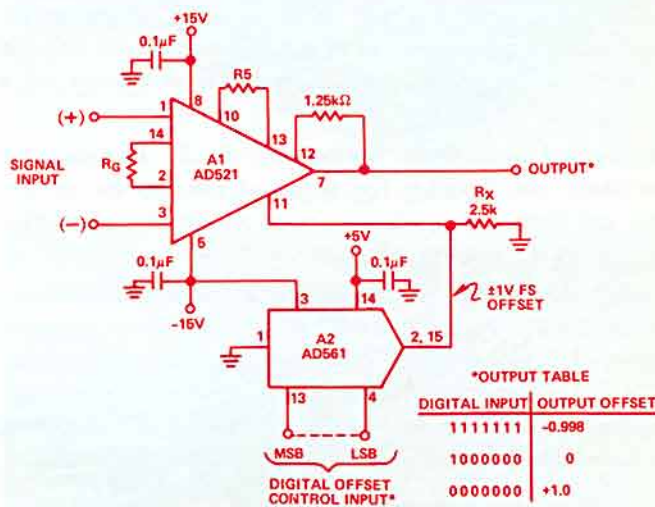


Figure 5. Programmable offset instrumentation amplifier.

## 4-20mA CURRENT CONTROLLER

A common requirement in industry is for transmission of analog data in the form of a 4-20mA current, to minimize the effects of ground-potential differences, series resistance, and voltage-noise pickup. 4mA corresponds to zero, 20mA to full scale.

Figure 6 shows a circuit to accomplish this with 10-bit resolution. An AD561 is used, in conjunction with an op amp and a Darlington transistor. With an all-0's digital input, the 1kΩ offset pot is adjusted for 4mA of output current. With all 1's, the *scale-adjust* pot is set for 20mA (or 19.98mA) of output current.

Although the load is shown here as being referred to a +15V supply, it may—in general—be returned to any positive voltage within the breakdown rating of the transistor used. The diode protects against reverse-polarity faults, the fuse against shorts.

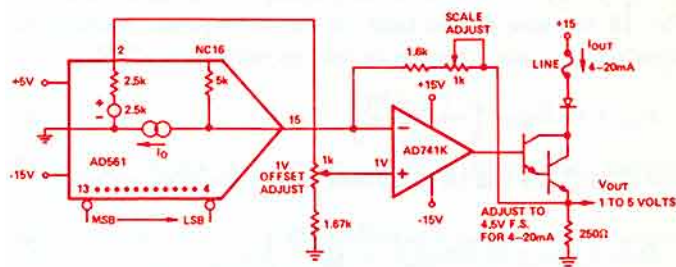


Figure 6. Process control current source.