

displayed. This, of course, is due to the latches or the 8255 IC's in the interface. Thus, the microcomputer can output numeric information once and then go on to perform any other required operations.

Another interfacing method is digit *multiplexing*. Multiplexing reduces the display-interface electronics (number of parts) to a minimum; however, at the expense of longer and more complex display-driver software. Multiplexing a display consists of enabling or turning on one particular digit with a *digit-enable code* and providing the BCD numeric information for that digit to a multidigit display interface. In this way each digit is turned on, one at a time, as the actual BCD data for each digit is provided. Multiplexing is usually only used with multidigit displays.

As an example, let's suppose the number "237" is to be displayed on a 3-digit multiplexed display. To display this number the BCD value for the digit "7" would be output to the interface along with the digit-enable code for the right-hand display. After a short period (1 μ s to 10 μ s) the BCD value for number "3" would be output along with the digit-enable code for the middle digit. Again, after a short delay, the BCD value for the number "2" and the digit-enable code for the left-hand display would be output to the interface. By performing this sequence 50 or more times every second, each digit in the display *appears* to be on *all the time*. This display method is used in hand-held calculators. Even though the digits are being turned on and off, it happens too fast for the eye to see. The interface for a 10-digit multiplexed display is shown in Fig. 2.

When an OUT125 instruction is executed, bits D3-D0 of register A determines which one of the 10 digits in the display will be enabled (turned on). Therefore, these 4 bits constitute the digit-enable code. Bits D3-D0 are latched (7475) and are decoded with a one-of-10 decoder (7442). The decoded outputs of the 7442 are wired to the common cathodes of the individual digits in the display. Bits D7-D4 provide the BCD code of the value to be displayed (0-9). These bits are also latched (7475) and are decoded by a 7-segment decoder/driver (DS8857, manufactured by National Semiconductor, Santa Clara, CA):

An additional display method involves the use of an external display controller IC to control the multiplexed display. The Intel Corporation manufactures some of these IC's that are compatible with the 4004/4040, 8080 and 8085; these IC's are the 4269, 8279 and 8279-5. National Semiconductor Corporation also has developed two display controller IC's that can be used with 6-digit displays. One of the devices (the MM74C912) can be used to display 0-9 and the other (the MM74C917) can be used to display hexadecimal numbers. **R-E**