

# Arrange LEDs as seven-segment displays

Charaf Laissoub, Valeo Engine and Electrical Systems, Créteil, France

When you need to drive three seven-segment LED displays, you typically need 10 I/O lines—and that's

without a decimal point. You might think that you cannot accomplish that task without a binary-to-seven-segment

decoder or a serial-to-parallel shift register (Reference 1). Many previous Design Ideas have shown how to maximize the number of LEDs you drive with a minimum number of I/O lines (references 2 through 5). This Design Idea shows how you can build a circuit that drives 21 LEDs, thus forming three pseudo-seven-segment displays.

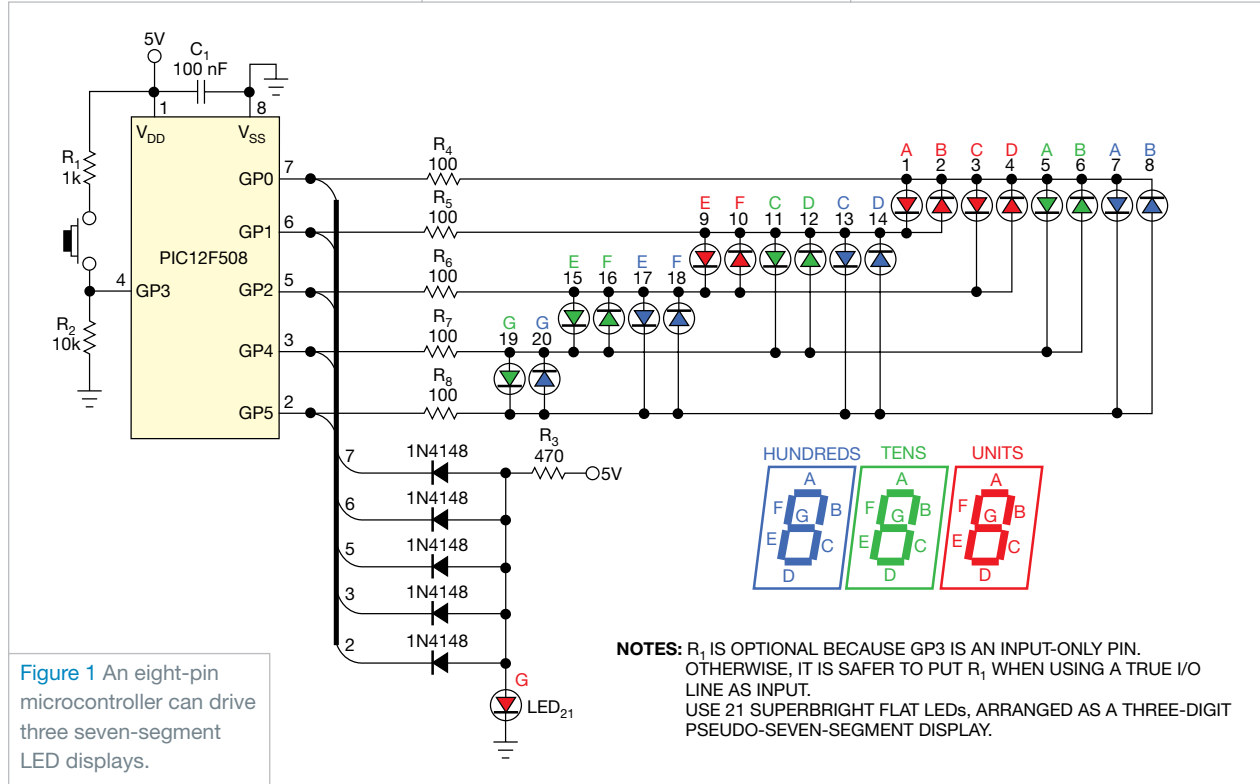


Figure 1 An eight-pin microcontroller can drive three seven-segment LED displays.

The circuit in **Figure 1** modifies the circuit in a previous Design Idea (**Reference 6**). It adds the 21st LED, but it modifies the assembler code to use just 98 words without the main routine. **Listing 1**, the assembler code, is available with the online version of this Design Idea at [www.edn.com/110526dia](http://www.edn.com/110526dia). It can also suit any of a Microchip ([www.microchip.com](http://www.microchip.com)) baseline or midrange PIC microcontroller's eight pins.

## THE CIRCUIT ADDS THE 21<sup>st</sup> LED, BUT IT MODIFIES THE ASSEMBLER CODE TO USE JUST 98 WORDS WITHOUT THE MAIN ROUTINE.

You can adapt this code for another type of microcontroller, such as those from Atmel ([www.atmel.com](http://www.atmel.com)) or STMicroelectronics ([www.st.com](http://www.st.com)), using the following steps:

1. Build a look-up table of 10 values for seven-segment coding (see **table "Code7Segment"** in **Listing 1**).
2. Build a look-up table of 3×7

values to store the successive configurations for I/O lines, each configuration containing only one high output and one low output to drive one LED at a time, for each digit (see **table "Cfg2LinesOut"** in **Listing 1**).

3. Build a look-up table of 3×7 values to store the successive high and low state for the I/O lines that are acting as outputs to light only one LED at a time for each digit (see **table "Light1LED"** in **Listing 1**).

4. The subroutine DispDigit rotates to the right seven times, through Carry flag, and the seven-segment code of a digit. It then calls the subroutine LEDon each time you set Carry.

5. The subroutine LEDon activates the LED related to the I/O configuration code, which you can extract from **table "Cfg2LinesOut,"** and lights it according to the high or low state code, which you extract from **table "Light1LED."** The subroutine ends by a jump to a critical 1- to 3-msec delay subroutine. Increasing this delay increases the flicker effect, and decreasing this delay dims the LED.

6. Cycle digits of units, tens, and hundreds through steps 4 and 5.

For the PIC10F2xx series, which contains only three I/O lines, **Figure 2** shows an example of driv-

ing one digit, and **Listing 2** shows the corresponding assembler code. You can access **Listing 2** from the Web version of this Design Idea at [www.edn.com/110526dia](http://www.edn.com/110526dia). **EDN**

## REFERENCES

1. Anonymous, "Microcontroller provides low-cost analog-to-digital conversion, drives seven-segment displays," *EDN*, May 10, 2007, pg 80, <http://bit.ly/hrcp8g>.
2. Raynus, Abel, "Squeeze extra outputs from a pin-limited microcontroller," *EDN*, Aug 4, 2005, pg 96, <http://bit.ly/gX723N>.
3. Jayapal, R, PhD, "Microcontroller's single I/O-port line drives a bar-graph display," *EDN*, July 6, 2006, pg 90, <http://bit.ly/fjb0MU>.
4. Lekic, Nedjeljko, and Zoran Mijanovic, "Three microcontroller ports drive 12 LEDs," *EDN*, Dec 15, 2006, pg 67, <http://bit.ly/dRIIBN>.
5. Gadre, Dhananjay V, and Anurag Chugh, "Microcontroller drives logarithmic/linear dot/bar 20-LED display," *EDN*, Jan 18, 2007, pg 83, <http://bit.ly/hJCs3j>.
6. Benabadji, Nouredine, "PIC microprocessor drives 20-LED dot- or bar-graph display," *EDN*, Sept 1, 2006, pg 71, <http://bit.ly/g7ZIQY>.

