

# Multiplexing technique yields a reduced-pin-count LED display

Saurabh Gupta and Dhananjay V Gadre,  
Netaji Subhas Institute of Technology, Dwarka, New Delhi, India

“Charlieplexing” as a method of multiplexing LED displays has recently attracted a lot of attention because it allows you, with  $N$  I/O lines, to control  $N \times (N - 1)$  LEDs (references 1 through 5). On the other hand, the standard multiplexing technique manages to control far fewer LEDs. Table 1 lists the number of LEDs that you can control using Charlieplexing and standard multiplexing by splitting the available number of  $N$  I/O lines into a suitable

number of rows and columns. Table 1 also shows the duty cycle of the current that flows through the LEDs when they are on.

Clearly, Charlieplexing allows you to control a much larger number of LEDs with a given number of I/O lines. However, the downside of this technique is the reduced duty cycle of the current that flows through the LEDs; thus, to maintain a given brightness, the peak current through the LEDs must increase proportion-

ately. This current can quickly reach the peak-current limit of the LED. Nonetheless, Charlieplexing is a feasible technique for as many as 10 I/O lines, allowing you to control as many as 90 LEDs. To control an equivalent number of LEDs using the standard

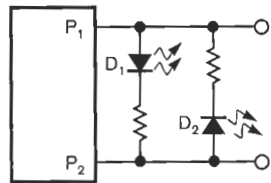



Figure 1 “Charlieplexing” with two I/O lines allows you to control two LEDs.

**TABLE 1 NO. OF LEDs AND DUTY CYCLE**

No. of I/O lines	Multiplexing-controlled LEDs	Duty cycle with multiplexing (%)	Charlieplexing-controlled LEDs	Duty cycle with Charlieplexing (%)
Two	Two	100	Two	50
Three	Three	100	Six	16.67
Four	Four	50	12	8.33
Five	Six	50	20	5
Six	Nine	33	30	3.33
Seven	12	33	42	2.4
Eight	16	25	56	1.78
Nine	20	25	72	1.38
10	25	20	90	1.11

**TABLE 2 OUTPUT VOLTAGE**

P <sub>1</sub>	P <sub>2</sub>	Voltage at node PR <sub>1</sub>
0	0	V <sub>CC</sub>
0	1	V <sub>CC</sub>
0	Z	V <sub>CC</sub>
1	0	0
1	1	0
1	Z	0
Z	0	V <sub>CC</sub> /2
Z	1	V <sub>CC</sub> /2
Z	Z	V <sub>CC</sub> /2

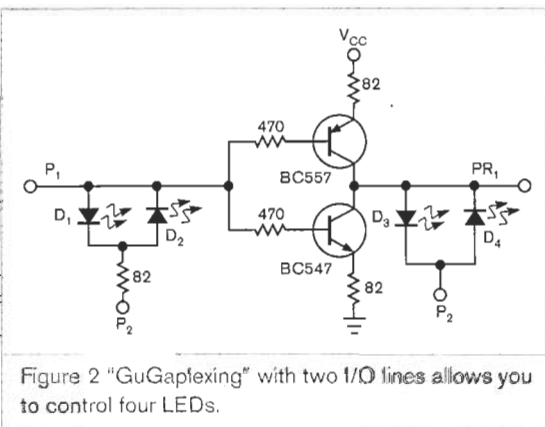

nique that allows you to control twice as many LEDs. Thus, the proposed method, "GuGaplexing," allows  $2 \times N \times (N-1)$  LEDs using only  $N$  I/O lines and a few additional discrete components (Figure 1). To turn on LED  $D_1$  using the Charlieplexing method, set  $P_1$  to logic one and  $P_2$  to logic zero. To turn on

multiplexing technique would require 19 I/O lines.

This Design Idea proposes a modification to the Charlieplexing tech-

LED  $D_2$ , set  $P_1$  to logic zero and  $P_2$  to logic one. Figure 2 shows the proposed GuGaplexing scheme with two I/O lines controlling four LEDs. The

**TABLE 3 I/O LINES AND PR<sub>1</sub> VOLTAGE**

P <sub>1</sub>	P <sub>2</sub>	Voltage at node PR <sub>1</sub>	LED that turns on
0	0	V <sub>CC</sub>	L <sub>3</sub>
0	1	V <sub>CC</sub>	L <sub>2</sub>
1	0	0	L <sub>1</sub>
1	1	0	L <sub>4</sub>
Z	Z	V <sub>CC</sub> /2	None

GuGaplexing technique exploits the fact that each I/O line has three states: one, zero, and high impedance. Thus, with two I/O lines, states 00, 01, 10, and 11 of eight possible states control the LEDs.

Table 2 lists the voltage at the output of the transistor pair for various states of the two I/O lines,  $P_1$  and  $P_2$ . The transistor pair comprises a BC547 NPN and a BC557 PNP transistor; matched transistor pairs are recommended. For  $N$  I/O lines, the GuGaplexing technique requires  $N-1$  transistor pairs. Table 3 shows the state of the I/O lines  $P_1$  and  $P_2$  and the voltage at node  $PR_1$  to control the four LEDs. The circuit requires that the LED turn-on voltage should be slightly more than  $V_{CC}/2$ . Thus, for red LEDs with a turn-on voltage of approximately 1.8V, a suitable supply voltage is 2.4V. Similarly, for blue or white LEDs, you can use a 5V supply voltage. Modern microcontrollers, especially the AVR series of microcontrollers from Atmel ([www.atmel.com](http://www.atmel.com)), operate at a wide variety of supply voltages ranging from 1.8 to

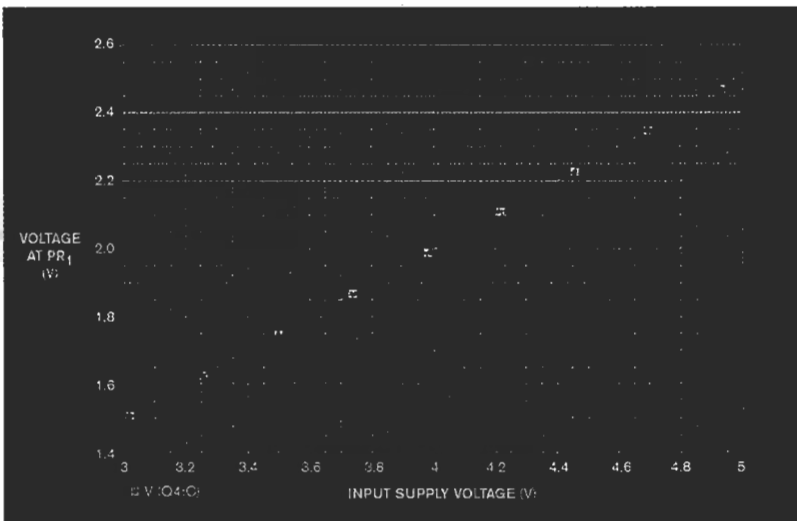


Figure 3 This graph plots the voltage at node  $PR_1$  for various supply-voltage values when the input to the transistor pair is floating.

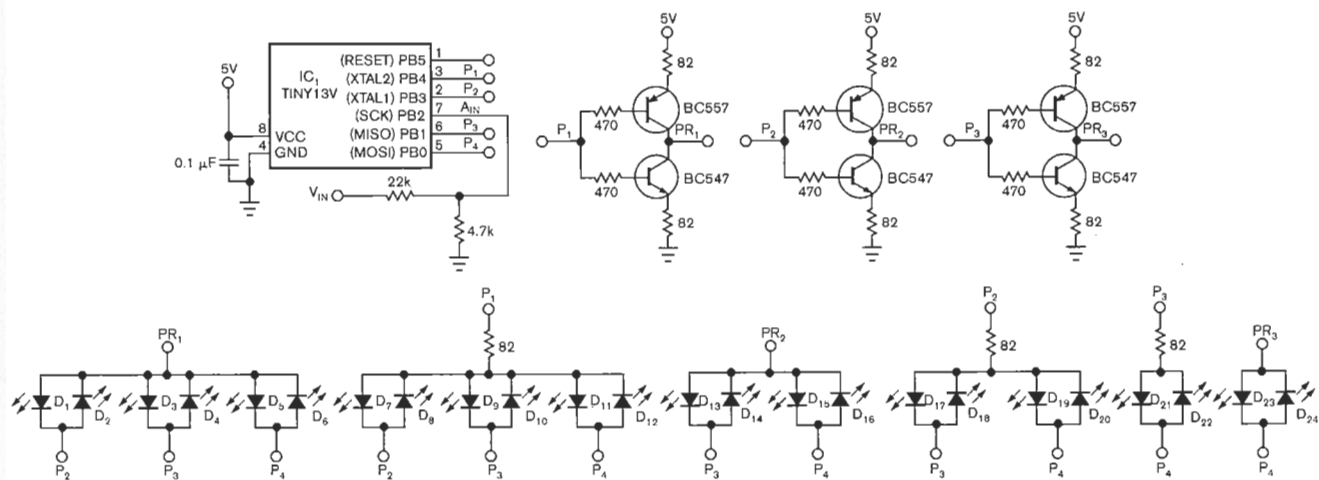


Figure 4 With the GuGaplexing technique, controlling 24 LEDs requires only four I/O lines and three sets of transistors.

5.5V, and this design uses a Tiny13 microcontroller to implement the GuGaplexing technique.

Figure 3 plots the voltage at node  $PR_1$  for various supply-voltage values when the input to the transistor pair is floating. The Spice simulation ensures that the circuit would work properly to provide  $V_{CC}/2$  at the  $PR_1$  node for wide operating-supply-voltage values when the input is floating.

A 24-LED bar display validates the scheme in a real application (Figure 4). The display is programmable and uses a linear-display scheme for the input analog voltage. The input analog voltage displays in discrete steps on the 24-LED display. Controlling 24 LEDs requires only four I/O lines and three pairs of transistors. The system uses 5-mm, white LEDs in transparent packaging and a 5V supply volt-

age. The GuGaplexing implementation uses an AVR ATtiny13 microcontroller. The analog input voltage connects to Pin 7 of the ADC input of the Tiny13 microcontroller.

The control program for the ATtiny13 microcontroller is available with the Web version of this Design Idea at [www.edn.com/081016di1](http://www.edn.com/081016di1). The source code is in C and was compiled using the AVR GCC freeware compiler. You can modify the source code to display only one range of input voltage between 0 and 5V. For example, it is possible to have a linear-display range of 1 to 3V or a logarithmic scale for **input voltage of 2 to 3V. EDN**

## REFERENCES

- 1 Lancaster, Don, *Tech Musings*, August 2001, [www.tinaja.com/glib/muse152.pdf](http://www.tinaja.com/glib/muse152.pdf).

- 2 "Charlieplexing: Reduced Pin-Count LED Display Multiplexing," Application Note 1880, Maxim, Feb 10, 2003, <http://pdfserv.maxim-ic.com/en/an/AN1880.pdf>.

- 3 Chugh, Anurag, and Dhananjay V Gadre, "Eight-Pin Microcontroller Handles Two-Digit Display With Multiple LEDs," *Electronic Design*, May 24, 2007, <http://electronicdesign.com/Articles/ArticleID/15512/15512.html>.

- 4 Gadre, Dhananjay V, and Anurag Chugh, "Microcontroller drives logarithmic/linear dot/bar 20-LED display," *EDN*, Jan 18, 2007, pg 83, [www.edn.com/article/CA6406730](http://www.edn.com/article/CA6406730).

- 5 Benabadji, Noureddine, "PIC microprocessor drives 20-LED dot-or-bar-graph display," *EDN*, Sept 1, 2006, pg 71, [www.edn.com/article/CA6363904](http://www.edn.com/article/CA6363904).