

THINK TANK

By John J. Yacono

The Bitgrabber Revisited

Back in the December 1990 issue of **Popular Electronics**, there was a project (which I designed) that generated a good deal of mail—luckily all of it was good. Many people came out with additions and modifications to the circuit, and since it is a very simple project, I though I'd present some of the mail here.

The project was called the *Bitgrabber*, and it was a very simple (read that "beginner's") computer project. In fact, even if you've never built a computer-oriented circuit, you needn't hesitate to try assembling the Bitgrabber; as long as you wire it correctly, it will work. (In fact, one of this month's contributors reduced the project to a one-IC circuit!)

What the Bitgrabber does

is monitor the parallel-printer connector of an IBM compatible and waits to see a particular character coming out from there. The character it looks for is set by the user through some switches. When the user-set character matches the computer-generated character, the output of the Bitgrabber goes low.

The Bitgrabber is as useful as it is simple. It can be used to troubleshoot parallel-printer cables and interfaces, or even serial cables. By using optocouplers, you can even use it to turn appliances in your house on and off at the command of your home computer.

HOW IT WORKS

Inside a computer, characters are represented

by 8-bit binary numbers. The number that represents each character can be taken off an ASCII or IBM character chart, which is contained in most computer books. When a computer sends a character to a parallel printer, it sends all of the character's eight bits at once (*i.e.*, in parallel). They exit the computer through pins 2–9 on a DB-25 connector.

The Bitgrabber circuit is shown in Fig. 1. The eight switches, S1-a–S1-h, are used to tell the Bitgrabber the pattern of the bits it is to look for. When the bit pattern from the computer matches the pattern of the switches, the Bitgrabber's output goes low. That's all there is to it. If you want a more in-depth explanation of the parallel-printer port or the operation of the Bitgrabber, see the December 1990 issue of **Popular Electronics**.

The Bitgrabber is really a springboard; a project that leaves it up to the builder to make it really useful. That's what many of you have done. Let's take a look at some of the ideas that you've sent in (all of them will of course be rewarded with a *Think Thank II* book), and permit me to throw in a few curves of my own.

THE ONE-CHIP BITGRABBER

I have been an avid reader of **Popular Electronics** for a number of years and although I normally get a chance to read the magazine when it arrives, I just got around to reviewing the December 1990 issue.

The Bitgrabber article starting on page 33 is a

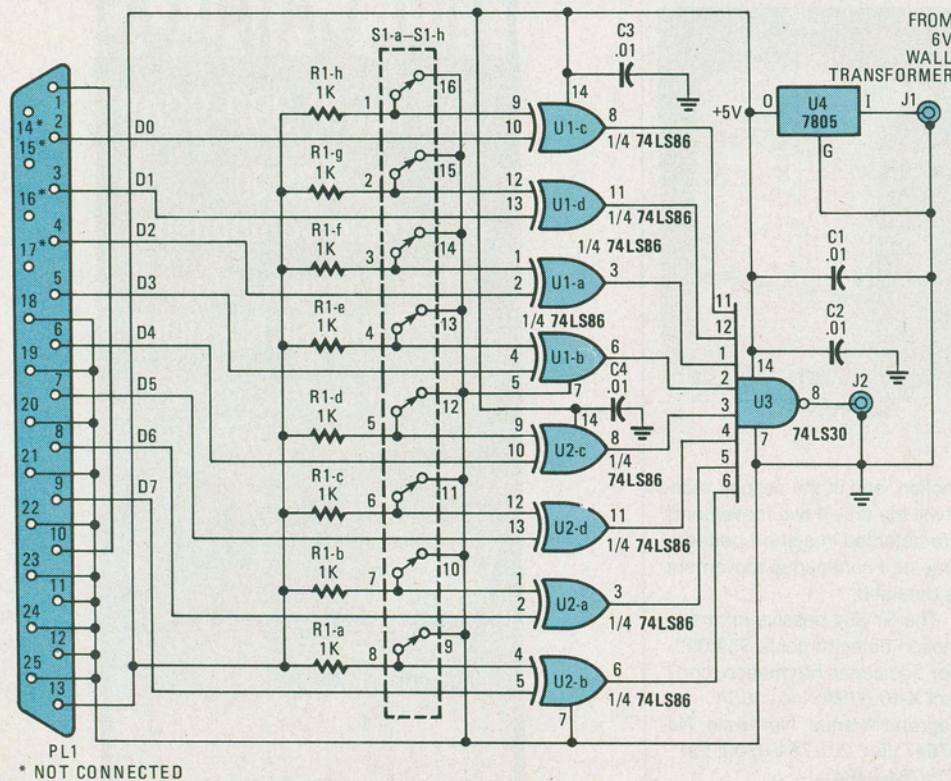


Fig. 1. The Bitgrabber in its earliest incarnation. It's a springboard that many ideas have sprung from.

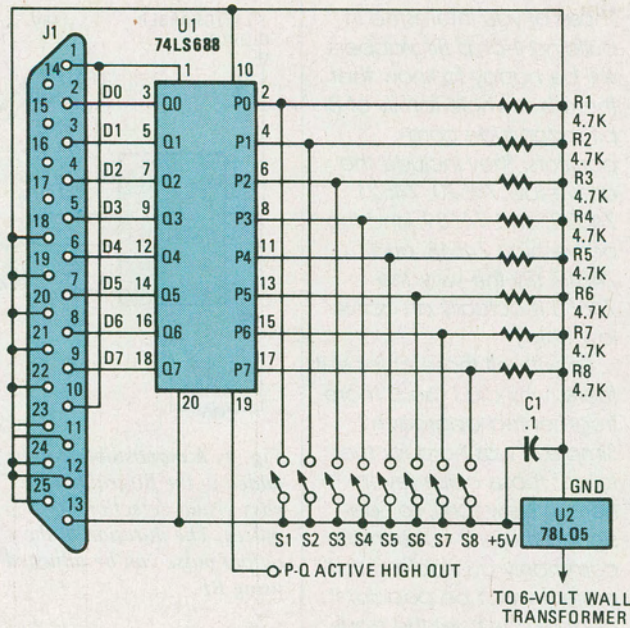


Fig. 2. One chip can replace all three of the chips in the old Bitgrabber. The trouble is getting the chip.

very interesting article and could be used as a basic building block for numerous computer projects. However, after a detailed inspection of the circuit I would like to suggest a simpler approach.

The IC used in my circuit (see Fig. 2) is a 74LS688 8-bit magnitude comparator. Amazingly enough, the functional blocks that make up the 74LS688 almost duplicates the circuit shown in your article. The chip is especially designed to accomplish exactly what the three chips in the Bitgrabber do. By placing the data from the comput-

er on the Q inputs and the user-selected data from the switches (S1-S8) on the P inputs, you'll get an active-high output on pin 19, if and only if, the two sets of data match.

The greatest advantage to using this IC in the circuit is that it reduces the number of components. An added advantage, from my viewpoint, is that the output is an active high, which generally makes it easier to interface with other circuits. Also since the chip provides a chip-enable input (pin 1), it allows handshaking to be tested also.

The additional circuit (shown in Fig. 3) can easily be added to latch onto the circuit's output. It eliminates having to repeatedly output a match to activate a slow test instrument (such as a multimeter). It is a very simple circuit that can be found in about all reference books on SCR's. I hope both circuits will be useful to someone. Keep up the good work with the magazine.

—Bobby D. Smith, Lake Charles, LA
Very, very well done!


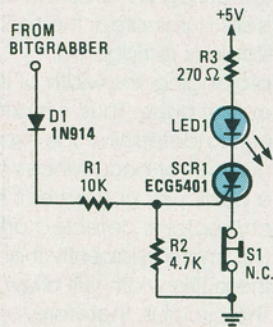


Fig. 3. A simple latching indicator can be made for the revised Bitgrabber (back in Fig. 2) with just a few components.

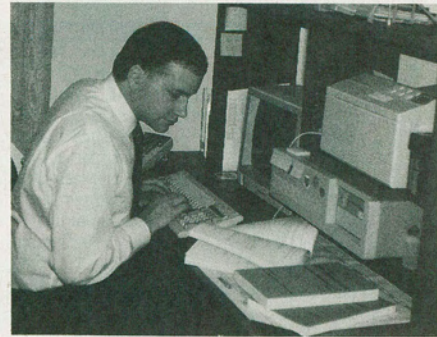Earn Your B.S. Degree in ELECTRONICS or COMPUTERS



By Studying at Home

Grantham College of Engineering, now in our 41st year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Our Computer B.S. Degree Program includes courses in BASIC, PASCAL and C languages — as well as Assembly Language, MS DOS, CADD, Robotics, and much more.

Our Electronics B.S. Degree Program includes courses in Solid-State Circuit Analysis and Design, Control Systems, Analog/Digital Communications, Microwave Engr, and much more.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by
the Accrediting Commission of the
National Home Study Council

GRANTHAM
College of Engineering
Grantham College Road
Slidell, LA 70460

SPECIAL FROM ETT

PCP101—PRACTICAL DIGITAL ELECTRONICS HANDBOOK ... \$9.95. Introduces digital circuits, logic gates, bistables and timers, as well as microprocessors, memory and input/output devices. Special section on digital test gear projects.



PCP102—INTRODUCING DIGITAL AUDIO ... \$9.95 Shows what is involved in the digital part of audio signals, particularly in the newest devices such as CD, DAT and sampling. Bridges the gap of understanding for the technician and enthusiast.



PCP103—PRACTICAL MIDI HANDBOOK ... \$9.95. Covers all MIDI based equipment you can use—keyboards, drum machines, sequencers, effects units, mixers, drum pads and guitars. Also a section on computer music that covers software and more.



PCP104—ELECTRONICS BUILD & LEARN, Second Edition ... \$9.95. You start by assembling a circuit demonstrator that is then used to build and investigate a variety of useful circuits including oscillators, multivibrators, bistables and logic circuits.



PCP105—MAKE MONEY FROM HOME RECORDING ... \$10.00. Now that you've spent all that money on all that recording gear, wouldn't it be nice to get some of it back? Well here's the book that can show you how.



PCP106—SYNTHESIZERS FOR MUSICIANS ... \$10.00. All current popular forms of synthesis explained; LA, additive, phase distortion, FM and sampling. Get the sounds you want from your synth. Written especially for musicians.



MAIL TO: Electronic Technology Today, Inc.
P.O. Box 240
Massapequa Park, NY 11762-0240

SHIPPING CHARGES IN USA AND CANADA

\$0.01 to \$5.00	... \$1.50	\$30.01 to 40.00	.. \$5.50
\$5.01 to \$10.00	.. \$2.50	\$40.01 to 50.00	.. \$6.50
\$10.01 to 20.00	.. \$3.50	\$50.01 and above	.. \$8.00
\$20.01 to 30.00	.. \$4.50		

SORRY, No orders accepted outside of USA and Canada

Total price of merchandise \$	_____
Shipping (see chart) \$	_____
Subtotal \$	_____
Sales Tax (NYS only) \$	_____
Total Enclosed \$	_____

Name _____
Address _____
City _____ State _____ Zip _____

Those of you interested in building 1-chip Bitgrabbers will be happy to know that there is a whole family of 8-bit magnitude comparators. They include the active-low 74520, 74521, 74522, and 74689, and the active-high 74518, and 74519. (By the way, the 74688 is actually an active-low chip.)

So with all those chips out there, why did I use a more fragmented approach? Simple, it was hard for me to get those chips (even here in New York), so I designed the unit out of more commonly available stuff. A project won't be popular if people can't get the parts to build it.

By the way, I really prefer active-low outputs on TTL circuits. The reasons for that are pretty strong. First of all, active-low outputs can operate optocouplers. Optocouplers can operate DC loads, rectified AC, and full-wave AC loads. All you need is an optocoupler with the right output (transistor, SCR, or Triac driver, respectively).

Also by using an active-low output, you can interface the circuit with CMOS circuitry operating with a higher supply voltage. That's one reason why most outputs on TTL devices are active low.

By the way, the enable-input feature you mentioned is an excellent improvement. Some output ports actually hold one or two of the eight data lines high when idle. Your circuit removes the chance of falsely detecting that idle data.

BITGRABBER ADDITION

Here's a simple addition to the Bitgrabber circuit from your December 1990 issue (see Fig. 4). In order to increase the usability of the circuit, an LED-driving circuit is added to the output. The

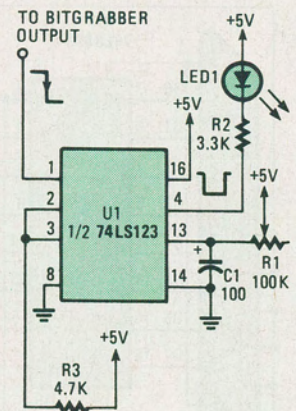


Fig. 4. A monostable can be added to the Bitgrabber for easy visual detection of pulses. The duration of the output pulse can be adjusted using R1.

circuit eliminates the need for hooking up a scope to the Bitgrabber's output and thus allows quick, portable use of the device.

In the circuit, the Bitgrabber's output drives half of a 74LS123 monostable multivibrator, which produces an output pulse with a duration long enough to illuminate LED1. The circuit is triggered by the falling edge of the Bitgrabber's output. The pulse width can be adjusted by varying R1. The values shown for R1 and C1 allow a maximum pulse duration of up to 4.5 seconds. When the desired character is detected, the LED will light for the duration of the pulse from the 74LS123.

If that character is detected again while the LED is still illuminated, the monostable is retriggered, prolonging the width of its output pulse. Thus, it is difficult to determine the exact number of occurrences of a particular character if the character is detected often (i.e., more frequently than the pulse width will allow). The circuit is, therefore, only useful for detecting an occurrence of a specific character.

—Brian Delsey, Hamilton, Ontario

You deserve a book for such a nice pulse stretcher.

RELAY DRIVER

I enjoy experimenting with transistors and other devices that allow you to control a high voltage with a low one. I built this circuit (see Fig. 5) awhile ago and forgot about it. I found it today and connected it to the Bitgrabber. The relay remains pulled in as long as the base of Q1 is held high. Diode D1 protects the circuit from the inductive kick-back produced by the coil of K1. Resistor R1 reduces the current flow out of the Bitgrabber and into the base of Q1. Hope this gets me a *Think Tank* book.

—Jon Caywood, Lynnwood, WA

Short and sweet. The reader should note that the printer port will have to output the selected character a couple of times to allow the relay (a pretty slow device) to deactivate.

Your interest in power control is well deserved; most of electronics is dedicated to that subject in one form or another.

MY OWN CURVE

At this point I'd like to throw in a twist of my own. By using SPDT center-off switches in place of the plain SPST units originally specified, you can set the

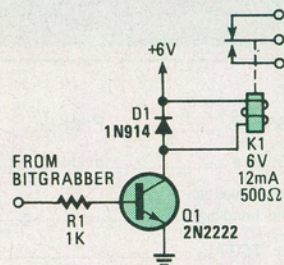


Fig. 5. A simple interface circuit can be made so that the Bitgrabber can operate powerful devices. Power control is one of the most important topics in electronics and its study accounts for most of the components we have today.

switches to a "don't-care" state, as well as to high and low. That will allow the unit to ignore the value of one or more of a character's bits if that bit is inconsequential.

Take a look at Fig. 6 to see how that is accomplished. In the figure, we only show the operation of one switch since they all function identically. As shown, the switch can be set in one of three positions: the "low" position, which ties an input of the XOR gate to ground; the "high" position, which allows the gate input to float high via a pull-up resistor; or the "don't care" position, which ties the gate input to its corre-

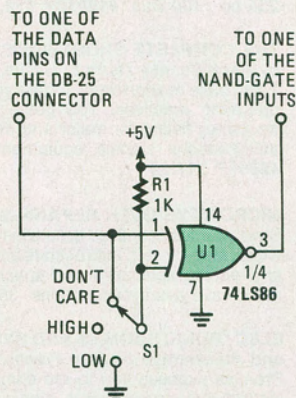


Fig. 6. The capability of the Bitgrabber can be greatly enhanced by using SPDT center-off switches. They allow the user to specify a "don't care" state for times when the value of a bit or two is unimportant.

sponding printer-port input, ensuring a match regardless of the port line's value. There is only one hitch to the modification: don't expect a Bitgrabber modified in this way to fit into a small case.

In the future, if you improve upon a project that you've seen in this magazine, let me know. If I get enough letters on a particular project, we can explore the possibilities together. Write to *Think Tank*, Popular Electronics, 500-B Bi-County Blvd., Farmingdale, NY 11735.

Protel Easytrax 2™

Outstanding value in Printed Circuit Board/CAD for your Macintosh and PC

Protel Easytrax 2 is a new, low-cost design package for PC and Macintosh users that includes everything required to produce professional quality Printed Circuit Board artwork.

Our easy-to-learn menu-driven design system breaks the "expert barrier" you'll be designing in minutes, not hours. Our comprehensive tutorials guide you through the program's extensive features that take the tedium out of board layout.

- Comprehensive library of Through-hole devices
- Gerber photoplotting and N/C drill tapes
- On-the-fly library components creation
- Intelligent Pad to Pad autorouting
- Switchable Metric/Imperial grid
- Auto-panning
- PostScript™ printing
- Powerful user-definable Macros
- Independent print/plot program
- Multi-layer boards of up to 32 X 32 inches.

At Protel, we offer free technical support, 24-hour BBS, and 30-day money back guarantee. Prices start at

\$450

Free Evaluation Package
Toll Free: 800-544-4186

Protel Technology, Inc.
50 Airport Parkway, San Jose, CA 95110
Tel: 408-437-7771 Fax: 408-437-4913



CIRCLE 7 ON FREE INFORMATION CARD

Enter A World Of Excitement with a Subscription to Popular Electronics®

Get the latest electronic technology and information monthly!

Now you can subscribe to the magazine that plugs you into the exciting world of electronics. With every issue of Popular Electronics you'll find a wide variety of electronics projects you can build and enjoy.

Popular Electronics brings you informative new product and literature listings, feature articles on test equipment and tools—all designed to keep you tuned in to the latest developments in electronics. So if you love to build fascinating electronics, just fill out the subscription form below to subscribe to Popular Electronics...It's a power-house of fun for the electronics enthusiast.

EXCITING MONTHLY FEATURES LIKE:

- CONSTRUCTION—Building projects from crystal sets to electronic roulette
- FEATURES—Educational training on digital electronics, Ohm's Law, Antennas, Communications, Antique Radio, Simplified Theory
- HANDS-ON-REPORTS—User test comments on new and unusual consumer products
- SPECIAL COLUMNS—Think Tank, Circuit Circus, Computer Bits, DX Listening, Antique Radio, Amateur, Scanner, Scene

PLUS: ALL OUR GREAT DEPARTMENTS!

You'll get 12 exciting and informative issues of Popular Electronics for only \$18.95. That's a savings of \$16.45 off the regular single copy price. Subscribe to Popular Electronics today! Just fill out the subscription order form below.



FOR FASTER SERVICE CALL TODAY
1-800-435-0715
(7:30AM-8:30PM)
EASTERN STANDARD TIME

Popular Electronics® SUBSCRIPTION ORDER FORM

P.O. Box 338, Mt. Morris IL, 61054

APEHI

YES! I want to subscribe to Popular Electronics for 1 Full Year (12 Issues) for only \$18.95. That's a savings of \$16.45 off the newsstand price.

Payment Enclosed Bill me later
Please charge my: Visa Mastercard

Acct. # | | | | | | | | | | | | | | | | | | | | | |

Signature

Exp. Date

PLEASE PRINT BELOW:

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Allow 6 to 8 weeks for delivery of first issue. U.S. Funds only. In Canada add \$5.00 Postage. All Other Foreign add \$12.50 Postage.

AUGUST 1991