



Programmable Logic Devices

ERNEST MEYER

The new reconfigurable logic devices revolutionize the design of logic systems

IF YOUR PROJECT DESIGNS USE 7400-SERIES discrete components for random-logic or state-machine control, you'll probably find that you can simplify both the design and the assembly by merely substituting Programmable Logic Devices (PLD's) for the 7400-series hardware.

Programmable logic devices contain gates and flip-flops, just like regular 7400-series IC's. However, in the 7400 series, which is often considered to be standard parts, the gates and flip-flops are wired together in fixed configurations. On the other hand, PLD's aren't hard-wired; instead, they contain small fuses that are blown or left open to connect their internal gates and flip-flops in any needed configuration.

A PLD's fuses are similar to those used in PROM's (Programmable Read-Only Memories), EPROM's (Erasable PROM's), and EEPROM's (Electrically Erasable PROM's). Usually, the fuse is blown by addressing the location and applying a high-volt-

age pulse (12–30 volts, depending on the device) across the fuse while the IC is in its *programming mode*. Most standard PROM programmers can be used to configure PLD's.

Erasable PLD's (like EPROM's and EEPROM's) can be wiped clean and reprogrammed—although the wiping is actually a way of bypassing the blown fuses. In that way, hobbyists can reuse a single PLD for a variety of projects or applications.

Circuit designers have traditionally used PLD's for logic functions that are not generally available in standard off-the-shelf components. If not for PLD's, a large number of conventional IC's would otherwise be required to perform a relatively simple non-standard logic task.

A lot for a little

Because they provide the circuit designer with an enormous array of user-programmable fuses, recent PLD designs can substitute for dozens of standard parts. Typically, a PLD can

replace about a half-dozen standard parts, although the exact number of required PLD's depends on the actual circuit. Without PLD's, the increased number of parts increases the size of the circuit board, which in turn lowers the system reliability while increasing the system's cost.

Because a single PLD replaces a variety of standard parts, manufacturers also prefer them to standard parts because inventory is minimized—the number of different IC's which must be stocked is sharply reduced. Also, the integration of discrete parts into a single device puts all the wiring inside an IC rather than on the circuit board, which means that the board's design is simpler and the logic can run faster.

Programmable logic is therefore an excellent choice in systems where board size, board complexity, system reliability, inventory considerations, or speed is important. Even if no single factor is crucial, their combined weight can easily swing the balance

toward a clean and simple PLD design rather than a large composite of standard parts.

Even so, as we will show, some standard parts are so complex they don't fit very well into a programmable logic architecture. To resolve the problem of complexity, there is now under development hybrid PLD's that contain many large standard-logic functions combined with a programmable logic array.

Since the proliferation of different logic architectures will inevitably bring PLD's into common use by both the hobbyist and the professional, we will look at the extraordinary development of complex reconfigurable PLD's, and examine their diverse capabilities.

Programmable logic technology

To understand how fuse technology works, we must look at the techniques used for fabricating integrated circuits. *Silicon processing*, as it is called, is very complicated; but a quick-and-dirty description will make it a little easier to understand.

To make a silicon-based chip, wafers of silicon crystal are first processed to make transistors. The silicon crystal itself does not really conduct electricity at all. The transistors are created by doping selected regions of the silicon with phosphorus or arsenic, and metal lines deposited on the wafer connect the transistor sites. The transistors and metal lines are called features.

Simply speaking, each feature is formed on the crystal at the selected locations by spraying a light-sensitive protective chemical, called *photoresist*, in a thin, even coating on the wafer's surface. The wafer is then bombarded with light at selected locations through a precise slide projector. The slide projector (called an *optical aligner*) uses a very small slide, called a *mask*, to screen out the light where it isn't wanted. The chemical decays where the light strikes the photoresist-covered wafer, and is simply washed off, leaving bare silicon at selected locations.

The precision of the optical aligner determines how fine a feature can be made. In the early 1970's, it was difficult to make transistors smaller than 10 microns. Now, transistors can be less than a micron in size, meaning the same-size chip can hold more than 100 times as many transistors. More-

 


FIG. 1—THE METAL LAYERS on two-level chips are insulated by a layer of SiO₂ (a). The first programmable IC (b) provided 64 cross-points (fuses).

over, as features get smaller, the transistors are packed more densely; hence, the devices can work faster.

The bared silicon can be treated in various ways. For example, the silicon can also be treated to recast the crystalline structure into an amorphous form called *polysilicon*, which conducts electricity and therefore can be used to form wires. Single-level metal chips use polysilicon wires to cross under the metal wires at intersection points. However, polysilicon conducts electricity over a hundred times worse than metal, which substantially degrades performance.

The wafer is heated after the application of each wiring level, which causes the silicon on the surface to oxidize. Since the resultant SiO₂ is more bulky than crystalline silicon, the oxide *blooms* over any raised features (such as previously deposited metal lines) during oxidization. Since SiO₂ does not conduct electricity, it forms an insulating sheet a few microns thick over the entire wafer surface. The oxide can again be selectively etched: Photoresist is again applied to the wafer, selectively etched away again, and the wafer is exposed to chemicals that attack the SiO₂ (but not the pure Silicon) at the chosen feature locations. Further

layers can be grown on top of the resultant *planarized* wafer to form a sandwich-like structure, with SiO₂ as the "bread," and metal or doped silicon as the "meat."

Several levels

The transistors on the chip are wired together with deposited strips or spots. The various layers are connected by holes (called *contacts*) through the SiO₂ layers. Although up to three levels of metal can be used, the metallization process is expensive, and so IC's are mostly made with two, or even only one, metal level. A cross section of a chip with two-level metal construction is shown in Fig. 1-a.

To make the first fuse-programmable chip, as shown in Fig. 1-b, eight 12-micron wide horizontal lines were deposited in first-level metal over the bare silicon substrate. The wafer was then heated up to cover the metal with the insulating SiO₂. After applying photoresist, sixty four very small holes (five microns in diameter) were etched into the insulator in eight rows over the first-level metal. The contacts could be much smaller than the first-level metal because they just needed to touch the edge of the metal line to provide a conducting path. (Small contacts were necessary for programmable technology, but such contacts greatly reduced the reliability of the device.)

Next, photoresist was applied again to the wafer, and aluminum was deposited in the holes (or *contacts*). Another eight metal lines were deposited in second-level metal, but those were stacked in the vertical direction, crossing over first-level metal at each contact site. The final product was therefore an 8 × 8 grid having a very small aluminum contact between each metal-1/metal-2 crosspoint.

Although the contacts—called *fuses*—are made as wide as the wires in standard silicon chips, they are narrower than the wires in programmable logic chips. The interconnecting aluminum is burned away (blown) by applying a very large current across the fuse connection. At lower voltage levels, the fuses that have not been burnt away conduct normally. That is why the metal lines were made so wide and the contacts so small—they had to be made larger than the contacts so that the contacts and not the metal lines would burn away.

Early PLD's

The earliest programmable chip is the one shown in Fig. 1-b; it contained nothing more than a fuse matrix and a wire grid. The crosses represent fuses that can be blown or left open.

The PLD pioneers were quick to stack transistors around the metal grid to make true *programmable devices*. Also, nichrome (nickel-chromium) fuses were used instead of contacts. In that kind of programmable technology, regular contacts are run from the lower metal to the upper metal layer; those contacts miss the actual wire intersection point by 3 microns. A 3-micron strip of nichrome compound is then deposited laterally to connect the contact site to the second-level metal strip. Because of its lower melting point, nichrome fuses out more cleanly than aluminum; in fact, the nichrome actually vaporizes during fuse programming. Therefore, a lower programming voltage is needed, which means that less power needs to be put into the chip. That simplifies programming while making the devices more reliable. Also, the metal lines are not much wider than the fuses themselves, which allows a greater density.

The PROM

The earliest fuse-programmable device was the PROM. As shown in Fig. 2, PROM input logic (the AND plane) is fixed, while the output logic (the OR plane) is programmable. The upper non-fused fixed-wire matrix feeds a set of AND gates. In the fixed AND array, the output of any one column is high only if all the connected inputs to the column are high. In PROM's, the fixed AND array provides one and only one high output for each possible condition that can exist on the inputs. The non-fused matrix is called a *fixed AND plane*.

The lower matrix is fuse-programmable. Simply speaking, each of the wiring rows feeds into a single enormous OR gate. That description is a simplification, of course, but it is adequate for our purpose.

TABLE 1

IN ₁	IN ₀	OUT ₂	OUT ₁	OUT ₀
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

 


FIG. 2—IN THE EARLIEST FUSE-PROGRAMMABLE device, the AND plane was fixed; only the OR plane was programmed.

The OR gate is set so that the output is high if any connected input to the fuse row is high, a configuration that is called a *programmable OR plane*. If the only fuses left connected in Fig. 2 are those indicated by a circled-X, the ones and zeros in Table 1 con-

stitute a truth table for a PROM programmed (blown) with the fuse pattern shown in Fig. 2

Conventionally, PROM's are regarded as programmable memories; however, the devices can obviously be used for logic as well. For example, logic equations can be written for the above device as follows:

$$\begin{aligned} \text{OUT}_0 &= \text{IN}_0 \text{ and NOT-}\text{IN}_1 \\ \text{OUT}_1 &= \text{NOT-}\text{IN}_0 \text{ and IN}_1 \\ \text{OUT}_2 &= (\text{NOT-}\text{IN}_0 \text{ and NOT-}\text{IN}_1) \text{ OR} \\ &(\text{IN}_0 \text{ and IN}_1) \end{aligned}$$

Obviously, OUT₂ is a genuine XOR (exclusive-OR) of IN₀ and IN₁. That may seem like a very clumsy way of making a simple gate, but by expanding the size of the array very complex logic terms can be created. In particular, that kind of architecture is very good for bus-decoding functions. For example, if an 8-bit-wide bus must be decoded in six different ways to provide six enable signals in a

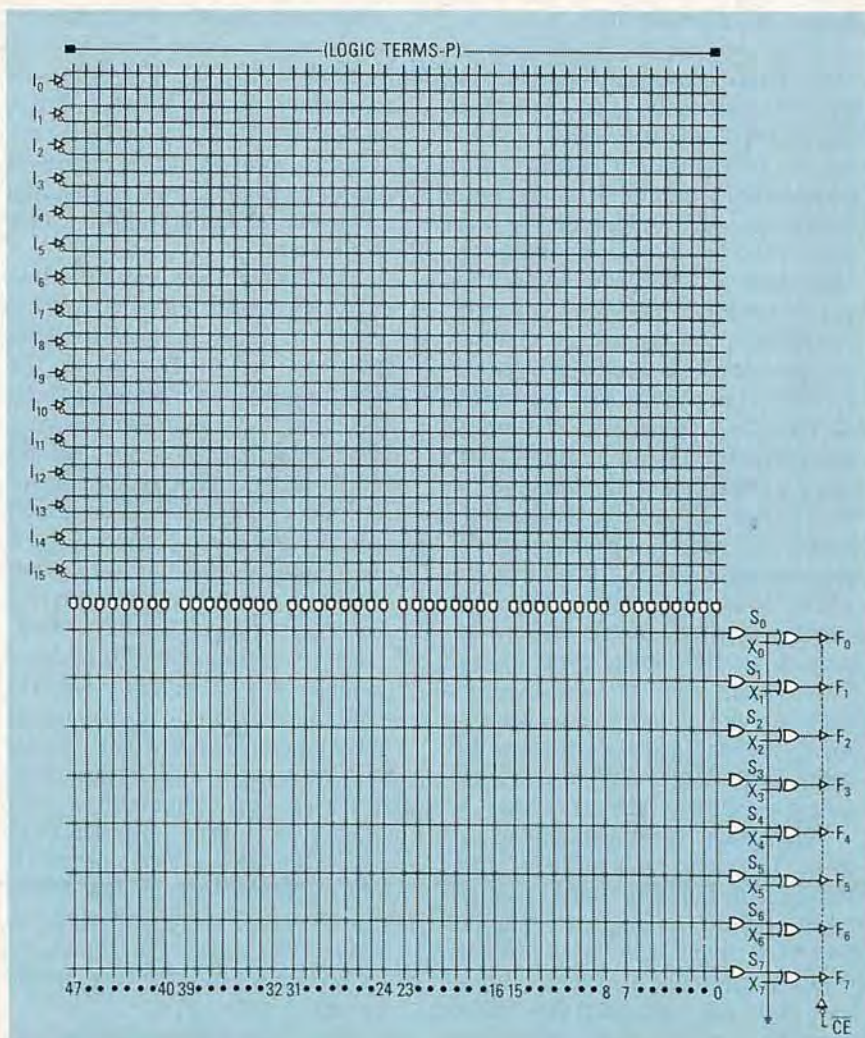


FIG. 3—THE FIRST COMMERCIALY AVAILABLE FPLA was a single-level device having approximately 2,000 fuses.

 


FIG. 4—IT'S EASY TO IMPLEMENT COMPLEX logic functions in an FPLA. As shown, the functions previously described for a PROM can also be mapped directly into an FPLA's architecture.

complex digital system (like a computer), one 16-pin device can replace at least a half-dozen IC's.

Since each possible input combination has a corresponding unique input to the fuse array, the fixed AND array in the above device is termed a *full decoder*. Of course, decoders can be constructed from simple logic gates in many ways, but we have depicted the logic structure in an array fashion to show how the AND gates themselves can be made part of an array structure.

PROM's are useful as memory components. When used as a memory, each input combination (on the left of Table 1) is considered an address. Similarly, the output resulting from any particular input combination (on the right of Table 1) is considered the data at that address. In that way, fuse-programmable ROM's provide the designer with a fast, static, long-term storage medium for fixed-data applications. However, even though PROM's are ideal for fixed memory, and even though they can be used for logic, they are not very efficient because they always contain a full decoder, which isn't always needed.

The full decoder increases the size of the fuse array, which restricts the number of possible input connections. To understand that, consider how two signals have four fully-decoded conditions, and three signals have eight fully-decoded conditions. Since every input is fully decoded in a PROM, each additional input doubles the number of fuses required. In a

PROM, the total fuse-array size is therefore:

$$2^I \times O$$

where I is the number of inputs and O is the number of outputs. However, for logic functions, not every input combination is crucial; therefore, a simpler and more compact approach is to make both the OR and the AND planes programmable.

Exploring PLA's

IBM, using an architecture called PLA (for Programmable Logic Array), was the first company to use a device having both programmable OR and programmable AND planes. In the earliest PLA's, the array was metal-programmed rather than fuse-programmed. In other words, the device was customized during the actual chip fabrication rather than by the chip user, and was therefore used only by manufacturers needing a large quantity of chips.

Signetics was the first company to manufacture *Fuse-Programmable Logic Arrays* (FPLA's), which have fuses both in the OR and the AND planes. The first commercially available FPLA, the 82S100 (Fig. 3), was introduced in 1977; it is a single-level metal device having approximately 2,000 fuses.

At the same time, a similar fusing technique was also applied to PROM design, resulting in a rapid movement from 256-bit to 2K-bit PROM's. Also, single-level metal technology was used, with polysilicon for the lower interconnection level and metal for the upper interconnection level. As mentioned earlier, that technique reduces chip cost. In fact, to further reduce chip cost, some vendors now use fuses made of polysilicon rather than nichrome.

Because there is no full binary decoding, each additional input added to an FPLA structure does not double the required number of fuses. Instead, the fuse array is increased in size by an amount directly proportional to the number of vertical channels (which are called *logic terms* or *product terms*). Note, however, that because both non-inverted and inverted signals are provided for each input, there are two inputs into the fuse array for each pin input.

Each product term added to an array allows one additional set of AND products to affect an output con-

dition. Therefore, in the 82S100, there are 48 possible unique AND products that can affect the output. Since the AND-products can be combined together in the OR plane, more than 48 unique input combinations can affect the output. Therefore, three numbers are used when measuring the size of an FPLA: the number of inputs, the number of product terms, and the number of outputs. Those numbers are combined to form the *IPO number*. To calculate the total number of fuses, the number of inputs is doubled (to provide noninverted and inverted inputs to the array), added to the number of outputs, and multiplied by the number of product terms, or:

$$((2 \times I) + O) \times P$$

For the 82S100, the IPO is 16:48:8. The total number of fuses is therefore $((16 \times 2) + 8) \times 48$, or 1,920. By contrast, a PROM having 16 inputs and 8 outputs, like the 82S100, would require $2^{16} \times 8$, or 52,488 fuses—more than 25 more.

The smaller size of the FPLA architecture yields four advantages to the logic designer: 1) The array size is smaller, which makes the devices less expensive to manufacture and therefore less expensive to sell; 2) The smaller number of fuses makes programming faster; 3) The reduced array size makes the devices quicker to test; 4) The smaller size of the array makes it possible to make larger programmable devices, which increases their usefulness and power.

Additional features

Architectural enhancements increase the flexibility of the device even farther. The Signetics 82S100 FPLA, for example, adds two additional programmable features to the basic AND/OR plane.

First, the FPLA can be permanently set to give inverted or non-inverted outputs. To achieve the complementary output, the outputs of the programmable OR plane feed into one input of an additional XOR gate. The other input to the XOR gate can be connected to ground. If the grounding fuse is left intact, the XOR gate inverts the output from the OR plane. If the fuse is blown, the input floats high, and the logic signal passes through the gate unaffected. Table 2 shows a truth table for the complementary-output feature.

TABLE 2

Output from array inverting fuse		Output from IC
0	0	0
1	0	1
0	X	1
1	X	0

The second feature, three-stated output, is not programmable but greatly improves the IC's usability. If many fuses are left intact in the programmable array, the increased loading slows the device's switching speed. Conversely, if there is a product term with only one or two intact fuses, the output switches much more quickly. As array size increases, the difference in switching speed between the least- and most-loaded gates can produce glitches in the IC's output. Erroneous logic states can be avoided by disabling the outputs until all the signals have settled.

Using an FPLA

It is easy to implement complex logic functions in an FPLA. For example, the functions previously described for a PROM can also be mapped into an FPLA's architecture. The connections required to do that are shown in Fig. 4.

Four fuse columns were necessary for a PROM, but note from Fig. 4 that the FPLA architecture and complementary output permits only two product terms to be used for the three functions, freeing the other inputs, outputs, and product terms for other logic operations.

Logic minimization

In Fig. 4, it is relatively easy to work out the connections to use. However, as logic complexity increases, it becomes more difficult to work out which fuse combinations use the product terms most efficiently. When large numbers of logic signals interact, the product-term columns can be tied to different combinations of inputs, and OR-ed together in respectively different ways to generate the same functions. Finding the optimal fuse map through *logic minimization* (the act of reducing logic equations to their most basic form) has two advantages: 1) The danger of running out of product terms is minimized; 2) The number of unblown fuses is minimized, which increases the speed and reliability of the device.

About the time when new software tools were developed to optimize fuse maps, a new development brought about a revolution in programmable-logic philosophy.

The PAL

The revolution in programmable logic was the 82S100 PAL (*Programmable Array Logic*). PAL's were marketed by Monolithic Memories as a simple alternative to standard parts—the emphasis being on *simple*. To that end, they supplied an easy-to-use programming language called PALASM, a FORTRAN IV program that translates logic equations into a fuse map suitable for use with a standard PROM programmer. At about the time that PAL's were released into the marketplace, 512×4 -bit (2048-bit) PROM programmers were also interfaced with IBM computers, making it possible for designers to design, document, and program a simple PAL within minutes.

PALASM accepts six distinct data entries as input. First, the PAL part number is entered so that the program knows what sort of fuse map to make. Second, the pattern number is entered, so that the generated file containing a fuse map can be named. Third, the name of the device and the author's name is entered for archiving (so when someone else looks at the file, they know who made it and what it's for). Fourth, a pin list is entered, which contains the symbolic names for the pins that are used in the equations. The symbolic names can be numbers, or signal names like INIT, RESET, NMI, etc. Fifth, the actual equations are entered. A field is left open for the designer to enter notes about the design.

PALASM removes the designer from the world of fuse maps and architectures. However, to use PAL's most efficiently, it is important to choose an architecture that maps on to the type of logic you want to have. Also, PALASM allows designers to generate fuse maps (now often called *JEDEC maps*) directly. But sometimes it is actually easier to type in a fuse map than the equations. Indeed, depending on the needed functions, sometimes it is easier to draw a truth table or a state diagram.

From the architectural point of view, PAL's are easier to use than PLA's because they don't have a programmable OR plane at all: in its place they have a programmable AND plane instead, making them the opposite of PROM's. However, as we'll see very shortly, additional architectural features make PAL's just as flexible to use as FPLD's. As shown in Fig. 5, a

 


FIG. 5—PLA'S DON'T HAVE A PROGRAMMABLE OR plane at all; they have a programmable AND plane instead, making them the opposite of PROM's.

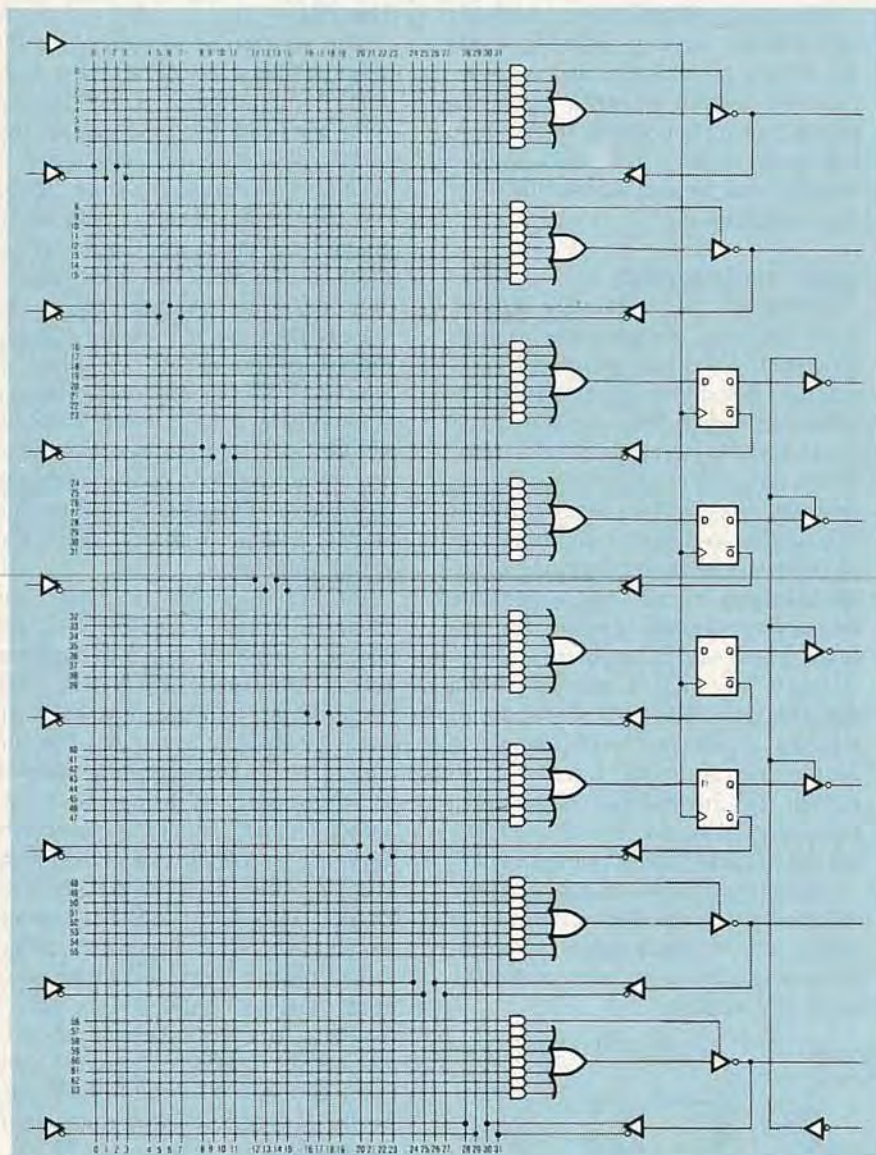


FIG. 6—THE COMMON PAL16R4 provides fuse-programmable three-stated outputs and four flip-flops.

PAL's inputs feed directly into the AND matrix.

Figure 5 also shows a new range of functions, called *macros*, at the output of the AND plane. In 1978, programmable logic components came to differ not only in their IPO ratios, but also in their macros, so that picking the best device for a particular application often hinged on choosing the one with the macros that incorporated the needed logic functions for that application.

In the top macro, the AND plane feeds a single AND gate with optional fuse-programmed inversion. That is a very simple macro; and because the inputs to the array are all inverted, we find that the output inversion is not needed at all.

The second macro down incorpo-

rates a very useful feature: the output of the AND gate is fed back into the programmable AND plane, permitting the output of the AND function to be used again in the array without feeding the output back around to the outside of the device into another input. Using a macro's outputs as inputs to other macros allows the chip to contain *multi-level* logic—which is to say, the signal can pass through a series of gates. By judicious manipulation of the logic equations, it is possible for an ingenious logic designer to put just about any digital function in a PAL architecture; we shall show you exactly how that's done in the next part of this series.

In the bottom macro, the output driver is replaced by a bidirectional driver consisting of dual fuses. De-

pending on how the fuses are blown, the macro can be configured as an output or as an input. If the output of the AND gate is broken, but the feedback path and the input driver are left intact, a signal can pass through the input driver and feedback path—however, the AND macro function then cannot be used at that location. On the other hand, if the output of the AND gate is broken and the input driver is taken out of the circuit, the AND macro functions normally, and the AND gate function is available for multi-level logic.

It should be obvious that there are a large number of possible macro constructions for combinational logic. However, that is just the beginning. Incorporating sequential logic elements in a PAL opens whole new dimensions of design. In Fig. 6 we see the architecture of the common



WHILE PAL's won't really relegate other technologies to the scrap heap, they do offer the designer another usable and useful alternative.

PAL16R4, which provides fuse-programmable three-stated outputs and four flip-flops.

That's all we have room for this month. In the next part of this series we will start off by seeing how *macrocells* containing flip-flops can be used for counters, for complex pattern generators, and even for state machines.

After that, we will also explore a number of more recent technologies, such as erasable and reprogrammable devices, universal programming systems, and advanced programmable-logic architectures; and to demonstrate the feasibility of the technology being used, we will show you how to actually program a programmable-logic device with commercially-available software.

R-E