

wireless world circard

Set 14: Digital counters

This set was the first in the revised format for Circards. But for this book, we re-set the first three cards so that they would conform to the rest. The four-column presentation allows greater flexibility of layout and we hope you agree that the "unjustified" type-setting makes for greater readability, with its equal word-spacing and jagged right-hand edge. We took this opportunity to up-date the title area and to rename "series" with the more logical "set".

Another excellent summary of the subject precedes this set of circuits. It covers all the essential points about the use of bistable circuits as counters, starting by setting out the different kinds (JK, RS, D and T, discussed in more detail on glossary card 12), defining ripple and parallel counters, design using Karnaugh maps, and concluding with sequence generators. In digital parlance notice that bistable circuits are referred to as flip-flops, whereas originally this term referred to monostable circuits, the words flip and flop indicating an unstable state and a stable state. (Anyone for flip-flip for astables and flop-flop for bistables?) Content of the cards calls for little comment. Card 12 is useful for newcomers, listing various binary codes against decimal number, and in describing the different kinds of "flip-flops". It also shows connections for RS and JK types to give D and T functions.

Basic binary counters	1
One out of n ring counter	2
Johnson counters	3
Reversible counters—I	4
Reversible counters—II	5
Divide by n counters	6
High-power counters	7
High-speed counters	8
Low-power counters	9
Decade counters	10
M-sequence generators	11
Glossary: flip-flops and b.c.d. codes	12

An introduction to digital counters

A digital counter comprises an interconnection of bistable or two-state memory circuits or, colloquially, flip-flops. The counter embraces those circuits which accumulate pulses according to a specific code as they appear at the input, frequency dividers, sequence generators and pulse waveform generators. The application requirement will generally determine how the collection of flip-flops is identified, but in this article the generic name of counter will be used.

The basic flip-flop has one or two control inputs, and two outputs termed Q and \bar{Q} (not $-Q$), where \bar{Q} represents the opposite state of Q . The logic state of these outputs may be termed set or reset, high or low, 1 or 0, and the change of state may occur on 0 to 1 or 1 to 0 transitions at the input, depending on the type used. The varieties of flip-flops used in counters are normally described by the control inputs and are termed D-type, T-type, RS and JK. The triggering input, called the clock-pulse input, ensures that a change of state will only take place on the occurrence of a pulse at the clock-input. Other facilities that may be available are preset and clear inputs which allow a flip-flop to be set ($Q = 1$) or reset ($Q = 0$), independently of the control inputs. Typical symbols for these flip-flops are shown in Fig. 1. Other variations include operation by positive or negative logic,

triggering on positive or negative pulse edges or a combination of these as in master-slave flip-flops.

A basic RS flip-flop using NAND gates is shown in Fig. 2. To represent the dependence of the Q output on the control inputs when a clock pulse occurs, a truth-table is used to demonstrate the state of Q at the n th clock pulse (Q_n), and after the next clock pulse (Q_{n+1})—Fig. 3. For example, if S and R are both at logic zero when a clock pulse occurs, the output Q will not change state, but remain as it was before the clock pulse. However, if $S = 1$, $R = 0$, then Q becomes logic 1, i.e. if it was previously logic 0 a change of state occurs, and if it was logic 1, it remains so.

The indeterminate state of Q for the condition that $R = S = 1$ exists because of a race condition between gates and is one disadvantage of this flip-flop—such a condition must be avoided. The JK flip-flop, however, does not have this disadvantage—all output conditions are predictable, as shown in Fig. 4. The last combination of $J = K = 1$ permits a useful toggle action in which the output changes state on the occurrence of every clock pulse.

Counters are generally classified as asynchronous or synchronous. The basic asynchronous circuit is implemented with cascaded toggle flip-flops, where the output of a previous flip-flop is the clock-

input for the next in sequence. Alternatively, the drive inputs may come from Boolean combinations of other outputs. In either case, a disadvantage is that each flip-flop changes state at a different time in a sequence. For each flip-flop a propagation delay exists between the occurrence of a trigger pulse and the next state of the output, and this delay “ripples-through” the counter. This restricts the maximum operational speed of the counter, since the maximum ripple-through delay must be less than the time between input pulses.

In integrated circuit technology, these counters have the advantage that each flip-flop operates at half the frequency of the preceding one. This allows a trade-off in high-speed (high-power dissipation) circuits to be used in the first stage, with lower speed (low-power) configurations being used in later stages. The maximum count (including zero) of a counter containing n flip-flops is 2^n , feedforward or feedback techniques allowing counts less than this to be achieved. The number of distinguishable states through which the counter cycles is known as the modulus of the counter, and this may be fixed when implemented with individual flip-flops, but some m.s.i. packages are available that permit variation of the modulus by a simple connection change or simple gating. If the outputs of ripple-counters are to be

 


Fig. 1. Four basic types of flip-flop.

 


Fig. 2. Nand-gate RS flip-flop.

S	R	Q_{n+1}
0	0	Q_n
1	0	1
0	1	0
1	1	undefined

Fig. 3. Truth table for Fig. 2.

J	K	Q_{n+1}
0	0	Q_n
1	0	1
0	1	0
1	1	\bar{Q}_n

Fig. 4. Truth table for JK flip-flop.

decoded, care must be taken to ensure that the decoder network is enabled only when it is certain that all intermediate state changes have occurred.

The disadvantage of the asynchronous counter is avoided by the synchronous or parallel counter, in which all flip-flops change state in synchronism with a common clock-pulse. The speed of operation is limited by one flip-flop delay and that of any gating necessary, and these will depend on the type of hardware being used, e.g. c.m.o.s., t.t.l., e.c.l. Recent Schottky synchronous counter packages have internal circuitry which eliminates all external gating, and counting speeds up to 70MHz are claimed, and e.c.l. packages are available for speeds up to 110MHz.

Any sequence may be generated using individual JK flip-flops and associated gating. The design is more complicated than the asynchronous types, but one technique simplifies the design problem using Karnaugh maps.¹

The map is a two-dimensional representation of all possible combinations of a number of variables, where each square is one unique combination and adjacent squares are identical except for one variable. The rows and columns are arranged in accordance with the Gray code representation of decimal numbers, in which only one bit changes as we progress through adjacent numbers (Fig. 5). A Karnaugh map for four variables, A, B, C and D, is shown in Fig. 6, where a 1 in a square means the existence of logical "ANDed" variables, identified by the row and column common to that square.

The 1 squares are connected by the logical OR function, and the Boolean expression represented by Fig. 6 is $F = \bar{A}.B.C.D + A.B.C.D + \bar{A}.B.C.D + A.B.C.D$. A 0 in a square indicates that this particular combination does not exist. The advantage of the map is that minimization of the Boolean expression is simplified by being able to group adjacent squares in pairs, fours, etc. Two squares can be combined to eliminate one variable, and these two squares can be combined with another two adjacent squares to eliminate one more variable. The four squares may be looped as shown, because of their adjacency, thus A and C become redundant as both states of each are included in these squares reducing the function to $F = B.D$. This can be confirmed by a Boolean minimization. Note that adjacency of squares exists at the extreme ends of horizontal rows, and at the extreme ends of vertical columns.

A design of a modulo-6 Johnson counter is considered as an example of the technique. The maximum modulus of an m -stage Johnson counter is $2m$, hence a minimum of three flip-flops is required. It is assumed that the outputs are taken from the Q output of the flip-flops designated A, B and C, and the map is used to minimize the gating necessary to obtain the prescribed sequence Fig. 8. As all possible combinations of the

variables are not used, the "can't happen" or redundant states are denoted by a combination of one and zero (⊙) in the state table (Fig. 9) because the states are not specified and may be made 1 or 0 at will. In this case they will be considered as 1s. The state table shows the desired outputs at A, B and C on the occurrence of the numbered clock pulse, where 0 and 6 are equivalent, i.e. the 6th pulse resets the counter to zero. It will be assumed that the counter commences from the zero state.

The design technique requires the pre-

paration of a Karnaugh map for the J and K input of each flip-flop to determine the control levels required at each input for every step of the sequence, by deriving a minimal Boolean expression for each map, though as these are derived independently the circuit may not necessarily be minimal. This then determines the internal gating required.

An excitation table for the JK flip-flop is derived from the JK truth-table shown earlier. This table (Fig. 7) shows the necessary J and K inputs to either hold the flip-flop in a 1 condition or a 0 con-

DECIMAL	GRAY-CODE			
	A	B	C	D
0	0	0	0	0
1	0	0	0	1
2	0	0	1	1
3	0	0	1	0
4	0	1	1	0
5	0	1	1	1
6	0	1	0	1
7	0	1	0	0

Fig. 5. Gray code for decimal numbers.

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0 0				
0 1		1	1	
1 1		1	1	
1 0				

Fig. 6. Karnaugh map for four variables.

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0	1	⊙	X	X
1	0	0	X	⊙

$$J_A = \bar{C}$$

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0	X	⊙	0	0
1	X	X	1	⊙

$$K_A = C$$

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0	0	⊙	X	1
1	0	X	X	⊙

$$J_B = A$$

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0	X	⊙	0	X
1	X	1	0	⊙

$$K_B = \bar{A}$$

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0	0	⊙	1	0
1	X	X	X	⊙

$$J_C = B$$

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0	X	⊙	X	X
1	1	0	0	⊙

$$K_C = \bar{B}$$

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Fig. 7. Excitation table for JK flip-flop.

C	B	A	input pulse no.1
0	0	0	0
0	0	1	1
0	1	1	2
1	1	1	3
1	1	0	4
1	0	0	5
0	0	0	6

Fig. 8. Johnson counter sequence.

C D	A 0	0 1	1 1	
	B 0	1 1	1 0	
0	0	⊙	2	1
1	5	4	3	⊙

Fig. 9. State table for Fig. 8.

dition, or to cause a 1 to 0 or 0 to 1 transition, all on the occurrence of an input clock-pulse. The X indicates that it does not matter what that particular J or K state is, provided the other control input is in the correct state.

For example, if it is assumed that $Q = 1$, and a transition to logic 0 is required on the occurrence of a clock-pulse, then from the truth-table either $J = 0, K = 1$, or $J = 1, K = 1$ will cause this change, i.e. provided $K = 1$, J may be either 0 or 1. As each input pulse occurs, the flip-flops should change in accordance with the truth-table of Fig. 8. The steps involved in filling the JK maps are as follows.

The can't-happen conditions of the state-table are transferred to equivalent squares on the separate J and K maps. Consider the J_A and K_A maps. On the occurrence of the first pulse, Q_A should hold at logic 1, hence an X is put in the J_A map square representing pulse no. 1, and a 0 in the K_A map square. This is repeated for pulse no. 2. At pulse no. 3 a 1 to 0 transition is required, hence an X is put in J_A map square for pulse no. 3, and a 1 in K_A map. A 0 is maintained for pulse no. 4, hence a 0 in J_A and X in the K_A square for pulse no. 4 is necessary. This is continued until all squares for each map are filled.

As an example of the minimization, notice that symbols 0 or X may be 1, hence a loop of four adjacent squares is available in the J_A map, i.e. the minimal solution for J_A is given by C. Similar loops of four are obtained for each of the other maps, the circuit being implemented in Fig. 11. No external gates are required in this circuit, because the complemented

outputs are already available from each flip-flop.

Common arrangements using this technique are b.c.d. counters, decade counters, up-down counters, though some are also available in m.s.i. packages.

The implementation of Fig. 11 has been described as a modulo-6 Johnson ring counter. However, examination of Fig. 8 shows that each output Q_A, Q_B and Q_C has one pulse for every six of the input so that the device could be regarded as a divide-by-six frequency divider. Most frequency dividers, on the other hand, allow one to divide by an arbitrary number so it cannot be regarded as a very good frequency divider.

The device of Fig. 11 can also be regarded as a sequence generator, in that, given an input pulse sequence, one obtains a different output pulse sequence—admittedly not a very interesting one.

There is an infinite number of sequence generators that one could build but of particular interest are those which produce so-called maximal length binary sequences (M-sequences). Used in many areas, such as data communication system identification and correlation methods, M-sequences are generated by synchronous shift registers with feedback from various stages being used to determine the next state to be fed in. Feedback complexity is not proportional to the register length and very long sequences can be generated by very simple feedback arrangements. Feedback is performed by modulo-2 addition, i.e. via exclusive-OR gates (Fig. 12).

The properties of these sequences depend on the clock rate, f_c , and on the number of stages in the shift register, n , but all of

the sequences possess to some degree properties close to those of band-limited white noise. (Hence the name pseudo-random binary sequences or p.r.b.s.) The signal bandwidth is given approximately by $f_c/3$ and the greater the value of n the more closely do the properties resemble those of random noise. The sequences are not in fact random because they are binary in nature and because they are cyclic, the cycle length being $2^n - 1$ clock periods. The binary nature of the signals is easily removed by passing them through simple first- or second-order filters so that the signal becomes continuous and has a probability density function which is close to Gaussian. The cyclic nature of the signal is in fact one of the advantages of M-sequence and is one of the non-random features one would wish to retain. This is because experiments can be repeated for checking purposes over a cycle length without the statistical difficulties of genuine random noise. From this point of view it is therefore desirable to limit n .

Design is greatly facilitated by tables which indicate what feedback paths are necessary to produce an M-sequence of given length.² The problem comes down to one of choice of f_c and of n for the particular application in mind.

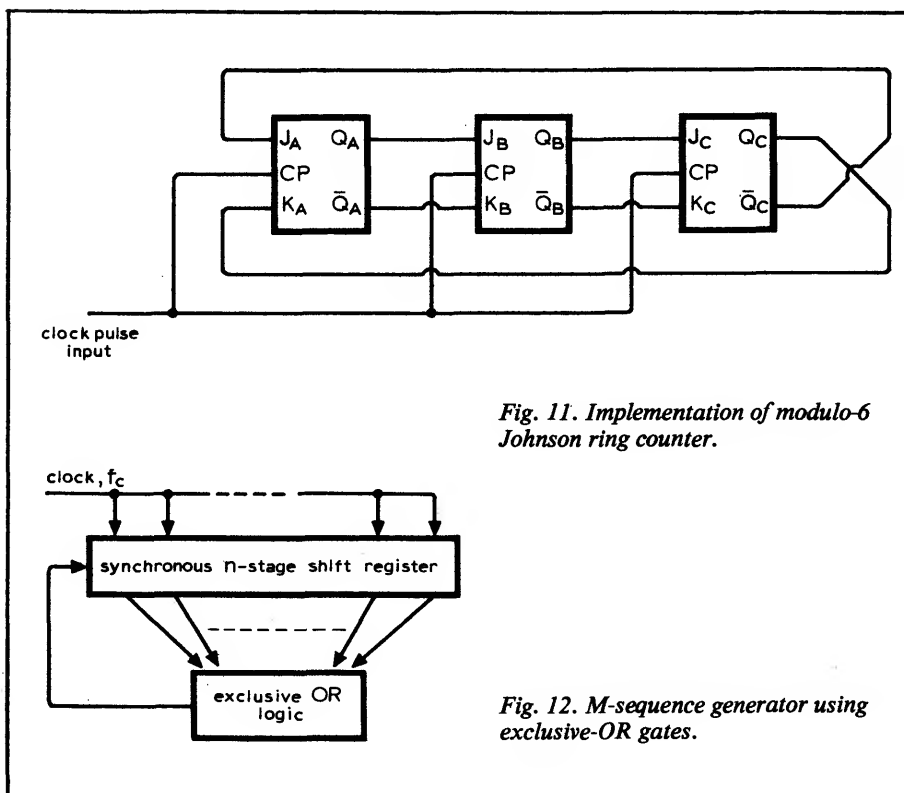


Fig. 11. Implementation of modulo-6 Johnson ring counter.


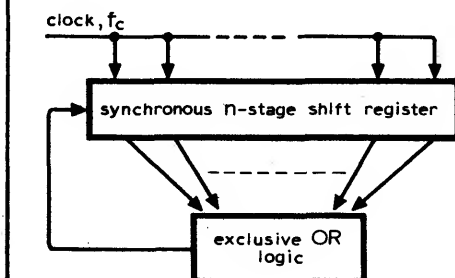


Fig. 12. M-sequence generator using exclusive-OR gates.

Basic binary counters

 

Circuit operation

The bistable circuit is a T-type "flip-flop" in which the output changes state for a negative-going transition at the trigger-input. If the base-drive current is arranged so that Tr_2 is in saturation, its collector voltage will be about 0.2V. This is too low to forward-bias the base-emitter junction of Tr_1 , about 0.7V, and hence Tr_1 will be off. This means its collector-emitter voltage is high, depending on R_1 and R_3 , and the base-drive current for Tr_2 flows through R_1 and R_3 . Hence the terminals identified (arbitrarily) as Q and \bar{Q} are low and high respectively (0 and 1 for binary coding).

When the trigger input is high, the circuit is in a stable state. When the trigger input is driven near ground the negative-going pulse-edge is steered to Tr_2 base as D_2 is forward-biased. The anode of D_1 is approximately at $V_{CE(sat)}$ and because its cathode is connected to a high potential via R_5 it is reverse-biased. Therefore Tr_2 collector current is reduced, causing a rise in its collector voltage, increasing base-drive current to Tr_1 . This causes Tr_1 collector voltage to drop and Tr_2 base current decreases causing a further increase in Tr_2 collector voltage. The process continues until the other stable state, Tr_1 conducting and Tr_2 off, is sustained. The next negative-going trigger pulse resets the

circuit to its previous state. It produces one output pulse for every two trigger pulses. The interconnection of these bistable circuits to give a binary ripple counter demands that the Q output of a previous flip-flop is connected to the trigger (or T-) input of the next flip-flop. This gives a natural count of 2^n where n is the number of stages, and 2^n is the number of states through which the counter progresses.

Circuit modification

Range of R_5, R_6 : 4.7k to 47k Ω
Frequency variation: 150 to 30kHz
Range of C_1, C_2 : 330 to 3300pF
Frequency variation: 140 to 90kHz
Increase turn-on speed with capacitors across resistors R_3 and R_4 typically 5 to 20% of C_1, C_2 .
Increased frequency of operation possible with additional diodes connected across R_5, R_6 (anode to collector).
High-speed transistors BSX19, BSX20 permit counting speeds up to 10MHz.

IC binary counter

The ripple binary counter is commonly implemented with integrated circuits using J-K flip-flops e.g. the SN7493 is a 4-bit binary counter within one package allowing a typical count rate up to 18MHz for d.c. supply +5V, and a typical

Typical data

Single bistable

 V_{CC} : +12V Tr_1, Tr_2 : BC108 R_1, R_2 : 3.3k Ω $\pm 10\%$ R_3, R_4 : 8.2k Ω $\pm 10\%$ R_5, R_6 : 6.8k Ω $\pm 10\%$ C_1, C_2 : 800pF D_1, D_2 : PS101

Frequency 100kHz typically

Trigger input $\approx 4V$ Trigger input width $> 1\mu s$ load of 400 Ω and 15pF.

Synchronous binary counters using dual J-K master-slave flip-flops are shown above. In all cases decouple the power supply—typically 0.01 μF per package.

In Fig M1, since $J_A = K_A = 1$ (high), the first flip-flop acts as a toggle. The second flip-flop is triggered by alternate clock pulses the third flip-flop is gated by the Q_A and Q_B outputs and only changes when $Q_A = Q_B = 1$. Similarly, the last flip-flop only changes state when $Q_A = Q_B = Q_C = 1$. This counter has the

disadvantage of long counter chains requiring AND gates with a large fan-in.

The situation is avoided with the counter of Fig. M2 where the fan-in is limited to two per gate. However this is a slower counter because the gated-pulses must propagate down the AND gates before the next clock-pulse arrives. For both these counters, use the SN7473 dual J-K flip-flop package.

Another example (Fig. M3) employs the SN7472 which has effectively 3-input AND gates for each J and K input, within the package, which eliminate the need for external gates.

Further reading





Electronic Counting, Mullard, 1967.

Designing with TTL Integrated Circuits (Texas), McGraw-Hill 1971.


Counter delay slashed in half with interconnection scheme, *Electronic Design* 13, 1972.

Cross references

Series 14, cards 4, 6 & 12.

    

One out of n ring counter

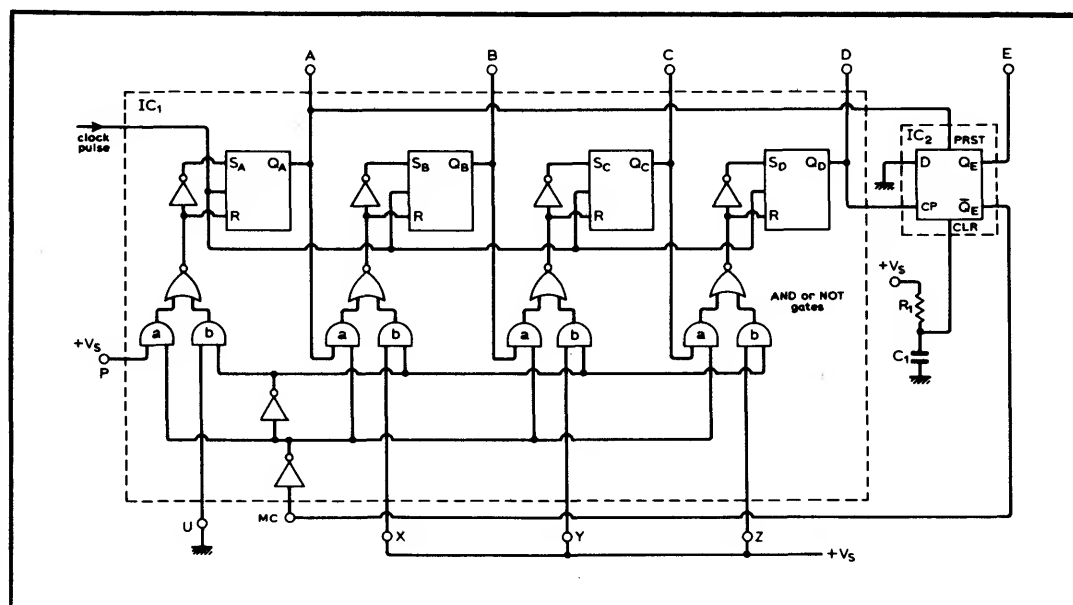

Typical data
 IC₁: SN7495
 IC₂: $\frac{1}{2}$ SN7474
 V_B: +5V
 R₁: 1k Ω
 C₁: 47pF

Circuit description

Component IC₁ is a 4-bit shift left or right register, comprising master-slave R-S flip-flops, with a parallel-loading capability via the AND-OR-NOT gates at terminals U, X, Y and Z. This is conditioned by mode-centre terminal MC equal

Clock pulse No.	Q _A	Q _B	Q _C	Q _D	Q _E
1	0	1	1	1	1
2	1	0	1	1	1
3	1	1	0	1	1
4	1	1	1	0	1
5	1	1	1	1	0
6	0	1	1	1	1

to binary one. When MC=0, information transfers serially through the register, the clock-pulses being applied to the commoned right-shift and left-shift inputs (not shown). When used in conjunction with a positive-edge triggered flip-flop, IC₂, this arrangement provides a self-starting, self-priming ring-counter for circulating a zero. When the supply V_s is switched on, the clear-input of IC₁ is pulled down to ground by CR network, setting Q_E=0, and Q_E=1. Hence MC=1, and the counter is in the parallel mode. The left-hand AND gates are inhibited, and the voltage levels at inputs U, X,

Y and Z are transferred to the set inputs, S_A to S_D, of IC₁. In master-slave flip-flops, the binary level at the set terminal is transferred to the Q terminal on the occurrence of the negative-going edge of the clock-pulse. After the first clock-pulse, Q_A=0, Q_B to Q_D=1. Also, Q_A is connected to the preset input of IC₁, and hence Q_E is set to binary one. Hence Q_E=0, and the counter is switched to a serial-mode. The right-hand AND gates are now inhibited. Therefore S_A=1, the low level of Q_A is gated to S_B, Q_B to S_C, and Q_C to S_D. After the second clock-pulse, the Q outputs are as shown in the truth table, the sequence continuing with each clock-pulse shifting the zero through the register. At the 5th pulse, Q_D changes from 0 to 1, and this positive-edge triggers IC₂. Q_E resets to zero, Q_E=1, and the parallel-mode is again entered. The 6th clock-pulse reloads the levels at U, X, Y and Z terminals and the cycle repeats.

Circuit modifications


- The number of bits can be extended by cascading IC₁ packages as in Fig. M1.
- Circulate a 1 by inverting the counter outputs with t.t.l. NAND gates (SN7400) or

c.m.o.s. hex buffers (CD4049).


- A 4-bit self-starting and correcting counter (Fig. M2) for circulating 1 uses J-K flip-flops and feedback via an AND gate. The flip-flops are connected as a shift register, where the state of Q_A is passed to Q_B, and Q_B to Q_C, etc. with each clock pulse. In general, for self-correcting, and when using J-K flip-flops, J_A should be the Boolean product of the complements of all but the first and last stages.

Further reading

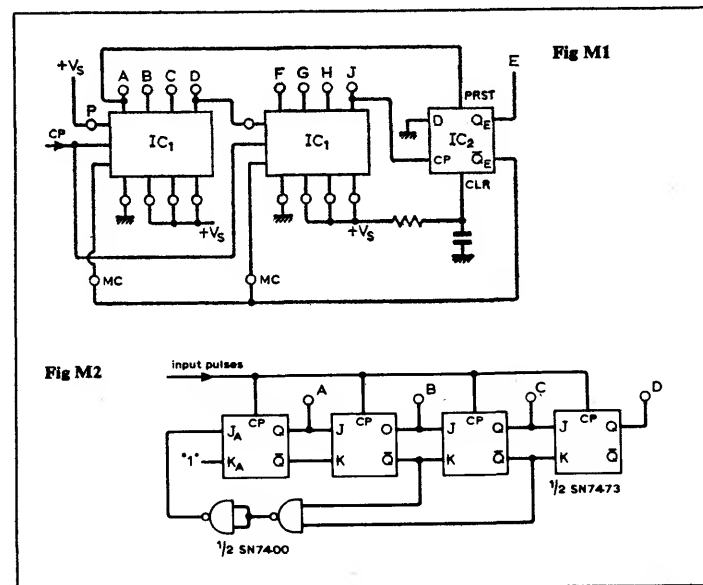Self-correcting ring counter requires no external gates, *Electronic Design* 9, 1973, p.138. Malmstadt and Enke, Digital Electronics for Scientists, Benjamin, 1969. Texas Instruments application report CA102, Electronic Counting, Mullard, 1967.



Johnson counters

 

Typical data

Supply: 4.75 to 5.25V

IC₁, IC₂: $\frac{1}{2}$ SN7400IC₃, IC₄: $\frac{1}{2}$ SN7473

Min. clock width: 20ns

(between 50% levels)

Typical pulse height: 3.5 to 4.5V

Circuit description

This counter, also called a switch-tail ring counter, allows $2n$ counts where n is the number of cascaded flip-flops. It is a synchronous counter in that changes at the Q outputs only take place on the occurrence of a clock-pulse. If $J = K$, the J input condition is transferred to the related Q output on the negative edge of the clock pulse, when the flip-flops are master-slave types. The above circuit has ten different states, the feedback via the AND gate causing self-correction after a few steps, should illegitimate states occur.

Consider all Q outputs to be in the 0 state. Hence $J_A = 1$ because $\bar{Q}_E = 1$. On the occurrence of the first clock pulse, the counter will load according to the truth-table. At each subsequent pulse, "1"s will be fed through the counter from the left until $Q_D = Q_E = 1$. It follows then that since $J_A = 0$, $K_A = 1$, that Q_A becomes 0 at the 6th clock-pulse. Zeros are subsequently transferred through the register according to the truth-table, until $Q_D = Q_E = 0$, then $J_A = 1$, $K_A = 0$, and the cycle repeats.

In general, when there are n stages in the counter, feedback via an AND gate from the last x stages, where x is the next larger integer to $n/3$ provides self-correction for n up to 25.

Decoding of each state is obtained using AND gates, as a unique pair exists for each state. These output pairs are indicated in the truth-table, and are applied to the gate inputs (these can be $\frac{1}{2} \times$ SN7400 in series).

Circuit modifications

The same output sequence is obtained from dual D-type flip-flops (SN7474) as Fig. M1. In general, assuming up to eight JK flip-flops are employed, A, B, C, D, E, F, G, H, then the

clock pulse	A	B	C	D	E	decoding outputs
1	0	0	0	0	0	A \bar{B}
2	1	1	0	0	0	B \bar{C}
3	1	1	1	0	0	C \bar{D}
4	1	1	1	1	0	D \bar{E}
5	1	1	1	1	1	A \bar{E}
6	0	1	1	1	1	$\bar{A}B$
7	0	0	1	1	1	$\bar{B}C$
8	0	0	0	1	1	$\bar{C}D$
9	0	0	0	0	1	$\bar{D}E$
10	0	0	0	0	0	$\bar{A}E$

feedback functions for an even cyclic pattern are

$$J_A = \bar{C}, K_A = B.C \quad (6)$$

$$J_A = \bar{D}, K_A = C.D \quad (8)$$

$$J_A = \bar{E}, K_A = D.E \quad (10)$$

$$J_A = \bar{F}, K_A = E.F \quad (12)$$

$$J_A = \bar{G}, K_A = E.F.G \quad (14)$$

$$J_A = \bar{H}, K_A = F.G.H \quad (16)$$

An odd sequence ($2N-1$) counter can be implemented by bypassing the all "1"s state of the normal Johnson sequence i.e. the last two bits of the 111...10 state is detected, and the gating arranged to the first flip-flop so that the next state is 011...11. (Texas ref.).

Other odd sequence counters can be implemented by J-K flip-flops without extra gating and are shown in Figs. M2 & 3. Fig. M2 uses feedforward gating and Fig. M3, feedback. In general, any $2n$ counter can be made $2n-1$ by obtaining the K input of the first-flop from the second last Q output (cf. Fig. M3).

Further reading


Davies, A. C., Design of feedback shift registers and other synchronous counters, *Radio and Electronic Engineer*, April 1969.

Texas Instruments application report CA102.

Kohonen, T. Digital circuits and devices, Prentice-Hall, 1972. Malvino, A. P. & Leach, D. P., Digital principles and applications, McGraw-Hill, 1969.

Cross references

Series 14, cards 9 & 12.

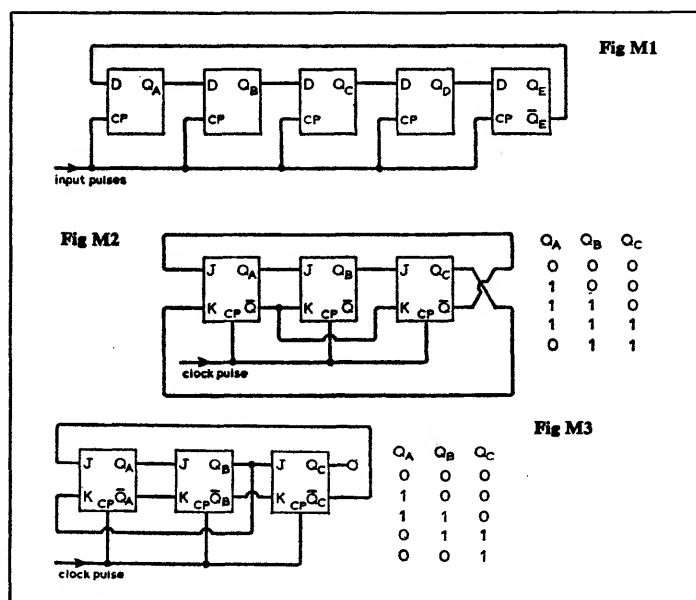

Reversible counters—1

Circuit description


Up-down or reversible counters alter their mode of counting under electrical control. The circuits shown are binary up-down counters in which the count direction is controlled by steering logic and either the flip-flop Q outputs are used for toggling subsequent flip-flops (UP) or the \bar{Q} outputs are used when the Q outputs are inhibited. Fig. 1 is an asynchronous type and Fig. 2, a synchronous counter. The equation for the output of the selector gate is, for example, $AX + \bar{A}\bar{X}$, the gating usually being implemented by the NAND gate interconnection of Fig. 3. When a logic 1 is applied to the up-down control line, the gates connected to \bar{Q} are inhibited, and the flip-flops change state when their clock inputs undergo a 1 to 0 transition i.e. the Q outputs will change according to the normal binary sequence. If the control line becomes 0, the Q outputs will reverse sequence. To avoid a false triggering condition, the count/inhibit line must be 0 when the controlling function is altered from up to down or vice-versa.

In the synchronous counter of Fig. 2 such a condition is avoided. Each flip-flop will change state only if previous Q outputs are in the 1 state (when $X = 1$) i.e. counting up, and for a down count ($\bar{X} = 1$), all the less significant Q outputs must be at 0 for a flip-flop to change on a 1 to 0 transition.

IC₅ (CD4029A) is a presettable synchronous up/down counter providing either a binary or b-c.d. decade sequence with appropriate mode control, i.e.

binary: B/D = 1
Decade: B/D = 0
Up: U/D = 1
Down: U/D = 0
Preset: PE = 1


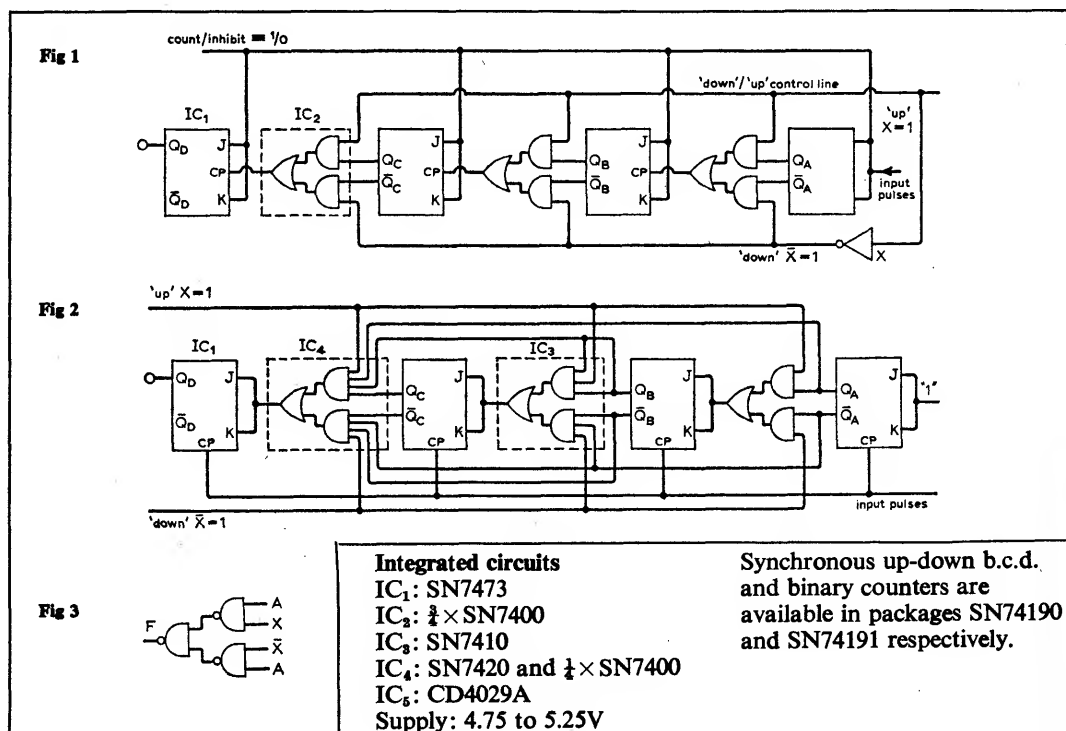
J1 to J4 = 1 or 0
Parallel clocking allows
cascading (Fig. 4)
Where separate "clock up" and



"clock down" clock pulses are available the circuit of Fig. 5 provides a simple interface to the up/down "clock" inputs.

Cross references

Series 14, cards 5 & 12.

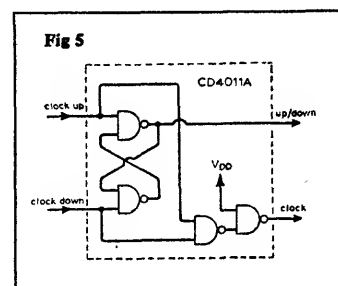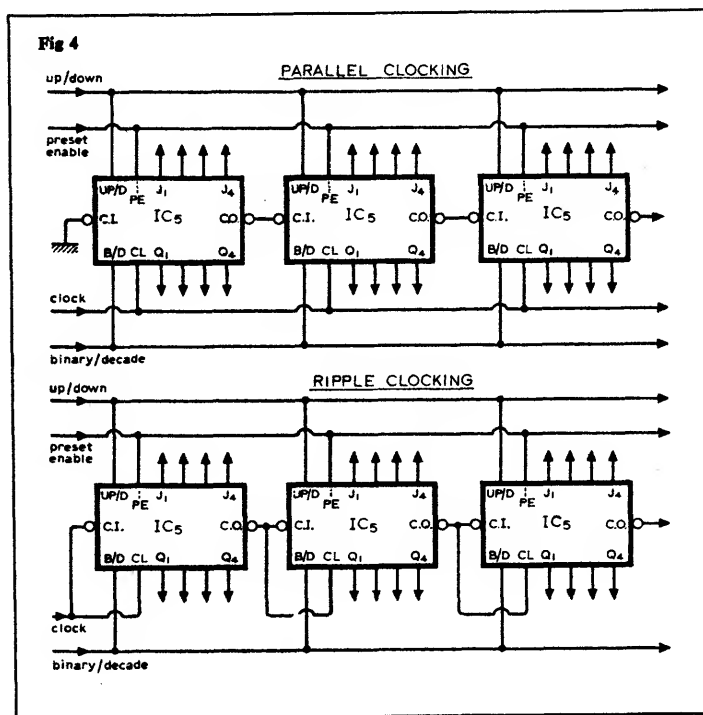

Reversible counters—2

The AND-OR-NOT gates provide gating control for the up/down mode. The Boolean expression for the P output is $(UP)Q_D + (DWN)Q_B$. If the control line = 0, then $P = Q_D = 0$. Hence $J_A = 1$, $K_A = 0$, and on the occurrence of the first clock pulse $Q_A = 1$. The counter would subsequently count up in Johnson code. However, if for example, the counter state is 1110 and control = 1, only the S output causes a change to make $Q_C = 0$ on the next pulse, and thus count down.

Circuit of Fig. 2 uses a 4-bit parallel adder and four D-type flip-flops. Consider the sum outputs $\Sigma_4 - \Sigma_1$ show 7_{10} i.e. 0111, where Σ_1 is the least significant bit, and that the next pulse should cause a decrement, hence control = 1. Each sum variable (Σ) is transferred to the Q output on the occurrence of the clock pulse via each D-type flip-flop. Inputs (B_1A_1), (B_2A_2) etc. are added and each produce 0 carry 1 except for (B_4A_4) which makes $\Sigma_4 = 1$. When the "carry's" ripple through, the result is 0110 with $C_{out} = 1$, which can be ignored. (This is 2's complement arithmetic, where negative-one, represented by 1111, is added to achieve subtraction).


IC₁: SN7483 (full adders)

IC₂: SN7495 (or 2 × SN7474)

Typical operating frequency ≈ 10MHz

An eight-bit shift register is used to provide a variable modulus counter in which maximum and minimum counts may be detected as shown in Fig. 3

Shorting any one pair of

 

external terminals decides the maximum counter loading at which the counter may then be considered to reverse.

Assume a counter cleared and a link at Q_C . Then, via gates X, Y, Z, $S_A = 1$, $R_A = 0$. The sequence of Q_A , Q_B , Q_C for the first three clock pulses is 100, 110, 111 and then $S_A = 0$, $R_A = 1$ and "detect max" goes high. For the next three pulses, the sequence is 011, 001, 000, when "detect min" goes high. IC₁: SN74164 (DM8570) IC₂: SN7400

Further reading

Malmstadt & Enke, Electronics for Scientists, Benjamin, 1969.

High-speed synchronous reversible binary and BCD counters. Texas Instruments application report B40.

Baccolini, G., Benetazzo, L., & Clements, G., Variable dead-zone counter as a maximum value follower, *IEEE Trans.* vol. ECI-20, Aug. 1973.

Cross references


Series 14, cards 4 & 12.

Integrated circuits

IC₁: $\frac{1}{2}$ SN7473

IC₂: $\frac{1}{2}$ SN7451

IC₃: $\frac{1}{2}$ SN7400

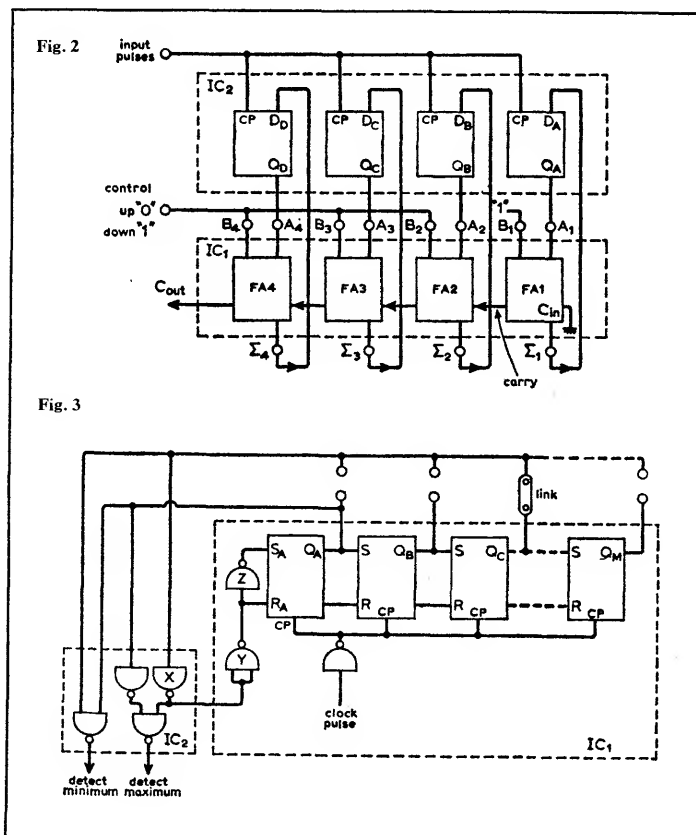

Divide by n counters

Counters with N states (modulus N) may comprise a sequence of counters with different moduli, integers n_1, n_2, n_3 etc. and $N = n_1 \times n_2 \times n_3 \dots$. Even numbers are achieved by cascading as in Fig. 2 (modulus 2^m , where m is the number of flip-flops). Synchronous circuits for smaller odd numbers are shown below. Q_A is the least significant bit, the natural binary sequence is followed and positive logic assumed.


Components (typical)

IC_1 : $\frac{1}{2}$ SN7473. IC_2 : $\frac{1}{2}$ SN7410.
 IC_3 : $\frac{1}{2}$ SN7400. IC_4 : SN7472 (or $\frac{1}{2}$ SN7473 plus 3 input gates).
 IC_5 : SN7493. IC_6 : $\frac{1}{2}$ SN7408 (or $\frac{1}{2}$ SN7400). IC_7 : $\frac{1}{2}$ SN7410.

Description

For the small prime numbers, it is sufficient to consider Fig. 3 as an example. Q_A flip-flop acts as a toggle and will change state on every input pulse while $Q_C = 1$ ($Q_C = 0$). Q_B changes state whenever Q_A goes from 1 to 0. Q_C will only be set to 1 when both Q_A and Q_B are logic one i.e. on the 4th clock-pulse, because $J_1 = J_2 = J_3 = 1$ and the K inputs are 0. Hence on the 5th pulse, since Q_C is now 0, Q_A will remain at 0 hence Q_B is logic zero, and Q_C will be reset to 0, because J_1 to $J_3 = 0$ and K_1 to $K_3 = 1$. The sequence then repeats.


Fig. 6 demonstrates an alternative technique. The counter is reset to zero when a negative-going edge is simultaneously applied to the CLEAR inputs. This is obtained from the NAND gate, when the predetermined binary number, 1101 (13), is detected. The minimum duration between input pulses depends on propagation delays of flip-flops, the gate delay, and the reset delay. If the output is to be read, the lines should be gated to avoid transmitting spikes that will appear on some lines depending on the divisor N .

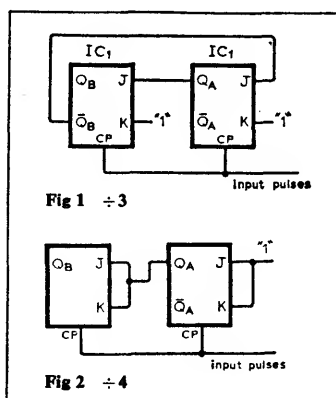

SN7493 connection

Divisor N	Feedback	Extra gate
9	A D	—
10	B D	—
11	A B D	2 I/P AND
12	C D	—
13	A C D	2 I/P AND
14	B C D	2 I/P AND
15	A B C D	3 I/P AND

 MSI integrated circuit packages e.g. SN7493 4-bit ripple counter contains a NAND gate for clearing, but additional gating is necessary for certain counts (see Table 1). Fig. 7 is the connection for $N=11$, the feedback being applied via reset terminals $R_0(1)$ and $R_0(2)$. A useful arrangement for division by large numbers is shown in Fig. 8, where N_1 and N_2 must be prime numbers



with respect to each other. The arrangement ($N_1 = 3, N_2 = 7$) provides $N = 21$; input pulses are applied simultaneously to each counter, and each cycles through its own modulus until all outputs are 1's together, thus enabling AND gates, and resetting to zero via reset terminals.


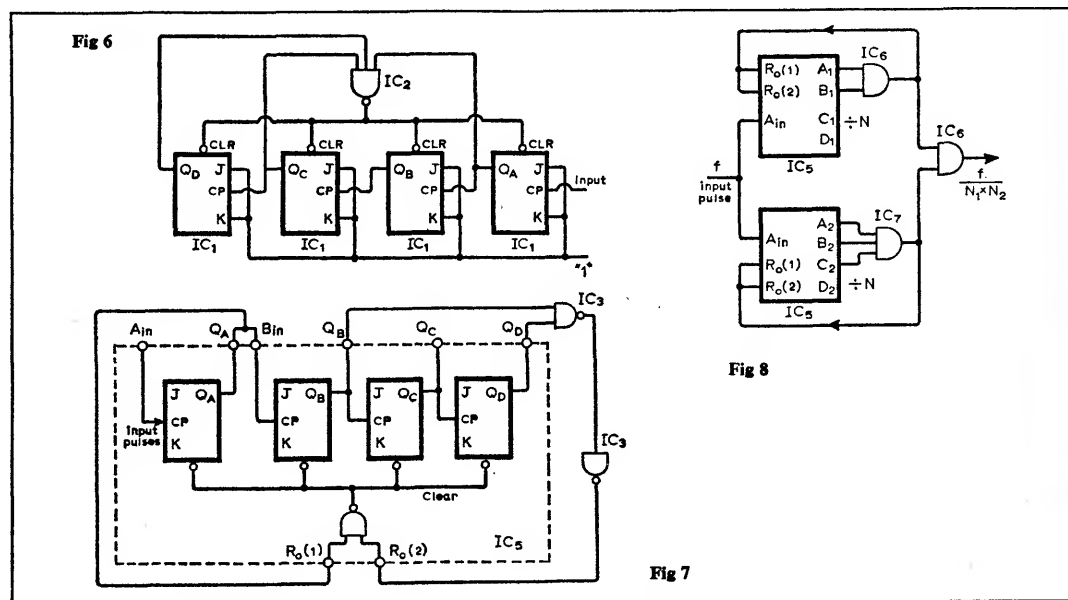


Fig 8

Fig 7

High-power counters

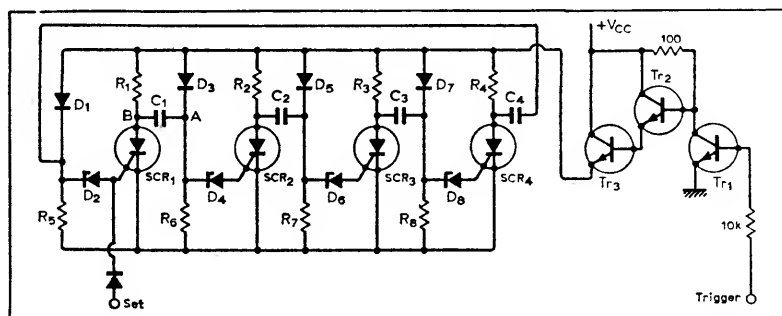

Component values

R_1, R_2, R_3, R_4 : 5 to 10Ω
 R_5, R_6, R_7, R_8 : $100k\Omega$
 C_1, C_2, C_3, C_4 : $0.47\mu F$
 D_2, D_4, D_6, D_8 : 1N757
 D_1, D_3, D_5, D_7 : 1N914
 SCRs: 2N1595
 Tr_1, Tr_2 : 2N1420
 Tr_3 : 2N657A

Performance

V_{CC} : 9V
 Trigger amplitude -6 to 9V
 width $>200\mu s$
 Set pulse: 3V max
 Maximum frequency: 1kHz
 Minimum frequency: depends on capacitor losses, s.c.r. leakage current, and diode leakage current

Circuit description-1

Circuit shows a four-stage dynamic ring counter with power capabilities per stage of 20W at between 2 and 5A. Consider first the situation where all the s.c.r.s are non-conducting. A set pulse applied at the gate of SCR₁ causes it to conduct freely via the load resistor R_1 and this continues in the absence of a set voltage until the supply is removed, which occurs when a trigger pulse is applied as base drive to Tr_3 is then shunted to ground, removing base drive to Tr_3 . While the supply is

applied to the counter and SCR₁ is conducting, point B is at ground voltage and C_1 charges via D_3 , so that $V_{AB} = V_{CC}$. When the supply is removed, C_1 retains this charge as there is no discharge path (apart from leakage). When the supply is reapplied, SCR₁ remains non-conducting and point B rises to the supply. Consequently, point A will rise to $2V_{CC}$. If D_4 is chosen so that its breakdown voltage lies between V_{CC} and $2V_{CC}$, breakdown occurs and SCR₂ conducts so that current flows in the second load, R_2 . Further


trigger pulses will cause each succeeding stage to conduct. Resistor R_8 allows C_1 to continue discharging below the zener voltage of D_4 . Diode D_3 arrests this discharge so that the final condition is zero charge on C_1 —which is the initial condition of C_1 prior to SCR₁ conducting. Continual rotation of a single logic 1 is what has been described so far. Two adjacent logic 1's cannot reliably be rotated by this scheme but there is no reason why any pattern cannot be rotated provided no two logic 1's are

adjacent. Should more than one logic 1 be rotated then the supply section comprising Tr_1, Tr_2 and Tr_3 will require re-design as the current drawn is $n +$ (current for one stage), n being the number of on stages.

To prevent noise falsely triggering any s.c.r., resistors between gate and ground should be provided.

Further reading

 Strangio, High power counter drives 20W loads, *Electronics*, March 1, 1973



Component values

R_1, R_2 : $33\Omega, 16W$
 C_1, C_2 : $100\mu F, 40V$
 W_1, W_2 : 9Ω stator coils
 Tr_3, Tr_4 : BSW 66
 IC: SN75451P

Performance

Controlled by the torque characteristics of the motor. The coil current was 550mA and the maximum speed was 6000 steps per second, corresponding to a counter clock frequency of 6000 pulses per sec. A and \bar{A} were normal t.t.l. voltage levels (5V and 0V).

only 4 of the phases at any one time. Two of these phases are shown in the diagram in the form of the 9Ω coils, W_1 and W_2 . The motor operation requires that current flows in one of these coils at a time and this is achieved as shown. A and \bar{A} are obtained from one stage of a 4-stage Johnson, up-down counter. If A is "high" then T_1 will not conduct and base drive is

presented to T_4 and consequently current from the 23V supply will flow through W_1 . Likewise no current flows through W_2 in this condition. However, if \bar{A} is high the position is reversed. Tr_4 and Tr_3 are high current transistors capable of feeding inductive loads. R_1, C_1 and R_2, C_2 serve to reduce the circuit time constant so that higher speeds may be achieved.

Further reading

Shakaiba, M. A. Digital control system for an 8-phase stepper motor, Project Report, Electrical Engineering Dept, Paisley College of Technology. King, D. S. Stepper motor for digital control systems, *Control and Instrumentation*, June 1971.

Cross reference
 Series 14, card 5.

Circuit description-2

A stepper motor drive is required to rotate a magnetic field pattern in either direction and at variable speed. This can be achieved by supplying the stator coils from an up-down counter with a variable pulse rate (see Card 4). Circuit shows $\frac{1}{4}$ of the drive circuitry for an 8-phase stepper motor with power consumption of 11W which is dissipated in

High-speed counters

Circuit description



In most counting arrangements the decoding of the end of the sequence and the resulting resetting of the counter occur in the same clock period. This can be avoided by using the philosophy of the circuit of Fig. 1 and thereby obtain increased counting speeds, irrespective of the logic family used. Circuit shows a frequency divider in which the second last number to appear on the output of the counters is decoded.

This is done by the AND gates A_1 and A_2 and occurs on the falling edge of the clock pulse when A_0 goes to logic 1, corresponding to the number 97. Inputs J' and K' are then in the logic 1 state and the next clock pulse triggers the flip-flop and also the strobe pulse. The counter remains in this state until the clock pulse at the end of the 99th state toggles the flip-flop back again. The counter is then ready to start up-counting again from the initial state, which is, of course, dictated by the b.c.d. data inputs.

This arrangement allows the reset pulse to be a full clock period wide and unaffected by the counter states. Further, the decoding time and the reset time occur in different clock periods, rather than in the same period as in other methods.

Hence the time taken for N to be fed in can be almost a full clock period and as a result higher clock frequencies can be handled.

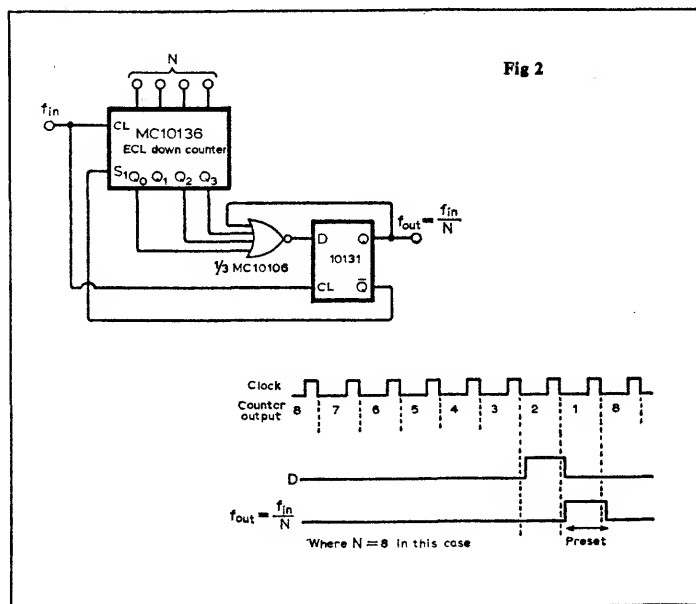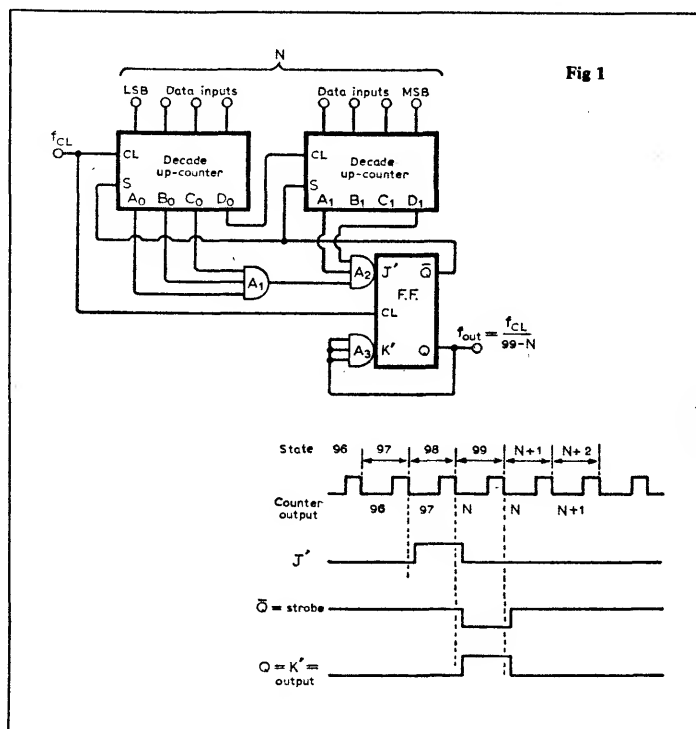With the devices quoted counting speeds of over 40MHz have been achieved. The second stage of the counter need not be such a high speed device (and, consequently, high power consuming device) as clock



Components

Counters: 8290, decade up-counter for which the input data is on output when S is logic 0.

Flip-flop: 74H102 (high speed)
A₁, A₂, A₃: $\frac{1}{4}$ MC3006

frequency to it is 1/10th of that to the first stage.


Higher frequencies are achievable if one uses faster logic families. Fig. 2 shows an e.c.l. device being used in a fashion similar to that of Fig. 1. In this case the device is a down counter, counting down from the preset state N and giving an output frequency $f_{CL/N}$. Clock frequencies in excess of 110MHz can be handled. Again the second last number in the sequence is decoded, in this case 0100, and this causes the flip-flop to change state on the next clock pulse, thereby resetting the counter to N .

Further reading

Clifford, D. Reset dividers faster with a single flip-flop, *Electronic Design*, Aug. 5, 1971.
Balph & Granden, Boost counting speeds to 110MHz, *Electronic Design*, April 1, 1973.
Tan, Z. C. New tunnel diode ring counter, *Proc. IEEE*, April 1973.

Low-power counters

Fig 1

 

Circuit description


The counter of Fig. 1 uses a Johnson configuration and obtains speeds in the region of 5 to 7MHz, each flip-flop operating at only one tenth of the input frequency. The counter is disabled if enable is high, reset to zero being achieved by applying a logic 1 level to reset. The counter sequences on the leading edge of each clock pulse, the Johnson code being maintained by ensuring that the D_C input is only high, when either Q_A and Q_B or Q_C and Q_B are high, via NOR gates 1 and 2. Additional gating (not shown) provides ten decoded outputs, which sequentially are high for one full clock period. For count < ten, use quad-NOR i.c. CD4001. In Fig. 2 the cross-coupled pair is a reset latch, to ensure reset when flip-flops have different reset propagation delays. The decimal zero output is low except when counter is cleared, hence when the N output goes high, point X→0, and a reset

pulse is generated while the clock is high. When counter resets, zero terminal goes high. This can drive another counter.

Programmable counter

$N = 1$ to 10 IC: CD4018 This is a 5-stage Johnson counter but with the Q outputs buffered with inverters to provide a Johnson BCD output. Counts less than ten achieved by feedback to the DATA input terminal, see Fig. 3. The odd count is obtaining by ANDing the two Q outputs (table) with $\frac{1}{2}$ CD4011. This ensures that the all '1's state of the counter is avoided. The counter may be preset to any combination fed to the J inputs, by pulsing the preset-enable input. Voltage levels and speeds are similar to CD4017AE. As a preset counter, counter will advance from preset state to 11110, where the right-most bit is Q₅. The presence of Q₄ and Q₅ should be detected as shown in Fig. 4 to reset the counter.

Fig 2

 

Ripple counters

CD 4020AE
14 stages but outputs available from stage 1 and stages 4 to 14 inclusive.
Typical speed: 7MHz at 10V
2.5MHz at 5V

Power dissipation:
typical 1mW at 1MHz at 5V
10mW at 1MHz at 15V

CD 4040AE
12 stages
All 12 buffered outputs available
Typical speed: 8MHz at 10V.

Up-Down counter CD 4029AE
4 stage: Either BCD decade or

binary by input control

Typical speed: 5MHz at 10V
Dissipation: 30mW
Load: 15pF
Typical speed: 100kHz at 3.5V
Dissipation: 1mW
Load: 15pF

Further reading

RCA Solid State Databook
Series SSD-203A 1973

Cross references

Series 14, cards 4 and 10.
Series 11, card 6.

Even count	DATA	N
	Q ₁	2
	Q ₂	4
	Q ₃	6
	Q ₄	8
	Q ₅	10
Odd count	DATA	N
	Q ₁ Q ₃	3
	Q ₂ Q ₃	5
	Q ₃ Q ₄	7
	Q ₄ Q ₅	9

Fig 3



 


Fig 4

 

Decade counters

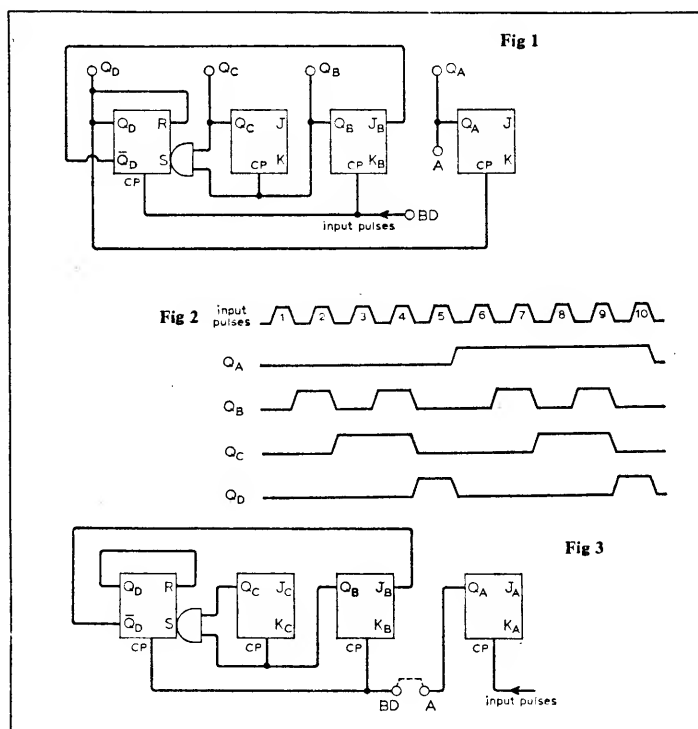

Circuit description

The four master-slave flip-flops of Figs. 1 and 3 are contained within one i.c. package, SN7490, and provides separate $\div 5$ and $\div 2$ facilities. A symmetrical decade counter where the period of the output pulse at Q_A is ten times the input pulse period with equal mark-to-space ratio is shown in Fig. 1, with the associated waveforms of Fig. 2. The J-K terminals with no inputs are internally connected to be logic 1. Flip-flop C toggles for all 1 to 0 transitions of Q_B , and Q_D is set on the 4th pulse ($S = 0, R = 1$), thus setting Q_A . Q_B cannot change because $J_B = 0, K_B = 1$. For the next five pulses, the sequence of flip-flops B, C and D is similar, when Q_A is reset on the tenth pulse.

The connections of Fig. 3 allow the counter to sequence in an 8 4 2 1 b.c.d. code, where flip-flop D has the maximum weighting: gated direct reset lines (not shown) are provided to inhibit count inputs and return outputs to zero. Typical frequency and power dissipation is up to 18MHz, and around 160mW.

Another asynchronous 8 4 2 1 b.c.d. counter uses J-K flip-flops in a toggle mode (Fig. 4), has no logical hazards, and may be implemented with two SN7473 and one SN7400.

Fig. 5 is an 8421 b.c.d. synchronous counter, which requires 3-input AND gates or triple input J-K flip-flops. Q_A changes state for every clock-pulse (unused J-K inputs

may be connected to logic '1'). Q_B changes on the 2nd, 4th, 6th, 8th clock pulses, but is inhibited from a 0 to 1 transition on the 10th pulse, since $\bar{Q}_D = 0$. Flip-flop C is toggled whenever $Q_A = Q_B = 1$, and Q_D undergoes a 0 to 1 transition when $Q_A = Q_B = Q_C = 1$, on the occurrence of the 8th pulse. Q_D resets to zero on the 10th pulse, because $J_1 = 0$ and the K inputs are high.

Implemented with either two SN7473 and three SN7410, or four off SN7472.



Figs. 6 & 7 are two other forms of b.c.d. synchronous counters. Fig. 6 counts in 8421 code, Fig. 7 in excess-3 code. In each case the least significant bit is flip-flop A.

Further reading


T.T.L. Integrated Circuits, Counters and Shift Registers, application report CA102. Texas Instruments. Malmstadt and Enke, Digital Electronics for Scientists, Benjamin, 1969. Kohonen, T. Digital Circuits and Devices, Prentice-Hall, 1972.

Cross references

Series 14, cards 3 & 9.

 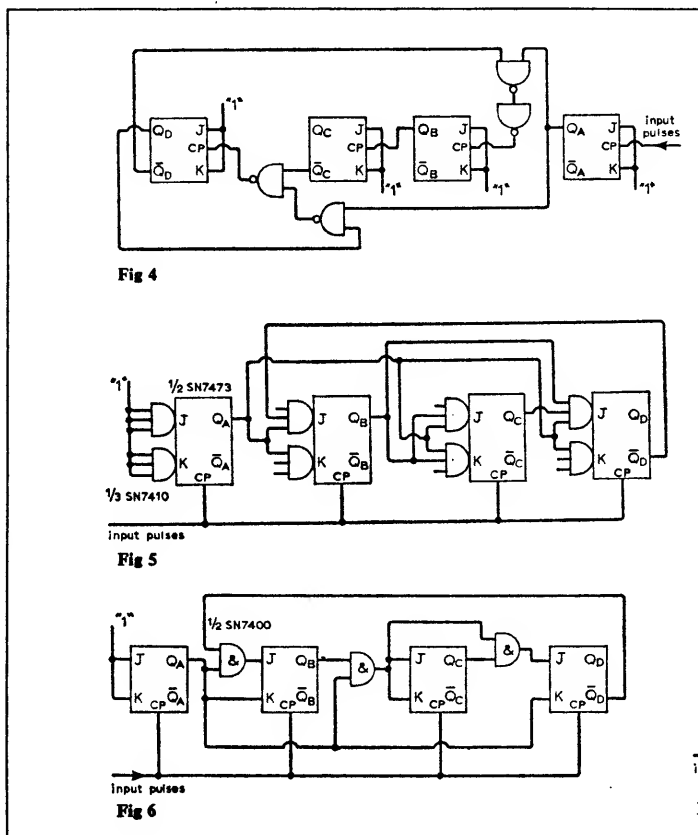

M-sequence generators

 

Description

Maximum length sequences (M-sequences) have many uses in data communications system identification and correlation methods. Some of them have properties very similar to that of band limited white noise, particularly if passed through simple first or second order R-C filters—hence the name pseudo-random-binary sequence (p.r.b.s.). They are produced by a simple synchronous shift register or counter with feedback from various stages determining the state of the first stage on receipt of each clock pulse. The feedback is basically by means of exclusive-OR gates (modulo-two gates). The basic diagram is as shown in Fig. 1, the output being taken from any stage. The sequence produced is cyclic and repeats itself after $2^n - 1$ pulses, the all-zero state being avoided. The maximum number of states for an n -stage register is 2^n but to prevent the all-zero state becoming a permanent

state requires considerable extra logic and, hence, this state is avoided and the length $2^n - 1$ is described as maximal.

Long sequences can be generated by simple feedback arrangements. The Table indicates the simplest feedback arrangements for all those registers up to length 18, and all those beyond 18 and up to 33 which require only one exclusive-OR gate. Fig. 2 shows how the characteristic polynomials of the Table are interpreted in terms of hardware for the particular case of $n = 8$. If JK flip-flops are used as the register stages some simplification is possible if the polynomial contains D to the power one. Column 3 or of the table indicates the logic necessary for the J input and column 4 indicates the K input. If the output of stage 1 is regarded as the output, versions of this sequence delayed by LAT , where AT is the clock period and $L = 0$ to $n - 1$, are clearly available from the

remaining stages. Delays of up to NAT , where $N = 2^n - 1$ can also be generated by modulo-two addition of several of the output stages (ref. 1).

When the sequence is being used as a noise source the output is arranged so that logic 1 = $+a$ volts and logic 0 = $-a$ volts. The r.m.s. value of the waveform is than a^2 and the mean value is a/N (this would be zero if $N = 2^n$ rather than $2^n - 1$). The power spectrum, which is discrete, is where $G(k)$ is the power in (volt)² of the k th harmonic. $G(k)$ is shown in Fig. 3. The small d.c. term is often ignored.

Spacing between the lines of Fig. 3 is $1/NAT$ and hence the power density spectrum (power per unit bandwidth) is $G(k)NAT$. The 3-dB point for the power density spectrum occurs at approximately $1/3AT$ so that for systems with bandwidth less than $1/3AT$ the signal appears as white noise. Further, the autocorrelation function for the signal is very similar to that for white noise (ref. 1). The probability distribution of the signal is not at all Gaussian because it consists of two lines at $\pm a$

respectively. However, when passed through a suitable R-C filter with a break point less than $1/3AT$ the distribution does become close to Gaussian i.e. that for band-limited white noise (ref. 2).

References


1. Davies, W. D. T., Generation and properties of M-sequences, *Control*, June, July and August 1966.
2. Roberts, P. D. & Davis, R. H., Some statistical properties of smoothed M-sequences, *Proc. I.E.E.* 1966 vol. 113, p.190.

Further reading

Davies, A. C., Design of feedback shift registers and other synchronous counters, *Radio and Electronic Engineer*, April 1969.
Peterson, W. W., Error Correcting Codes, MIT Technical Press 1961.
Golomb, S. W., Shift Register Sequences, Holden Day 1967.

$$G(k) = \frac{a^2}{N^2} + \sum 2a^2 \frac{(N+1)}{N^2} \left(\frac{\sin \frac{\pi k}{N}}{\frac{\pi k}{N}} \right)^2$$

n	Characteristic Polynomial	J input	K input
2	1 ⊕ D ⊕ D ²	2	J
3	1 ⊕ D ⊕ D ³	3	⊕ ⊕ ⊕
4	1 ⊕ D ⊕ D ⁴	4	⊕ ⊕ ⊕ ⊕
5	1 ⊕ D ⊕ D ⁵	2 ⊕ 5	⊕ ⊕ ⊕ ⊕ ⊕
6	1 ⊕ D ⊕ D ⁶	6	⊕ ⊕ ⊕ ⊕ ⊕ ⊕
7	1 ⊕ D ⊕ D ⁷	7	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
8	1 ⊕ D ⊕ D ⁸ ⊕ D ⁵ ⊕ D ³	3 ⊕ 5 ⊕ 8	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
9	1 ⊕ D ⊕ D ⁹	4 ⊕ 9	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
10	1 ⊕ D ⊕ D ¹⁰	3 ⊕ 10	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
11	1 ⊕ D ⊕ D ¹¹	2 ⊕ 11	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
12	1 ⊕ D ⊕ D ¹² ⊕ D ⁶ ⊕ D ⁴	4 ⊕ 6 ⊕ 12	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
13	1 ⊕ D ⊕ D ¹³	3 ⊕ 13	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
14	1 ⊕ D ⊕ D ¹⁴ ⊕ D ⁷ ⊕ D ⁵ ⊕ D ⁴	6 ⊕ 10 ⊕ 14	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
15	1 ⊕ D ⊕ D ¹⁵	15	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
16	1 ⊕ D ⊕ D ¹⁶ ⊕ D ⁸ ⊕ D ⁵ ⊕ D ⁴	3 ⊕ 12 ⊕ 16	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
17	1 ⊕ D ⊕ D ¹⁷	3 ⊕ 17	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
18	1 ⊕ D ⊕ D ¹⁸	7 ⊕ 18	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
20	1 ⊕ D ⊕ D ²⁰	3 ⊕ 20	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
21	1 ⊕ D ⊕ D ²¹	2 ⊕ 21	⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕ ⊕
22	1 ⊕ D ⊕ D ²²	22	⊕ ⊕
23	1 ⊕ D ⊕ D ²³	5 ⊕ 23	⊕ ⊕
25	1 ⊕ D ⊕ D ²⁵	3 ⊕ 25	⊕ ⊕
28	1 ⊕ D ⊕ D ²⁸	3 ⊕ 28	⊕ ⊕
31	1 ⊕ D ⊕ D ³¹	3 ⊕ 31	⊕ ⊕
33	1 ⊕ D ⊕ D ³³	13 ⊕ 33	⊕ ⊕

 


Glossary: flip-flops and b.c.d. codes


Integrated circuit flip-flops are usually clocked i.e. the change of state is initiated by a timing pulse called the clock pulse. The outputs are commonly termed Q and \bar{Q} . If $Q = 1$, $\bar{Q} = 0$ (and vice versa). These states are dependent on the logical states of the flip-flop (or bistable) inputs and this dependence is shown in each associated TRUTH table, where Q_n is the state of the Q output after the n th pulse, and Q_{n+1} is the new state after the next pulse.

When Q is made to be logical '1', the flip-flop is said to have been SET, and when Q is made '0', the flip-flop has been RESET or CLEARED. Edge-triggered and master-slave types are available. The time for which data must be present before the clock pulse threshold (set-up time) and the time for which data must be maintained after the clock edge (hold time) are normally specified. The transfer of information in the master-slave flip-flop is according to the numbers marked on the pulse shown, and it may be considered that the master and slave flip-flops are distinct, but isolated or connected by gates.

 - (1) slave isolated from master
- (2) data entered into master
- (3) master is isolated from input terminals
- (4) data is transferred from master-to-slave



R-S flip-flop

 


S	R	Q_{n+1}
0	0	Q_n
1	0	1
0	1	0
1	1	X

X = indeterminate
TRUTH TABLE

$R = S = 1$ must be avoided because the logical value of the Q output is uncertain.


J-K flip-flop

 

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n


This has two data inputs termed J and K (and may be considered to be similar to S and R of the R-S flip-flop), but no indeterminate state exists for any combination of

 the inputs. Multi-input J and K terminals are achieved on some i.c.s with internal gating, where the J and K inputs are for example the ANDED inputs $J_1 J_2 J_3$ and $K_1 K_2 K_3$. CP is



the clock-pulse terminal, Preset and Clear terminals may also be available. These inputs are maintained normally at logical '1'. A negative edge applied to PRESET, sets $Q = 1$, and if applied to CLEAR, makes $\bar{Q} = 1$. The negative edge triggering can be indicated by the small circle at the terminal as in diagram.

D-type flip-flop

 


D	Q_{n+1}
0	0
1	1

TRUTH TABLE

This has one data input, and may also have both outputs available. In the table, D is the input before clocking and Q_{n+1} is the Q output after clocking. Note—CMOS flip-flops are cleared by a positive-going edge at the clear input.

T-type flip-flop

 

T	Q_{n+1}
0	Q_n
1	\bar{Q}_n

TRUTH TABLE

This may be considered as the basic binary or toggle flip-flop. When $T = 0$, the Q output will not change state on the occurrence of a clock pulse. If $T = 1$, Q takes up the opposite state when the flip-flop is clocked.


Further reading

Walters, D. J. Integrated Circuit Systems, Iliffe Books, 1971.
Malmstadt & Elke, Digital Electronics for Scientists, W. A. Benjamin, 1969.
Texas Instruments Inc. Designing with TTL Integrated Circuits.

Cross references

Series 14, card 5.
Series 14, card 3.

Alternative toggle flip-flops

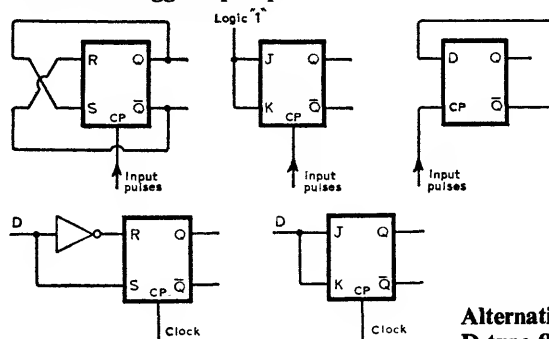

Alternative D-type flip-flops


Decimal codes

These are listed with the least significant bit (LSB) rightmost for the weighted codes, i.e.

those in which a decimal numerical weighting is assigned to each bit position.


JOHNSON	NATURAL BCD 8-4-2-1	4-2-2-1	GRAY	EXCESS-3	DECIMAL NUMBER
0 0 0 0 0	0 0 0 0	0 0 0 0	0 0 0 0	0 0 1 1	0
0 0 0 0 1	0 0 0 1	0 0 0 1	0 0 0 1	0 1 0 0	1
0 0 0 1 1	0 0 1 0	0 0 1 0	0 0 1 0	0 1 0 1	2
0 0 1 1 1	0 0 1 1	0 0 1 1	0 0 1 1	0 1 1 0	3
0 1 1 1 1	0 1 0 0	1 0 0 0	0 1 1 0	0 1 1 1	4
1 1 1 1 1	0 1 0 1	0 1 1 1	0 1 1 1	1 0 0 0	5
1 1 1 1 0	0 1 1 0	1 1 0 0	0 1 1 0	1 0 0 1	6
1 1 1 0 0	0 1 1 1	1 1 0 1	0 1 1 1	1 0 1 0	7
1 1 0 0 0	1 0 0 0	1 1 1 0	1 1 0 0	1 0 1 1	8
1 0 0 0 0	1 0 0 1	1 1 1 1	1 1 0 1	1 1 0 0	9

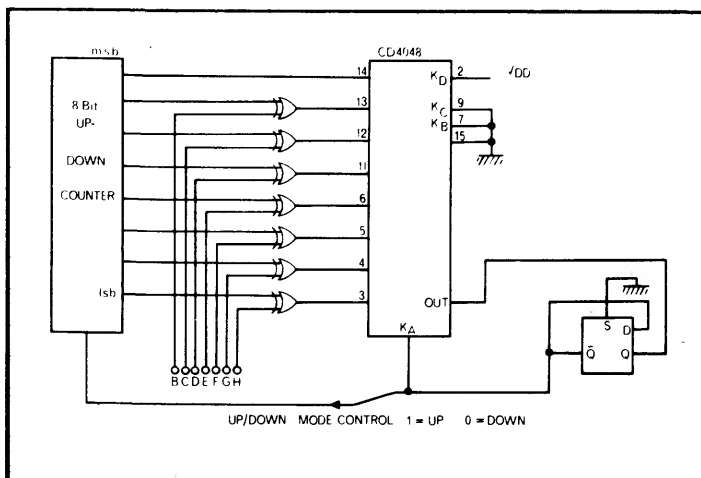1. Control primarily depends on the logic simulation of the CD4048 gate where, if $K_B=K_C=0$, $K_A=1$, the gate acts like an eight-input AND gate i.e. output is 1 if all inputs are high. Also if $K_A=0$, the gate acts like an eight-input NOR gate, and the output is 1 if all inputs are logic 0. Using exclusive-OR gates between the counter and the CD4048, the counter can then be arranged to cycle between any two symmetrical binary states by programming inputs B to H inclusive, e.g. if BCDEFGH is programmed



to be 0001111, then when the counter reaches 11110000, the CD4048 will see all logic 1s at the inputs and provide an output which can be used to clock the D-type flip-flop, i.e. the maximum output is 240_{10} . When the counter then starts to count down, an output is again obtained when the counter reaches 00001111, where the exclusive-OR gates will provide all 0s to the gate-inputs and as K_A is then 0. The effective NOR gate senses the 0s to provide a changeover signal.

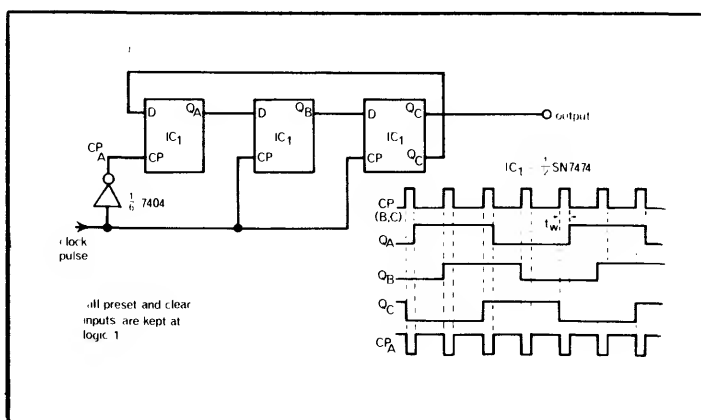2. The odd synchronous counter provides symmetrical high and low output levels although driven from an unsymmetrical clock pulse source. Flip-flop A is driven from an inverted waveform and hence will change state, depending on the D input, at a clock pulse rising edge, one clock pulse width earlier than any changes that occur in flip-flops B and C. Observe at clock pulse marked t_w , flip-flop C changes at the leading edge of the clock



pulse and flip-flop edge changes at the trailing, since it is driven via the inverter. The minimum clock pulse allowable depends on the propagation delay of flip-flop C and the data set up time of flip-flop 1. Figures quoted are 45 and 20ns respectively giving a minimum pulse width of 65ns.


Reference

Greenberg, M. Ideas for Design, *Electronic Design* 20, Sept. 27, 1974.

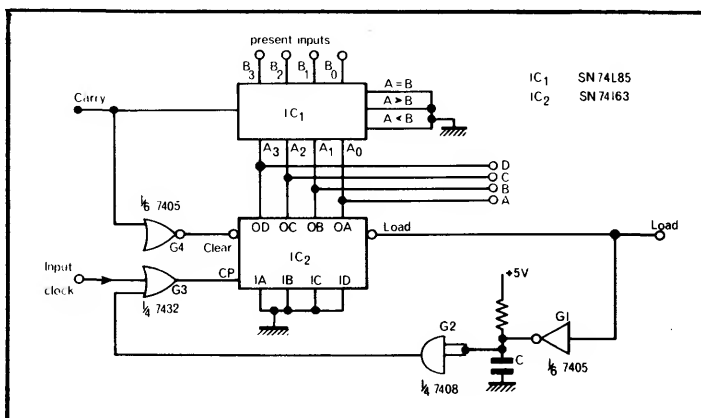3. This arrangement of a 4-bit comparator and a 4-bit synchronous counter provides a programmable variable modulus counter in the range decimal 2 to 15. A binary number N is set up at the preset inputs B_0 to B_3 (where B_0 is the least significant bit), i.e. over the range 0001 to 0111. The clock input causes the counter to reach the number $(N+1)$, where the counter outputs compared with the programmed comparator value will show equality by generating an output pulse at the carry terminal. This is used to reset

the counter to zero, and the sequence repeats. For

initialising the counter, gate G_2 ensures that the



exponential rise of voltage that will occur across C when the load terminal is driven low at commencement, will provide a fast logic level change at gate G_3 when the capacitance voltage reaches the threshold level of G_2 . Cascade connexions of comparators allow an extension of the modulus to 256 for two stages, the carry from the first counter being ANDed with the driving clock pulse.

Reference

Panzitta, J. Ideas for Design, *Electronic Design* 11, May 24, 1974.