

# Pulse-width counter sorts 16 pulse-width ranges

by Vladimir Shvartsman,  
Electronic Design & Research Inc., Louisville, Ky.

Highly precise pulse-width discrimination and demodulation is possible with this perpetual pulse-width counter. Unlike conventional pulse-width counters, this design has a very short dead time, enabling it to detect pulses with very small spacings. Moreover, it can be realized as a 28-pin integrated circuit that can sort 16 ranges.

A perpetual pulse-width counter works by comparing the duration of an input pulse width to a time interval developed by a precision oscillator in combination with a counter. An input signal arrives simultaneously at the enabled input of oscillator O and at monovibrator M<sub>1</sub> (Fig. 1a). The input signal enables a train of clock pulses from O to be applied to counter C. At time t = t<sub>2</sub> (Fig. 1b), a negative-going transition of an input pulse causes M<sub>1</sub> to produce a very short pulse. M<sub>1</sub> generates a pulse with the shortest possible duration in order to maximize the accuracy of the pulse-width counter.

For example, if an SN74123 serves as monovibrator M<sub>1</sub>, the dead time can be calculated as follows:

$$T_d = T_{\text{phl}} + T_w(\text{out})$$

where T<sub>phl</sub> is the propagation delay time, high-to-low



output, and equals 36 ns; T<sub>w</sub>(out) is the width of the pulse at M<sub>1</sub>'s output Q and is 65 ns.

If the above choice was made, the pulse-width counter would adequately react to every input signal, so long as the pause between pulses is greater than 101 ns. For higher-frequency applications, a monovibrator circuit solution should be chosen appropriately.

Counter C in Fig. 1a counts a predetermined number of precisely spaced pulses from the crystal oscillator for a duration of the unknown input signal. Its ripple clock output produces an output pulse only when an input signal is of sufficient duration; that is, when the number of the clock pulses passed to the counter must be greater than or equal to the number set by counter C. If each oscillator cycle is 10 ns and the counter is set to 10, the input signal's duration has to be at least 100 ns to enable a ripple clock output of the counter. Input signals with a width of less than 100 ns will be neglected.

The counter pulse initiates monovibrator M<sub>2</sub>. The output pulse duration of this monovibrator can be adjusted for the appropriate bandwidth. The adjustment has one limitation in that the duration of the M<sub>2</sub> output pulse must be smaller than the pause between pulses. An input signal is detected only when both pulses from M<sub>1</sub> and M<sub>2</sub> coincide at AND gate G.

As shown in Fig. 1b, the pulse on the output of the pulse-width counter (line 5) will exist only when the output pulses from M<sub>2</sub> (line 3) and M<sub>1</sub> (line 4) coincide. This results from the matching of the input-signal duration (line 1) with the interval developed by the clock pulses (line 2) in combination with the counter (line 3). In addition, the output pulse from M<sub>1</sub> is used to reset

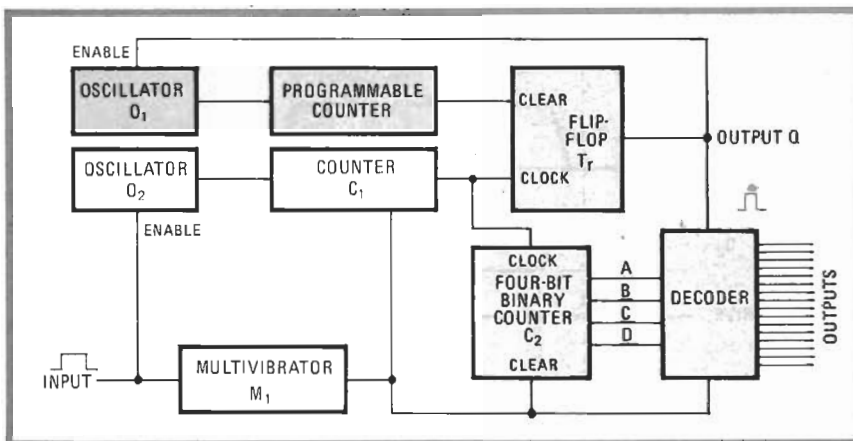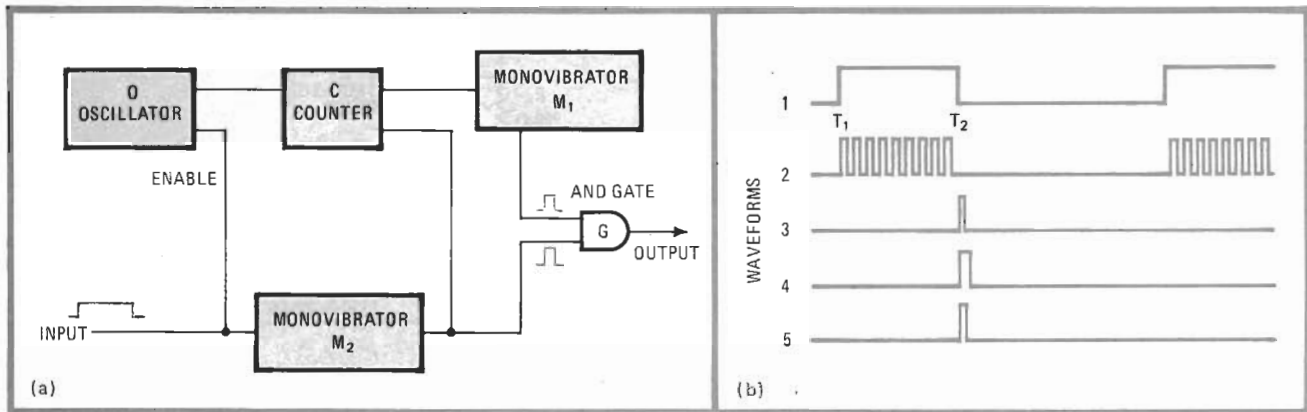

**1. Interval matching.** Simplified block diagram of the perpetual pulse-width counter (1a), which generates an output pulse only if the output pulses of M<sub>1</sub> and M<sub>2</sub> coincide in the AND gate G. The pulse chart (1b) shows the case when the duration of the input signal is equal to the developed interval.

**2. Programmable tolerance.** Oscillator O<sub>2</sub>, the programmable counter, and the flip-flop circuit replace the monovibrator M<sub>2</sub> in the block diagram of Fig. 1 to ease adjustment of bandwidth and tolerance of windows. The counter generates an output pulse when a number of pulses reach a preset value.