

3

It is the simplicity of this exclusive OR-gate that makes its application instead of TTL-circuits so attractive. It functions as follows. When both inputs are

unequal, the output signal is always HIGH. Equal input signals give a low output level because in that case both transistors are either 'on' or 'off', so that the output signal is governed by input A.

EXOR

