

Do-It-Yourself LOGIC CHIPS

By Forrest M. Mims

IN THIS day of ultra-sophisticated semiconductor technology, large-scale and very-large-scale integrated circuits (LSI and VLSI respectively) containing hundreds or even thousands of logic gates have become commonplace. Nevertheless, examine any board containing one or more LSI or VLSI chips and you'll probably find an assortment of small- and medium-scale integrated circuits (SSI and MSI) with relatively few gates or flip-flops package.

Circuit designers have long wanted to combine in a few packages the relatively small number of gates and flip-flops required to support most LSI and VLSI chips. Custom ICs are usually out of the question because of their high price and long development time. And what happens if a design change is necessary?

Semi-custom integrated circuits are a better choice. These chips contain arrays of gates which have not been *metalized*. In other words, the gates are independent of one another since they've not yet been connected together electrically by a metalization pattern on the top surface of the chip. The customer tells the custom IC house how he wants the gates interconnected, and the gate chips are

then metalized according to the customer's specifications and installed in DIPs.

This procedure is faster and cheaper than the custom IC route, but it's still relatively expensive since the customer usually must agree to buy a thousand or more chips. And as in the case of the

custom IC, what happens if a design change is necessary?

A third alternative is the do-it-yourself logic chip. Included in this category are *field programmable logic array* (FPLA) and *programmable array logic* (PAL, a trademark of Monolithic Memories, Inc.) chips. These chips contain arrays of logic gates interconnected via the same kind of fusible links used to make programmable read-only memories (PROMs). By selectively applying high-current pulses to the programming pins of an FPLA or PAL, fusible links can be opened in various patterns to produce a customized integrated circuit.

The PROM is itself a versatile do-it-yourself logic chip since it can be used to implement any truth table for which it has sufficient inputs and outputs.

You can better understand the operation and compare the differences of PROMs, FPLAs and PALs by referring to Figs. 1, 2 and 3. They show the internal circuitry of ultra-simple, hypotheti-

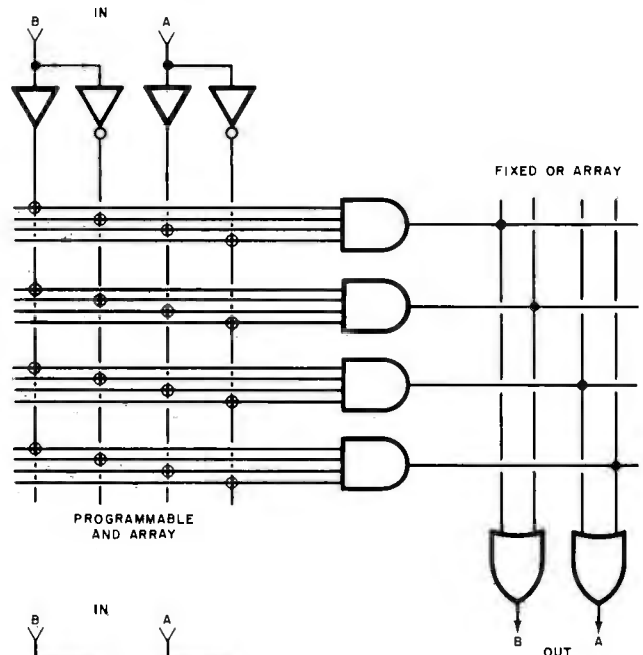


Fig. 2. A hypothetical PAL of two four-bit words. It is a backward PROM since the AND array is programmable while the OR is fixed.

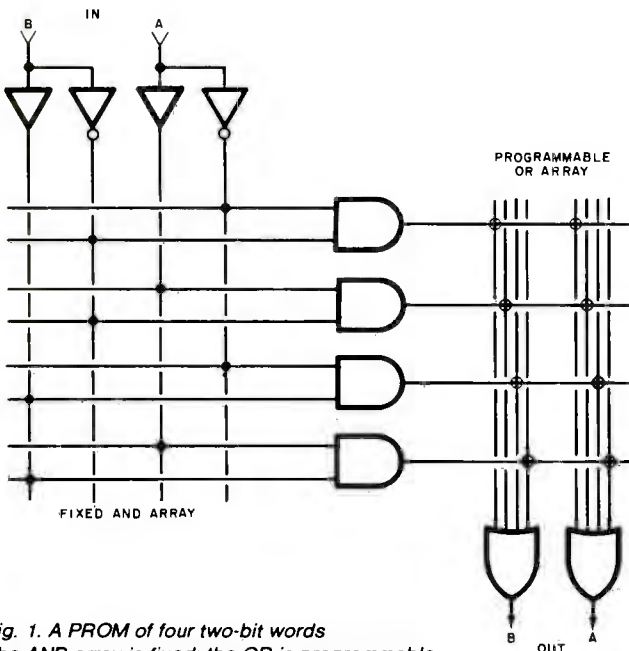


Fig. 1. A PROM of four two-bit words. The AND array is fixed; the OR is programmable.

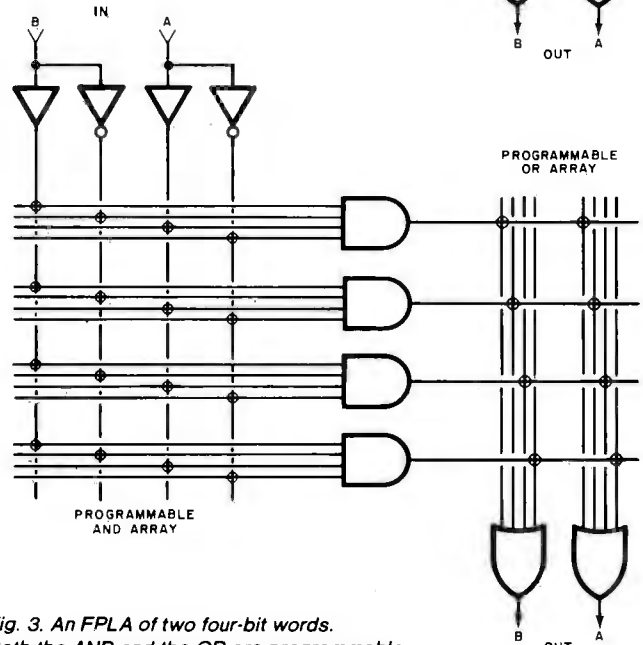


Fig. 3. An FPLA of two four-bit words. Both the AND and the OR are programmable.

Do-It-Yourself Logic Chips

cal versions of each of these three kinds of programmable logic arrays.

As is readily apparent from these figures, all three circuits contain an AND array followed by an OR array. The input word applied to the AND array can be considered an address, data word or bit pattern. In any case, the effect is the same since a particular input switches the output of one of the AND gates from low to high. The outputs then reflect whether or not connections are

present at the junction of the output line from a selected AND gate and the input lines to the OR gates.

A solid dot at the intersection of two array lines means the connection was unalterably programmed when the chip was made. User programmable fusible links are indicated by small circles at intersection array lines.

In the PROM (Fig. 1), the AND array is permanently programmed or *fixed* while the OR array is program-

mable. The AND array in Fig. 1 is programmed to address in turn each of the AND gates from top to bottom according to a standard 00, 01, 10, 11 input sequence.

The PAL (Fig. 2) is a backward PROM since the AND array is programmable while the OR array is fixed. In real PALs the OR array is factory programmed to give some of the most commonly used logic functions.

The FPLA (Fig. 3) is the ultimate do-

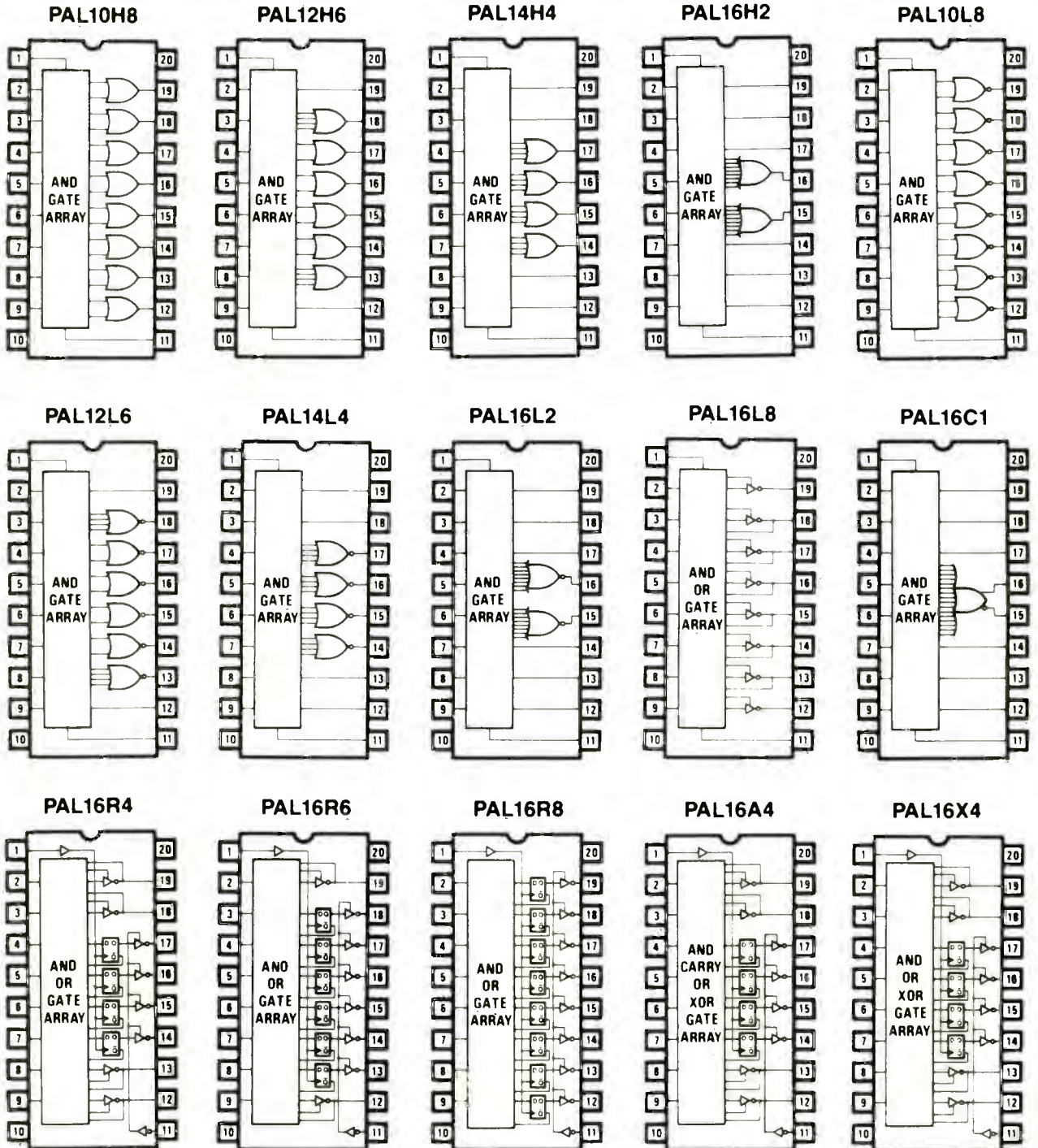


Fig. 4. Pin outlines and internal block diagrams of the PAL family of chips.

it-yourself logic chip since both the AND and OR arrays are programmable. While this provides the highest degree of flexibility, in practice the FPLA is much more difficult to use and more expensive than either the PROM or the PAL. All three kinds of chips can be programmed using standard PROM programmers, but the programming procedure for the FPLA is at least twice as cumbersome since both the AND and OR arrays must be programmed.

Some PALs and FPLAs include flip-flops to store output states and feed results back to the inputs. This makes possible such functions as counting, shifting and sequencing.

PALs without flip-flops can perform virtually any task now accomplished with SSI and MSI logic chips up to and including a 4-bit arithmetic logic unit! In many applications a single PAL can replace up to ten SSI/MSI packages.

A clever feature of PAL chips is a data security fuse. After the PAL has been programmed, the security fuse is blown to disable the circuit's internal verification logic. This prevents the internal program from being read out by a potential copier, thereby making the chip proprietary.

The PAL concept was pioneered by John Birkner of Monolithic Memories, Inc., and that firm now makes a family of fifteen PAL chips with National Semiconductor as a second source. Figure 4 shows the pin outlines and internal block diagrams for all fifteen chips. As you can see, considerable flexibility is provided by this lineup.

Information about PALs and FPLAs is not too abundant. The best way to learn more about PALs is to contact a Monolithic Memories or National distributor or representative. Try to obtain a copy of the excellent "PAL Programmable Array Logic Handbook" published by Monolithic Memories (1165 E. Arques, Sunnyvale, CA 94086).

Signetics (P.O. Box 9052, Sunnyvale, CA 94086) is a major maker of FPLAs. Their "Bipolar and MOS Memory Data Manual" contains FPLA data sheets and related information. Two Signetics engineers, Napoleone Cavlan and Stephen J. Durham, have written an excellent two-part article of the subject for *Electronics* (July 5, 1979, pp. 109-114 and July 19, 1979, pp. 132-139). In an article for *Computer Design* (April 1980, pp. 141-147), Mr. Durham described a complete 60-character keyboard encoder complete with key debouncing and made from a single Signetics 82S105 FPLA!

You can find the aforementioned articles in any good public or university library. For manufacturer's literature, check the yellow pages and call local electronics distributors or reps. If they can't help you, ask for the phone number of an authorized rep in any nearby city or state. If necessary, call the company direct. The cost of a few long dis-

tance calls may be well worth the results you'll harvest.

Do-it-yourself logic chips require careful design procedure and a PROM programmer so they're not necessarily suited for the typical hobbyist or experi-

menter. But if you want to greatly simplify a favorite logic circuit while learning about one of the latest trends in digital circuit design, get your hands on some manufacturer's literature and warm up your PROM zapper.

Fast, Accurate, Transparent, Quiet . . . Affordable

PHOENIX SYSTEMS 91 ELM STREET
MANCHESTER CONNECTICUT 06040 203-643-4484

KNAPCO

G.E. MOV Spike Eliminators 10/9.90 \$1.09 115V	Varactor Diodes Hyper-Abrupt Diode Above 1 Ghz Mini-L Pack Motorola BB 105 39¢	"AUTO LIGHT-OFF" AUTO LIGHT OFF UNIT — ADJUSTABLE DELAY — 2/12V 10 AMP RELAY TRIGGERED CIRCUITS SOLD SEARS \$39.95 \$4.95
Tri-Color LEDs Red/Green reverse volt Yellow A.C. 100/50.00 2/\$1.50	Solder Paste 35 Grams Liquid Solder 60/40 Rosin Base 49¢ Injection Pack Per Tube	Voltage Regulators +5V. 7805 +8V. 7808 +12V. 7812 +18V. 7818 5/\$5.50 10/\$9.95 +24V. 7824
3 CONDUCTOR EQUIPMENT CORDS 6' SHIELDED - MATES TO RFI FILTER \$2.49	DELUXE PROJECT CASE Blk. Injection Molded Recessed Panel w/Strain Relief. 4" x 4 1/2" x 1 1/2" 10/\$30.00 100/\$225.00 1000/\$2000.00 \$3.25	MOTOROLA PIEZO SPEAKERS Ultra Sonic Transducers KSN1005A 3 1/2" \$6.95 RESPONSE 10/\$55.00 60 TO 30,000 Hz 100/\$450.00
115 V. BLOCK FANS 3" SQ. \$6.95 # FAN 31 2/\$10.00	PROJECT CASE Plastic Case w/Base Flange HINGE FRONT Cord-Out Hole 3"x4"x2"H. 99¢ 10/\$8.90 100/\$75.00	Milton Bradley Computer Perfection new boards w/ microprocessor 10/\$6.95 99¢
ULTRASONIC BUG ELIMINATOR IC BASE CIRCUITRY WITH PIEZO BOARD W/COMPONENTS CASE AND A.C. ADAPTOR ELIMINATE COCKROACHES, FLEAS, BUGS. KIT \$15.95	Dual Computer Chip Set 2 CPU & MPU Systems Dual Clocks, ACU. 512 X 8 Bi Polar Ram 50 usec. & support R 29623 Bi Polar Ram 74LS624 Volt Cont. Osc. 74121 (2) 7413 (2) 29701 64 X 8 Prom MC 8601 Monostable, Retrig. Multivibrator (2) CA 3746 Quad 20 MA. OP AMP 6503 CPU 8048 MPU 723 Reg. TMS 9901 Prog. Keyboard Interface \$9.95	POWER INVERTER 12V. TO 115V. Tripp Lite 450 Watt \$89.95 PV400 Full Warranty Reg. OEM \$139.95
SEND FOR FREE CATALOG or call us at (813) 392-0406	ITT Power Supply Triple or Dual Choice Of +12V. 7A. 12V 7A or 24V. 7A. And 5V. 10A \$300.00 Orig. Teletype Cost 5" X 5" High X 14" \$59.95	Voltage Regulator Boards Just hook up to transformer Choice Of: 12V., 9V., 6V. @ 1.5A. \$1.29 ADJUSTABLE BOARDS 4.5V. TO 18V. DC \$1.95
4 WATT AMPLIFIER TI SN 76002ND (LM 384) 99¢ add 10% for shipping and handling min. shipping charge \$2.50	RFI FILTERS 2 AMP HOPKINS # F-85010 \$1.99	Piezo Elements 100/20. 39¢ Fantastic Murata Transducers!
	Dip Tantalum Caps 6.8 10 15 22 33 47 in 6.3V 22 68 in 10V 1.5 3.3 4.7 6.8 in 16V 15 in 20V 47 68 1.5 2.2 3.3 4.7 6.8 in 35V 22 68 1 in 50V dipped and sold 29¢	TRANSFORMERS 10V./8 A +46 V./2.5 A. C.T. 6, 7, 9, 12's @ 1 to 1.7 A. \$6.95
	Jumbo LEDs 100/ \$5.00	Specialty Chips TMS99001 CPU \$1.95 6514-S CMOS RAM \$3.50 MM5280K 4K RAM \$3.00 IM6402 Uarts \$4.95 MC10125P Bus Driver \$3.50 MNI400ML CPU \$5.59 4164-15NL 18-50 RAM 64K AMI 1702 13.95 Eeprom 4116 200NS 8 115.50 Ram 8080A CPU 1.95

H.J. Knapp of Florida, Inc.
4750 96th St. N. St. Petersburg, Florida 33708