

DRAWING BOARD

continued from page 88

inputs are grounded. Since the \bar{Q} output is also connected to one of the legs of the first NAND gate we have two highs there and the Q output will be low. If we switch the s input to +V, the output of the second NAND gate won't change because the other leg is still being held low. Suppose we now connect the R input to ground while the s input is switched to +V. With one leg grounded, the Q output will go high and the two highs at the inputs of the second NAND gate will make the \bar{Q} output low. As you could predict, that flip-flop only responds to negative triggering because of the basic operation of the NAND gate.

The only thing to watch out for when you're using this flip-flop is to make sure that the s and R inputs aren't grounded at the same time. If that does happen, both outputs will be high and the circuit will be unstable. In practice, the last input to be grounded will decide the ultimate state of the flip-flop. But don't believe us—build it and try it yourself.

We can build the same sort of circuit with NOR gates and the flip-flop will respond to positive triggering. Use the previous discussion as a guide and trace through the operation of the NOR gate flip-flop so you understand how it works.

Now let's get back to our original problem. The circuit in Fig. 3 uses a NOR gate flip-flop to control the operation of the reset pin on the 4017. We're using NOR gates because they respond to positive triggering and the outputs of the 4017 are active high. The truth table for the flip-flop is shown in Table 1. The not-allowed state with NOR gates is having both the flip-flop inputs high. This isn't a problem, since the internal gating of the 4017 guarantees that only one output can be high at any one time.

As long as none of the switches are closed, R1 holds the input of the flip-flop low. That means that the \bar{Q} output will be low regardless of what is happening at the s input. The reset pin of the 4017 is also held low and the chip is enabled. Now let's close one of the switches and see how the circuit works.

When the selected output goes high, the R input of the flip-flop goes high and a high appears at the \bar{Q} output. This resets the 4017, the selected output goes low, and the 0 output, pin 3, goes high. Remember that the 4017 outputs go high in turn and whatever output you select will be low immediately following a reset pulse. That makes the R input low and control of the flip-flop moves over to the s input. You can see from the truth table in Table 1 that we need a positive pulse there to make the flip-flop change state and put a low at the \bar{Q} output to release the 4017's RESET pin.

The 0 output of the 4017 is inverted by NOR gate IC2-a and presents a low to one leg of NOR gate IC2-b. The other leg of the gate is connected to the input clock and when a low appears there, IC2-b goes high and resets the flip-flop. That releases the RESET pin and enables the 4017. If you keep the switch closed at the keyboard, the circuit will reset over and over at the same point. The result will be a series of pulses at the \bar{Q} output equal to the input frequency divided by whatever number you chose.

That circuit gives the 4017 a reset operation that is both synchronous and locked to the input clock. By following everything carefully you should have no trouble understanding how we did it. Remember that the reset operation starts on the positive half of the incoming clock cycle and is ended on the negative half of the same clock cycle. Since the input clock will be running faster than the pulses at any of the 4017 outputs, we don't have to worry about glitching in the count.

A side advantage of that approach is that the Q output of the flip-flop will give us an output wave that is equal in frequency to the \bar{Q} output but opposite in sign. That can come in handy for some things and is especially nice since we're getting it for free.

If you want to cascade several 4017's together to increase the range of division, you won't be able to use the carry output, pin 12. Since that pin is high for the first half of the 4017's full count and low for the second half, frequency division of less than six will mean that the carry pin never goes low. The 0 output will, however, always go through a full cycle no matter what division you're doing, so you can take your signal from there.

The duty cycle problem

Now that we've solved the reset problem, let's look at the duty-cycle problem. In case you forgot what it is, we discovered that the duty cycle of the output would change every time we divided by a different number. It would follow the form $1/N$ where N is the number you're dividing by. More specifically, the high time would be equal to the period of the incoming clock, and the low time would be equal to $N - 1$ times the period.

If you're dividing by an even number, some simple gating would let you get an output with a nice 50% duty cycle but trying to do the same thing with an odd number would be—well, odd.

One of the basic rules of design is that there's a better way to do everything and that's true here. When simple problems generate overly complex solutions, it's time to scrap your whole approach and start over with a different color paper. In this case, squaring up the duty cycle not only calls for a different approach, it calls for a different IC—a different kind of counter. We'll examine that—and other mysteries—in next month's column. **R-E**