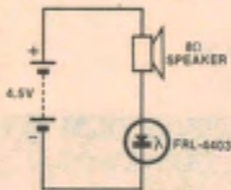


Simple Audible Flasher



By connecting a small loudspeaker in series with a "flashing" LED, a "ticking" will be heard every time the LED circuit is energised.

J. Rogers,
Glenelg, SA.