

ELCOM 200 Watt Dual Lamp Flasher

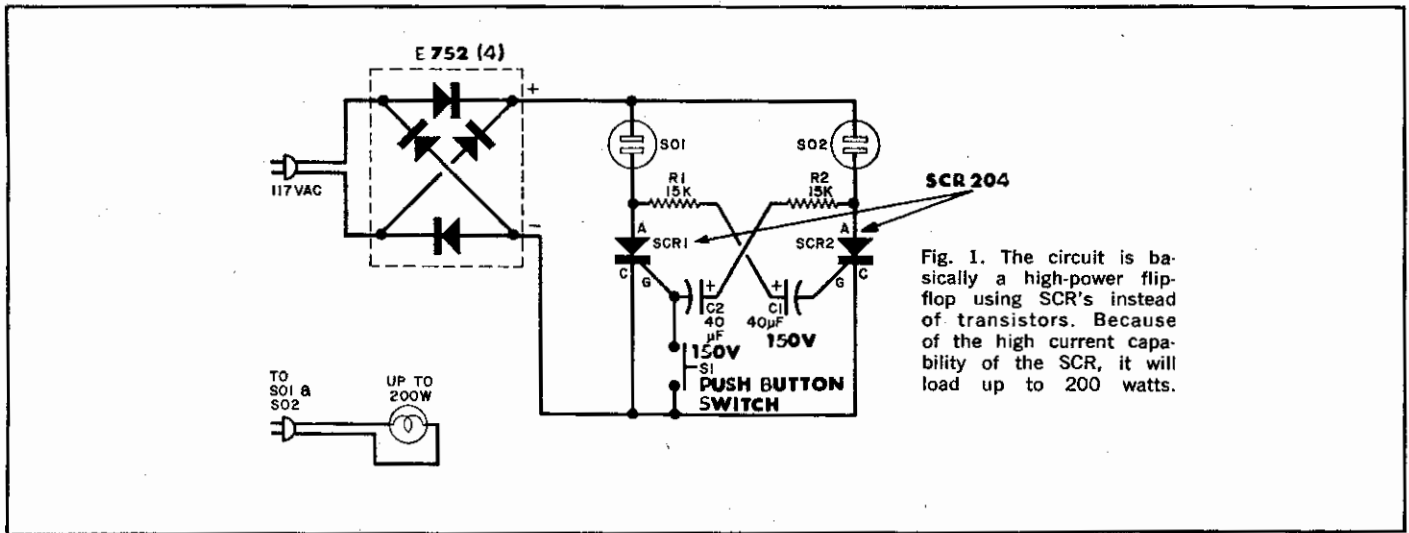


Fig. 1. The circuit is basically a high-power flip-flop using SCR's instead of transistors. Because of the high current capability of the SCR, it will load up to 200 watts.