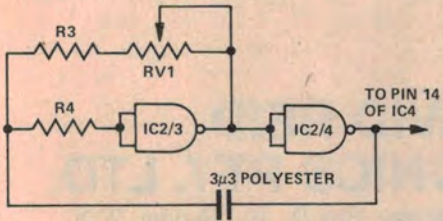


## ETI 551 oscillator

Ian Beagrie of Auckland has had a few problems with the oscillator in the ETI 551 Light Chaser. He found that it would only give an output with some 'digital' help – touching part of the circuit with his finger! The circuit here proved somewhat more reliable, he found.



NOTE: C3 & R7 HAVE BEEN REMOVED FROM ORIGINAL CIRCUIT