

EXPERIMENTER'S CORNER

Experimenting with Electronic Flash Circuits

By Forrest M. Mims, III

THE brilliant white light emitted by a xenon flash tube has many practical applications. It's used for photographic illumination, solar simulation, and laser stimulation optical (pumping of laser materials), as well as for many kinds of safety, rescue, and warning lights.

Though specially designed high-pressure xenon lamps can be operated continuously if suitable cooling is provided, most xenon-filled lamps are operated in a flash mode. Such lamps can have many different configurations. A few have envelopes of metal and glass, but most are glass cylinders or bulbs containing discharge and trigger electrodes. The cylinder configuration, the most common of all, is merely a hollow glass or quartz tube with an electrode at each end.

Cylindrical xenon flash tubes can be as small as a matchstick or, in the case of very high-power glass lasers used in fusion research, as big as a fence post. The glass tubes can be straight or shaped in the form of an L, U, or spiral.

Figure 1 is a block diagram of the essential ingredients of a circuit for operating a xenon lamp in the flash mode. A high-voltage supply simultaneously charges a large energy storage capacitor and a much smaller trigger capacitor. After the main capacitor is charged, the lamp is flashed by dumping the charge on the trigger capacitor through the primary of the trigger transformer. The high-voltage spike appearing at the secondary of the transformer is coupled to a small metal strap or wire wrapped around the flash tube.

This voltage spike ionizes some of the gas within the tube and provides an electrically conductive path for the charge in the main capacitor. The capacitor then discharges through the tube and excites the xenon atoms into emitting an intense white flash.

Figure 2 is a circuit that implements the operation of the block diagram in Fig. 1. Note that C_1 , the main energy storage capacitor, is connected directly across the flash tube. No leakage of charge occurs since the xenon does not conduct unless it is first ionized by a voltage higher than that across C_1 .

After both C_1 and C_2 are charged,

the flash tube is triggered by closing S_1 . This dumps C_2 's charge through trigger transformer T_1 's primary. Since T_1 has a very high turns ratio, several thousand volts appear across its secondary. This voltage is coupled to the flash tube's trigger electrode where it ionizes some of the xenon gas and provides a low resistance path for the energy stored in capacitor C_1 .

The discharge of C_1 through the xenon is accompanied by a brilliant flash of light. The xenon resumes its nonconductive state immediately after C_1 is discharged. As soon as C_1 and C_2 are recharged, S_1 can again be closed to obtain another flash.

The energy in joules stored in the main flash capacitor is one-half the product of the capacitance and the square of the voltage. For example, a 400- μ F photoflash capacitor charged to 350 V has a stored energy of 24.5 joules.

The duration of the flash is determined by the RC time constant of the flash capacitor and the discharge path

through the flash tube. Sometimes intervening networks are included to shape the discharge event into a square pulse with fast rise and fall times.

A very large C implies a long discharge time and, hence, a long flash. For short flashes it is necessary to use small values of C. To obtain equal illumination, V must then be increased. For example, to match the 24.5 joules in the preceding example, a 10- μ F capacitor would have to be charged to 2.214 kV.

Alternatively, the flash can be electronically ended at almost any time by an appropriate solid-state switch. This is the method used by "computer" strobe flashes so popular with photographers. Thus, fast pulses are obtained with low energy levels. One plus is that the energy remaining in the capacitor can be used for one or more subsequent flashes, thereby extending battery life and reducing recycle time.

You may be wondering why R_1 is included in the circuit in Fig. 2 since it plays no role in the charge-discharge cycle. Its only role is to bleed the charge from C_1 should the high-voltage supply be turned off. Even if the flash tube is triggered after the high-voltage supply is turned off, some residual charge may remain in C_1 which will be discharged through R_1 .

The circuit will operate without R_1 , but including it is a very important safety precaution. The hazards of the high voltage required to operate xenon flash circuits are so profound that it's important to discuss them in detail before looking at some working circuits you may wish to assemble.

Important Flash Tube Precautions.

Though the power supplies of some specialized xenon flash units may deliver several thousand volts, most produce from 150 to 500 V. You should, therefore, exercise considerable caution when working with such circuits. Always keep one hand well away from the circuit to prevent a potentially dangerous or even lethal through-the-body shock.

You can eliminate the shock hazard of a high-voltage supply simply by disconnecting the power. But this alone will not eliminate the hazard posed by capacitors that may have been charged by the supply. For example, in Fig. 2 the high voltage is stored in both C_1 and C_2 .

Capacitor C_2 usually has a capacity of a few tenths of a microfarad, but C_1 may have a capacity of several hundred microfarads. Therefore, C_1 poses far

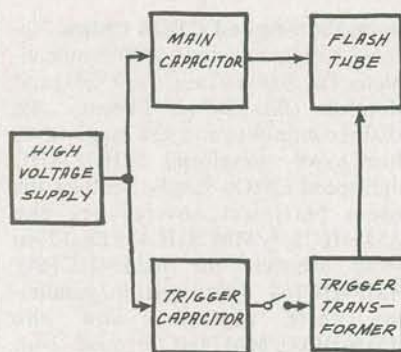


Fig. 1. Block diagram of a flash-tube trigger circuit.

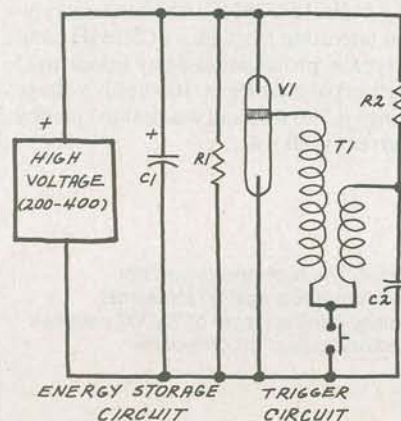


Fig. 2. Basic flash-tube circuit.

more of a hazard than C2. A charge of several hundred volts on a capacitor of several hundred microfarads is enough to vaporize and melt away a small crater in a steel screwdriver tip! Since considerable residual charge can be retained by such a capacitor for hours, days or even weeks, it is imperative that you treat all photoflash capacitors with the respect due a loaded gun. *Never* handle this kind of capacitor without first discharging it by bridging across its terminals the blade of an insulated screwdriver, or a power resistor with well insulated leads. Use only one hand to bridge the capacitor terminals and be sure the capacitor is *fully* discharged before handling it.

Charged photoflash capacitors are so hazardous that even taking precautions sometimes does not help. For example, ten years ago I was experimenting with a voltage divider I had assembled from a string of 10- μ F, 450-V capacitors. The input to the multiplier was connected to a 350-V miniature power supply powered by a 3-V battery. The output from the multiplier was about 1000 V.

Because of the shock hazard, I followed the traditional safety practice of keeping one hand in my pocket. All went well until the springy ladder of capacitors and diodes suddenly slid from the workbench and into my lap. I grabbed one end of the multiplier with my free hand just as its high-voltage output lead touched my pants. Suddenly there was a loud pop and a puff of smoke, and a terrific jolt threw me to the floor. I was not only "shocked," but got a bad burn on my leg to boot. Suffice it to say that this unsettling experience left a lasting impression on me about the hazards of charged capacitors.

A Single-Shot Flash Circuit. Figure 3 shows a single-shot flash circuit designed around commonly available components. Transformer *T1* is a standard filament transformer. Transistors *Q1* and *Q2* form a simple oscillator. In operation, the fast-risetime pulses from the oscillator are directed through the 6.3-V winding of *T1*. When powered by a 1.5-V dry cell, the initial part of the output pulse appearing at *T1*'s 120-V winding has a peak potential of about 170-V and a duration of about 40 ms. The pulse amplitude then falls to about 100 V for the remainder of the 110-ms pulse.

The high voltage from *T1* is stored in *C2* and *C3*. Diode *D1* prevents these capacitors from discharging through *T1*. Resistor *R3* is a bleeder resistor that dis-

