
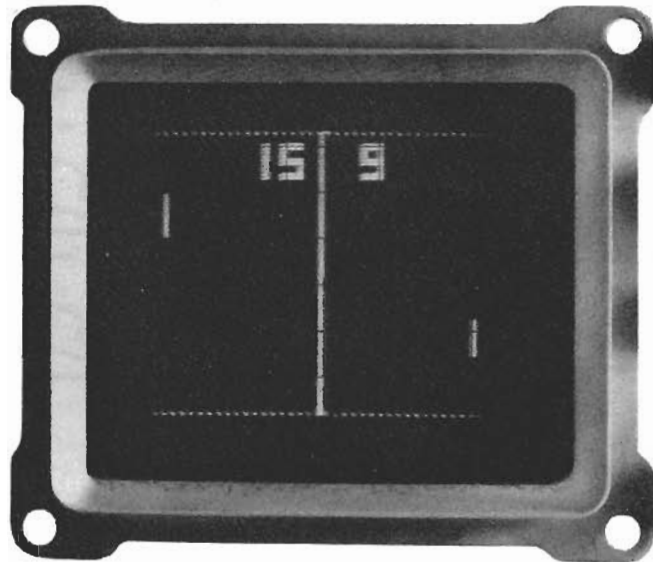

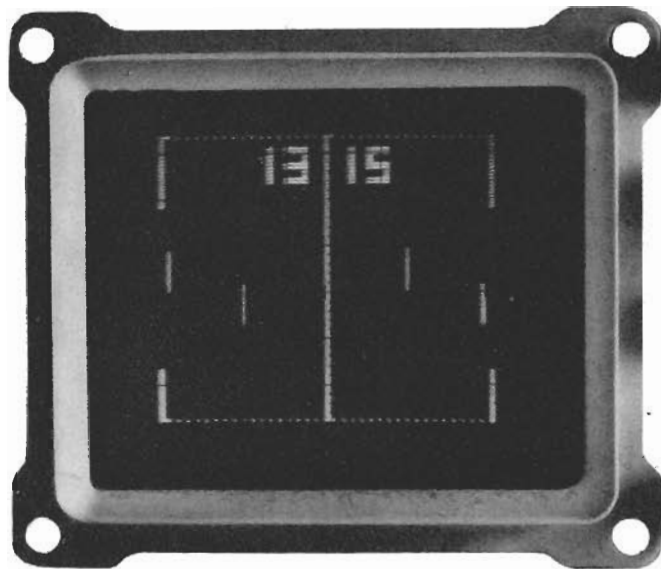
# Play Video Games with "SCOPE-ONG"

BY AL PLAVCAN

*Now you can play hockey,  
tennis, and other games  
on your oscilloscope*



**T**HERE IS a way to build a video-game project and avoid problems meeting FCC regulations. Moreover, it frees your TV receiver for normal use. Simply use your *oscilloscope* instead of a TV receiver to display game graphics. This way, you avoid the possibility of TV interference and do not have to pay a premium for an FCC-approved Class I device (r-f modulator and isolation switch). The "Scope-Ong," described here, works just this way.

The circuit uses the readily available General Instruments AY-3-8500-1 game chip, found in many video games on the market. Programmed into this chip are squash, hockey/soccer, and tennis. Automatic on-screen scoring and user-selectable paddle size, ball angle, ball speed, and auto/manual ball serve round out the chip's features. The only requirements for the oscilloscope to be used as the graphics display are that it have provisions for external sync and a Z-axis input.

**About the Circuit.** Sections A and B of IC2 in Fig. 1 are used as a crystal-controlled oscillator circuit to drive

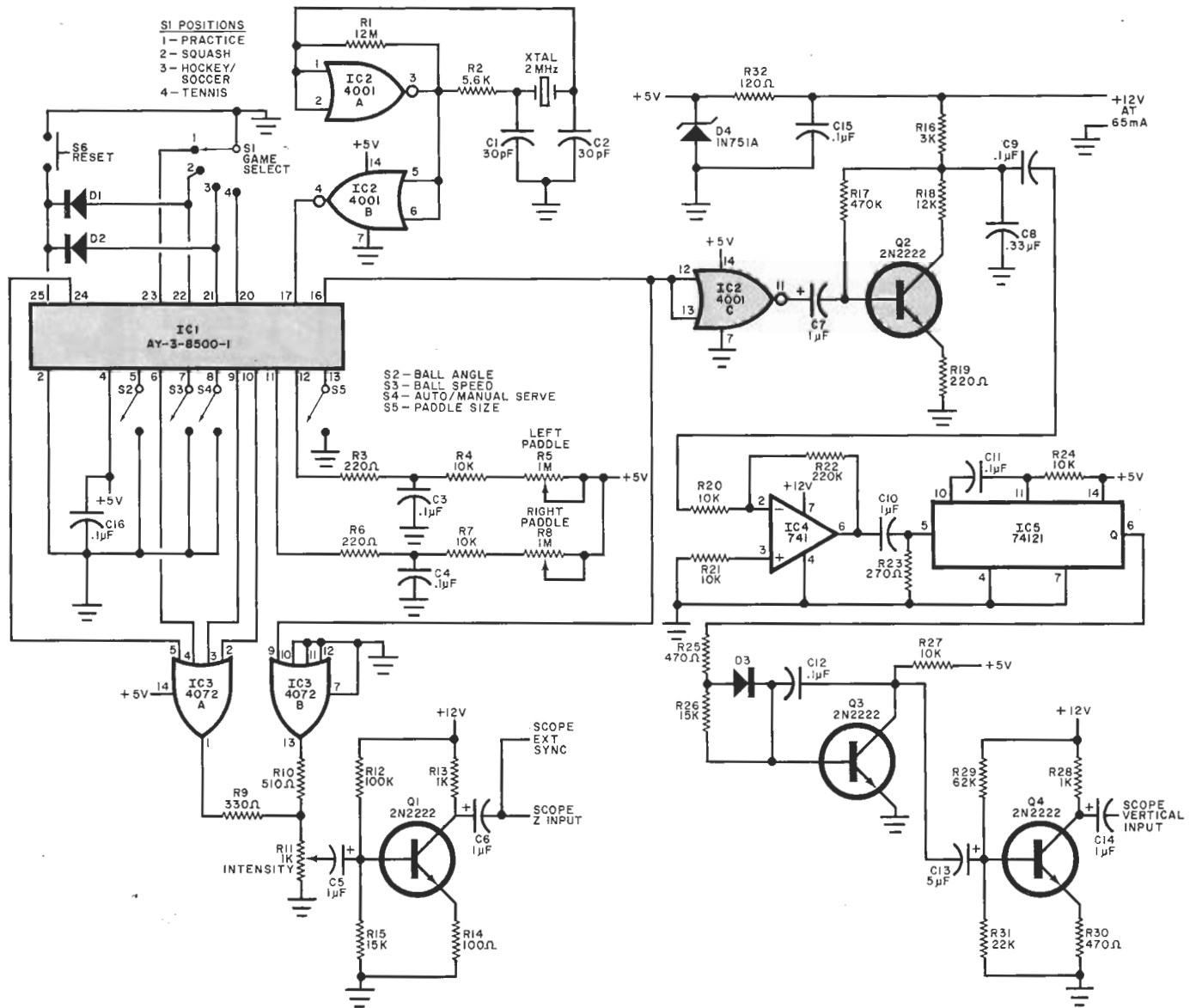


Fig. 1. Adding vertical sweep generator to basic game circuit permits use with conventional oscilloscope.

### PARTS LIST

C1,C2—30-pF disc capacitor  
 C3,C4,C9,C11,C12,C15,C16—0.1- $\mu$ F, 20-V capacitor  
 C5,C6,C7,C10,C14—1- $\mu$ F, 20-V capacitor  
 C8—0.33- $\mu$ F, 20-V capacitor  
 C13—5- $\mu$ F, 20-V capacitor  
 D1,D2,D3—1N914  
 D4—1N751A, 5-V zener  
 IC1—AY-3-8500-1 game chip (General Instruments) (available from Poly Paks, James Electronics, and other advertisers at the back of this magazine)  
 IC2—4001 (or 4011) quad 2-input NOR gate  
 IC3—4072 dual 4-input OR gate  
 IC4—741 op amp  
 IC5—74121 monostable multivibrator

Q1 through Q4—2N2222 transistor  
 The following are  $\frac{1}{4}$ -watt, 10% resistors unless otherwise noted:  
 R1—12 megohms  
 R2—5600 ohms  
 R3,R6,R19—220 ohms  
 R4,R7,R20,R21,R24,R27—10,000 ohms  
 R5,R8—1-megohm potentiometer  
 R9—330 ohms  
 R10—510 ohms  
 R11—1000-ohm, pc-mount potentiometer  
 R12—100,000 ohms  
 R13,R28—1000 ohms  
 R14—100 ohms  
 R15,R26—15,000 ohms  
 R16—3000 ohms

R17—470,000 ohms  
 R18—12,000 ohms  
 R22—220,000 ohms  
 R23—270 ohms  
 R25,R30—470 ohms  
 R29—62,000 ohms  
 R31—22,000 ohms  
 R32—120-ohm, 1-watt resistor  
 S1—4-position rotary switch  
 S2 through S5—Spst switch  
 S6—Normally open pushbutton switch  
 XTAL—2.0-MHz crystal  
 Misc.—Paddle cable; scope interconnecting cable; power supply (12 V, 65 mA); suitable enclosure; dry-transfer lettering kit; machine hardware; hookup wire; etc.

game chip IC1. Composite sync pulses generated within IC1 are available at pin 16; they are buffered by IC2C and fed to sync separator Q2 to extract the vertical-sync pulse.

The vertical pulse is amplified by IC4

and applied to pulse stretcher IC5. The output of IC5 drives linear ramp generator Q3, whose output signal is inverted by Q4 and used as the vertical input of the scope.

The video outputs from IC1 available

at pins 6, 9, 10, and 24 are combined in IC3A to form a composite-video signal, which is then combined with the sync pulse present at the output of IC3B to generate the composite sync/video signal across INTENSITY control R11. Am-

# Fun Projects

continued

plification and inversion of the composite signal occurs in *Q1*, which then feeds the EXT SYNC and Z-axis scope inputs.

Available Z-axis output potential from the project is approximately 10 volts peak-to-peak. To determine if your scope can use this signal, apply at least +5 volts dc to the Z-axis input while a trace is on the screen. If the trace extinguishes or at least changes considerably in intensity, the circuit shown in Fig. 1 can be used.

**Construction.** The circuit can be assembled on a small printed-circuit board, the etching-and-drilling and components-placement guides for which are shown in Fig. 3. Once the pc-board assembly is wired, it and a 12-volt, 65-mA power supply (Fig. 2) can be mounted inside an appropriate enclosure. Mount the five selector switches, RESET push-

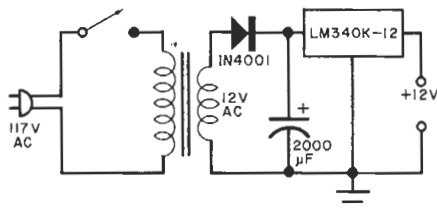


Fig. 2. This simple supply can be built to power the project.

button switch, and game "paddles" *R5* and *R8* on the top of the enclosure.

If desired, the game paddles can be housed in small separate boxes and connected into the circuit via cables and jack/plug assemblies. The jacks for the three scope signals can be mounted on the rear of the box. Finally, if you use a power supply with a power switch, mount the switch wherever convenient on the box. Label the controls, switches, jacks, etc., with dry-transfer lettering.

**Checkout and Use.** Set your scope's controls as follows: vertical input to 1 volt/cm, horizontal sweep to 5  $\mu$ s/cm, and sync to EXT. Connect the three leads from the Scope-Ong to the X, Y, and Z inputs of the scope (don't forget


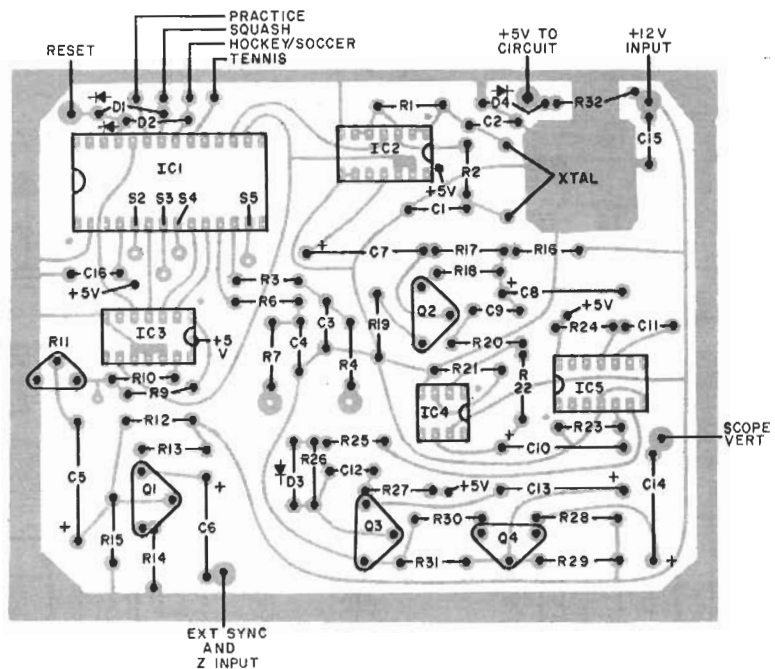


Fig. 3. Actual-size foil pattern for "Scope-Ong" is below. Component installation layout is shown above.

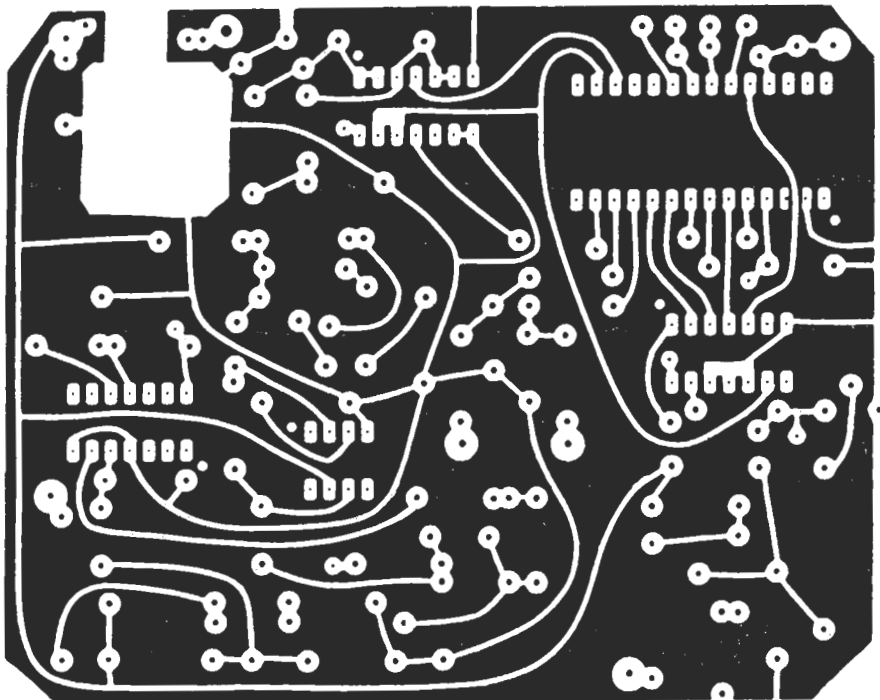

the ground connection). Now, set INTENSITY control *R11* to midrange and turn on both scope and game player.

Select a game via *S1* and note the activity on the scope's screen. Adjust *R11* and the scope's horizontal and sync controls for the best image of the selected game.

Press and release RESET switch *S6*; the score displayed should be 0-0. Closing AUTO/MANUAL SERVE switch *S4* (AUTO position) causes the ball to be served automatically until the end of the

game. If desired, *S4* can be opened and then closed each time you wish the ball to be served. Among the project's other options are *S2* that changes ball angle, *S3* that changes ball speed, and *S5* that changes paddle size.

**In Closing.** The Scope-Ong provides most of the functions and all of the features found in similar video-game devices on the market. The one thing it does not give you is possible trouble with your neighbors over TVI.  $\diamond$

(More Fun Projects on page 60)