
10 LED flasher

Here's an unusual LED dasher that uses soulight to charge its battery—just like the system used in space satellites. The basic flasher uses the LAD909 integrated circuit. The 3909 contains all of the required circuitry except for the LED itself and a timing capacitor. During the day, the sun hits the

solar panel's cells, charging the NiCad battery. At night, the battery provides the power to flash as many as 15 LM3909 LED flashers.

If you'd prefer to run the show from an ordinary battery, a single AA penlight battery can power one LMS999 flasher for three months while aD battery will run it for well over one year. Adding more flasher units will shorten the battery life, but a single number six dry cell should power a dozen flashers for well over a year.

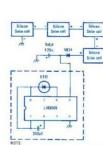Since the circuit consists of just a single IC and capacitor, you can mount as many as you want on a



Duplicate "hound in" circleir for each additional flashing EEO devices Boxed or part (390), EEO, 300cH corn approximately one dallar.

small perfboard. Then, just string some fine-gauge wire to your LEDs, which can be arranged in any artistic manner you'd like.