



LED 'logicator'

This circuit, submitted by Michael Kyrannis of Pascoe Vale Vic, can be used as a logic monitoring device to plug into an IC socket. A 'high' level on each of the pins will light its corresponding LED. One good idea might be to build the indicator onto the pins of an IC test clip. The indicator could then be simply clipped over the top of an operating IC. Be careful though that the circuitry can drive the LEDs.