

Circuit Ideas



Regulating l.e.d. outputs

Using a simple compensation circuit based on an opto-coupler, the power output of l.e.d.s in series can be maintained to within $\pm 5\%$ of the value at 25deg. C over their full operating temperature range. Compensation is required to overcome the negative temperature coefficient of near-infrared l.e.d.s which decreases the power output by 0.9% per deg. C increase. Fig. 1 maintains the output power by varying the forward current I_f through the l.e.d. string. The l.e.d. in the opto-coupler is used as a reference device and the collector-base photodiode is used as an output monitor. A CA3140 op-amp regulates I_f by maintaining a steady current through the sensor. In addition, the l.e.d. output power can be controlled by the potentiometer. The supply must provide adequate voltage for the l.e.d.s, i.e. 2.4V + 1.4 times the number of l.e.d.s in the string. Tem-

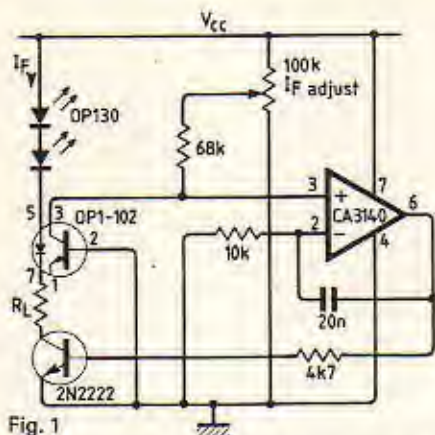


Fig. 1

perature performance will be improved if the l.e.d.s are matched. Resistor R_L limits the current through the string and is determined by calculating the maximum current required and the value of V_{CC} above the minimum value required.

If, due to a low V_{CC} , the l.e.d.s cannot be

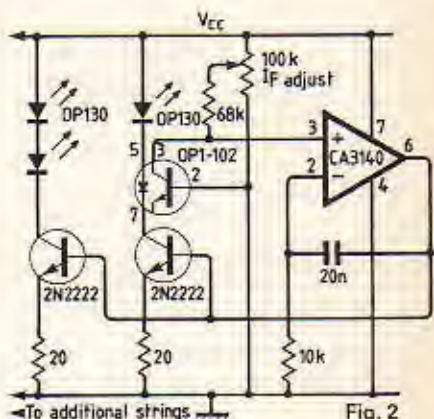


Fig. 2


used in a single string, several groups can be controlled as shown in Fig. 2. The transistors should be matched to provide equal I_f regulation in each string.

Norbain Electro-Optics
Reading
Berks.

C.m.o.s. to mains interface

Mains control by c.m.o.s. logic can be safely achieved using this isolation circuit. Almost 360° conduction is assured for all a.c. voltages, and higher currents can be switched by using larger triacs.

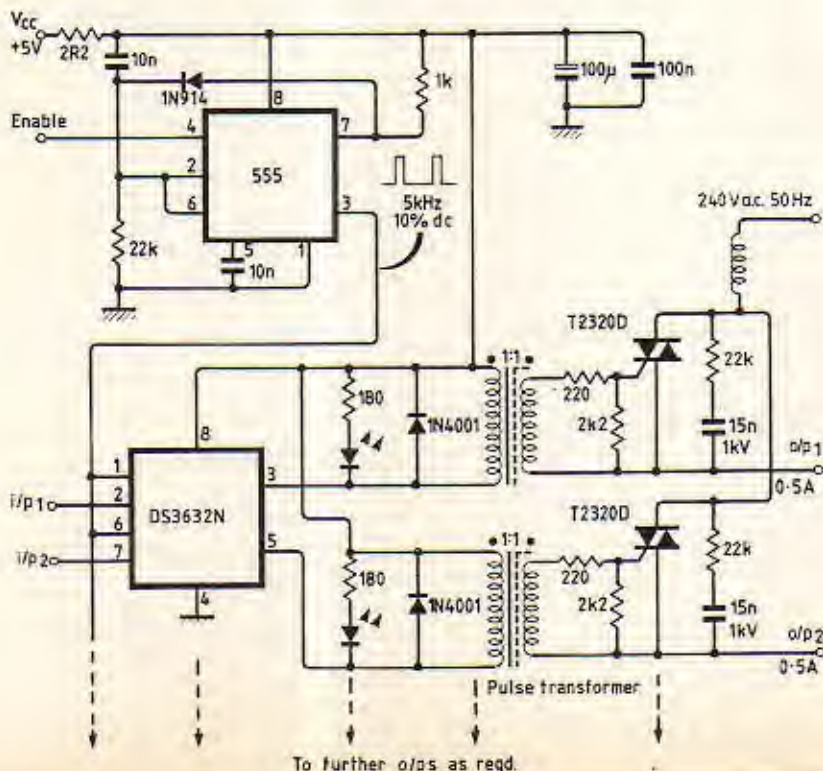enable input and can drive extra switching stages as shown.
L. Hurst
Auckland
N. Zealand



Piezoelectric-crystal driver

Because piezoelectric sounders are most efficient at their resonant frequency, drive circuits should be adjusted to suit individual crystals. This oscillator drives a crystal and does not need to be adjusted with a pre-set control. The circuit is a non-inverting a.c. amplifier whose gain approaches the open-loop gain of the op-amp, and has positive feedback applied via the piezoelectric device. The ceramic element acts as a stable mechanical vibrator which determines the frequency of oscillation so the circuit automatically oscillates at the sounder's resonant frequency. The circuit shown requires about 3.5mA with a 10V supply.

M. L. Ford
Worcester

