


LED CIRCUIT QUIZ

BY ROBERT P. BALIN

The seven-segment LED digital read-out has become a popular and important addition to many electronic devices. But getting them to light up may not always be a simple matter.

For example, in the circuit shown

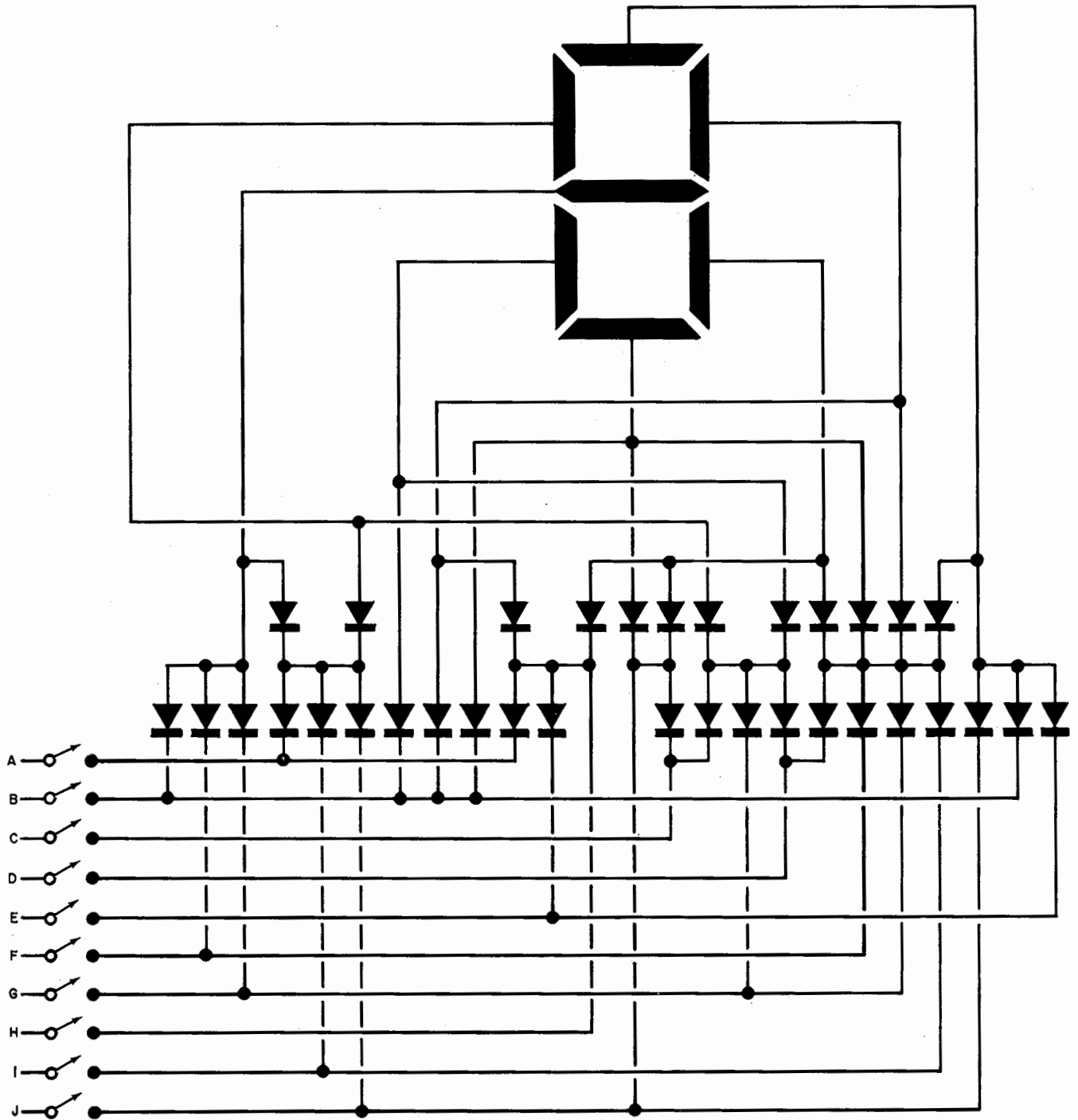here, as each of the switches (A-J) is closed, providing the segments with the proper voltage, a different digit is displayed. To test your ability at circuit tracing, see if you can determine what the numbers will be.



- A-4
- B-2
- C-6
- D-0
- E-7
- F-3
- G-8
- H-1
- I-9
- J-5

Answers