

Single-port pin drives dual LED

Tom Gay, Dornstadt, Germany

Most current microcontrollers offer I/O ports that can change their functions during program execution. As outputs, the circuits can sink and source reasonably large amounts of current. This Design Idea shows three alternative methods for driving a two-pin, two-color LED from a single I/O pin. **Figure 1** illustrates one possible approach that uses external inverter IC_1 to drive D_1 , a red/green bidirectional LED. A logic-high output on the port pin forces current through the green (upper) LED and pulls the inverter's input high, which drives the inverter's output high, which drives the red (lower) LED; the microcontroller's output sinks current from the red LED. A logic-low output on the port pin raises the inverter's output high, delivering current to the red (lower) LED; the microcontroller's output sinks current from the red LED.

To turn off both LEDs, you reconfigure the microcontroller's port pin from output to input or switch the pin to tri-state mode, either of which prevents the microcontroller's port pin from

sourcing or sinking current. This circuit's primary disadvantage is that it yields no control over each LED's brightness; instead, resistor R_5 determines forward current for both LEDs.

Figure 2 presents an approach that also involves a major disadvantage. Zener diodes D_3 and D_4 and resistors R_3 and R_4 form a low-impedance voltage divider that applies $V_{CC}/2V$ to one end of LED D_5 . The value of V_{CC} drives the selection of the zener diodes' voltage, V_Z , with lower voltage zener diodes allowing more LED current and higher voltage ones limiting maximum LED current. Given that the microcontroller's outputs can deliver rail-to-rail voltages, the difference between V_{CC} and V_Z limits maximum forward current for both LEDs. For example, if V_{CC} is 5V and V_Z is 3V, the forward voltage across either LED is less than 2V. Once a designer selects the zener-diode voltage, only small variations in V_{CC} can occur; otherwise, the LEDs' brightness would fluctuate.

Using discrete components, another circuit offers an inexpensive approach that avoids the other circuits' disadvantages (**Figure 3**). When the microcontroller's output port goes high, current flows through the green (upper) LED, R_2 , D_2 , and FET Q_2 , which the port's high level turns on. When the microcontroller's output port goes low, transistor Q_1 turns on and delivers current to the port pin through R_2 and the red (lower) LED. The circuit operates symmetrically because silicon diode D_2 's forward-voltage drop is present

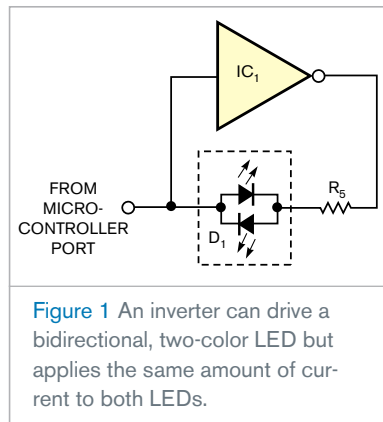


Figure 1 An inverter can drive a bidirectional, two-color LED but applies the same amount of current to both LEDs.

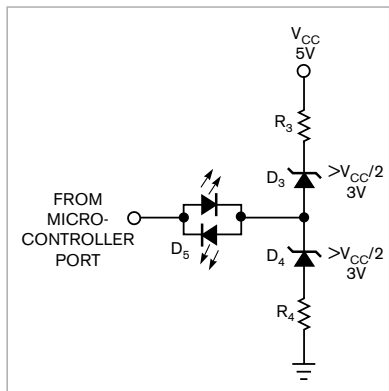


Figure 2 A zener-diode and resistor-voltage divider exhibits sensitivity to supply-voltage variations and allows LED brightness to vary.

regardless of whether the microcontroller's port pin goes high or low. V_{CC} may vary during operation but must remain higher than 3V.

You can individually adjust the LEDs' currents to equalize brightness or compensate for a difference between the microcontroller's power-supply voltage

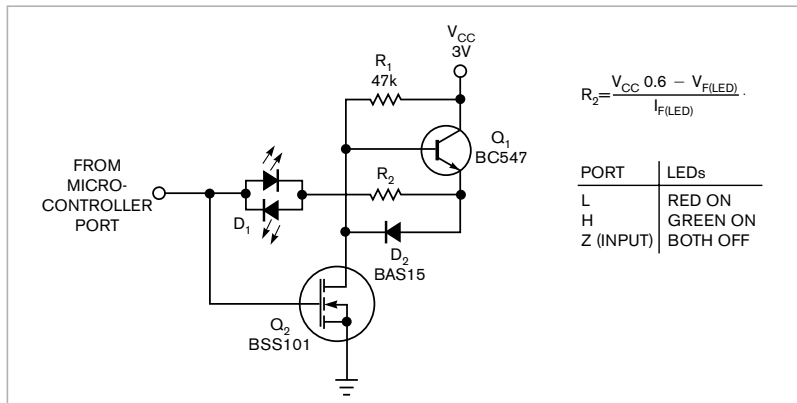


Figure 3 This circuit provides immunity to supply-voltage fluctuations and more uniform LED brightness.

and the LED-driver circuit's V_{CC} . Replace R_2 with two resistors connected in series between Q_1 's emitter and D_2 's anode. Connect the midpoint of the two resistors to the LEDs.

With the microcontroller's port pin configured as an "input with pullup," the port delivers a small current to the green LED. However, pullup-resistor

values of 22 k Ω or higher do not cause misleading light output from LEDs in the off-state. When the input signal from the port pin floats—that is, with V_{CC} at 5V and the port configured as an input with no pullup resistor—the circuit draws no additional current, and the quiescent current, which R_1 determines, averages less than 100 μ A. **EDN**