

K.S. SANKAR

noise and false triggering. Capacitor C3 and resistor R3 also avoid false triggering of monostable NE555. The monostable acts as a 1-second hysteresis unit to restrict the flip-flop from getting retriggered within one second. To activate any other 12V logic device, use the output across the relay coil terminals.

